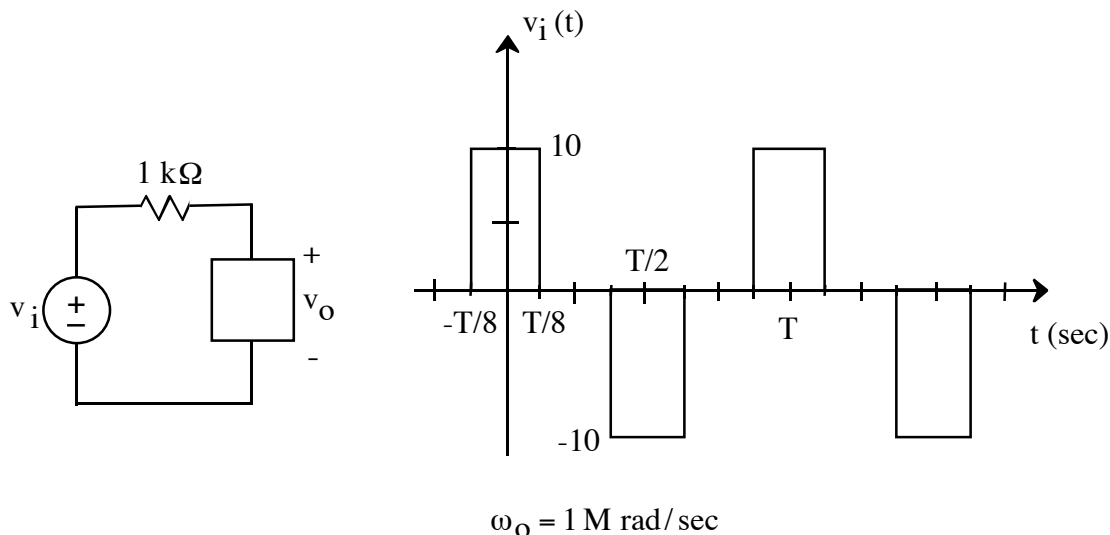


2. (50 points)



- a. Determine the coefficients of the Fourier series, a_v , a_n , and b_n , for the periodic waveform $v_i(t)$. Also, use these Fourier coefficients to find the coefficients of the first five terms of the Fourier series written in terms of inverse phasors:

$$v_1(t) = a_v + \sum_{n=1}^{\infty} A_n \cos(n\omega_o t + \theta_n)$$

Note any symmetry properties of the waveform that you use to determine coefficients.

- b. The circuit on the left is a filter with output $v_o(t)$. Design a circuit to be placed in the box such that the filter rejects the fundamental frequency of $v_i(t)$ and has a bandwidth of 10,000 rad/sec. Specify the component values. Show how the components are connected in the circuit.

ans: a) $a_v = 0$

$$a_n = \begin{cases} \frac{40}{\pi n} \sin \frac{\pi n}{4} & n \text{ odd} \\ 0 & n \text{ even} \end{cases}$$


$$b_n = 0 \text{ for all } n$$

$$A_1 = \frac{20\sqrt{2}}{\pi}, \theta_1 = 0^\circ \quad A_2 = 0, \theta_2 = 0^\circ \quad A_3 = \frac{20\sqrt{2}}{3\pi}, \theta_3 = 0^\circ$$

$$A_4 = 0, \theta_4 = 0^\circ \quad A_5 = \frac{-4\sqrt{2}}{\pi}, \theta_5 = 0^\circ$$

Symmetries used: even function, half wave (shift-flip symmetry), and quarter wave symmetry.

b)

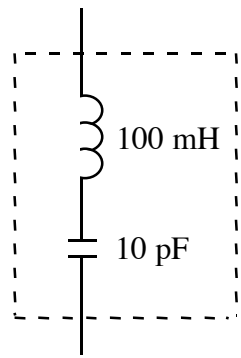

sol'n: (a) $a_v = \text{ave value of } v_i(t) = 0$ since equal positive and negative areas are under the $v_i(t)$ curve.

$v_i(t)$ is symmetric around vertical axis so $v_i(t)$ is an even function. This means we need only even functions—cosine terms—in our Fourier series.

$\therefore b_n = 0$ for all n (no $\sin(n\omega_0 t)$ terms in Fourier series)


If we shift $v_i(t)$ one-half period and flip it upside down, we have $v_i(t)$ again.

Thus, we have half-wave symmetry or, as refer to it, shift-flip symmetry.

$\therefore a_n = 0$ for n even ($b_n = 0$ for n even, too, but we already know $b_n = 0$ all n)

For the question of quarter wave symmetry, we look for symmetry around $T/4$ and $3T/4$. What we find is that $v_i(t)$ is odd around $T/4$ and $3T/4$. In other words, if the vertical axis for $T = 0$ were shifted to $T/4$ or $3T/4$, $v_i(t)$ would be an odd function. If we superimpose the $\cos(n\omega_0 t)$ term for $n = 1$ on $v_i(t)$ and consider the signs of the product $v_i(t)\cos(n\omega_0 t)$, as shown below, we discover that we can calculate a_1 by quadrupling the integral from 0 to $T/4$ in the formula for a_1 :
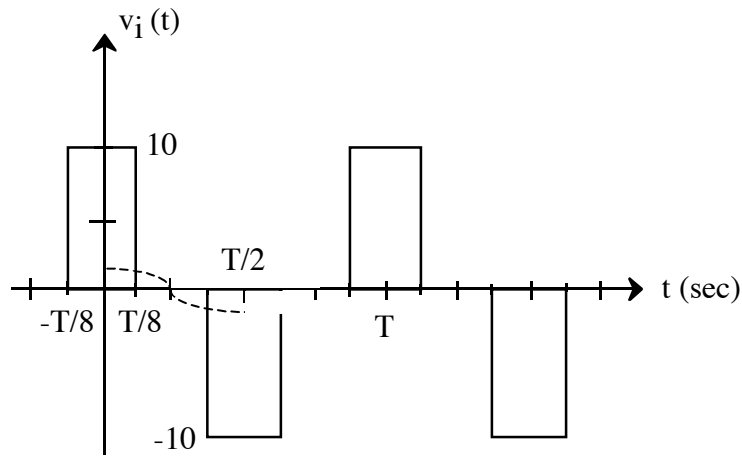
$$a_1 = 4 \cdot \frac{2}{T} \int_0^{T/4} v_i(t) \cos(1 \cdot \omega_o t) dt$$



$$\omega_o = 1 \text{ M rad/sec}$$

The same will hold true for every odd numbered n .

Now we define $v_i(t)$ from 0 to $T/4$:

$$v_i(t) = \begin{cases} 10 & 0 \leq t \leq T/8 \\ 0 & T/8 < t \leq T/4 \end{cases}$$

Thus,

$$a_n = \frac{8}{T} \left[\int_0^{T/8} 10 \cos(n\omega_o t) dt + \underbrace{\int_{T/8}^{T/4} 0 \cdot \cos(n\omega_o t) dt}_{\int 0 dt = 0} \right]$$

or

$$a_n = \frac{8}{T} \int_0^{T/8} 10 \cos(n\omega_o t) dt$$

$$= \frac{8}{T} \frac{10 \sin(n\omega_o t)}{n\omega_o} \Big|_0^{T/8}$$

Now substitute:

$$\omega_o \equiv \frac{2\pi}{T}$$

$$\begin{aligned}
 a_n &= \frac{8}{T} \left[\frac{10 \sin \left(n \frac{2\pi}{T} \right)}{n \frac{2\pi}{T}} \right]_0^{T/8} \\
 &= \frac{40}{\pi n} \left[\sin \left(\frac{2\pi n}{T} \cdot \frac{T}{8} \right) - \sin 0 \right] \\
 a_n &= \frac{40}{\pi n} \sin \left(\frac{\pi n}{4} \right) \quad \text{for } n \text{ odd}
 \end{aligned}$$

If we compute the values of $\sin(\pi n/4)$ for $n = 0, 1, \dots$ we get 0, $1/\sqrt{2}$, 1, $1/\sqrt{2}$, 0, $-1/\sqrt{2}$, $-1/\sqrt{2}$, 0, in a repeating pattern.

Therefore, a_n coefficients for n odd up to the fifth harmonic are:

$$a_1 = \frac{\sqrt{2}}{2} \cdot \frac{40}{\pi}, \quad a_3 = \frac{\sqrt{2}}{2} \cdot \frac{40}{3\pi}, \quad a_5 = \frac{-\sqrt{2}}{2} \cdot \frac{40}{5\pi}$$

Now we convert to phasor form, $a_n \cos(n\omega_0 t) + b_n \sin(n\omega_0 t)$. The time-domain rectangular representation of the n th term of the Fourier series is

$$a_n \cos(n\omega_0 t) + b_n \sin(n\omega_0 t)$$

Recalling that the phasor for pure $\cos()$ is 1 and for pure $\sin()$ is $-j$, the phasor for the n th term of the Fourier series is

$$a_n \text{ (or } a_n \angle 0^\circ) + -jb_n \text{ (or } b_n \angle -90^\circ)$$

Thus, our phasor is $a_n - jb_n$. Incidentally, if we convert to polar form, $A_n \angle \theta_n$, we have:

$$\begin{aligned}
 A_n &= \sqrt{a_n^2 + b_n^2} \\
 \theta_n &= \tan^{-1} \left(\frac{-b_n}{a_n} \right)
 \end{aligned}$$

Here, however, all $b_n = 0$. So we have $A_n = a_n$, $\theta_n = 0^\circ$. In other words, we have only $\cos()$ terms, and the phase angle for $\cos()$ terms is zero since they are real.

$$\begin{aligned}
 A_1 &= a_1 = \frac{20\sqrt{2}}{\pi}, \quad \theta_1 = 0^\circ \\
 A_3 &= a_3 = \frac{20\sqrt{2}}{3\pi}, \quad \theta_3 = 0^\circ
 \end{aligned}$$

$$A_5 = a_5 = \frac{-20\sqrt{2}}{5\pi}, \quad \theta_5 = 0^\circ$$

Note: You may find it easier to derive symmetry results by drawing $v_i(t)$ and the $\cos(\)$ or $\sin(\)$ waveforms on a plot and multiplying them point by point (a rough sketch will do). The area under the curve corresponds to

$$\int_0^T v_i(t) \cos(\) \quad \text{or} \quad \int_0^T v_i(t) \sin(\)$$

If the positive and negative areas under the product curves cancel, a_n (or b_n) = 0.

sol'n: (b) We want a band reject filter with center frequency = $\omega_o = 1\text{M rad/s}$, (see diagram in problem statement), and bandwidth $\beta = 10\text{k rad/s}$ (see problem statement).

Note: By coincidence, in this problem ω_o for the Fourier series (which is determined by the value of the period, T), happens to be the same as the center frequency, ω_o , of the filter (which is determined the values of R , L , and C). This need not always be the case.

Our transfer function is $H(s) \equiv V_o(s)/V_i(s)$.

We use V-divider formula for $V_o(s)$ in terms of $V_i(s)$, letting z_L denote the impedance in the box.


$$V_o(s) = V_i(s) \cdot \frac{z_L}{1\text{ k}\Omega + z_L}$$

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{z_L}{1\text{ k}\Omega + z_L}$$

We need $z_L = 0$ at $\omega = 1\text{M}$ to get

$$\frac{V_o(s = j\omega = j1\text{Mr/s})}{V_i(s = j\omega = j1\text{Mr/s})} = 0$$

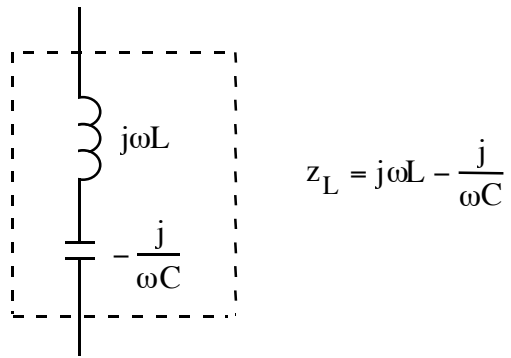We use an L in series with a C to get z cancellation:



To get cancellation, $\omega L = 1/\omega C$ at $\omega = 1\text{M}$ or

$$LC = \frac{1}{\omega^2} = \frac{1}{(1\text{M})^2} = 1 \text{ ps}$$

We have RLC in series, and for a series RLC band-reject filter, we have

$\beta = R/L$. For $\beta = 10\text{k rad/s}$ and $R = 1 \text{ k}\Omega$, we get

$$L = R/\beta = 0.1 \text{ H.}$$

Knowing L , we can now solve for C :

$$C = \frac{1}{L\omega^2} = \frac{1}{0.1\text{H}(1\text{M/s})^2}$$

$$\therefore C = 10 \text{ pF}$$