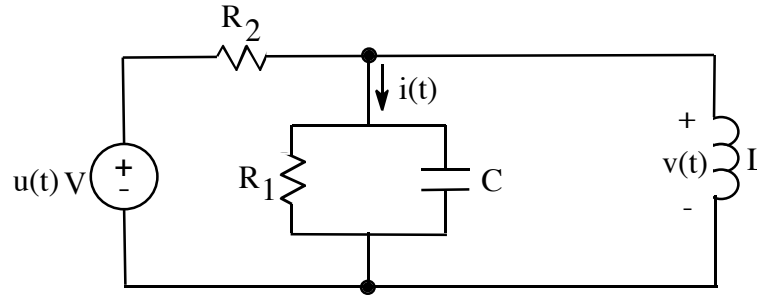


3. (50 points)



The initial energy stored in the circuit is zero.

$$R_2 = 500 \, \Omega$$

$$L = 200 \, \text{mH}$$

- a. Choose values of  $R_1$  and  $C$  to accomplish the following:
  - (1)  $v(t)$  and  $i(t)$  are decaying sinusoids  $90^\circ$  out of phase with each other.
  - (2)  $1/\alpha = T$ , where  $\alpha$  is the exponential decay constant and  $T$  is the period of oscillation of the decaying sinusoid.
- b. With the component values you chose in the circuit, write numerical expressions for  $v(t)$  and  $i(t)$ .

**ans: a)**  $R_1 = 500 \, \Omega$ ,  $C = 32.4 \, \mu\text{F}$

**b)**  $v(t) = 159 e^{-61.7t} \sin(388t) \, \text{mV}$


$$i(t) = 2 e^{-61.7t} \cos(388t) \, \text{mA}$$

**sol'n: (a)** This problem could actually be solved by solving the RLC problem with the general solution to the differential equation for a parallel RLC (obtained by taking the Thevenin equivalent of the voltage source and two resistors). The Laplace transform approach is a bit more straightforward, however, and would also work for input sources other than a step function.

We begin by Laplace transforming the source and circuit components. Since no initial energy is stored in the circuit, we have no extra current or voltage sources in the component models. In general, we would have to include such sources to account for the initial conditions.


$$\mathcal{L}\{u(t)\} = \frac{1}{s} \quad R \xrightarrow{\mathcal{L}} R \quad L \xrightarrow{\mathcal{L}} sL \quad C \xrightarrow{\mathcal{L}} \frac{1}{sC}$$

s-domain model:

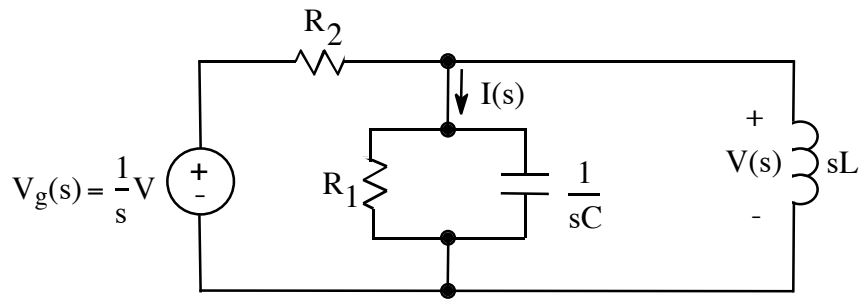

First, we find  $V(s)$ . We can then find  $I(s)$  from  $V(s)$  using Ohm's law.

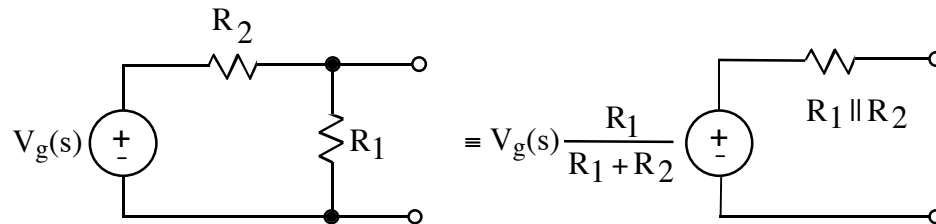Our calculations are cleaner if we use a Thevenin equivalent for  $V_g(s)$ ,  $R_1$ , and  $R_2$ .




**Note:** After we replace  $V_g(s)$ ,  $R_1$ , and  $R_2$  with the Thevenin equivalent, we no longer have a point in the circuit where  $I(s)$  is flowing. Nevertheless, we may still compute  $I(s)$  from  $V(s)$ :

$$I(s) = \frac{V(s)}{R_1 \parallel \frac{1}{sC}}$$

(Note that  $V$  is across  $R_1$  and  $1/sC$  as well as across  $sL$ .)

Our circuit model becomes:

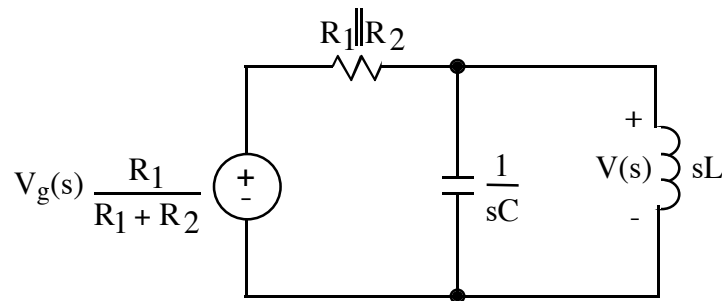

The impedance of the  $L$  and  $C$  in parallel is

$$\frac{1}{sC} \parallel sL = \frac{\frac{sL}{sC}}{\frac{1}{sC} + sL} = \frac{sL}{1 + s^2 LC} = \frac{\frac{s}{C}}{s^2 + \frac{1}{LC}}$$

Use V-divider to find V:

$$V(s) = V_g(s) \frac{R_1}{R_1 + R_2} \cdot \frac{\frac{1}{sC} \parallel sL}{\frac{1}{sC} \parallel sL + R_1 \parallel R_2}$$

Now simplify the expression.

$$V(s) = V_g(s) \frac{R_1}{R_1 + R_2} \cdot \frac{\frac{\frac{s}{C}}{s^2 + \frac{1}{LC}}}{\frac{\frac{s}{C}}{s^2 + \frac{1}{LC}} + R_1 \parallel R_2}$$

Multiply top and bottom by  $s^2 + 1/LC$ :

$$V(s) = V_g(s) \frac{R_1}{R_1 + R_2} \cdot \frac{\frac{s}{C}}{\frac{s}{C} + \left(s^2 + \frac{1}{LC}\right) R_1 \parallel R_2}$$

Rewrite the voltage divider as  $R_1 \parallel R_2 / R_2$ :

$$V(s) = V_g(s) \frac{R_1 \parallel R_2}{R_2} \cdot \frac{\frac{s}{C}}{\frac{s}{C} + \left(s^2 + \frac{1}{LC}\right) R_1 \parallel R_2}$$

Divide top and bottom by  $R_1 \parallel R_2$ :

$$V(s) = V_g(s) \frac{\frac{s}{R_2 C}}{\frac{s}{R_1 \parallel R_2 C} + \left(s^2 + \frac{1}{LC}\right)}$$

Tidy up the denominator and substitute  $V_g = 1/s$ :

$$V(s) = \frac{1}{s} \frac{\frac{s}{R_2 C}}{s^2 + \frac{s}{R_1 \parallel R_2 C} + \frac{1}{LC}} = \frac{\frac{1}{R_2 C}}{s^2 + \frac{s}{R_1 \parallel R_2 C} + \frac{1}{LC}}$$

V has the form of a decaying sine wave:

$$\mathcal{L}\{ke^{-\alpha t} \sin(\omega t)\} = \frac{k\omega}{(s + \alpha)^2 + \omega^2} = \frac{k\omega}{s^2 + 2\alpha s + \alpha^2 + \omega^2}$$

where  $k$  is a real constant and

$$k\omega = \frac{1}{R_2 C}, \quad \alpha^2 + \omega^2 = \frac{1}{LC}, \quad \text{and } 2\alpha = \frac{1}{R_1 \parallel R_2 C}.$$

**ASIDE:** The fundamental form of the polynomials appearing in  $V(s)$  is independent of the value of  $R_1$ ,  $R_2$ ,  $L$ , or  $C$ . If  $I(s)$  is to be  $90^\circ$  out of phase with  $V(s)$ , we must hope that it can be made to have the form of a decaying cosine:

$$\mathcal{L}\{k_2 e^{-\alpha t} \cos(\omega t)\} = \frac{k_2(s + \alpha)}{(s + \alpha)^2 + \omega^2} = \frac{k_2(s + \alpha)}{s^2 + 2\alpha s + \alpha^2 + \omega^2}$$

where  $k_2$  is a real constant (positive or negative).

$I(s)$  is  $V(s)$  divided by the parallel impedance of  $R_1$  and  $C$ :

$$I(s) = \frac{V(s)}{R_1 \parallel \frac{1}{sC}}$$

The parallel impedance of  $R_1$  and  $C$  is

$$R_1 \parallel \frac{1}{sC} = \frac{\frac{R_1}{sC}}{R_1 + \frac{1}{sC}} = \frac{R_1}{1 + sR_1 C}.$$

Substituting for  $V(s)$  gives

$$\begin{aligned} I(s) &= \frac{\frac{\frac{1}{R_2 C}}{s^2 + \frac{s}{R_1 \parallel R_2 C} + \frac{1}{LC}}}{\frac{R_1}{1 + sR_1 C}} = \frac{\frac{1}{R_2 C}}{s^2 + \frac{s}{R_1 \parallel R_2 C} + \frac{1}{LC}} \cdot \frac{1 + sR_1 C}{R_1} \\ I(s) &= \frac{\frac{1 + sR_1 C}{R_1 R_2 C}}{s^2 + \frac{s}{R_1 \parallel R_2 C} + \frac{1}{LC}} \end{aligned}$$

Above, we concluded that  $I(s)$  must be of form

$$I(s) = \frac{k_2(s + \alpha)}{s^2 + 2\alpha s + \alpha^2 + \omega^2}$$

The denominator polynomial in  $s$  is in the correct form. Matching the numerators gives:

$$\frac{1}{R_2} \left( s + \frac{1}{R_1 C} \right) = k_2(s + \alpha)$$

We must have  $k_2 = 1/R_2$  and  $\alpha = 1/R_1 C$ . Earlier, we found

$$\alpha = \frac{1}{2(R_1 \parallel R_2)C}.$$

We conclude that

$$R_1 = 2(R_1 \parallel R_2).$$

The solution to this equation is  $R_1 = R_2 = 500 \, \Omega$ , (value given in problem statement):

$$R_1 = 500 \, \Omega$$

A standard value for  $R_1$  would be  $510 \, \Omega$ .

Now we find  $C$ . We look for an equation with  $C$  as the only unknown. The problem states that  $1/\alpha = T$  or  $\alpha = 1/T = \omega/2\pi$ :

$$\alpha = \frac{1}{2(R_1 \parallel R_2)C} = \frac{1}{2\pi} \omega$$

From the constant term in denominator of  $V(s)$  and  $I(s)$ , as noted earlier, we have an equation involving  $\alpha$  and  $\omega$ :

$$\alpha^2 + \omega^2 = \frac{1}{LC}$$

Substituting for  $\alpha$  and  $\omega$ , we have

$$\left[ \frac{1}{2(R_1 \parallel R_2)C} \right]^2 \left[ 1 + (2\pi)^2 \right] = \frac{1}{LC}.$$

Inverting both sides, we have

$$\left[ 2(R_1 \parallel R_2)C \right]^2 \frac{1}{1 + (2\pi)^2} = LC.$$

Rearranging and canceling one power of  $C$  on both sides gives a value for  $C$ :

$$C = \frac{1 + (2\pi)^2}{4(R_1 \parallel R_2)^2} L$$

$$C = \frac{1 + (2\pi)^2}{4(500\Omega \parallel 500\Omega)^2} 200\text{mH}$$

$$C = \frac{1 + (2\pi)^2}{4 \cdot 250 \cdot 250\Omega^2} 200\text{mH} = \frac{1 + (2\pi)^2}{1\text{k} \cdot 250\Omega^2} 200\text{mH}$$

$$C = \left[1 + (2\pi)^2\right] \frac{200}{250} \frac{\mu\text{H}}{\Omega^2}$$

$$C = 32.4\mu\text{F}$$

A standard value for C would be 33  $\mu\text{F}$ .

**sol'n: (b)** From (a) we know

$$v(t) = ke^{-\alpha t} \sin(\omega t) \text{ and}$$

$$i(t) = k_2 e^{-\alpha t} \cos(\omega t).$$

From (a) we also know

$$k = \frac{1}{R_2 C \omega} = \frac{1}{R_2 C \frac{2\pi}{\alpha}} = \frac{R_2 C}{R_2 C \cdot 2\pi} = \frac{1}{2\pi} \text{ and } k_2 = \frac{1}{R_2}.$$

$$k = \frac{1\text{V}}{2\pi} = 159 \text{ mV}$$

$$k_2 = \frac{1\text{V}}{500\Omega} = 2 \text{ mA}$$

Note: We use 1V in the numerators because  $V_g(t)$  actually transforms to 1V/s rather than 1/s. We leave out the 1V to avoid clutter and confusion in the calculations. We might mistakenly think of the 1V as V(s).

For  $\alpha$  and  $\omega$ , we have

$$\alpha = \frac{1}{500\Omega \cdot 32.4 \mu\text{F}} = 61.7/\text{s} \text{ and } \omega = 2\pi\alpha = 388\text{rad/s}.$$

Substituting numerical values for  $k$ ,  $k_2$ ,  $\alpha$ , and  $\omega$  in the time-domain forms for  $i(t)$  and  $v(t)$  gives our final answer.

$$v(t) = 159 e^{-61.7t} \sin(388t) \text{ mV}$$

$$i(t) = 2 e^{-61.7t} \cos(388t) \text{ mA}$$

Consistency check:

$$\begin{aligned} i(t) &= i_{R1} + i_C = \frac{v(t)}{R_1} + C \frac{dv(t)}{dt} = \frac{k}{R_1} e^{-\alpha t} \sin(\omega t) + C \frac{d}{dt} [k e^{-\alpha t} \sin(\omega t)] \\ &= \frac{k}{R_1} e^{-\alpha t} \sin(\omega t) + Ck [(-\alpha) e^{-\alpha t} \sin(\omega t) + e^{-\alpha t} \cos(\omega t)] \\ &= k \left[ \frac{1}{R_1} + (-\alpha C = -\frac{\omega}{R_1}) \right] e^{-\alpha t} \sin(\omega t) + (Ck = \frac{1}{R_1}) e^{-\alpha t} \cos(\omega t) \\ &= \frac{1}{R_1} e^{-\alpha t} \cos(\omega t) = i(t) \quad \checkmark \quad (\text{since } R_1 = R_2) \end{aligned}$$