
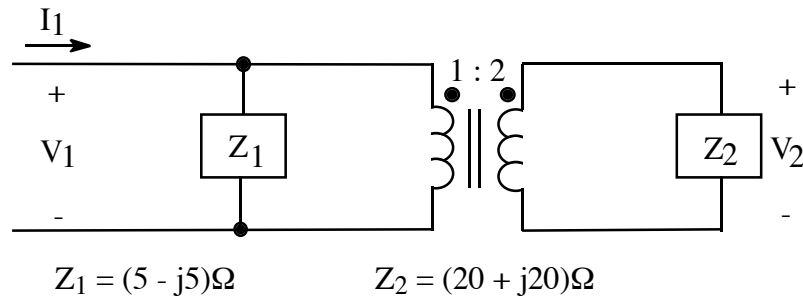



4. (50 points)

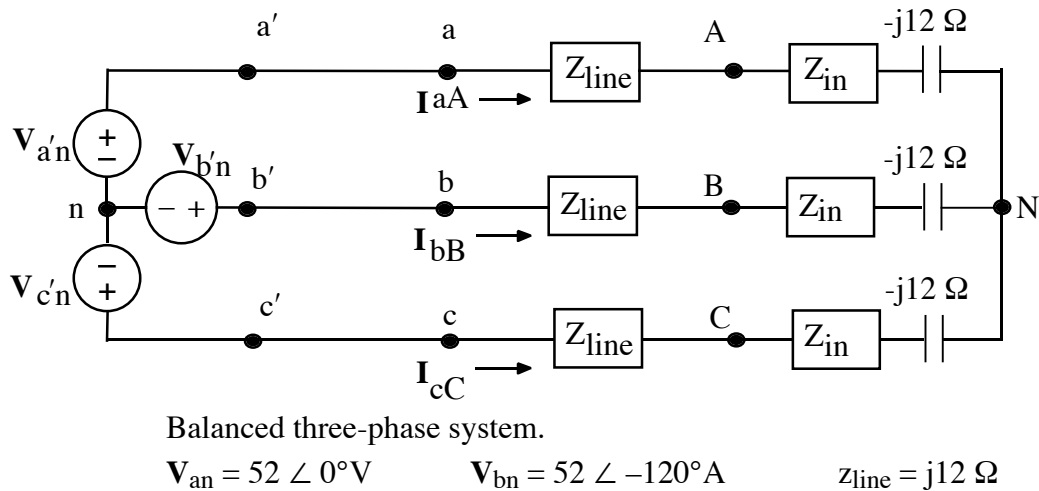

- Find the input impedance,  $z_{in} = V_1/I_1$ , for the above circuit.
- Using  $z_{in}$  from (a), find a numerical expression for  $V_{AB}$  in the circuit below.

ans: a)  $z_{in} = 5 \Omega$ b)  $V_{AB} \approx 234 \angle -37.38^\circ \text{V}$ 

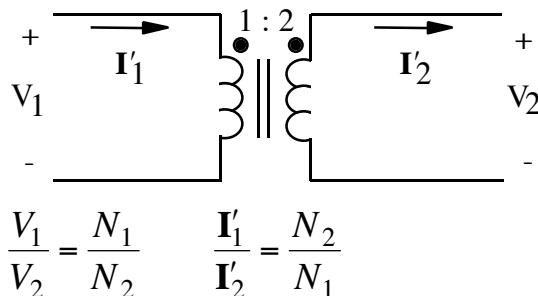
**sol'n:** (a) Transformer is ideal. To distinguish currents in the transformer itself from other currents, we use a prime to denote the transformer currents. The current flowing into the dot on the primary side is  $I'_1$ , and the current flowing out of the dot on the secondary side is  $I'_2$ :



Using the above model, we can derive the formula (or we can just look up the formula) for secondary impedance reflected into the primary:

$$z_r = \left( \frac{N_1}{N_2} \right)^2 z_2$$

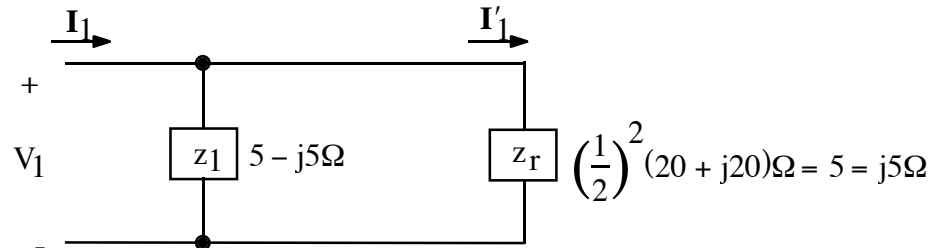
Our model, given  $N_1/N_2 = 1/2$  turns ratio, is:



$$z = z_1 \parallel z_r = (5 - j5) \parallel (5 + j5) \Omega$$

$$z = \frac{(5 - j5)(5 + j5)}{5 - j5 + 5 + j5} = \frac{5^2 + 5^2}{10} = 5 \Omega$$

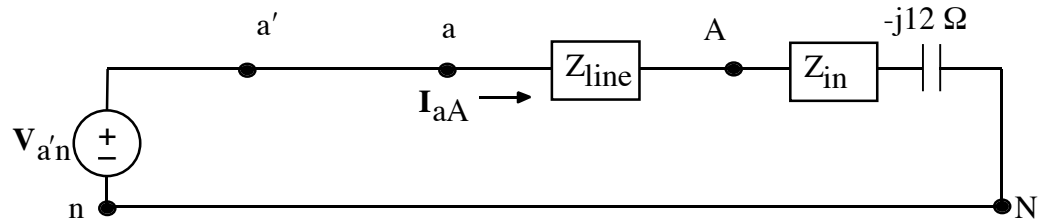**sol'n: (b)** Our first step is to convert our circuit to a Y – Y form so we can use a single-phase equivalent model. In this problem, the circuit is already in Y – Y form and we may draw the single-phase equivalent directly:




We find  $V_{AN}$  and then calculate  $V_{AB}$  using phasor diagrams. We obtain  $V_{AN}$  from the voltage divider formula:

$$V_{AN} = V_{a'n} \frac{z_{in} - j12\Omega}{z_{line} + z_{in} - j12\Omega}$$

$$V_{AN} = 52\angle 0^\circ V \frac{5\Omega - j12\Omega}{j12\Omega + 5\Omega - j12\Omega} = 52\angle 0^\circ V \frac{5\Omega - j12\Omega}{5\Omega}$$

$$V_{AN} = 52\angle 0^\circ V \frac{13\angle -67.38^\circ \Omega}{5\Omega}$$

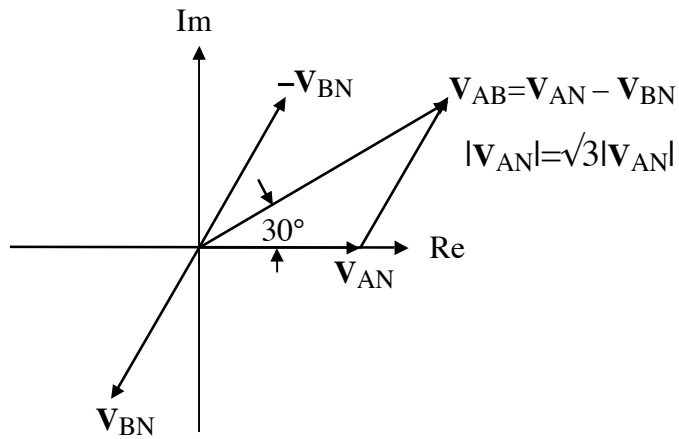We use a phasor diagram to relate  $V_{AN}$  to  $V_{AB}$ . The diagram shows the relationship between  $V_{AN}$  and  $V_{AB}$ , and we assume  $V_{AN}$  has phase angle zero so we can find the relative phase angle of  $V_{AB}$ .



From the diagram, we deduce that

$$\mathbf{V}_{AB} = \mathbf{V}_{AN} \cdot \sqrt{3} \angle 30^\circ$$

Plugging in the value of  $\mathbf{V}_{AN}$  gives the numerical value of  $\mathbf{V}_{AB}$ .

$$\mathbf{V}_{AB} = 52 \angle 0^\circ \text{ V} \frac{13 \angle -67.38^\circ \Omega}{5 \Omega} \sqrt{3} \angle 30^\circ = \frac{52 \cdot 13 \cdot \sqrt{3}}{5} \angle -37.38^\circ \text{ V}$$

$$\mathbf{V}_{AB} \approx 234 \angle -37.38^\circ \text{ V}$$