
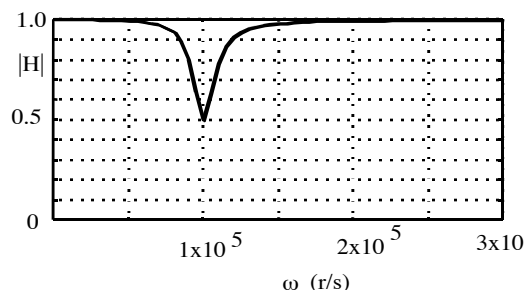


1. (30 points)

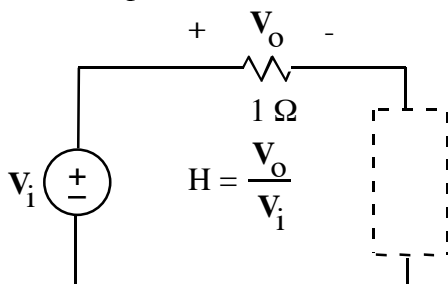


Using not more than one each R, L, and C, design a circuit to go in the dashed-line box that will produce the $|H|$ vs. ω shown above, that is:

$$|H| = 0.5 \text{ at } \omega = 10^5 \text{ rps}$$

$$|H| = 1 \text{ at } \omega = 0$$

$$|H| \rightarrow 1 \text{ as } \omega \rightarrow \infty$$

Specify values of R, L, and C, and show how they would be connected in the circuit. Note that a bandwidth is not specified, and you do not have to satisfy any more than the three requirements specified above.

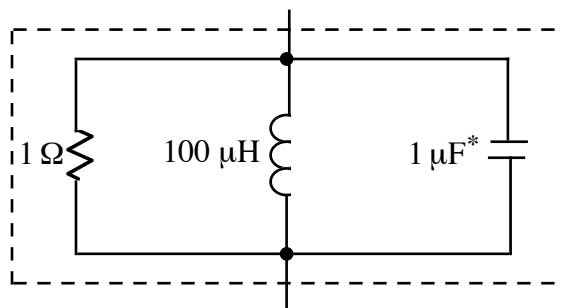Ans:

* Any LC = 100 ps is acceptable (if part values are practical).

Sol'n:

Given the frequency response plot, we want something resembling a band-reject filter. Since V_o is measured across R_1 , rather than across the dashed box, we want an L and C configuration that has maximum impedance at resonant frequency. Thus, we need an L in parallel with a C inside the dashed box.

If we denote dashed box by z , we have

$$V_o = V_i \cdot \frac{R_1}{R_1 + z} \quad (\text{V-divider}). \quad \therefore H(j\omega) \equiv \frac{V_o}{V_i} = \frac{R_1}{R_1 + z}$$

Note that if

$$z = j\omega L \parallel \frac{1}{j\omega C} = \frac{j\omega L}{j\omega C} = \frac{L/C}{j\omega L + \frac{1}{j\omega C}}$$

then, at ω_o , we have $j\omega L = -\frac{1}{j\omega C}$.

$$\text{So } z = \frac{L/C}{0} \Big|_{\omega=\omega_o} = \infty \text{ at } \omega = \omega_o \equiv \frac{1}{\sqrt{LC}}.$$

$$\text{Thus, } |H(j\omega)|_{\omega=\omega_o} = \frac{R_1}{R_1 + \infty} = 0.$$

We want a value of 1/2, which we'll correct later on. We do have the desired response at high and low frequencies:

$$\text{At } \omega = 0, \quad z = \frac{L/C}{j \cdot 0 \cdot L + \frac{1}{j \cdot 0 \cdot C}} = \frac{L/C}{0 + \infty} = 0$$

$$\therefore |H(j\omega)|_{\omega=0} = \left| \frac{R_1}{R_1 + z} \right| = \left| \frac{R_1}{R_1} \right| = 1 \quad \checkmark$$

$$\text{At } \omega \rightarrow \infty, \quad z = \frac{L/C}{j \cdot \infty \cdot L + \frac{1}{j \cdot \infty \cdot C}} = \frac{L/C}{j \cdot \infty \cdot L + 0} = 0$$

$$\therefore |H(j\omega)|_{\omega \rightarrow \infty} = \left| \frac{R_1}{R_1 + z} \right| = \left| \frac{R_1}{R_1} \right| = 1 \quad \checkmark$$

The remaining problem is to add an R_2 in the dashed box so that

$|H(j\omega)|_{\omega=\omega_o} = \frac{1}{2}$ instead of zero. For the parallel L and C, we have

$$|H(j\omega)| = \left| \frac{R_1}{R_1 + R_2} \right| \text{ at } \omega = \omega_o.$$

If we put R_2 in series with the L parallel C, then we would still have $z = R_2 + \infty = \infty$, at $\omega = \omega_o$. Thus, we must try something else.

If we put R_2 in parallel with L parallel C, then we have $z = R_2 \parallel \infty = R_2$ at $\omega = \omega_o$. This gives

$$|H(j\omega)| = \left| \frac{R_1}{R_1 + R_2} \right| \text{ at } \omega = \omega_o.$$

We use $R_2 = R_1 = 1\Omega$ to get the required $|H(j\omega)| = 1/2$ at $\omega = \omega_o$.

Now we must verify that we have the correct gain at $\omega = 0$ and $\omega \rightarrow \infty$. For both cases we have

$j\omega L \parallel 1/j\omega C = 0$. The extra R_2 in parallel still gives $z = 0$, as desired.

$$\therefore R_2 = 1\Omega.$$

Finally, we need $\omega_o = 10^5$ rad/s (dip in plot). Since we have L parallel C even with the addition of R_2 , we have the standard resonant frequency:

$$\omega_o = \frac{1}{\sqrt{LC}}.$$

Therefore, we have

$$LC = \frac{1}{\omega_o^2} = \frac{1}{(10^5)^2} = \frac{100}{10^{12}} = 100 \text{ ps}^2.$$

Any $LC = 100 \text{ ps}^2$ is acceptable unless the L or C are too large or small to be reasonable. For example, one practical solution is

$C = 1 \mu\text{F}$ and $L = 100 \mu\text{H}$.