



3. (30 points)



$$v_g(t) = \frac{16}{\pi} \sum_{n \text{ odd}}^{\infty} \frac{1}{n} \sin(n\omega_0 t)$$

Write the time-domain expression of v(t) for the first through third harmonics.

Ans: $v(t) = 1.6 \cos (300 k t - 69.4^{\circ}) V$

Sol'n: Summary of steps expanded upon below:

- 1. We turn each frequency of $v_g(t)$ into a phasor.
- 2. We pass each frequency, $k\omega_o$, through the circuit by multiplying by the transfer function H(jk ω_o).
- 3. The result is the phasor for frequency $k\omega_0$ in the output signal.
- 4. We convert the output signal phasor back to the time domain, (through the 1st 3 harmonics).

Note: We only have 1st and 3rd harmonics to worry about since we only have odd harmonics in $v_g(t)$ and we were only asked to find the output signal's 1st through 3rd harmonics.

1. We turn each frequency of $v_g(t)$ into a phasor.

$$k = 1: \quad \frac{16}{\pi} \sin \left(\omega_o t \right) \xrightarrow{\mathbf{P[1]}} -j \frac{16}{\pi} \text{ or } \frac{16}{\pi} \angle -90^\circ$$
$$k = 3: \quad \frac{16}{\pi} \frac{1}{3} \sin \left(3\omega_o t \right) \xrightarrow{\mathbf{P[1]}} -j \frac{16}{3\pi} \text{ or } \frac{16}{3\pi} \angle -90^\circ$$

2. We pass each frequency, $k\omega_o$, through the circuit by multiplying by the transfer function H(jk ω_o).

$$H(j\omega) = \frac{V}{V_g} = \frac{j\omega + \frac{1}{j\omega C}}{R + j\omega L + \frac{1}{j\omega C}}$$
(V-divider)

k = 1:

$$H(j\omega_o) = \frac{(j\omega_o)^2 LC + 1}{j\omega_o RC + (j\omega_o)^2 LC + 1}$$
$$H(j\omega_o) = \frac{-(100k)^2 0.1m \ 1\mu + 1}{j100k \ 10k \ 1\mu - (100k)^2 0.1m \ 1\mu + 1}$$
$$H(j\omega_o) = \frac{-100^2 \cdot 0.1m + 1}{j1k - 100^2 0.1m + 1} = \frac{0}{j1k} = 0$$

In this case, the L and C together behave like a wire at frequency ω_0 . The voltage drop across the wire is zero, as is the circuit output. Consequently, $H(j\omega_0) = 0$.

Note: In this case, the ω_0 for the $v_g(t)$ Fourier series happens to be the same as the center (or resonant, or characteristic) frequency of the L and C:

$$\omega_{\rm o} = \sqrt{\frac{1}{LC}}$$

Typically, the ω_o for the Fourier series is different from the ω_o for an L and C.

$$k = 3: \quad H(j3\omega_{0}) = \frac{-3^{2} + 1}{j3k - 3^{2} + 1} = \frac{-8}{j3k - 8}$$
$$= \frac{8}{8 - j3k} = \frac{1}{1 - j\frac{3}{8}k} = \frac{1}{\frac{\sqrt{73}}{8} - 20.6^{\circ}}$$
$$= \frac{8}{\sqrt{73}} \angle 20.6^{\circ}$$

3. The result is the phasor for frequency $k\omega_0$ in the output signal.

Input phasor is

$$V_{i3} = -j\frac{16}{3\pi} = \frac{16}{3\pi} \angle -90^{\circ}.$$

Output phasor is

$$V_{o3} = V_{i3}H(j3w_o) = \frac{16}{3\pi} \angle -90^\circ \cdot \frac{8}{\sqrt{73}} \angle 20.6^\circ.$$
$$V_{o3} = \frac{128}{3\pi\sqrt{73}} \angle -69.4^\circ$$

4. We convert the output signal phasor back to the time domain, (through the 1st 3 harmonics, of which only the third harmonic is nonzero).

$$v(t) = \frac{128}{3\pi\sqrt{73}} \cos (300 \text{ kt} - 69.4^{\circ}) \text{ V}$$