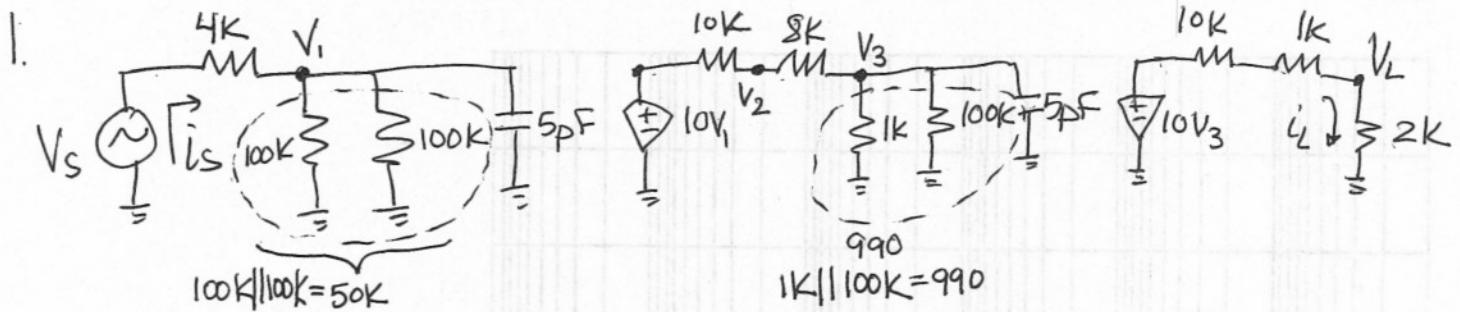


Homework 3 Solution



$$R \parallel \frac{1}{Cs} = \frac{R(\frac{1}{Cs})}{R + \frac{1}{Cs}} = \frac{R}{RCs + 1}$$

$$V_L = \frac{10V_3(2K)}{13K} = \frac{20}{13} V_3$$

$$V_3 = \frac{10V_1 (990 \parallel \frac{1}{5p \cdot s})}{(990 \parallel \frac{1}{5ps}) + 18K} = \frac{10(990)}{(990(5ps) + 1)} = \frac{10(990) \cdot V_1}{990 + 8.91e^{-5}s + 18K}$$

$$= \frac{990}{990(5ps) + 1} + \frac{18K(990(5ps) + 1)}{(990(5ps) + 1)} = \frac{990 + 8.91e^{-5}s + 18K}{990(5ps) + 1}$$

$$V_3 = \frac{9,900 \cdot V_1}{18,990(1 + \frac{8.91e^{-5}s}{18,990})} = \frac{0.52 \cdot V_1}{(1 + \frac{s}{213M})}$$

$$V_1 = \frac{V_s (50K \parallel \frac{1}{5ps})}{(50K \parallel \frac{1}{5ps}) + 4K} = \frac{V_s (50K)}{50K(5ps) + 1} = \frac{V_s(50K)}{50K + 4K(50K(5ps) + 1)} = \frac{V_s(50K)}{50K(1 + \frac{1e^{-3}s}{54K})} = \frac{0.93 \cdot V_s}{(1 + \frac{s}{54M})}$$

$$\frac{V_L}{V_s} = \frac{20}{13} \cdot \frac{0.52}{(1 + \frac{s}{213M})} \cdot \frac{0.93}{(1 + \frac{s}{54M})} = \frac{0.74}{(1 + \frac{s}{213M})(1 + \frac{s}{54M})}$$

Note that these are in rad/sec - NOT Hz

$$3. \quad b. \quad i_L = \frac{V_L}{2K}$$



$$i_s = \frac{V_s}{4K + (50K \parallel \frac{1}{5ps})} = \frac{V_s}{4K + \frac{50K}{50K(5p)s + 1}} = \frac{V_s}{4K \frac{(50K(5p)s + 1) + 50K}{(50K(5p)s + 1)}}$$

$$i_s = \frac{V_s \left(\frac{s}{4M} + 1 \right)}{54K \left(\frac{1e^{-3}s}{54K} + 1 \right)} = \frac{V_s \left(\frac{s}{4M} + 1 \right)}{54K \left(\frac{s}{54M} + 1 \right)}$$

$$\frac{i_L}{i_s} = \frac{\left(\frac{V_L}{2K} \right)}{\left(\frac{V_s \left(\frac{s}{4M} + 1 \right)}{54K \left(\frac{s}{54M} + 1 \right)} \right)} = \frac{V_L 54K \left(\frac{s}{54M} + 1 \right)}{2K \cdot V_s \cdot \left(\frac{s}{4M} + 1 \right)}$$

$$\frac{i_L}{i_s} = \frac{V_L}{V_s} \cdot \frac{27 \left(\frac{s}{54M} + 1 \right)}{\left(\frac{s}{4M} + 1 \right)} = \frac{0.74 \cdot 27 \left(\frac{s}{54M} + 1 \right)}{\left(1 + \frac{s}{213M} \right) \left(1 + \frac{s}{54M} \right) \left(\frac{s}{4M} + 1 \right)}$$
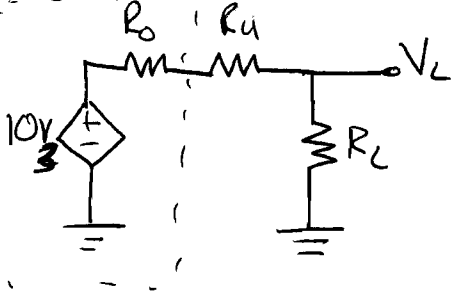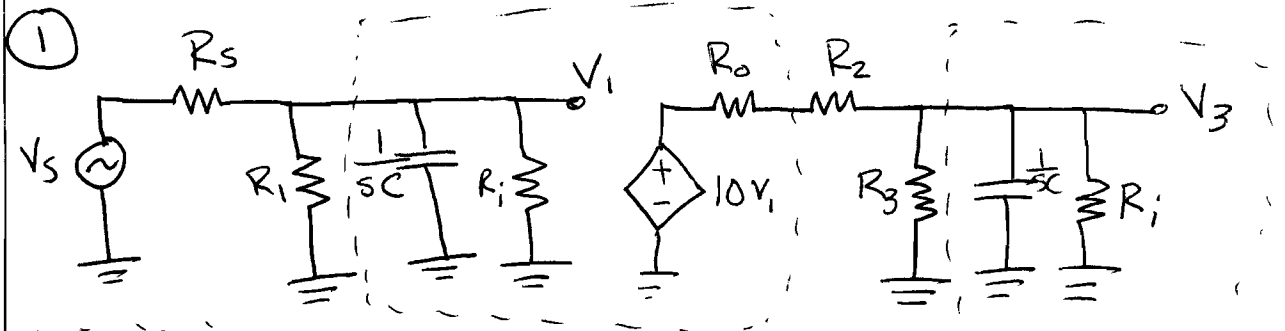
$$\frac{i_L}{i_s} \approx \frac{20}{\left(1 + \frac{s}{213M} \right) \left(\frac{s}{4M} + 1 \right)}$$



- $R_5 = 4k\Omega$ $R_1 = 100k\Omega$ $R_i = 100k\Omega$
- $C = 5pF$ $R_0 = 10k\Omega$ $R_2 = 8k\Omega$
- $R_3 = 1k\Omega$ $R_4 = 1k\Omega$ $R_L = 2k\Omega$

$$\frac{V_1}{V_s} = \frac{R_1 \parallel R_i \parallel \frac{1}{sC}}{R_5 + R_1 \parallel R_i \parallel \frac{1}{sC}} = \frac{\frac{1}{\frac{1}{R_1} + \frac{1}{R_i} + sC}}{R_5 + \frac{1}{\frac{1}{R_1} + \frac{1}{R_i} + sC}} = \frac{1}{R_5 \left(\frac{1}{R_1} + \frac{1}{R_i} + sC \right) + 1}$$

$$\frac{V_1}{V_s} = \frac{1}{sCR_5 + \frac{R_5 R_i}{R_1 R_i} + \frac{R_5 R_1}{R_i R_1} + \frac{R_5 R_i}{R_1 R_i}} = \frac{R_1 R_i}{sCR_5 R_1 R_i + (R_5 R_i + R_5 R_1 + R_1 R_i) + 1}$$

$$\frac{V_3}{V_1} = 10 \frac{R_3 \parallel R_i \parallel \frac{1}{sC}}{(R_0 + R_2) + R_3 \parallel R_i \parallel \frac{1}{sC}} = \text{Follow the same algebra as before where } R_1 = R_3, R_5 = (R_0 + R_2)$$


$$\frac{V_3}{V_1} = 10 \frac{R_3 R_i}{sC(R_0 + R_2) R_i R_3 + ((R_0 + R_2) R_i + (R_0 + R_2) R_3 + R_3 R_i) + 1}$$

$$\frac{V_L}{V_3} = 10 \frac{R_L}{R_0 + R_4 + R_L}$$

$$\therefore \frac{V_L}{V_s} = 10 \frac{R_L}{R_0 + R_4 + R_L} \cdot 10 \frac{\frac{R_3 R_i}{(R_0 + R_2)(R_i + R_3) + R_3 R_i}}{s \frac{C R_i R_3 (R_0 + R_2)}{(R_0 + R_2)(R_i + R_3) + R_3 R_i} + 1} \cdot \frac{R_1 R_i}{(R_5 (R_i + R_1) + R_1 R_i) + 1}$$

$$\therefore \frac{V_L}{V_s} = \frac{20}{13} \cdot \frac{0.550}{\frac{s}{202M} + 1} \cdot \frac{0.926}{\frac{s}{54M} + 1}$$

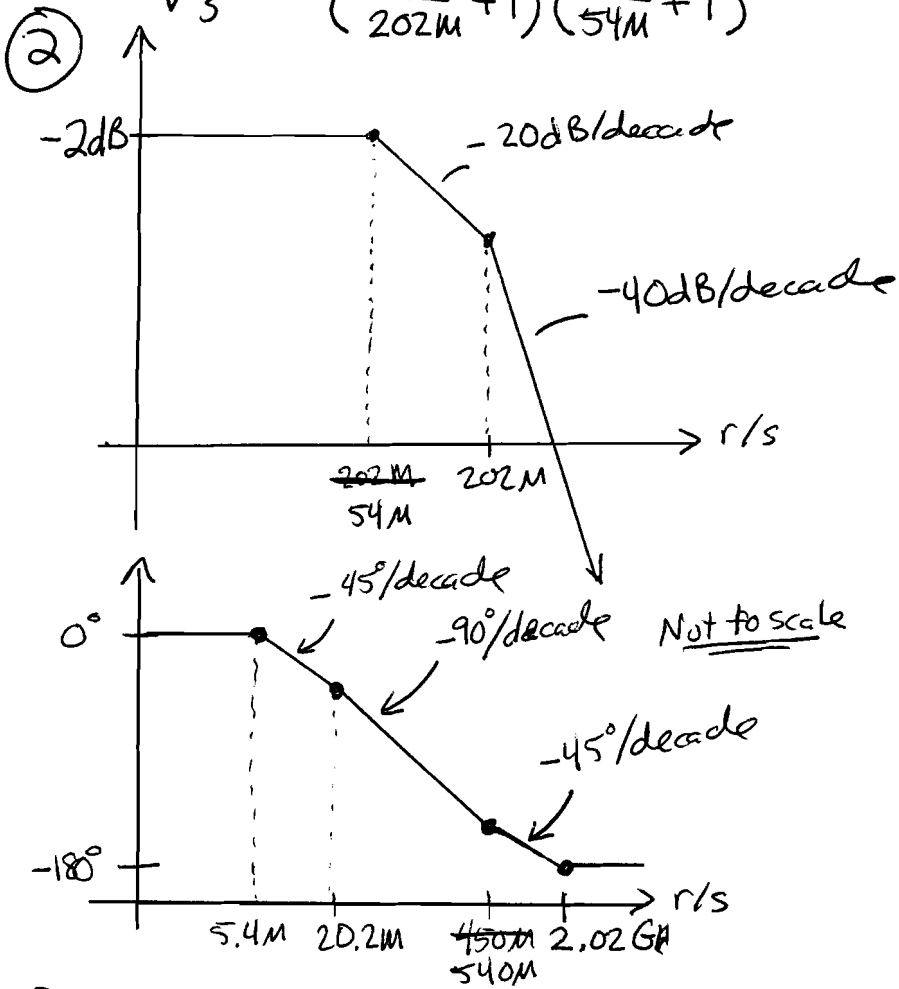$\therefore \frac{V_L}{V_S} = \frac{0.784}{\left(\frac{s}{202M} + 1\right)\left(\frac{s}{54M} + 1\right)}$



③ a) Gain = $0.784 V/V$ or $-2.11 dB$

c) $f_{3dB}: \left| \frac{1}{(j\omega/202M + 1)(j\omega/54M + 1)} \right| = 0.707$

$$\Rightarrow \left(\frac{\omega^2}{(202M)^2} + 1 \right) \left(\frac{\omega^2}{(54M)^2} + 1 \right) = 2$$


$$\Rightarrow \omega^4 + 4.372 \times 10^{16} \omega^2 - 1.190 \times 10^{32} = 0$$



Applying the solution to the quadratic twice and taking the only positive, real result, we find that:

$$f_{3dB} = \frac{50.7 \text{ Mr/s}}{2\pi} = \boxed{8.07 \text{ MHz}}$$

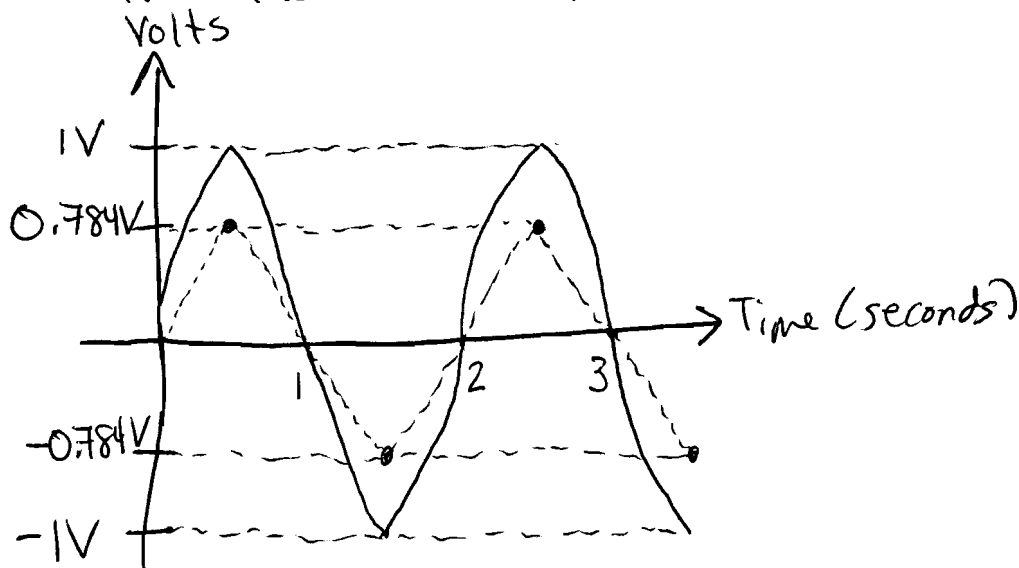
d) At $\pi \text{ rad/s}$, both poles are negligible,

so the amplification is an attenuation by the factor 0.784.



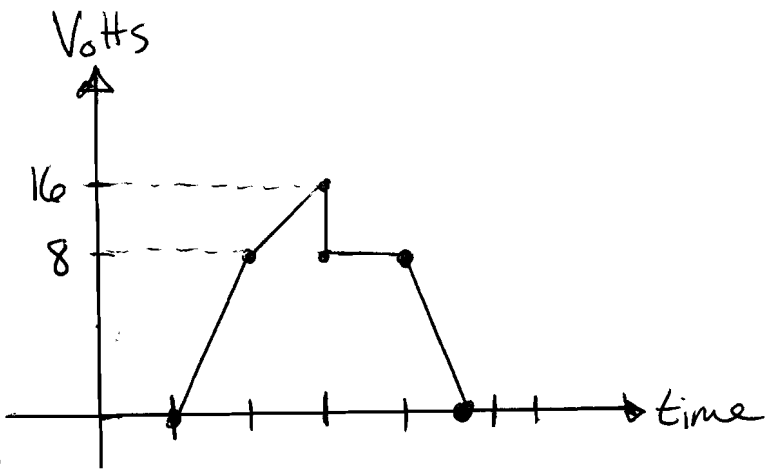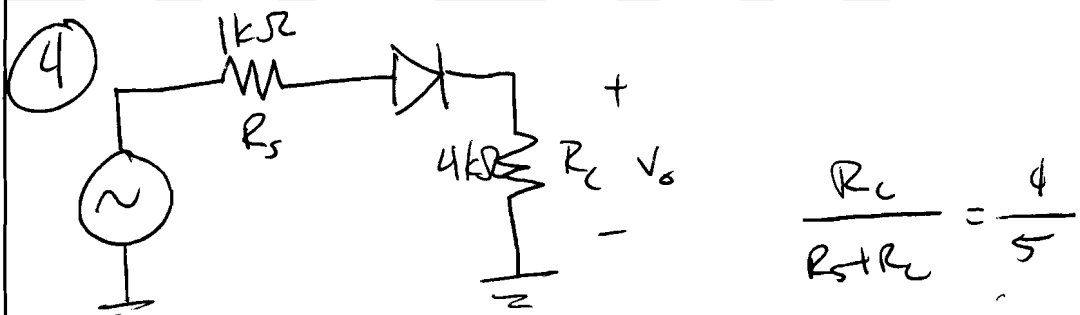

5 Assume D_1 off and D_2 ON

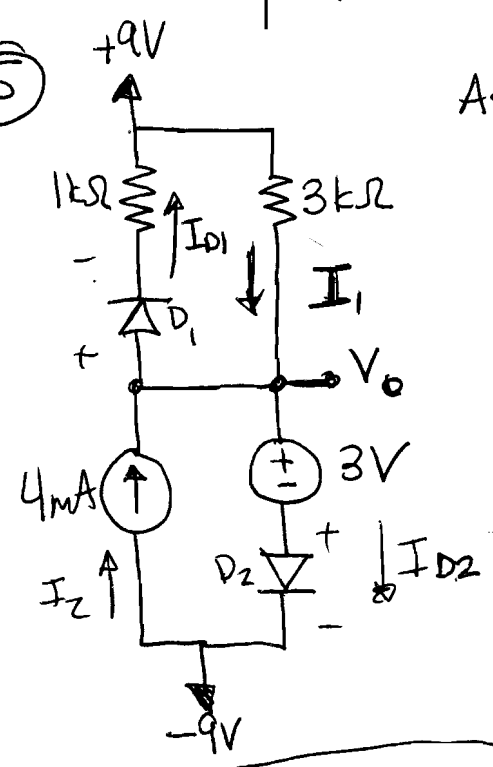

Then $I_1 = \frac{9V - (-5.3V)}{3k\Omega} = \frac{14.3}{3k\Omega} = 4.6mA$


$V_{D2} = 0.7V$, $I_{D2} = I_1 + 4mA = 8.6mA$
Diode ON

$V_{D1} = -5.3V - 9V = -14.3V$
 $I_{D1} = 0A$ Diode OFF

$I_1 = 4.6mA$
 $I_2 = 4mA$
 $V_o = -9V + 3.7 = -5.3V$
 $I_{D1} = 0A$
 $I_{D2} = 8.6mA$

Since this works, it must be the solution.

6. Assume D2, D3 off and D1 on

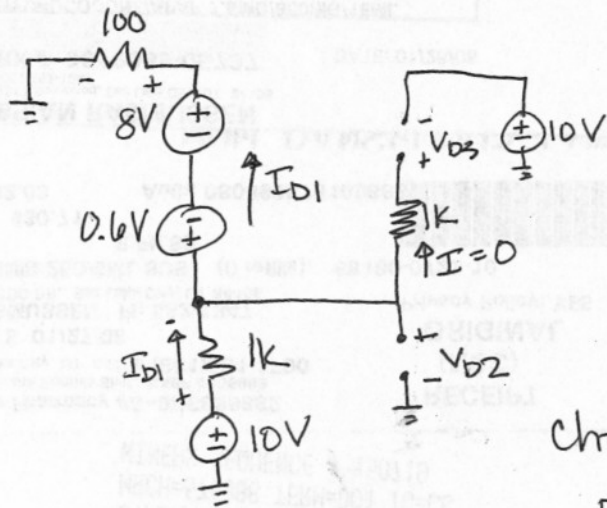

$$+10V - I_{D1}(1k) - 0.6 + 8 - I_{D1}(100) = 0$$

$$I_{D1} = \frac{10 - 0.6 + 8}{1k + 100} = \boxed{15.8 \text{ mA}}$$

$$\boxed{I_{D3} = I_{D2} = 0}$$

check assumptions:

D1 on: $I_{D1} > 0$ ✓ correct


D2 off: $+10 - I_{D1}(1k) - V_{D2} = 0$

correct ✓ $V_{D2} = 10 - 15.8m(1k) = \underline{-5.8V} < 0.6V$

D3 off: $+10 - I_{D1}(1k) - 0 - V_{D3} - 10 = 0$

$V_{D3} = 10 - 15.8 - 10 = \underline{-15.8V} < 0.6V$ ✓ correct

⑥

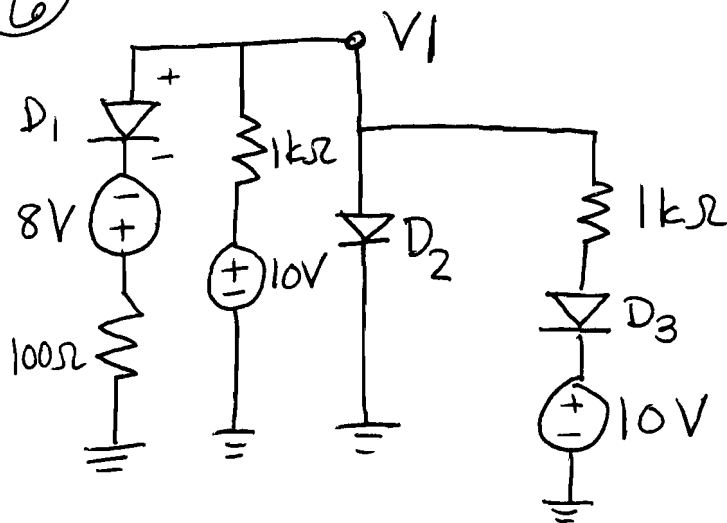Assumptions D_3, D_2 off. D_1 on.With D_1 on, apply node voltage:

$$\frac{V_1 - 10V}{1k\Omega} + \frac{V_1 - 0.6 + 8V}{100\Omega} = 0A$$

$$V_1 \left(\frac{1}{1k\Omega} + \frac{1}{100\Omega} \right) = \frac{10}{1k} + \frac{-7.4}{100} = -0.063 \frac{V}{\Omega}$$

$$\therefore V_1 = -5.73V$$

$$a) I_{D1} = \frac{V_1 - 0.6 + 8V}{100\Omega} = 16.7mA$$

$$b) I_{D2} = 0A \quad (D_2 \text{ off})$$

$$c) I_{D3} = 0A \quad (D_3 \text{ off})$$


Checks on Diodes: $D_1 \Rightarrow V_1 - (-8V + 16.7mA \cdot 100\Omega) = V_{D1}$
 $\therefore V_{D1} = 0.6V$ I_{D1} correct ✓

$D_2 \Rightarrow I_{D2} = 0A$ $V_{D2} = V_1 - 0 = -5.73V$ correct ✓

$D_3 \Rightarrow I_{D3} = 0A$ $V_{D3} = V_1 - 10 = -15.73V$ correct ✓

⑦

a) Since V_o is not attached to a load, and D_2 is reverse biased, there can be no current flowing through either diode, (no loops exist).

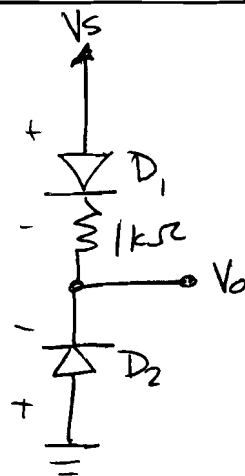DC-circuit

$$I_{D1} = I_{D2} = 0A$$

D_1 is forward-biased

D_2 is reverse-biased

$$b) V_{ODC} = 10V - 0.5V = 9.5V$$

$$\therefore V_{ODC} = 9.5V$$

$$c) r_d = \frac{nV_T}{I_D} = \frac{3(25mV)}{0} = \infty \Omega$$

$$i_d = \frac{V_d}{\infty} = 0A$$

$$d) v_o = \sin(10kt) V$$

e) Total Output for V_o

$$V_o = 9.5 + \sin(10kt) V$$

AC circuit