

Complex Numbers

ECE 3510

A.Stolp
10/18/00
2/2/06

$$j = \sqrt{-1} \quad \text{the imaginary number}$$

Rectangular Form $\mathbf{A} = a + b \cdot j$

$$\operatorname{Re}(\mathbf{A}) = a \quad \operatorname{Im}(\mathbf{A}) = b$$

Polar Form $\mathbf{A} = A \cdot e^{j\theta}$

$$\operatorname{Re}(\mathbf{A}) = A \cdot \cos(\theta) \quad \operatorname{Im}(\mathbf{A}) = A \cdot \sin(\theta)$$

Conversions $\mathbf{A} = |\mathbf{A}| = \sqrt{a^2 + b^2}$ $\theta = \arg(\mathbf{A}) = \tan^{-1}\left(\frac{b}{a}\right)$

$$a = A \cdot \cos(\theta) \quad b = A \cdot \sin(\theta)$$

$$\mathbf{A} = A \cdot e^{j\theta} = A \cdot \cos(\theta) + A \cdot \sin(\theta) \cdot j \quad \mathbf{A} = a + b \cdot j = \left(\sqrt{a^2 + b^2}\right) \cdot e^{j \cdot \tan^{-1}\left(\frac{b}{a}\right)}$$

Special Cases $j := \sqrt{-1} = e^{j \cdot 90^\circ}$ $\frac{1}{j} = -j = e^{-j \cdot 90^\circ}$ $e^{j \cdot 0^\circ} = 1$ $e^{-j \cdot 180^\circ} = e^{-j \cdot 180^\circ} = -1$
 $j \cdot e^{j\theta} = e^{j \cdot (\theta + 90^\circ)}$

Define a 2nd number: rect: $\mathbf{D} = c + d \cdot j$ polar: $\mathbf{D} = D \cdot e^{j\phi}$

Equality $\mathbf{A} = \mathbf{D}$ if and only if $a = c$ and $b = d$ OR $\mathbf{A} = \mathbf{D}$ and $\theta = \phi$

Addition and Subtraction $\mathbf{A} + \mathbf{D} = (a + b \cdot j) + (c + d \cdot j) = (a + c) + (b + d) \cdot j$

$$\mathbf{A} - \mathbf{D} = (a + b \cdot j) - (c + d \cdot j) = (a - c) + (b - d) \cdot j$$

Convert polars to rectangular form first

Multiplication and Division $\mathbf{A} \cdot \mathbf{D} = (a + b \cdot j) \cdot (c + d \cdot j) = (a \cdot c - b \cdot d) + (b \cdot c + a \cdot d) \cdot j$

$$\text{Rectangular: } \frac{\mathbf{A}}{\mathbf{D}} = \frac{a + b \cdot j}{c + d \cdot j} = \frac{a + b \cdot j \cdot c - d \cdot j}{c + d \cdot j \cdot c - d \cdot j} = \frac{a \cdot c + b \cdot d}{c^2 + d^2} + \frac{b \cdot c - a \cdot d}{c^2 + d^2} \cdot j$$

$$\text{Polar: } \mathbf{A} \cdot \mathbf{D} = A \cdot e^{j\theta} \cdot D \cdot e^{j\phi} = A \cdot D \cdot e^{j(\theta + \phi)}$$

$$\frac{\mathbf{A}}{\mathbf{D}} = \frac{A \cdot e^{j\theta}}{D \cdot e^{j\phi}} = \frac{A}{D} \cdot e^{j(\theta - \phi)}$$

Powers $\mathbf{A}^n = A^n \cdot e^{j \cdot n \cdot \theta} = A^n \cdot \cos(n \cdot \theta) + A^n \cdot \sin(n \cdot \theta) \cdot j$ Convert rectangulairs first, usually

Conjugates complex number

$$\mathbf{A} = a + b \cdot j$$

$$\mathbf{A} = A \cdot e^{j\theta}$$

$$\mathbf{F} = \frac{3 + 5 \cdot j}{(2 - 6 \cdot j) \cdot e^{j \cdot 40^\circ}}$$

Conjugate

$$\overline{\mathbf{A}} = a - b \cdot j$$

$$\overline{\mathbf{A}} = A \cdot e^{-j\theta}$$

$$\overline{\mathbf{F}} = \frac{3 - 5 \cdot j}{(2 + 6 \cdot j) \cdot e^{-j \cdot 40^\circ}}$$

$$\overline{\overline{\mathbf{A}}} = \mathbf{A}$$

Euler's equation

$$e^{j\alpha} = \cos(\alpha) + j \cdot \sin(\alpha)$$

$$\text{OR: } \cos(\alpha) = \frac{e^{j\alpha} + e^{-j\alpha}}{2}$$

$$\sin(\alpha) = \frac{e^{j\alpha} - e^{-j\alpha}}{2j}$$

$$e^{j(\omega t + \theta)} = \cos(\omega t + \theta) + j \cdot \sin(\omega t + \theta)$$



$$\operatorname{Re}[e^{j(\omega t + \theta)}] = \cos(\omega t + \theta)$$

If we freeze this at time $t=0$, then we can represent $\cos(\omega t + \theta)$ by $e^{j\theta}$

Calculus Remember, when we write $e^{j\theta}$, we really mean $e^{j(\omega t + \theta)}$

$$\frac{d}{dt} \mathbf{A} = \frac{d}{dt} (A \cdot e^{j\theta}) = j \cdot \omega \cdot A \cdot e^{j\theta} = \omega \cdot A \cdot e^{j(\theta + 90^\circ)}$$

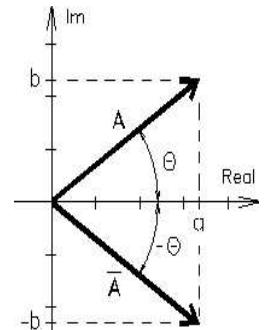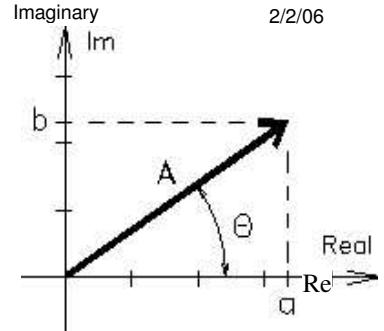
$$\int \mathbf{A} dt = \int A \cdot e^{j\theta} dt = \frac{1}{j \cdot \omega} \cdot A \cdot e^{j\theta} = \frac{1}{\omega} \cdot A \cdot e^{j(\theta - 90^\circ)}$$



For BIBO Systems

The sinusoidal response of a system is the output when the input is a sinusoidal (which starts at time = 0).

System Sinusoidal Response

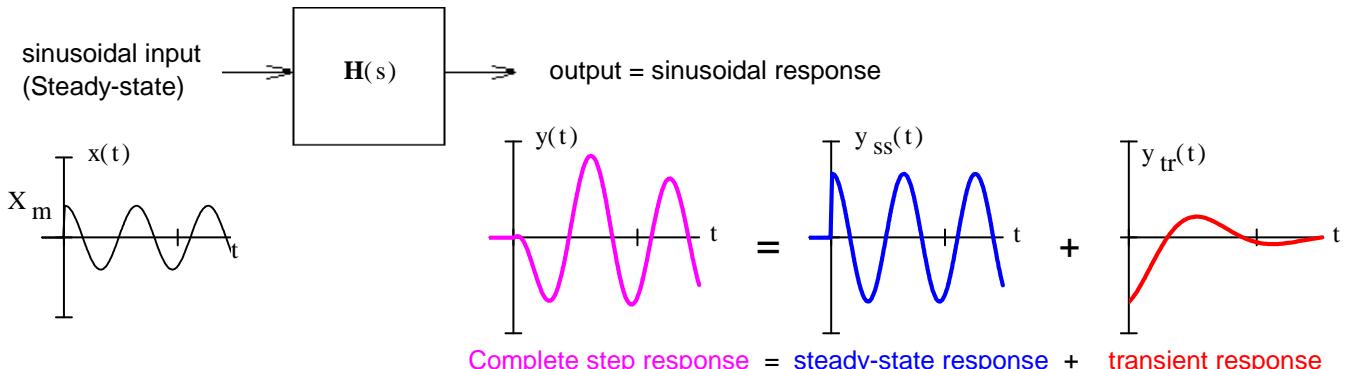

Sinusoidal Input

$$\cos(\omega t) \cdot u(t) \Leftrightarrow \frac{s}{s^2 + \omega^2}$$

$$\sin(\omega t) \cdot u(t) \Leftrightarrow \frac{\omega}{s^2 + \omega^2}$$

$$\text{General sinusoidal input: } [X_{mc} \cdot \cos(\omega t) + X_{ms} \cdot (\sin(\omega t) \cdot u(t))] \cdot u(t)$$

$$X(s) = \frac{X_{mc} \cdot s + X_{ms} \cdot \omega}{s^2 + \omega^2}$$

$$\text{OR } X_m \cdot \cos(\omega t + \theta) \cdot u(t) = [X_{mc} \cdot \cos(\omega t) + X_{ms} \cdot (\sin(\omega t) \cdot u(t))] \cdot u(t)$$

$$X_{mc} = X_m \cdot \cos(\theta) \quad X_{ms} = -X_m \cdot \sin(\theta)$$

note that the sine carries the opposite sign as you might expect.

Steady-State Response & $H(j\omega)$

$$Y(s) = X(s) \cdot H(s) = \frac{X_{mc} \cdot s + X_{ms} \cdot \omega}{s^2 + \omega^2} \cdot H(s) = \text{Complete sinusoidal response}$$

$$= \frac{A \cdot s + B \cdot \omega}{s^2 + \omega^2} + \frac{C}{(s + i\omega)} + \frac{D}{(s - i\omega)} + \frac{E}{(s^2 + \omega^2)} + \dots$$

$$\text{partial fraction expansion: } Y(s) = \frac{X_{mc} \cdot s + X_{ms} \cdot \omega}{s^2 + \omega^2} \cdot H(s) = \frac{A \cdot s + B \cdot \omega}{s^2 + \omega^2} + \left[\frac{C}{(s + i\omega)} + \frac{D}{(s - i\omega)} + \frac{E}{(s^2 + \omega^2)} \right] \cdot s$$

$$= \text{steady-state response} + \text{transient response}$$

$$\text{multiply both sides by: } (s^2 + \omega^2) \quad (X_{mc} \cdot s + X_{ms} \cdot \omega) \cdot H(s) = A \cdot s + B \cdot \omega + \left[\frac{C}{(s + i\omega)} + \frac{D}{(s - i\omega)} + \frac{E}{(s^2 + \omega^2)} \right] \cdot (s^2 + \omega^2)$$

$$\text{set } s := j\omega \quad (X_{mc} \cdot j\omega + X_{ms} \cdot \omega) \cdot H(j\omega) = A \cdot j\omega + B \cdot \omega + \left[\frac{C}{(j\omega + i\omega)} + \frac{D}{(j\omega - i\omega)} + \frac{E}{(j\omega)^2 + \omega^2} \right] \cdot 0$$

$$\text{divide both sides by } j\omega \quad (X_{mc} - X_{ms} \cdot j) \cdot H(j\omega)$$

$$X(\omega) \cdot H(j\omega) = A - B \cdot j = Y_{ss}(\omega) = \text{steady-state response in phasor form}$$

(real is cosine, imaginary is -sine)

$X(\omega)$ = the input expressed in phasor form NOT $X(s)$ with $s := \omega$ or $s := j\omega$

$H(j\omega)$ = the steady-state sinusoidal transfer function

(that would be ∞)

= phasor-type transfer function

Steady-State Response by Phasors

Time-domain sinusoids

T = Period



$$f = \text{frequency, cycles / second} \quad f = \frac{1}{T} = \frac{\omega}{2\pi}$$

$$\omega = \text{radian frequency, radians/sec} \quad \omega = 2\pi f$$

A = amplitude

$$\text{Phase: } \phi = -\frac{\Delta t}{T} \cdot 360 \cdot \text{deg} \quad \text{or: } \phi = -\frac{\Delta t}{T} \cdot 2\pi \cdot \text{rad}$$

$$y(t) = A \cdot \cos(\omega t + \phi)$$

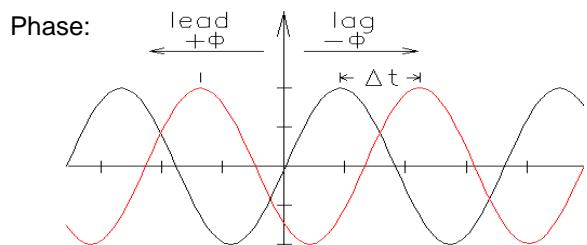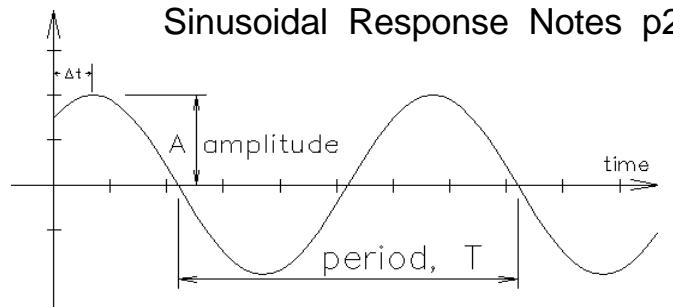

Expression of signals as phasors

Phasor

$$\text{voltage: } v(t) = V_p \cdot \cos(\omega t + \phi)$$

$$V(\omega) = V_p e^{j\phi}$$

$$\text{current: } i(t) = I_p \cdot \cos(\omega t + \phi)$$

$$I(\omega) = I_p e^{j\phi}$$

Ex1 What if a signal is the sum of two sinusoids of the same frequency.

$$v_1(t) = 3.2 \cdot V \cdot \cos(\omega t + 40^\circ)$$

$$v_2(t) = 4.5 \cdot V \cdot \sin(\omega t + 75^\circ)$$


$$v_3(t) = v_1(t) + v_2(t)$$

I'm going to drop the (ω) notation from the phasor notation, it gets cumbersome, but remember that phasors are in the frequency domain.

Express the time-domain voltages as phasors:

$$V_1 := 3.2 \cdot V \cdot e^{j40^\circ} = 3.2V / 40^\circ$$
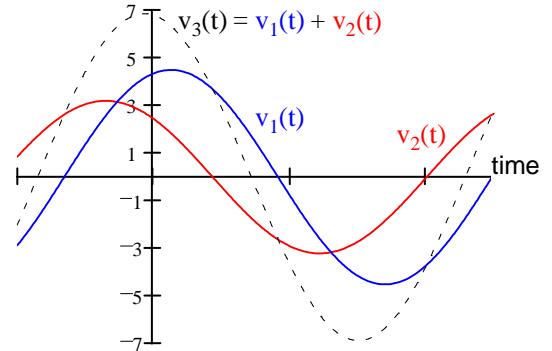
$$\text{Convert to rectangular: } 3.2 \cdot V \cdot \cos(40^\circ) = 2.451 \cdot V \quad 3.2 \cdot V \cdot \sin(40^\circ) = 2.057 \cdot V \quad V_1 = 2.451 + 2.057j \cdot V$$



Phasors are based on cosines, so express $v_2(t)$ as a cosine. Remember: $\sin(\omega t) = \cos(\omega t - 90^\circ)$

$$\text{So: } v_2(t) = 4.5 \cdot V \cdot \cos(\omega t + 75^\circ - 90^\circ) = 4.5 \cdot V \cdot \cos(\omega t - 15^\circ)$$

$$V_2 = 4.5V / -15^\circ \quad \text{or: } V_2 := 4.5 \cdot V \cdot e^{-j15^\circ}$$

$$4.5 \cdot V \cdot \cos(-15^\circ) = 4.347 \cdot V$$

$$4.5 \cdot V \cdot \sin(-15^\circ) = -1.165 \cdot V$$

$$V_2 = 4.347 - 1.165j \cdot V \quad \begin{matrix} \backslash \\ \end{matrix} \quad \begin{matrix} / \\ \end{matrix} \quad \text{add}$$

$$V_3 := V_1 + V_2$$

$$V_3 = 6.798 + 0.892j \cdot V \quad \text{sum}$$

$$\text{Add real parts: } 4.347 + 2.451 = 6.798$$

$$\text{Add imaginary parts: } -1.165 + 2.057 = 0.892$$

Change V_3 back to polar coordinates:

$$\sqrt{6.798^2 + 0.892^2} = 6.856 \quad \text{atan}\left(\frac{0.892}{6.798}\right) = 7.475^\circ$$


OR, in Mathcad notation (which you'll see a lot more):

$$|V_3| = 6.856 \cdot V \quad \arg(V_3) = 7.48^\circ$$

$$V_3(\omega) = 6.856V / 7.48^\circ \quad \text{or: } V_3(\omega) = 6.856 \cdot V \cdot e^{-j7.48^\circ}$$

V_3 may also be converted back to the time domain:
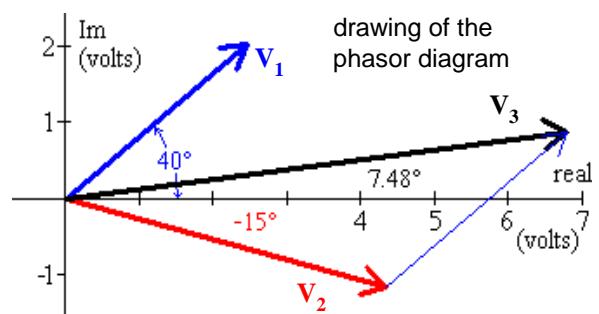
$$v_3(t) = v_1(t) + v_2(t) = 6.856 \cdot \cos(\omega t + 7.48^\circ) \cdot V$$



Impedances

Resistor

$$v_R = i_R \cdot R$$

$$V_R(s) = R \cdot I(s)$$

$$Z_R = R$$

Inductor

$$v_L(t) = L \frac{d}{dt} i_L(t)$$

$$V_L(s) = s \cdot L \cdot I_L(s)$$

$$Z_L = L \cdot s$$

Capacitor


$$i_C(t) = C \frac{d}{dt} v_C(t)$$

$$I_C(s) = C \cdot s \cdot V_C(s)$$


$$V_C(\omega) = \frac{1}{C \cdot s} \cdot I(s)$$

$$Z_C = \frac{1}{C \cdot s}$$


series:

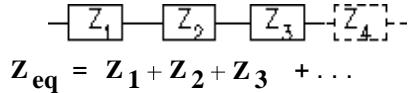


Example:

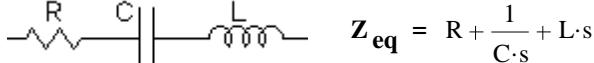

parallel:

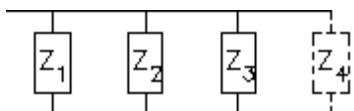

Example:

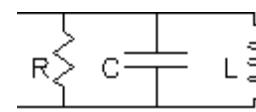


Current divider:

$$I_{Zn} = I_{total} \cdot \frac{\frac{1}{Z_n}}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} + \dots}$$

For Steady-State Response, replace s with $j\omega$ & $1/s$ with $-j\omega$.

Ex2 Find V_R , V_L , and V_C in polar phasor form. $f := 2\text{-kHz}$

Steady-state

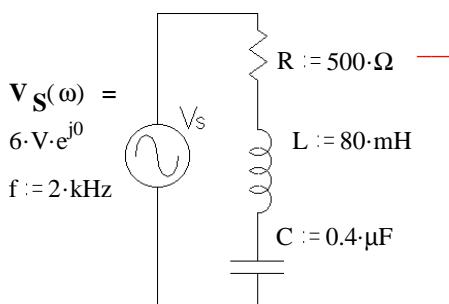

$$\omega := 2 \cdot \pi \cdot f$$

$$\omega = 12566 \cdot \frac{\text{rad}}{\text{sec}}$$

$$Z_L := j \cdot \omega L$$

$$Z_L = 1.005j \cdot k\Omega$$

$$= 1005\Omega / 90^\circ$$

$$Z_C := \frac{1}{j \cdot \omega C}$$

$$Z_C = -0.199j \cdot k\Omega$$

$$= -199\Omega / 90^\circ = 199\Omega / -90^\circ$$


$$Z_{eq} := R + j \cdot \omega L + \frac{1}{j \cdot \omega C}$$

$$Z_{eq} = 500 + 806.366j \cdot \Omega$$

$$\sqrt{500^2 + 806^2} = 948.491$$

$$\text{atan}\left(\frac{806}{500}\right) = 58.187^\circ \text{deg}$$

$$Z_{eq} = 948.5\Omega / 58.2^\circ$$

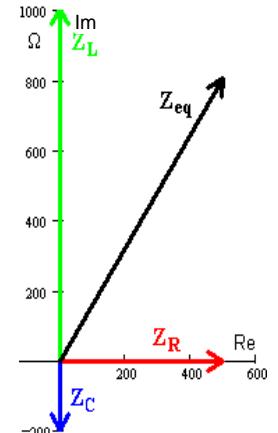

$$\text{b) find the current: } I := \frac{6 \cdot V \cdot e^{j0}}{Z_{eq}}$$

$$\text{magnitude: } \frac{6 \cdot V}{948.5 \cdot \Omega} = 6.326 \cdot \text{mA}$$

$$\text{angle: } 0^\circ - 58.2^\circ \text{deg} = -58.2^\circ \text{deg}$$

$$I = 6.326 \text{mA} / -58.2^\circ$$

c) Draw a phasor diagram of V_s , V_R , V_L , and V_C

$$V_R := I \cdot R$$

$$\text{magnitude } 6.326 \cdot \text{mA} \cdot 500 \cdot \Omega = 3.163 \cdot \text{V}$$

$$\text{angle } -58.2^\circ \text{deg} + 0^\circ \text{deg} = -58.2^\circ \text{deg}$$

$$V_R = 3.163\text{V} / -58.2^\circ$$

$$V_L := I \cdot Z_L$$

$$6.326 \cdot \text{mA} \cdot 1005 \cdot \Omega = 6.358 \cdot \text{V}$$

$$-58.2^\circ \text{deg} + 90^\circ \text{deg} = 31.8^\circ \text{deg}$$



$$V_L = 6.358\text{V} / 31.8^\circ$$

$$V_C := I \cdot Z_C$$

$$6.326 \cdot \text{mA} \cdot (199) \cdot \Omega = 1.259 \cdot \text{V}$$

$$-58.2^\circ \text{deg} + (-90^\circ) \text{deg} = -148.2^\circ \text{deg}$$

$$V_C = 1.259\text{V} / -148.2^\circ$$

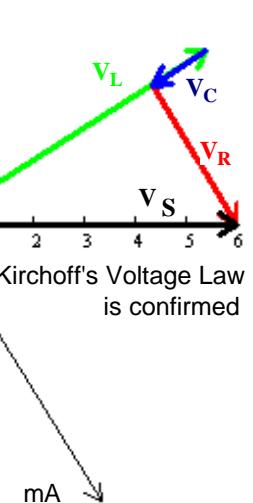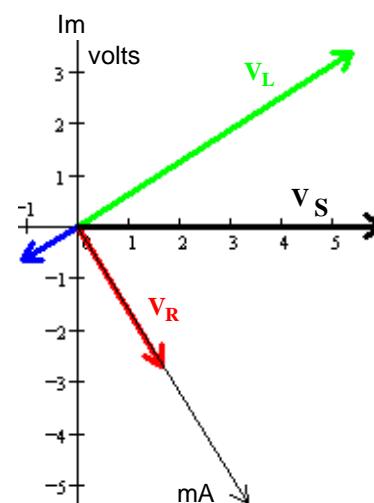

Sinusoidal Response Notes p4

Ex3 a) Find the steady-state V_C and $v_c(t)$

given $v_{in}(t)$ is a 12-V cosine wave at: $f := 2.5 \text{ kHz}$

with a 20° leading phase angle. $V_{in} := 12 \cdot V \cdot e^{j \cdot 20^\circ \cdot \text{deg}}$

Transfer function for V_C as the output: $H(s) = \frac{V_C(s)}{V_{in}(s)}$

$$H(s) = \frac{\frac{1}{R + L_2 \cdot s}}{L_1 \cdot s + \frac{1}{R + L_2 \cdot s} + C \cdot s} = \frac{\left(\frac{1}{R + L_2 \cdot s} + C \cdot s \right)}{\left(\frac{1}{R + L_2 \cdot s} + C \cdot s \right)}$$

$$= \frac{1}{L_1 \cdot s \cdot \left(\frac{1}{R + L_2 \cdot s} + C \cdot s \right) + 1} = \frac{1}{L_1 \cdot (j \cdot \omega) \cdot \left[\frac{1}{R + L_2 \cdot (j \cdot \omega)} + C \cdot (j \cdot \omega) \right] + 1}$$

$$H(j\omega) = \frac{1}{0.002 \cdot (j \cdot 15708) \cdot \left[\frac{1}{200 + 0.008 \cdot (j \cdot 15708)} + 10^{-6} \cdot (j \cdot 15708) \right] + 1}$$

$$= \frac{1}{31.416 \cdot j \cdot [3.585 \cdot 10^{-3} - 2.252 \cdot 10^{-3} \cdot j + (j \cdot 0.015708)] + 1} = \frac{1}{1 - 0.423 + 0.113 \cdot j} = \frac{1}{0.588 \cdot e^{j \cdot 11.039^\circ \cdot \text{deg}}}$$

$$= 1.7 \cdot e^{-j \cdot 11.039^\circ \cdot \text{deg}}$$

$$V_C = V_{in}(\omega) \cdot H(j\omega) = 12 \cdot V \cdot e^{j \cdot 20^\circ \cdot \text{deg}} \cdot 1.7 \cdot e^{-j \cdot 11.039^\circ \cdot \text{deg}} = 12 \cdot V \cdot 1.7 / 20 - 11.039^\circ = 20.4V / 8.96^\circ$$

$$v_c(t) = 20.4 \cdot V \cdot \cos \left(15708 \cdot \frac{\text{rad}}{\text{sec}} \cdot t + 8.96^\circ \right)$$

a) Find the steady-state I_{L2} and $i_{L2}(t)$.


Transfer function for I_{L2} as the output: $H(s) = \frac{I_{L2}(s)}{V_{in}(s)} = \frac{\left(\frac{V_C(s)}{R + L_2 \cdot s} \right)}{V_{in}(s)} = \frac{V_C(s)}{V_{in}(s)} \cdot \frac{1}{R + L_2 \cdot s}$

$$H(s) = \frac{1}{L_1 \cdot s \cdot \left(\frac{1}{R + L_2 \cdot s} + C \cdot s \right) + 1} \cdot \frac{1}{(R + L_2 \cdot s)} = \frac{1}{L_1 \cdot s + L_1 \cdot s \cdot C \cdot s \cdot (R + L_2 \cdot s) + (R + L_2 \cdot s)}$$

$$H(j\omega) = \frac{1}{L_1 \cdot (j \cdot \omega) + L_1 \cdot C \cdot (j \cdot \omega)^2 \cdot [R + L_2 \cdot (j \cdot \omega)] + [R + L_2 \cdot (j \cdot \omega)]} = 5.249 \cdot 10^{-3} - 4.926 \cdot 10^{-3} j \cdot \frac{1}{\Omega} = \frac{7.198}{k\Omega} \cdot e^{-j \cdot 43.181^\circ \cdot \text{deg}}$$

$$I_{L2} = V_{in}(\omega) \cdot H(j\omega) = 12 \cdot V \cdot e^{j \cdot 20^\circ \cdot \text{deg}} \cdot \left(\frac{7.198}{k\Omega} \cdot e^{-j \cdot 43.181^\circ \cdot \text{deg}} \right) = 12 \cdot V \cdot \frac{7.198}{k\Omega} / 20 - 43.181^\circ = 86.38 \text{ mA} / -23.18^\circ$$
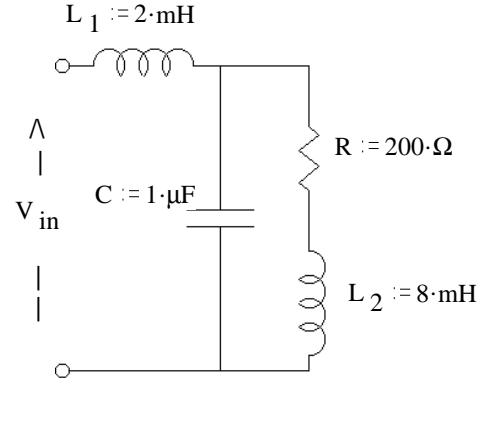
$$i_{L2}(t) = 86.38 \cdot \text{mA} \cdot \cos \left(15708 \cdot \frac{\text{rad}}{\text{sec}} \cdot t - 23.18^\circ \cdot \text{deg} \right)$$



$$f = 2.5 \text{ kHz}$$

$$\omega := 2 \cdot \pi \cdot f \quad \omega = 15708 \cdot \frac{\text{rad}}{\text{sec}}$$

Magnitude and Phase of transfer functions

With steady-state sinusoidal inputs which start at $t = 0$

Ex4 a) Find the magnitude and phase of the following transfer function at this frequency: $f := 5 \cdot \text{Hz}$ $\omega := 2 \cdot \pi \cdot f$

$$\mathbf{H}(s) = \frac{s^2 + \frac{20}{\text{sec}} \cdot s + \frac{1000}{\text{sec}^2}}{s^2 + \frac{8}{\text{sec}} \cdot s + \frac{800}{\text{sec}^2}}$$

$$s := j \cdot \omega = j \cdot 31.42 \cdot \frac{\text{rad}}{\text{sec}} \quad \mathbf{H}(j \cdot \omega) = \frac{(j \cdot \omega)^2 + \frac{20}{\text{sec}} \cdot (j \cdot \omega) + \frac{1000}{\text{sec}^2}}{(j \cdot \omega)^2 + \frac{8}{\text{sec}} \cdot (j \cdot \omega) + \frac{800}{\text{sec}^2}} = \frac{(j \cdot 31.42)^2 + 20 \cdot (j \cdot 31.42) + 1000}{(j \cdot 31.42)^2 + 8 \cdot (j \cdot 31.42) + 800} \quad \text{without units}$$

$$= \frac{13.04 + 628.319 \cdot j}{-187.2164 + 251.36 \cdot j} = 1.583 - 1.231j$$

$$|\mathbf{H}(j \cdot \omega)| = M = \sqrt{(1.583)^2 + (1.231)^2} = 2.005 \quad \underline{\mathbf{H}(j\omega)} = \text{atan}\left(\frac{-1.231}{1.583}\right) = -37.87^\circ \text{deg} \quad \mathbf{H}(j \cdot \omega) = 2.005 \angle -37.87^\circ$$

b) Find the **steady-state** sinusoidal output if the input is: $x(t) = 4 \cdot \cos(2 \cdot \pi \cdot 5 \cdot \text{Hz} \cdot t)$ $\mathbf{X}(\omega) = 4 + 0j$

$$\text{and then } \mathbf{Y}(\omega) = \mathbf{X}(\omega) \cdot \mathbf{H}(j \cdot \omega) = 4 \cdot (1.583 - 1.231j) = 6.332 - 4.924j$$

Note that you can use the rectangular form of $\mathbf{H}(j \cdot \omega)$

$$y_{ss}(t) = \left(6.332 \cdot \cos\left(31.42 \cdot \frac{\text{rad}}{\text{sec}} \cdot t\right) + 4.924 \cdot \sin\left(31.42 \cdot \frac{\text{rad}}{\text{sec}} \cdot t\right) \right) \cdot u(t) \quad \text{note that the sine carries the opposite sign as the imaginary part of phasor.}$$

$$\sqrt{6.332^2 + 4.924^2} = 8.021 \quad \text{atan}\left(\frac{-4.924}{6.332}\right) = -37.87^\circ \text{deg} \quad y_{ss}(t) := 8.021 \cdot \cos(31.42 \cdot t - 37.87^\circ) \cdot u(t)$$

c) Find the **transient response** for the same input. $x(t) = 4 \cdot \cos(2 \cdot \pi \cdot 5 \cdot \text{Hz} \cdot t)$ $\mathbf{X}(s) = 4 \cdot \frac{s}{s^2 + 31.42^2}$

$$\mathbf{Y}_{tr}(s) = \frac{4 \cdot s}{s^2 + 31.42^2} \cdot \frac{s^2 + 20 \cdot s + 1000}{s^2 + 8 \cdot s + 800} \quad a := -4 \quad b := \sqrt{800 - 4^2} \quad b = 28$$

$$= A \cdot \frac{s + 4}{s^2 + 8 \cdot s + 800} + B \cdot \frac{28}{s^2 + 8 \cdot s + 800} + C \cdot \frac{s}{s^2 + 31.42^2} + D \cdot \frac{31.42}{s^2 + 31.42^2}$$

multiply both sides by $(s^2 + 8 \cdot s + 800)$ and let $s := -4 + 28 \cdot j$

$$\frac{4 \cdot (-4 + 28 \cdot j) \cdot [(-4 + 28 \cdot j)^2 + 20 \cdot (-4 + 28 \cdot j) + 1000]}{(-4 + 28 \cdot j)^2 + 31.42^2} = -115.969 - 65.365j = A((-4 + 28 \cdot j) - 4) + B \cdot 28$$


$$\frac{-115.969 - 65.365j}{28} = -4.142 - 2.334j = A \cdot j + B$$

$$A := -2.334 \quad B := -4.142$$

$$y_{tr}(t) := (-2.334 \cdot e^{-4 \cdot t} \cdot \cos(28 \cdot t) - 4.142 \cdot e^{-4 \cdot t} \cdot \sin(28 \cdot t)) \cdot u(t)$$

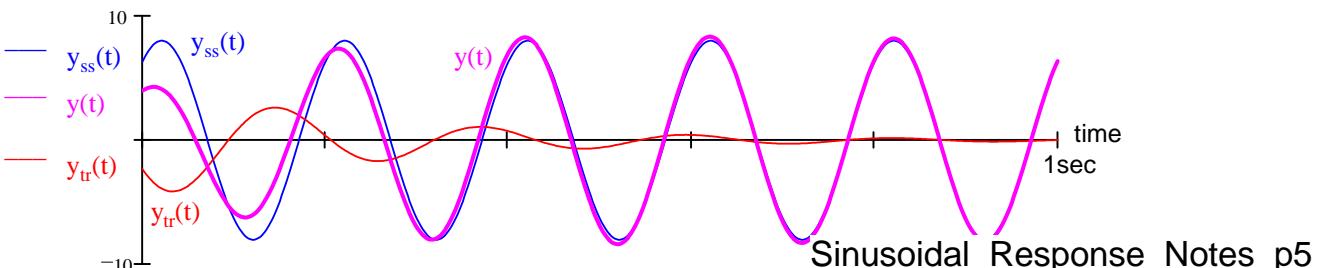d) Find the **total response** for the same input.

$$y(t) := (-2.334 \cdot e^{-4 \cdot t} \cdot \cos(28 \cdot t) - 4.142 \cdot e^{-4 \cdot t} \cdot \sin(28 \cdot t) + 8.021 \cdot \cos(31.42 \cdot t - 37.87^\circ)) \cdot u(t)$$



Sinusoidal Response Notes p6

Ex4 a) Find the magnitude and phase of the following transfer function at this frequency: $\omega := 2 \frac{\text{rad}}{\text{sec}}$

$$H(s) = \frac{2s^2 + 5s + 20}{s^2 + 2s + 10} = \frac{2s^2 + \frac{5}{\text{sec}} \cdot s + \frac{20}{\text{sec}^2}}{s^2 + \frac{2}{\text{sec}} \cdot s + \frac{10}{\text{sec}^2}} \cdot V$$

Expressed with proper units.
In this case the transfer function is for a circuit where both the input and output are voltages.

$$s := j \cdot \omega$$

$$H(j \cdot \omega) = \frac{2 \cdot (j \cdot \omega)^2 + 5 \cdot (j \cdot \omega) + 20}{(j \cdot \omega)^2 + \frac{2}{\text{sec}} \cdot (j \cdot \omega) + \frac{10}{\text{sec}^2}} = \frac{(20 - 2 \cdot \omega^2) + (5 \cdot \omega) \cdot j}{(10 - \omega^2) + (2 \cdot \omega) \cdot j} = \frac{(20 - 2 \cdot 2^2) + (5 \cdot 2) \cdot j}{(10 - 2^2) + (2 \cdot 2) \cdot j} = \frac{12 + 10 \cdot j}{6 + 4 \cdot j}$$

without units

$$|H(j \cdot \omega)| = M = \frac{\sqrt{12^2 + 10^2}}{\sqrt{6^2 + 4^2}} = 2.166 \quad /H(j\omega) = \tan\left(\frac{10}{12}\right) - \tan\left(\frac{4}{6}\right) = 6.12^\circ \text{deg} \quad H(j \cdot \omega) = 2.166 \angle 6.12^\circ$$

b) Find the **steady-state response** if the input is: $v_{\text{in}}(t) = 3.2 \cdot \cos(2 \cdot t + 15^\circ \text{deg})$ $V_{\text{in}} := 3.2 \cdot V \cdot e^{j \cdot 15^\circ \text{deg}} = 3.2V \angle 15^\circ$

$$V_{\text{out_ss}}(\omega) = V_{\text{in}}(\omega) \cdot H(j \cdot \omega) = (3.2 \cdot V \cdot e^{j \cdot 15^\circ \text{deg}}) \cdot (2.166 \cdot e^{j \cdot 6.12^\circ \text{deg}}) = 3.2 \cdot V \cdot 2.166 \cdot e^{j \cdot (15^\circ \text{deg} + 6.12^\circ \text{deg})} = 6.931 \cdot V \cdot e^{j \cdot 21.12^\circ \text{deg}} = 6.465 + 2.497j \cdot V$$

$$v_{\text{out_ss}}(t) = 6.931 \cdot V \cdot \cos(2 \cdot t + 21.12^\circ \text{deg}) \cdot u(t) = (6.465 \cdot \cos(2 \cdot t) - 2.497 \cdot \sin(2 \cdot t)) \cdot u(t)$$

Note that the sine carries the opposite sign as the imaginary part of phasor.

c) Find the **transient response** for the same input.

$$\text{Phasor: } V_{\text{in}} = 3.091 + 0.828j \cdot V \quad V_{\text{in}}(s) = 3.091 \cdot \frac{s}{s^2 + 2^2} - 0.828 \cdot \frac{2}{s^2 + 2^2} = \frac{3.091 \cdot s - 0.828 \cdot 2}{s^2 + 2^2} \quad \text{Note the sign change for the sine.}$$

$$V_{\text{out_tr}}(s) = \frac{(3.091 \cdot s - 0.828 \cdot 2) \cdot (2s^2 + 5s + 20)}{s^2 + 2^2} = \frac{6.182 \cdot s^3 + 12.143 \cdot s^2 + 53.54 \cdot s - 33.12}{(s^2 + 4) \cdot (s^2 + 2s + 10)}$$

$$= A \cdot \frac{s+1}{s^2 + 2s + 10} + B \cdot \frac{3}{s^2 + 2s + 10} + C \cdot \frac{s}{s^2 + 4} + D \cdot \frac{2}{s^2 + 4}$$

Multiply both sides by $(s^2 + 2s + 10)$ and let $s := -1 + 3j$

$$\frac{6.182 \cdot s^3 + 12.143 \cdot s^2 + 53.54 \cdot s - 33.12}{(s^2 + 4)} = A \cdot ((-1 + 3j) + 1) + B \cdot 3$$

$$\frac{6.182 \cdot (-1 + 3j)^3 + 12.143 \cdot (-1 + 3j)^2 + 53.54 \cdot (-1 + 3j) - 33.12}{(-1 + 3j)^2 + 4} = \frac{-23.072 - 23.514j}{-4 - 6j} = 4.488 - 0.853j = A \cdot 3j + B \cdot 3$$

$$\frac{4.488 - 0.853j}{3} = 1.496 - 0.284j \quad A := -0.284 \quad B := 1.496$$

$$v_{\text{out_tr}}(t) = (-0.281 \cdot V \cdot e^{-1t} \cdot \cos(3t) + 1.496 \cdot V \cdot e^{-1t} \cdot \sin(3t)) \cdot u(t)$$

d) Find the **total response** for the same input.

$$v_{\text{out}}(t) = (-0.281 \cdot V \cdot e^{-1t} \cdot \cos(3t) + 1.496 \cdot V \cdot e^{-1t} \cdot \sin(3t) + 6.931 \cdot V \cdot \cos(2t + 21.12^\circ \text{deg})) \cdot u(t)$$

See Bodson text, section 3.5

Best explained by example, IF: $\mathbf{H}(s) = \frac{b_2 s^2 + b_1 s + b_0}{s^2 + a_1 s + a_0} \cdot \mathbf{X}(s)$

We would normally say:

$$\mathbf{Y}(s) = \frac{b_2 s^2 + b_1 s + b_0}{s^2 + a_1 s + a_0} \cdot \mathbf{X}(s)$$

But that ignores initial conditions. So let's deconstruct and then reconstruct with initial conditions included.

$$\mathbf{Y}(s) \cdot (s^2 + a_1 s + a_0) = (b_2 s^2 + b_1 s + b_0) \cdot \mathbf{X}(s)$$

$$s^2 \cdot \mathbf{Y}(s) + a_1 s \cdot \mathbf{Y}(s) + a_0 \cdot \mathbf{Y}(s) = b_2 s^2 \cdot \mathbf{X}(s) + b_1 s \cdot \mathbf{X}(s) + b_0 \cdot \mathbf{X}(s)$$

$$\frac{d^2}{dt^2} y(t) + a_1 \frac{d}{dt} y(t) + a_0 y(t) = b_2 \frac{d^2}{dt^2} x(t) + b_1 \frac{d}{dt} x(t) + b_0 x(t)$$

Laplace Properties

<u>Operation</u>	<u>$f(t)$</u>	<u>$F(s)$</u>
Time differentiation	$\frac{d}{dt} f(t)$	$s \cdot F(s) - f(0^-)$
	$\frac{d^2}{dt^2} f(t)$	$s^2 \cdot F(s) - s \cdot f(0^-) - \frac{d}{dt} f(0^-)$ initial slope
	$\frac{d^2}{dt^2} y(t) + a_1 \frac{d}{dt} y(t) + a_0 y(t)$	$b_2 \frac{d^2}{dt^2} x(t) + b_1 \frac{d}{dt} x(t) + b_0 x(t)$
	$\left(s^2 \cdot \mathbf{Y}(s) - s \cdot y(0^-) - \frac{d}{dt} y(0^-) \right) + a_1 \cdot (s \cdot \mathbf{Y}(s) - y(0^-)) + a_0 \cdot \mathbf{Y}(s) =$	$b_2 \cdot \left(s^2 \cdot \mathbf{X}(s) - s \cdot x(0^-) - \frac{d}{dt} x(0^-) \right) + b_1 \cdot (s \cdot \mathbf{X}(s) - x(0^-)) + b_0 \cdot \mathbf{X}(s)$
	$(s^2 \cdot \mathbf{Y}(s) + a_1 s \cdot \mathbf{Y}(s) + a_0 \cdot \mathbf{Y}(s)) - s \cdot y(0^-) - a_1 y(0^-) =$	$(b_2 s^2 \cdot \mathbf{X}(s) + b_1 s \cdot \mathbf{X}(s) + b_0 \cdot \mathbf{X}(s)) - b_2 s \cdot x(0^-) - b_2 \frac{d}{dt} x(0^-) - b_1 x(0^-)$
	$\mathbf{Y}(s) \cdot (s^2 + a_1 s + a_0) = (b_2 s^2 + b_1 s + b_0) \cdot \mathbf{X}(s) + \left(s \cdot y(0^-) + \frac{d}{dt} y(0^-) + a_1 y(0^-) - b_2 s \cdot x(0^-) - b_2 \frac{d}{dt} x(0^-) - b_1 x(0^-) \right)$	

$$\mathbf{Y}(s) = \frac{b_2 s^2 + b_1 s + b_0}{s^2 + a_1 s + a_0} \cdot \mathbf{X}(s) + \frac{s \cdot y(0^-) + \frac{d}{dt} y(0^-) + a_1 y(0^-) - b_2 s \cdot x(0^-) - b_2 \frac{d}{dt} x(0^-) - b_1 x(0^-)}{s^2 + a_1 s + a_0}$$

Response to input

Response to initial conditions

$$\mathbf{Y}(s) = \frac{b_2 s^2 + b_1 s + b_0}{s^2 + a_1 s + a_0} \cdot \mathbf{X}(s) + \frac{s \cdot y(0^-) + \frac{d}{dt} y(0^-) + a_1 y(0^-) - b_2 s \cdot x(0^-) - b_2 \frac{d}{dt} x(0^-) - b_1 x(0^-)}{s^2 + a_1 s + a_0}$$

Forced response

Natural response

Zero-state response

Zero-input response

$$Y(s) = \frac{H(s)}{s^2 + a_1 s + a_0} \cdot X(s) + \frac{s \cdot y(0^-) + \frac{d}{dt} y(0^-) + a_1 \cdot y(0^-) - b_2 \cdot s \cdot x(0^-) - b_2 \cdot \frac{d}{dt} x(0^-) - b_1 \cdot x(0^-)}{s^2 + a_1 s + a_0}$$


Observations

1. The total response is the sum of two independent components.
2. These values together fully describe the *state* of the 2nd-order system at time $t=0^-$ (the initial state): $y(0^-)$ $\frac{dy}{dt}(0^-)$ $x(0^-)$ $\frac{dx}{dt}(0^-)$
3. Similar denominator for both parts = Share poles = Similar responses
4. Response to Initial conditions always go to zero if system is BIBO.
5. Pole-zero cancellations in right-half plane can cause major problems with internal states of the system.




A simple first-order example

The switch has been closed for a long time and is opened at time $t=0$.

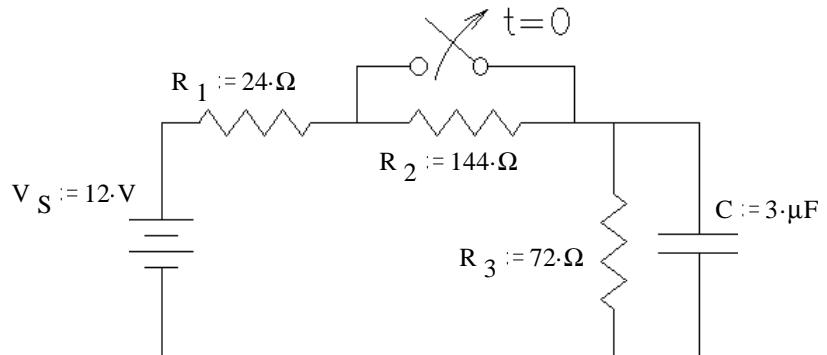Find the complete expression for $v_C(t)$.




The way you've solved it before:

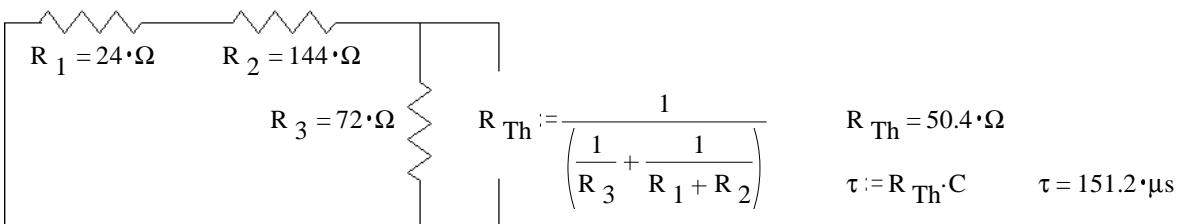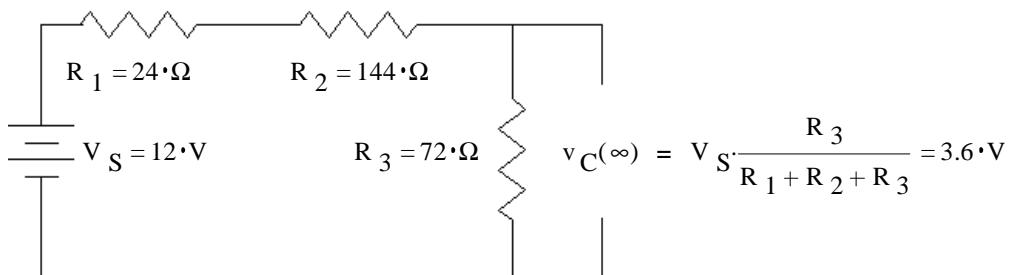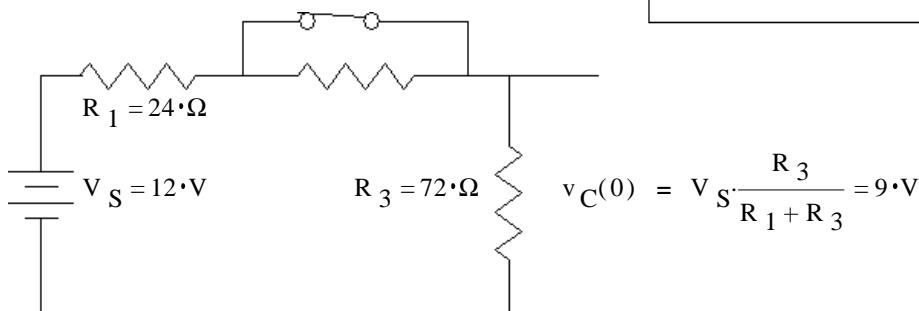

$$v_C(t) = v_C(\infty) + (v_C(0^-) - v_C(\infty)) \cdot e^{-\frac{t}{\tau}} = 3.6 \cdot V + (9 \cdot V - 3.6 \cdot V) \cdot e^{-\frac{t}{151 \cdot \mu\text{s}}} = 3.6 \cdot V + 5.4 \cdot V \cdot e^{-\frac{t}{151 \cdot \mu\text{s}}}$$

ECE 3510 Effect of initial conditions p3

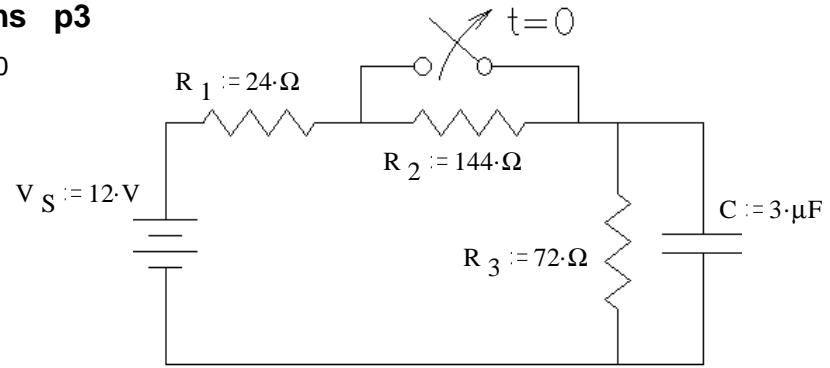The way we would do the same thing in 3510



$$\begin{aligned}
 H(s) = \frac{V_C(s)}{V_S(s)} &= \frac{\frac{1}{R_3 + C \cdot s}}{R_1 + R_2 + \frac{1}{\frac{1}{R_3 + C \cdot s} + \frac{1}{R_3}}} \cdot \frac{\left(\frac{1}{R_3} + C \cdot s\right)}{\left(\frac{1}{R_3} + C \cdot s\right)} = \frac{1}{\frac{R_1 + R_2}{R_3} + (R_1 + R_2) \cdot C \cdot s + 1} \cdot \frac{\left[\frac{1}{(R_1 + R_2) \cdot C}\right]}{\left[\frac{1}{(R_1 + R_2) \cdot C}\right]} \\
 &= \frac{1}{\frac{R_1 + R_2}{R_3} + (R_1 + R_2) \cdot C \cdot s + 1} \cdot \frac{\left[\frac{1}{(R_1 + R_2) \cdot C}\right]}{\left[\frac{1}{(R_1 + R_2) \cdot C}\right]} = \frac{\frac{1}{(R_1 + R_2) \cdot C}}{s + \left[\frac{1}{R_3 \cdot C} + \frac{1}{(R_1 + R_2) \cdot C}\right]}
 \end{aligned}$$

First-order version of $Y(s)$ with initial conditions

$$Y(s) = \frac{H(s)}{s + a_0} \cdot X(s) + \frac{y(0^-) - b_1 \cdot x(0^-)}{s + a_0} \quad \begin{array}{l} \text{Initial conditions} \\ b_1 = 0 \quad b_0 := \frac{1}{(R_1 + R_2) \cdot C} \quad b_0 = 1984 \cdot \text{sec}^{-1} \\ a_0 := \frac{1}{R_3 \cdot C} + \frac{1}{(R_1 + R_2) \cdot C} \quad a_0 = 6614 \cdot \text{sec}^{-1} \end{array}$$

$$X(s) = \frac{12 \cdot V}{s}$$

$$\begin{aligned}
 Y(s) &= \frac{b_0}{s + a_0} \cdot \frac{12 \cdot V}{s} + \frac{y(0^-)}{s + a_0} \\
 y(0^-) &= 9 \cdot V \quad \begin{array}{l} \frac{b_0}{s + a_0} \cdot \frac{12 \cdot V}{s} = \frac{A}{s} + \frac{B}{s + a_0} \quad A = H(0) \cdot 12 \cdot V \\ \frac{b_0}{s + a_0} = \frac{b_0}{a_0} \cdot \frac{12 \cdot V}{s} = \frac{b_0}{a_0} \cdot 12 \cdot V = 3.6 \cdot V \end{array} \\
 &\text{from above}
 \end{aligned}$$

$$\begin{aligned}
 B &= b_0 \cdot \frac{12 \cdot V}{s} \Big|_{s = -a_0} = \frac{b_0}{-a_0} \cdot 12 \cdot V = -3.6 \cdot V \\
 &= \frac{3.6 \cdot V}{s} + \frac{-3.6 \cdot V}{s + a_0} + \frac{y(0^-)}{s + a_0}
 \end{aligned}$$

$$y(t) = v_C(t) = (3.6 \cdot V - 3.6 \cdot V \cdot e^{-a_0 t} + 9 \cdot V \cdot e^{-a_0 t}) \cdot u(t)$$

$$\text{Same as above } v_C(t) = 3.6 \cdot V + (9 \cdot V - 3.6 \cdot V) \cdot e^{-\frac{t}{151 \cdot \mu s}} \quad \text{where } \tau = \frac{1}{a_0} = \frac{\text{sec}}{6614} = 151.2 \cdot \mu s$$

ECE 3510 Effect of initial conditions p3

A completely different method where all math is done in the time-domain using linear algebra. See Bodson, section 3.6.

$x(t)$ = The state vector ($n \times 1$ matrix)
 n = order of the system

$\frac{d}{dt}x(t)$ = Time derivative of the state vector ($n \times 1$ matrix)

$u(t)$ = The input vector ($n_u \times 1$ matrix)

n_u = number of inputs

$y(t)$ = The state vector ($n_y \times 1$ matrix)

n_y = order of the system

A = The system matrix ($n \times n$ matrix)

B = The input matrix ($n \times n_u$ matrix)

C = The output matrix ($n_y \times n$ matrix)

D = The feed-forward matrix ($n_y \times n_u$ matrix)

$$\text{State Equation: } \frac{d}{dt}x(t) = A \cdot x(t) + B \cdot u(t)$$

A third-order, 2-input, 2-output system

$$\begin{pmatrix} \cdot \\ \cdot \\ \cdot \end{pmatrix} = \begin{pmatrix} \cdot & \cdot & \cdot \\ \cdot & \cdot & \cdot \\ \cdot & \cdot & \cdot \end{pmatrix} \cdot \begin{pmatrix} \cdot \\ \cdot \\ \cdot \end{pmatrix} + \begin{pmatrix} \cdot & \cdot \\ \cdot & \cdot \\ \cdot & \cdot \end{pmatrix} \cdot \begin{pmatrix} \cdot \\ \cdot \end{pmatrix}$$

$$\text{Output Equation: } y(t) = C \cdot x(t) + D \cdot u(t)$$

$$\begin{pmatrix} \cdot \\ \cdot \end{pmatrix} = \begin{pmatrix} \cdot & \cdot & \cdot \\ \cdot & \cdot & \cdot \\ \cdot & \cdot & \cdot \end{pmatrix} \cdot \begin{pmatrix} \cdot \\ \cdot \\ \cdot \end{pmatrix} + \begin{pmatrix} \cdot & \cdot \\ \cdot & \cdot \\ \cdot & \cdot \end{pmatrix} \cdot \begin{pmatrix} \cdot \\ \cdot \end{pmatrix}$$

$$\text{State Equation: } \frac{d}{dt}x(t) = A \cdot x(t) + B \cdot u(t)$$

A third-order, single-input, single-output system

$$\begin{pmatrix} \cdot \\ \cdot \\ \cdot \end{pmatrix} = \begin{pmatrix} \cdot & \cdot & \cdot \\ \cdot & \cdot & \cdot \\ \cdot & \cdot & \cdot \end{pmatrix} \cdot \begin{pmatrix} \cdot \\ \cdot \\ \cdot \end{pmatrix} + \begin{pmatrix} \cdot \\ \cdot \\ \cdot \end{pmatrix} \cdot u(t)$$

$$\text{Output Equation: } y(t) = C \cdot x(t) + D \cdot u(t)$$

$$y(t) = \begin{pmatrix} \cdot & \cdot & \cdot \end{pmatrix} \cdot \begin{pmatrix} \cdot \\ \cdot \\ \cdot \end{pmatrix} + D \cdot u(t)$$

Advantages of the state-space method

Easily handles multiple inputs, multiple outputs and initial conditions

Can be used with nonlinear systems

Can be used with time-varying systems

Reveals unstable systems that have stable transfer functions (pole-zero cancellations). You can determine:

Controllability: State variables can all be affected by the input

Observability: State variables are all "observable" from the output

Basis of Optimal control methods

Advantages and disadvantages of the classical frequency-domain method used in this class

Simpler to understand and model interconnected systems.

Rapidly provide stability and transient response information.

Easy to see the effects of varying system parameters to get a good design.

Limited to linear, time-invariant systems or systems that can be approximated as such.