

This method is based on the method of Linear Graphs. In Linear Graphs, all systems are reduced to a universal symbology peculiar to Linear Graphs (system graph) and then analyzed by methods very similar to those used with electric circuits. Since we, as electrical engineers, are already well versed in the symbology of electric circuits, my variation of linear graphs reduces mechanical systems to electric circuits and leaves them in that symbology for ready analysis by methods, tools and computer programs that we are already familiar with.

### Across and Through Variables

	<u>Across Variable</u>	<u>Through Variable</u>
<b>Electrical</b>	V = voltage (volts) or (V)	I = current (Amps) or (A)
<b>Mechanical translational</b>	v = velocity $\left(\frac{\text{m}}{\text{sec}}\right)$	F = force (newtons) or (N) or $\left(\text{Kg}\cdot\frac{\text{m}}{\text{sec}^2}\right)$
<b>Mechanical rotational</b>	$\omega$ = angular velocity $\left(\frac{\text{rad}}{\text{sec}}\right)$	T = torque (N·m)
<b>Fluid</b>	P = pressure $\left(\frac{\text{N}}{\text{m}^2}\right)$ or (Pa)	Q = flow $\left(\frac{\text{m}^3}{\text{sec}}\right)$

	<u>Dissipation</u>	<u>Across Variable Energy Storage</u>	<u>Through Variable Energy Storage</u>
<b>Electrical</b>	R = resistance $\left(\frac{\text{V}}{\text{A}}\right)$ or ( $\Omega$ )	C = capacitance $\left(\frac{\text{A}\cdot\text{sec}}{\text{V}}\right)$ or (F)	L = inductor $\left(\frac{\text{V}\cdot\text{sec}}{\text{A}}\right)$ or (H)
<b>Mechanical translational</b>	B = damping $\left(\frac{\text{N}\cdot\text{sec}}{\text{m}}\right)$	M = mass (Kg) or $\left(\frac{\text{N}\cdot\text{sec}^2}{\text{m}}\right)$	k = Spring constant $\left(\frac{\text{N}}{\text{m}}\right)$
<b>Mechanical rotational</b>	B = damping $\left[\frac{\text{N}\cdot\text{m}}{\left(\frac{\text{rad}}{\text{sec}}\right)}\right]$ (N·m·sec) or $\left[\frac{\text{rad}}{\text{sec}}\right]$	J = moment of inertia $\left(\frac{\text{N}\cdot\text{m}^3}{\left(\text{Kg}\cdot\text{m}^2\right) \text{ or } \left(\frac{\text{N}\cdot\text{m}^3}{\text{sec}^2}\right)}\right)$	k = Spring constant $\left(\frac{\text{N}\cdot\text{m}}{\text{rad}}\right)$
<b>Fluid</b>	R <sub>f</sub> = fluid resistance $\left(\frac{\text{N}\cdot\text{sec}}{\text{m}^5}\right)$	C <sub>f</sub> = fluid capacitance $\left(\frac{\text{m}^5}{\text{N}}\right)$	I = fluid inertia $\left(\frac{\text{Kg}}{\text{m}^4}\right)$

### Basic Electric Circuit Analysis

Element	Parts like resistors, capacitors, inductors & transformers
Wires and connections	Direct the current, but do not affect voltage
Circuit	Wires and elements connected to form loops
Voltage	Measured as a difference <b>across</b> an element
Current	Flows <b>through</b> a wire or element
Kirchhoff's Current Law (KCL)	Current in = current out of all elements, wires & connections
Kirchhoff's Voltage Law (KVL)	Voltage gains = voltage "losses" around any circuit loop
Node	Connected wires and connections which all have the same voltage
Ground	Zero-reference node for all other nodal voltages
Branch	Connected wires and elements which all have the same current
Power P = V·I	Power = Across variable x Through variable

Voltage Source



Constant voltage regardless of current in or out


Current Source



Constant current regardless of voltage + or -

# Passive Electrical Elements

## Resistors

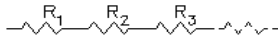

**series:**  $R_{eq} = R_1 + R_2 + R_3 + \dots$

Exactly the **same current** through each resistor

**voltage divider:**


$$V_{Rn} = V_{total} \cdot \frac{R_n}{R_1 + R_2 + R_3 + \dots}$$

**parallel:**  $R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots}$

Exactly the **same voltage** across each resistor

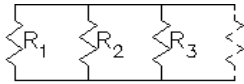**current divider:**

$$I_{Rn} = I_{total} \cdot \frac{\frac{1}{R_n}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots}$$



Resistors dissipate power  $P = V \cdot I = I^2 \cdot R = \frac{V^2}{R}$


## Capacitors

$$C = \frac{Q}{V} \quad \text{farad} = \frac{\text{coul}}{\text{volt}} = \frac{\text{amp} \cdot \text{sec}}{\text{volt}} \quad v_C = \frac{1}{C} \int_{-\infty}^t i_C dt = \frac{1}{C} \int_0^t i_C dt + v_C(0) \quad i_C = C \cdot \frac{d}{dt} v_C$$


Energy stored in electric field:  $E_C = \frac{1}{2} \cdot C \cdot V^2$

Capacitor voltage **cannot** change instantaneously

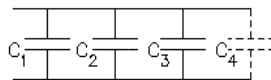**parallel:**  $C_{eq} = C_1 + C_2 + C_3 + \dots$



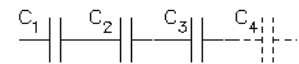**series:**  $C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots}$



**Steady-state sinusoids:**

Impedance:  $Z_C = \frac{1}{j \cdot \omega \cdot C} = \frac{-j}{\omega \cdot C}$

**Laplace:**

Impedance:  $Z_C = \frac{1}{C \cdot s}$

Current leads voltage by 90 deg


## Inductors

$$\text{henry} = \frac{\text{volt} \cdot \text{sec}}{\text{amp}} \quad i_L = \frac{1}{L} \int_{-\infty}^t v_L dt = \frac{1}{L} \int_0^t v_L dt + i_L(0) \quad v_L = L \cdot \frac{d}{dt} i_L$$


Energy stored in magnetic field:  $E_L = \frac{1}{2} \cdot L \cdot I_L^2$

Inductor current **cannot** change instantaneously

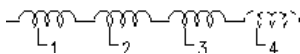**series:**  $L_{eq} = L_1 + L_2 + L_3 + \dots$



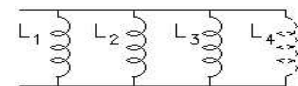**parallel:**  $L_{eq} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots}$



**Steady-state sinusoids:**

Impedance:  $Z_L = j \cdot \omega \cdot L$

**Laplace:**

Impedance:  $Z_L = L \cdot s$

Current lags voltage by 90 deg



## Transformers (ideal)

Ideal:  $P_1 = P_2$  power in = power out

Turns ratio =  $N = \frac{N_1}{N_2} = \frac{V_1}{V_2} = \frac{I_2}{I_1}$

Note: some books define the turns ratio as  $N_2/N_1$

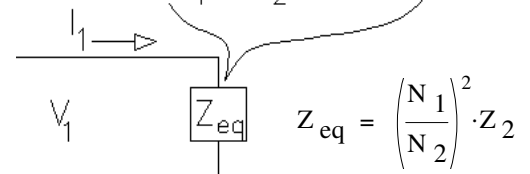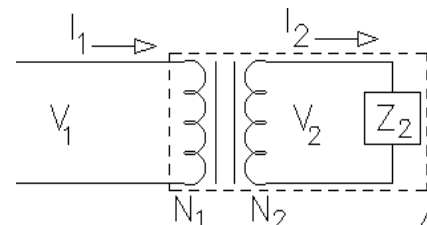Equivalent impedance in primary:  $Z_{eq} = N^2 \cdot Z_2 = \left(\frac{N_1}{N_2}\right)^2 \cdot Z_2$



You can replace the entire transformer and load with ( $Z_{eq}$ ).

This "impedance transformation" can work across systems.

# Mechanical system with linear motion (translational)



## Mechanical translational

Through Variable:

$F = \text{Force (N)}$

Across Variable:

$v = \text{velocity } \left(\frac{\text{m}}{\text{sec}}\right)$

$$\int v \, dt = \frac{V(s)}{s}$$

$x = \text{displacement (m)}$

$X(s) = \text{displacement (m}\cdot\text{sec)}$   
(in freq domain)

## Electrical

$I = \text{current (A)}$

Source: /

$V = \text{voltage (V)}$

Source: \

Source: \  $v = \frac{d}{dt}x$   
or  $s \cdot X(s)$


Dissipation element:

power


$$P = v \cdot F = \frac{F^2}{B}$$

$$= v^2 \cdot B$$

### Damper or friction

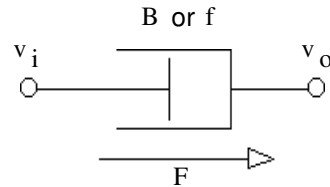

### Resistor

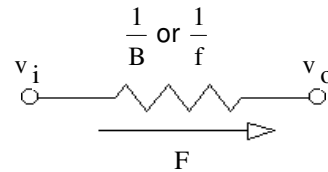

### Impedance


$$\frac{1}{B} \text{ or } \frac{1}{f}$$

Through variable energy storage:


$$E = \frac{1}{2} \cdot \frac{1}{k} \cdot F^2 = \frac{1}{2} \cdot k \cdot x^2$$

(F=kx)

### Spring

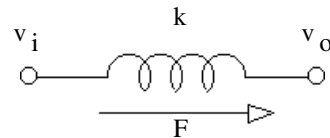


### Inductor

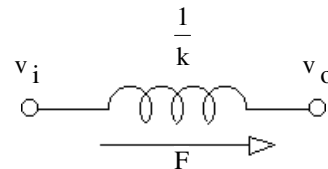

$$\frac{s}{k}$$


Springs are sometimes shown like this:

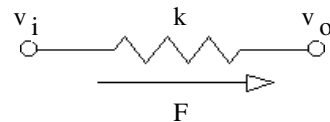


Through variable energy storage:

$$E = \frac{1}{2} \cdot M \cdot v^2$$

### Mass

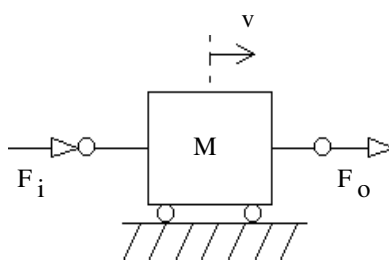


### Capacitor hooked to ground

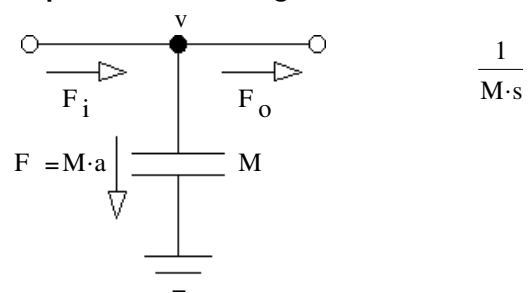


$$\frac{1}{M \cdot s}$$

### Mass with friction

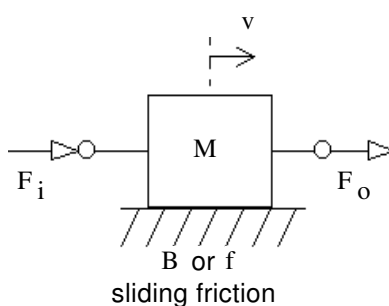

### Capacitor and resistor

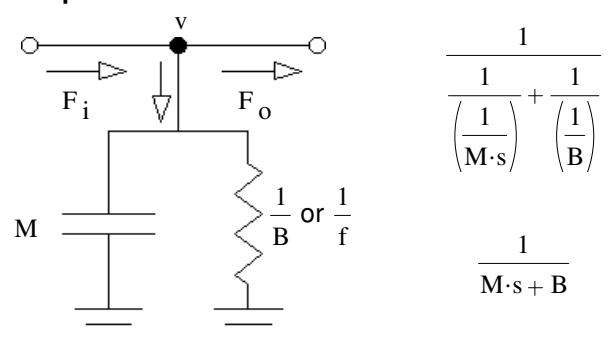

$$\frac{1}{\left(\frac{1}{M \cdot s}\right) + \left(\frac{1}{B}\right)}$$

$$\frac{1}{M \cdot s + B}$$

# Mechanical system with circular motion (rotational)

Through Variable:

Across Variable:

$$\int \omega dt$$

$$\frac{\omega(s)}{s}$$

Dissipation element:

power

$$P = v \cdot T = \frac{T^2}{B}$$

$$= \omega^2 \cdot B$$

Through variable energy storage:

$$E = \frac{1}{2} \cdot \frac{1}{k} \cdot T^2$$

Through variable energy storage:

$$E = \frac{1}{2} \cdot J \cdot \omega^2$$

## Mechanical rotational

$T$  = Torque (N·m)

$\omega$  = angular velocity ( $\frac{\text{rad}}{\text{sec}}$ )

$\theta$  = angular displacement (rad)


$\theta(s)$  = angular displacement (rad·sec) (in freq domain)

## Electrical


$I$  = current (A)

$V$  = voltage (V)

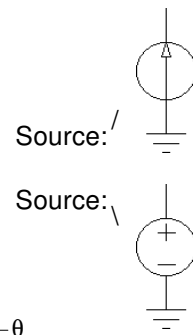
Source:  $\omega = \frac{d}{dt} \theta$  or  $s \cdot \theta(s)$



### Damper or friction

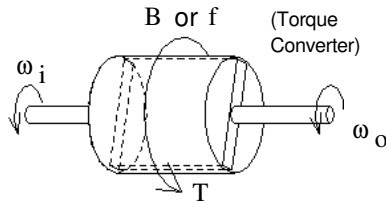


### Resistor

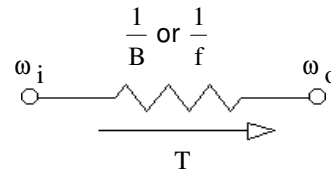


### Impedance

$$\frac{1}{B} \text{ or } \frac{1}{f}$$

### Springs

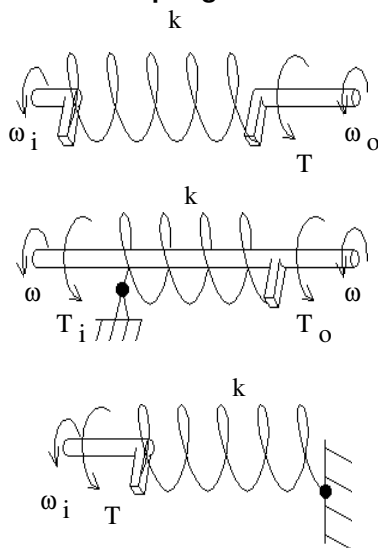


### Inductor

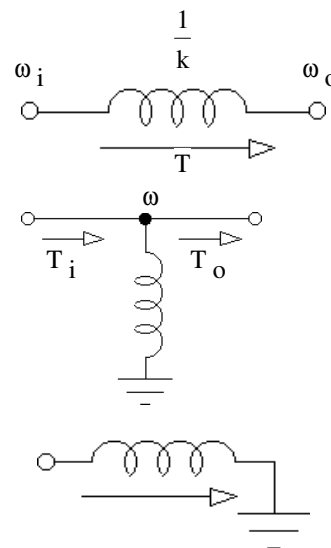


$$\frac{s}{k}$$

### Moment of Inertia, J

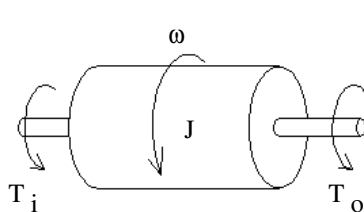


### Capacitor hooked to ground

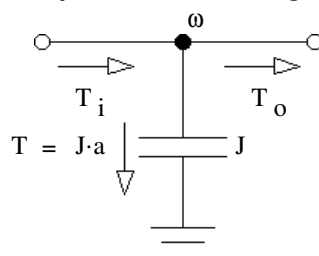


$$\frac{1}{J \cdot s}$$

### J with friction

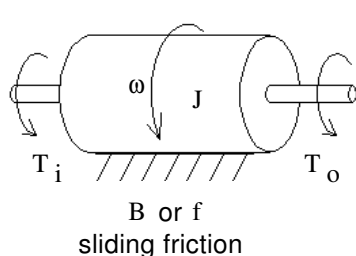

### Capacitor and resistor

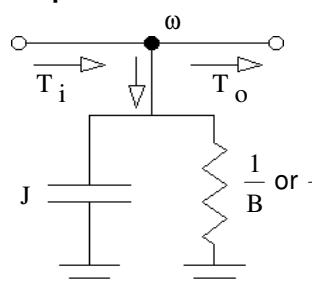


$$\frac{1}{\left(\frac{1}{J \cdot s}\right) + \left(\frac{1}{B}\right)}$$

$$\frac{1}{J \cdot s + B}$$


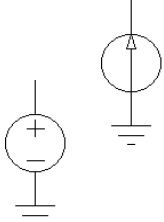
# Fluid (hydraulic) system

**Fluid**  
 Through Variable:  $Q = \text{volumetric flow rate} \left( \frac{\text{m}^3}{\text{sec}} \right)$   
 Across Variable:  $P = \text{Pressure} \left( \frac{\text{N}}{\text{m}^2} \right)$  or (Pa)



**Electrical**  
 Sources  
 $I = \text{current (A)}$   
 $V = \text{voltage (V)}$





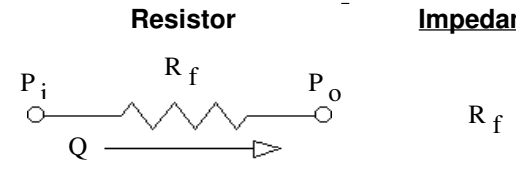
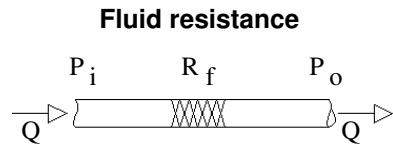
Dissipation element:  
 power  
 $P = P \cdot Q = \frac{Q^2}{R_f}$   
 $= P^2 \cdot R_f$



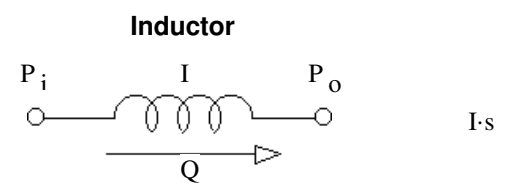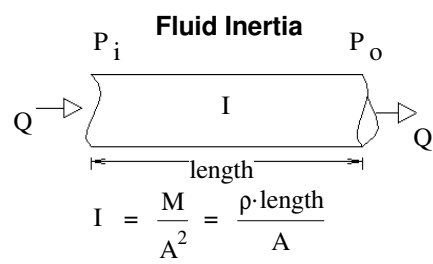Through variable  
 energy storage:  
 $E = \frac{1}{2} \cdot I \cdot Q^2$




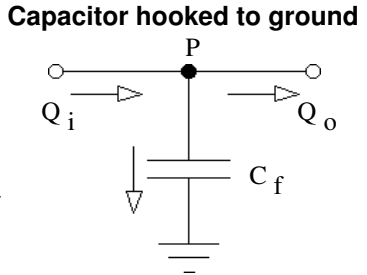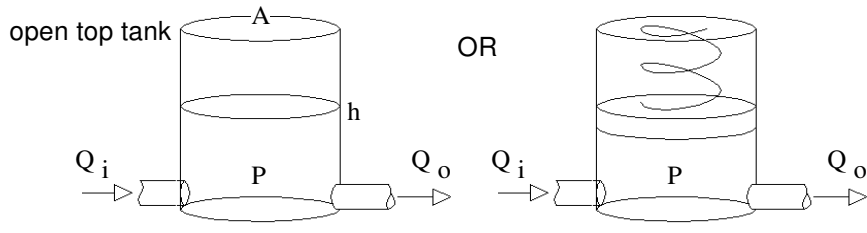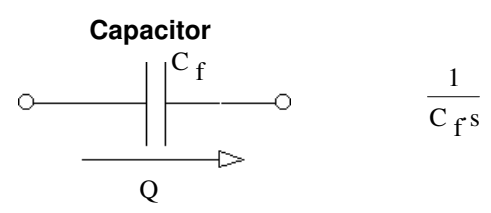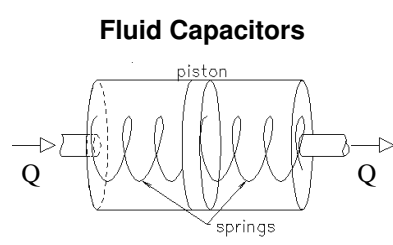Through variable  
 energy storage:  
 $E = \frac{1}{2} \cdot C_f \cdot P^2$



$C_f = \frac{\Delta \text{volume}}{\Delta \text{pressure}}$  for all capacitors  
 $= \frac{\Delta h \cdot A}{\Delta h \cdot \rho \cdot g} = \frac{A}{\rho \cdot g}$  For open top tank


## Turbine or Pump

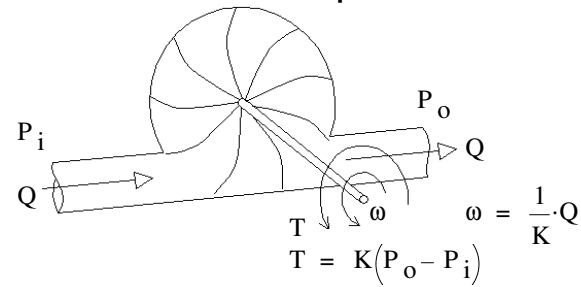

Turbines & pistons convert through variables to across variables & vice versa, so there are no good electrical analogies.

Yet you can still transform an impedance from a mechanical system into the fluid system. You'll find that capacitors become inductors, inductors become capacitors and parallel swaps with series.

## Piston & Cylinder

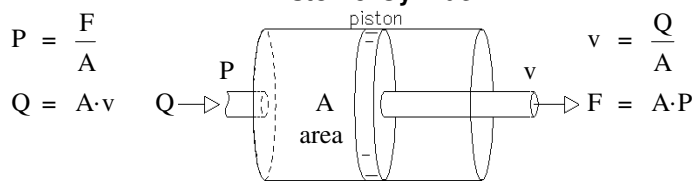


$Z_{eq} = \frac{\Delta \cdot P}{Q} = \frac{\left( \frac{T}{K} \right)}{K \cdot \omega} = \frac{1}{K^2} \cdot \frac{T}{\omega} = \frac{1}{K^2} \cdot \frac{1}{Z_2} = \frac{1}{K^2 \cdot Z_2}$

$Z_{eq} = \frac{P}{Q} = \frac{\left( \frac{F}{A} \right)}{A \cdot v} = \frac{1}{A^2} \cdot \frac{F}{v} = \frac{1}{A^2} \cdot \frac{1}{Z_2} = \frac{1}{A^2 \cdot Z_2}$

# Transducers and Transformers


A transducer converts power from one type to another. We can model many of them with transformers. Transformers increase the through variable and correspondingly decrease the across variable or vice-versa.

## Lever

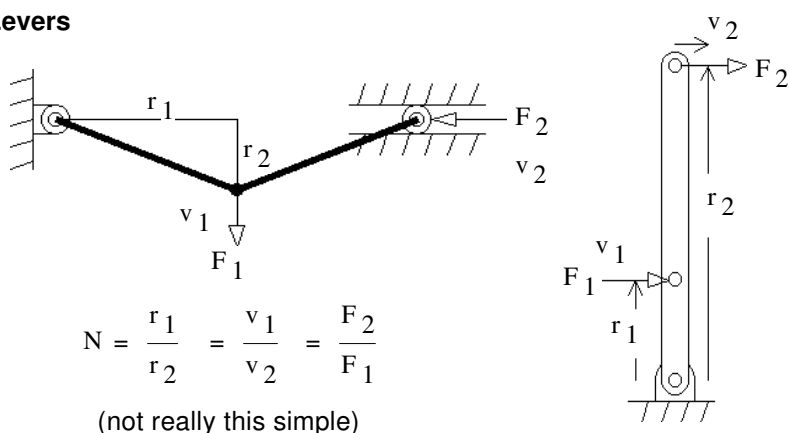

$$N = \frac{r_1}{r_2} = \frac{v_1}{v_2} = \frac{F_2}{F_1}$$


(not really this simple)

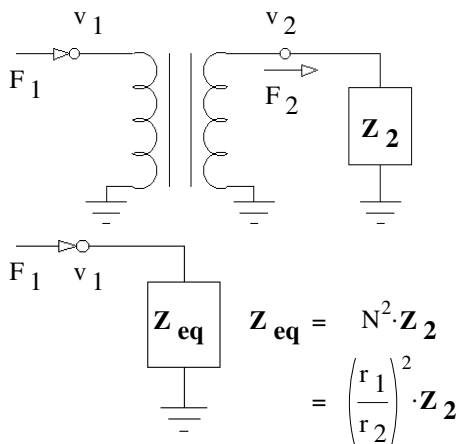


$$Z_{eq} = N^2 \cdot Z_2 = \left(\frac{r_1}{r_2}\right)^2 \cdot Z_2$$
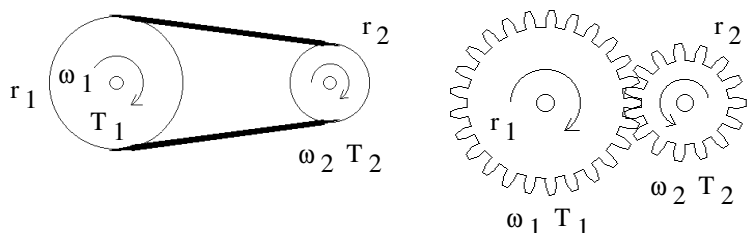
## Belts, chains, & gears

r = radius of pulley or pitch radius of gears



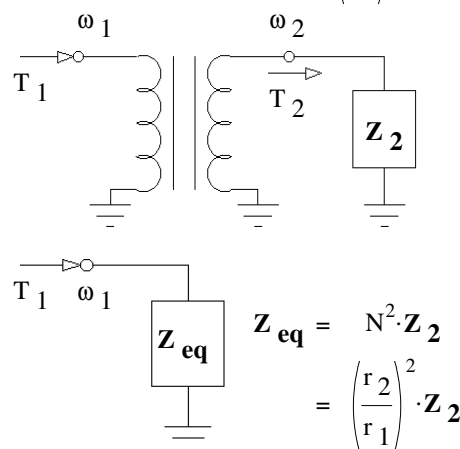
$$N = \frac{r_2}{r_1} = \frac{\omega_1}{\omega_2} = \frac{T_2}{T_1} = \text{gear tooth ratio} \left(\frac{N_2}{N_1}\right)$$



$$Z_{eq} = N^2 \cdot Z_2 = \left(\frac{r_2}{r_1}\right)^2 \cdot Z_2$$

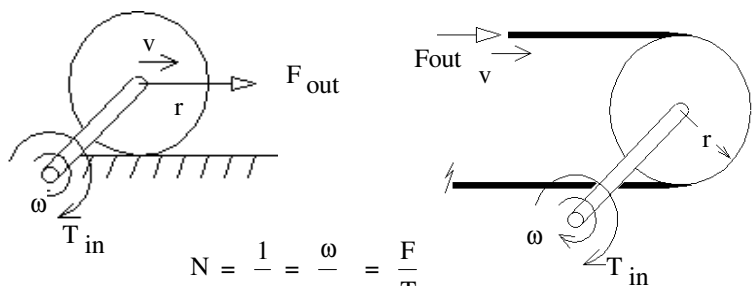
## Tires, racks, & conveyors

r = radius of wheel or pitch radius of pinion gear




$$N = \frac{1}{r} = \frac{\omega}{v} = \frac{F}{T}$$

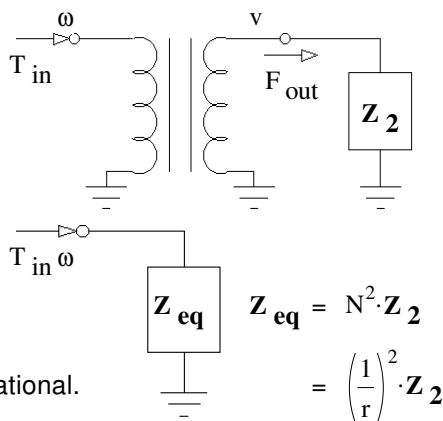Note:  $N = r$  if the input is linear motion and output is rotational.




$$Z_{eq} = N^2 \cdot Z_2 = \left(\frac{1}{r}\right)^2 \cdot Z_2$$

## DC Motors

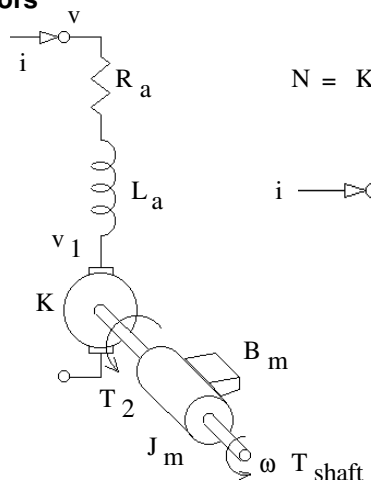


$$N = K = \frac{v_1}{\omega} = \frac{T_2}{i}$$

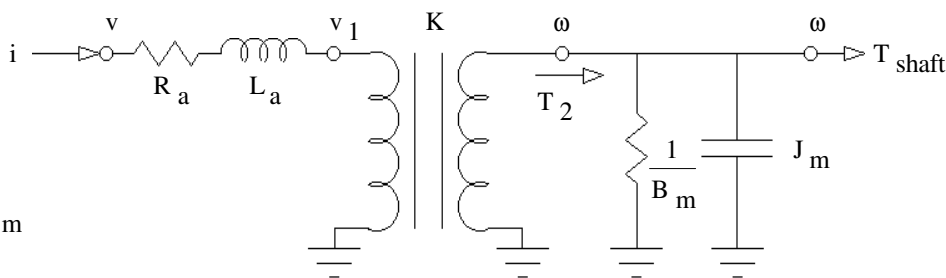


**Example 1**


Mechanical system

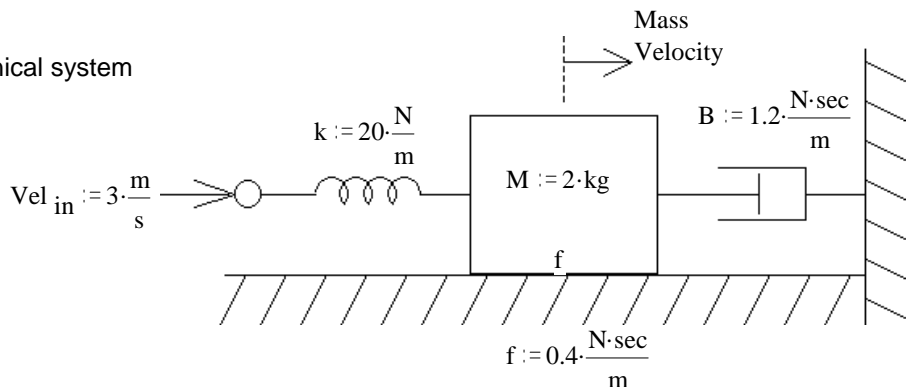

Elements

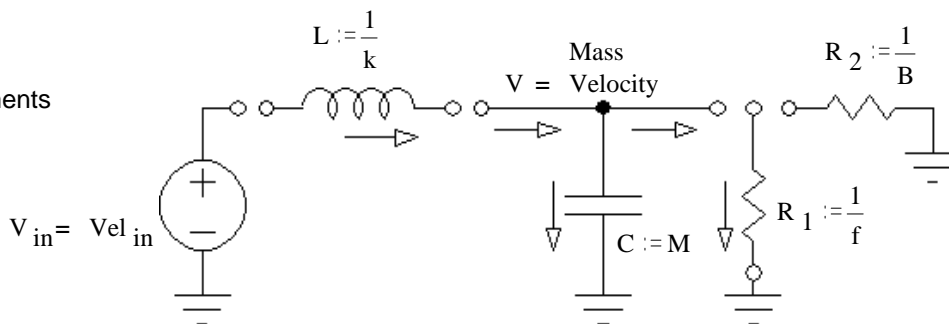

Circuit

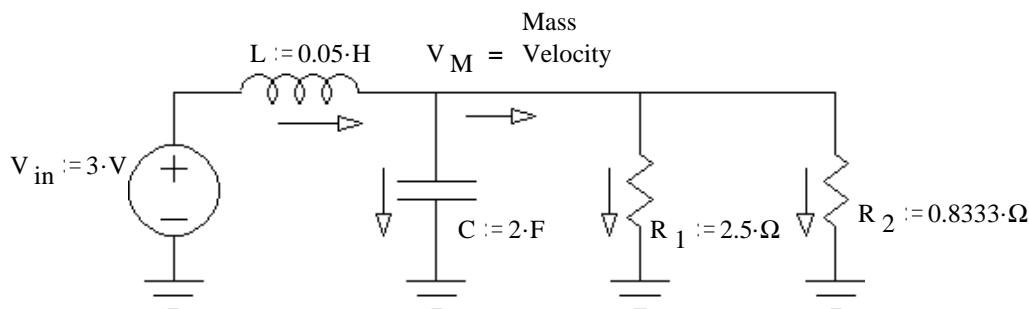

$$R_{eq} := \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} \quad R_{eq} = 0.625 \cdot \Omega$$

$$B_{eq} := \frac{1}{R_{eq}}$$

Transfer function


$$\frac{V_M(s)}{V_{in}(s)} = \frac{\frac{1}{C \cdot s + \frac{1}{R_{eq}}}}{L \cdot s + \frac{1}{C \cdot s + \frac{1}{R_{eq}}}} \cdot \frac{\left( C \cdot s + \frac{1}{R_{eq}} \right)}{\left( C \cdot s + \frac{1}{R_{eq}} \right)} = \frac{1}{L \cdot C \cdot s^2 + \frac{L}{R_{eq}} \cdot s + 1} \cdot \frac{\left( \frac{1}{L \cdot C} \right)}{\left( \frac{1}{L \cdot C} \right)} = \frac{\frac{1}{L \cdot C}}{s^2 + \frac{1}{C \cdot R_{eq}} \cdot s + \frac{1}{L \cdot C}}$$

$$\frac{V_M(s)}{Vel_{in}(s)} = \frac{\frac{k}{M}}{s^2 + \frac{B_{eq}}{M} \cdot s + \frac{k}{M}} = \frac{\frac{20 \cdot N}{2 \cdot kg \cdot m}}{s^2 + \frac{1.6 \cdot N \cdot sec}{2 \cdot kg \cdot m} \cdot s + \left( \frac{20 \cdot N}{2 \cdot kg \cdot m} \right)} = \frac{10}{s^2 + 0.8 \cdot s + 10} \quad \text{same, either way}$$


without units

**ECE 3510 Mechanical to Electrical Examples p.2**


**Example 2**

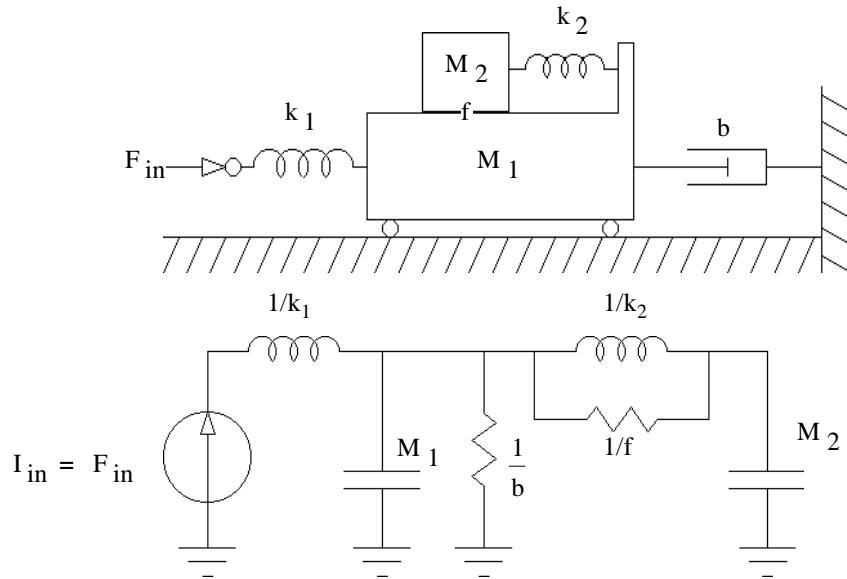


**Example 3**

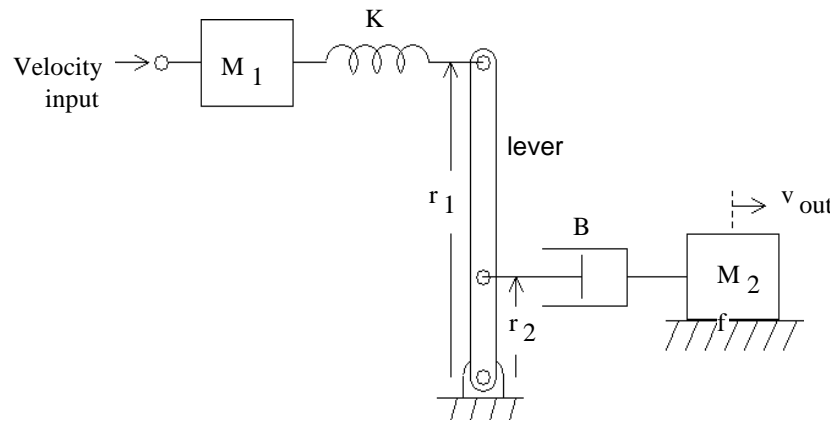

Circuit with a transformer.

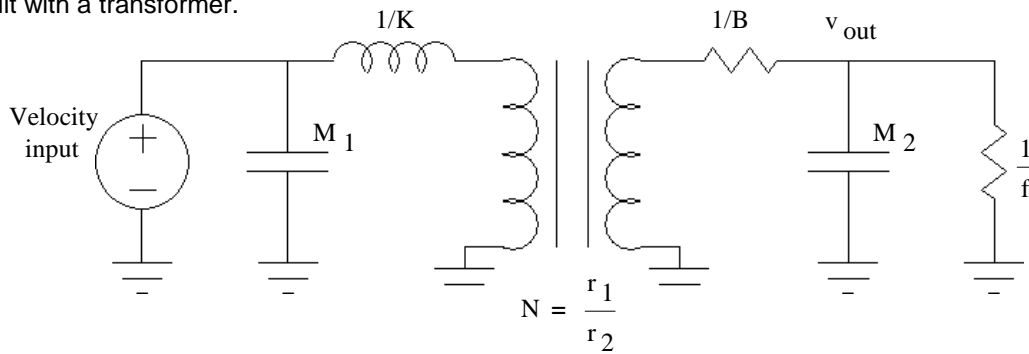


Circuit without a transformer.

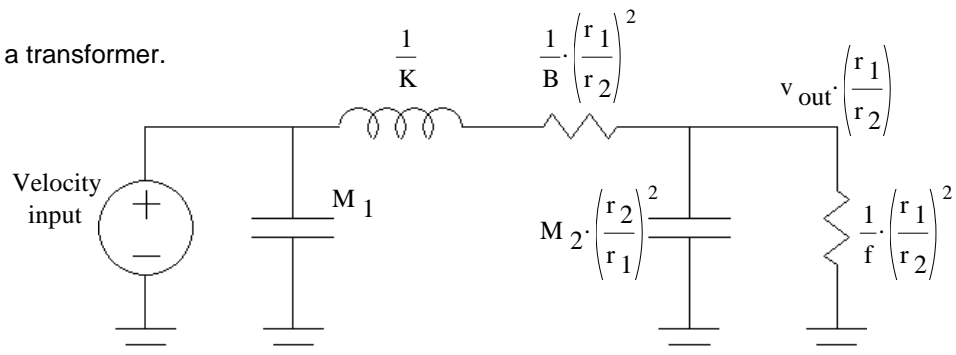




# ECE 3510 Mechanical to Electrical Examples p.3


## Example 4

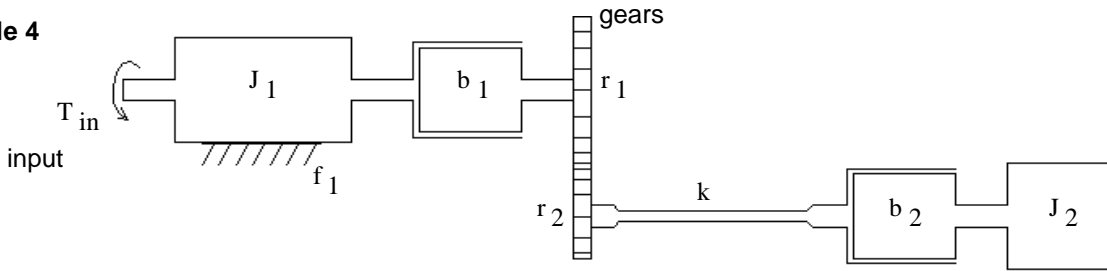



Circuit with a transformer.

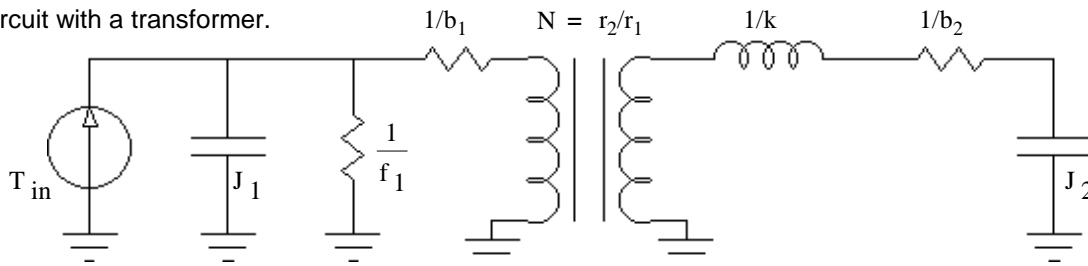

Circuit without a transformer.

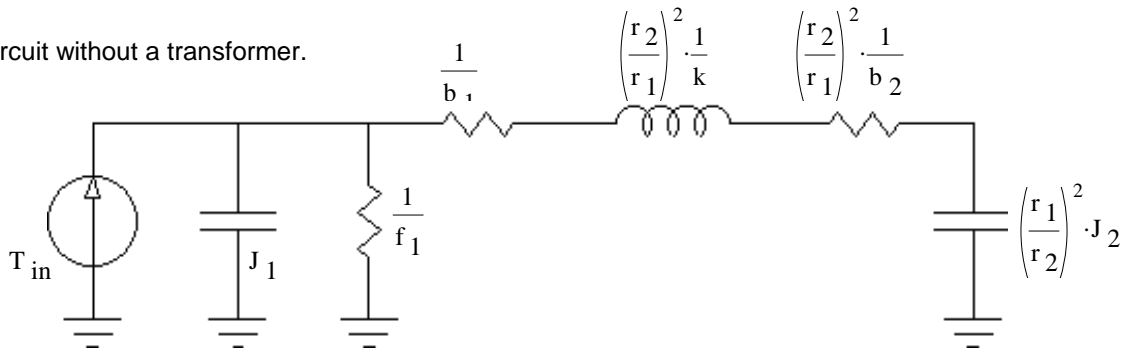


## Example 5, fluids

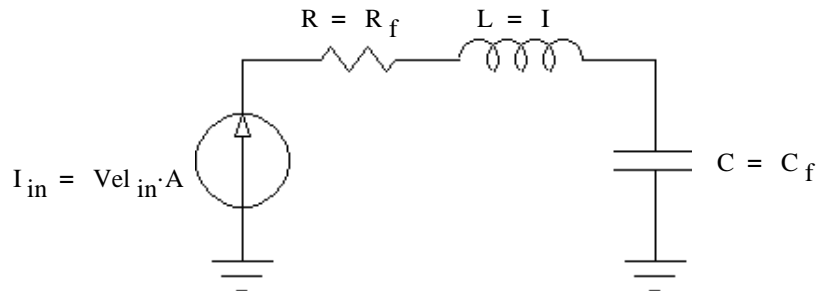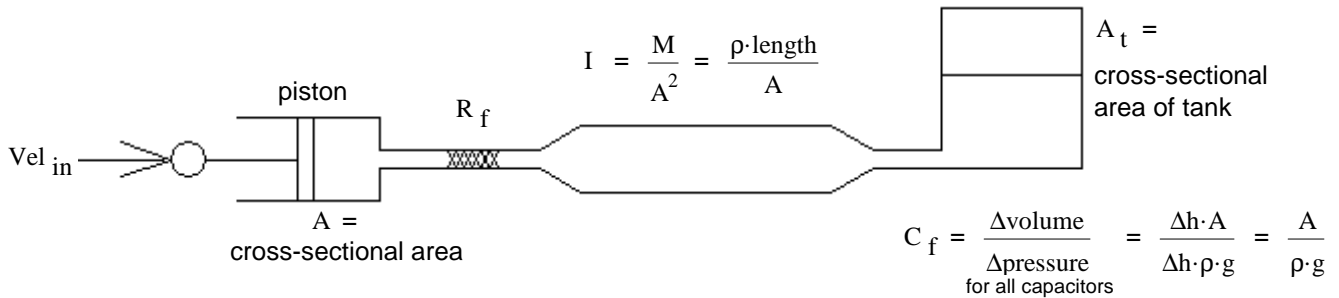


# ECE 3510 Mechanical to Electrical Examples p.4


## Example 6

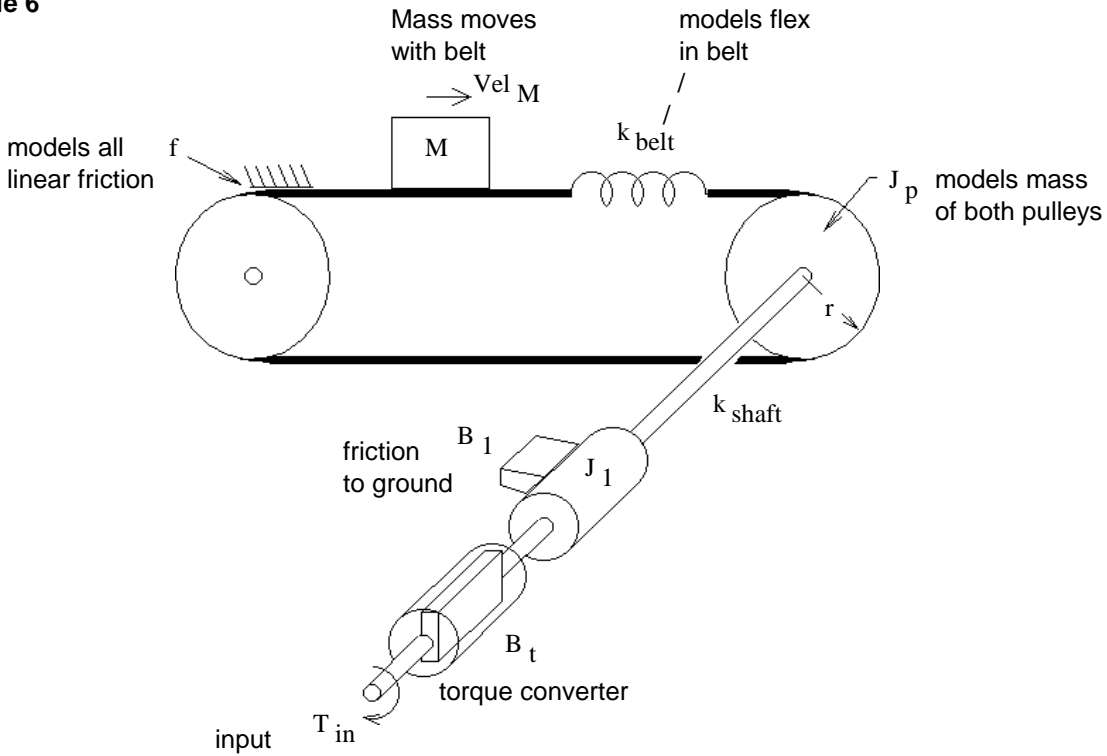

Circuit with a transformer.

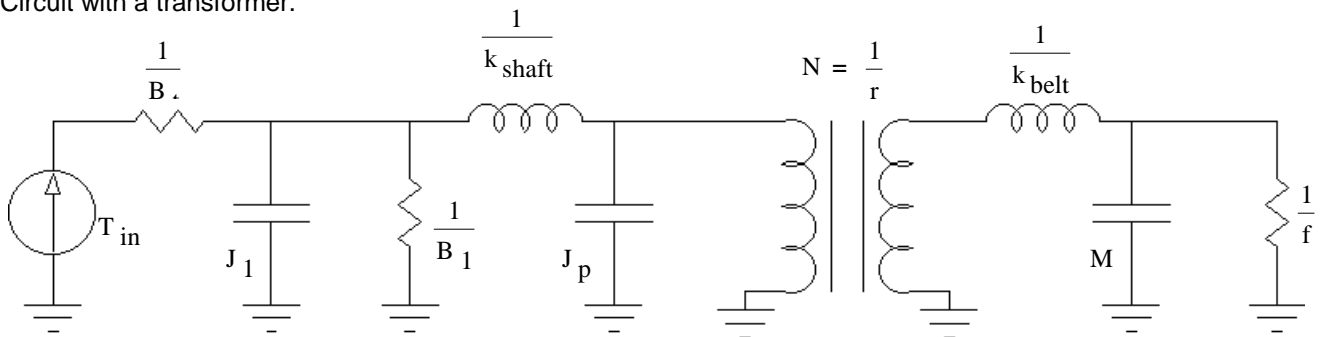

Circuit without a transformer.

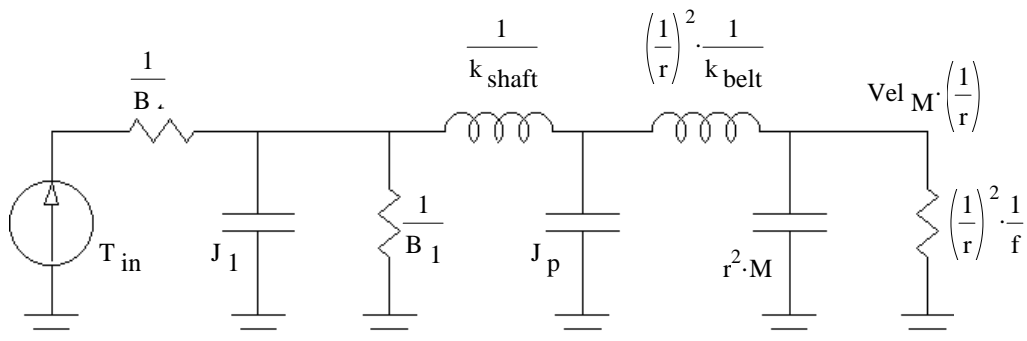

Use the current-force analogy discussed in class for the following problems.

1. a) Find the equivalent electric circuit for the mechanical system shown.  $F_{in}$  is an input.


b) Find the transfer function for the system. Put it in the standard form.  $\frac{v_{out}(s)}{F_{in}(s)}$

c) Check the units of all coefficients of the transfer function to make sure they agree and work out to the units of velocity over force.


Recall that the units of  $s = \frac{1}{\text{sec}}$

d) The resonant frequency of an electrical circuit can be found from  $\frac{1}{\sqrt{L \cdot C}}$ . What is it for this system?

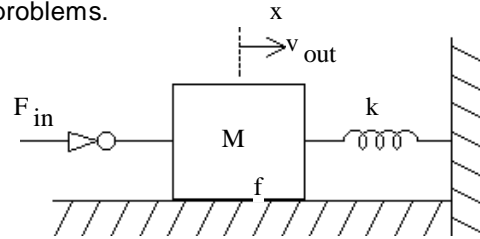e) Find the transfer function for the system. Put it in the standard form.  $\frac{x_{out}(s)}{F_{in}(s)}$  Where  $x$  is the displacement of the mass rather than its velocity.





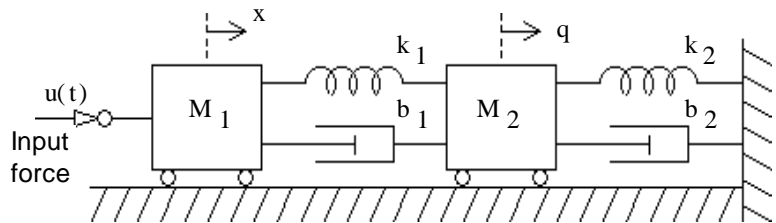2. Find the equivalent electric circuit for the mechanical system shown.  $u(t)$  is an input. Show  $x$ -velocity and  $q$ -velocity on the circuit.








3. Find the equivalent electric circuit for the mechanical system shown.  $r(t)$  is an input. Show  $v_1$  &  $v_2$  on the circuit.

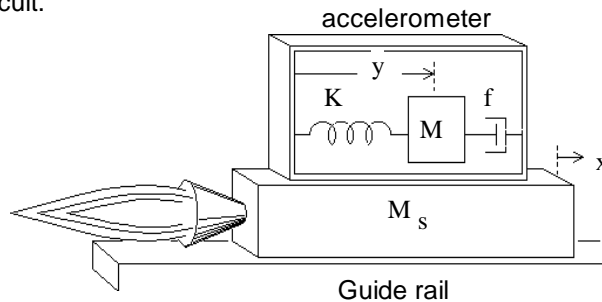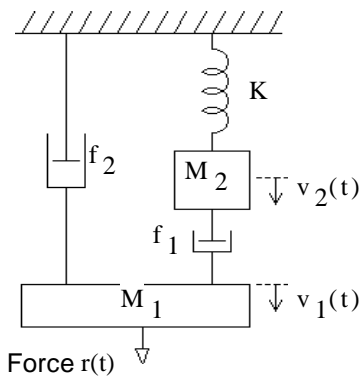4. Find the equivalent electric circuit for the levitated rocket sled shown. The rocket is a force input. There is no friction between the sled and guide rail, but there is air resistance (which can be modeled in exactly the same way as friction between the sled and guide rail) The accelerometer is firmly mounted onto the sled. Show  $x$ -velocity and  $y$ -velocity on the circuit.




**Answers**

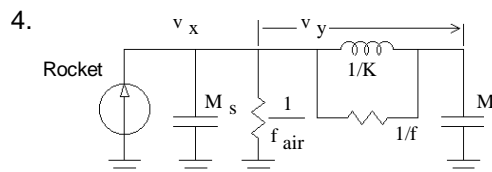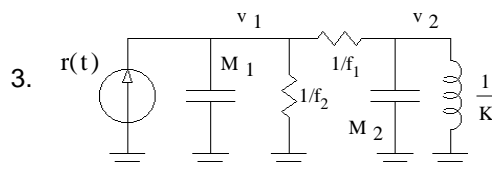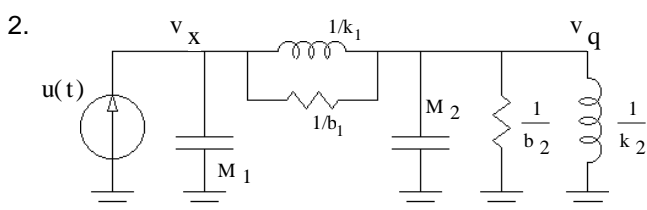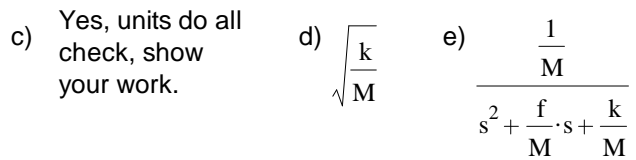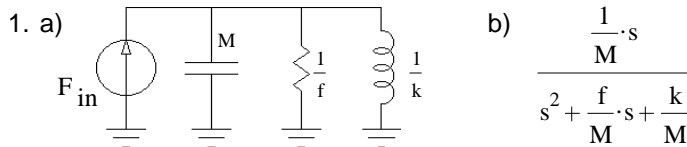


Use the current-force analogy discussed in class for the following problems.

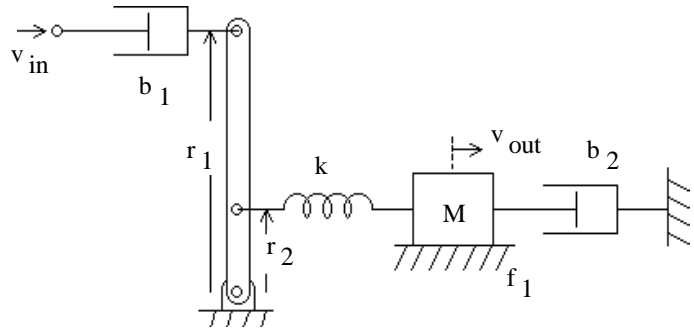1. Find the equivalent electric circuit for the mechanical system shown.  $v_{in}$  is the input.




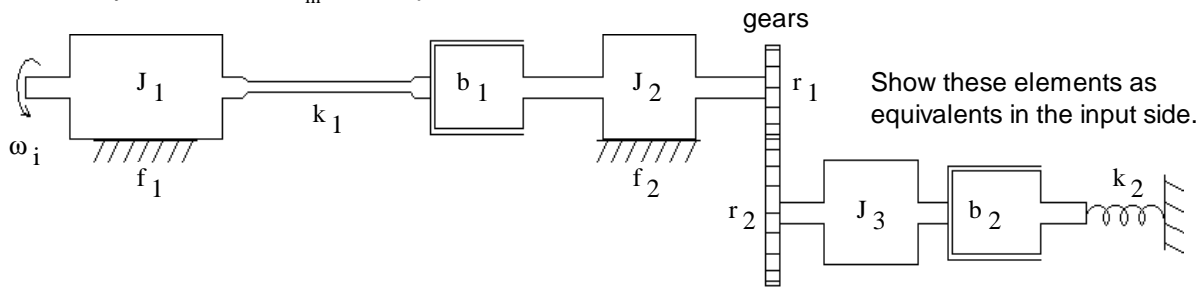2. Find the equivalent electric circuit for the mechanical system shown.  $\omega_{in}$  is the input.



Show these elements as equivalents in the input side.

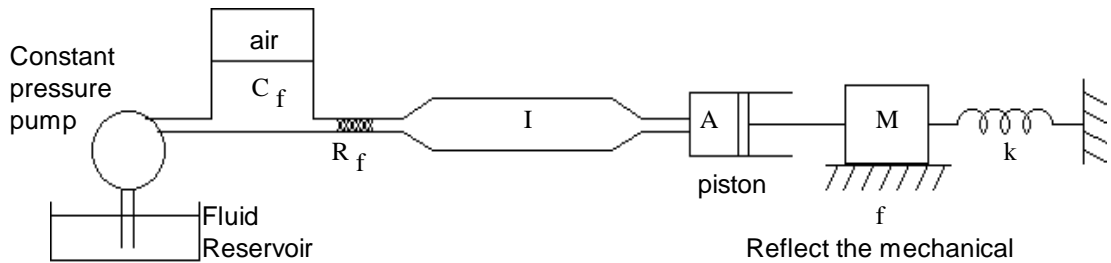3. Find the equivalent electric circuit for the fluid system shown.



Reflect the mechanical elements into the fluid system.

**Answers**

