

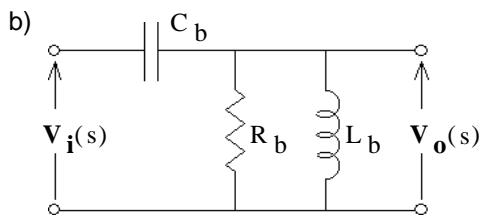


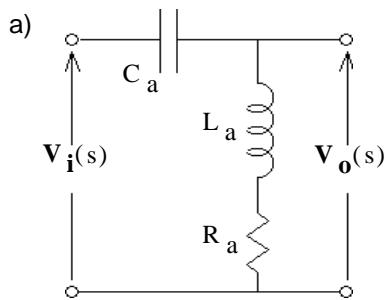1. Find the input impedance (
- $Z_{in}(s)$
-) and output impedance (
- $Z_{out}(s)$
-) of each of the circuits below.




2. Now hook circuit b), above to the output of circuit a). Find the input impedance (
- $Z_{in}(s)$
-) and output impedance (
- $Z_{out}(s)$
-) of the combination circuit.

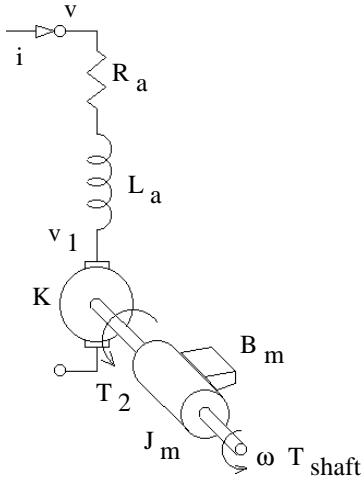3. The following is a model of a DC motor. Find the input and output impedances.


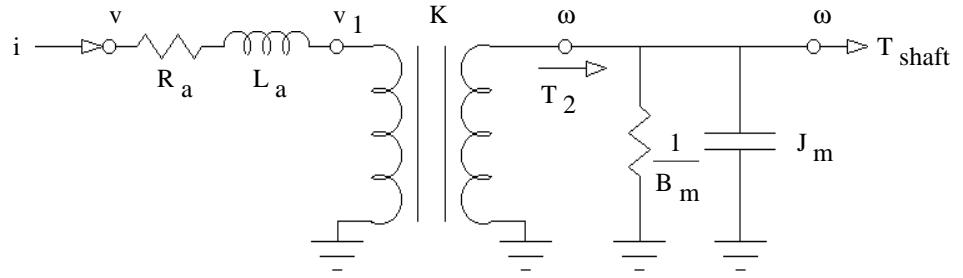
$$N = K = \frac{v_1}{\omega} = \frac{T_2}{i}$$



Answers

$$1. \text{ a) } Z_{in} = \frac{1}{C_a \cdot s} + R_a + L_a \cdot s$$

$$\frac{1}{C_b} \cdot s$$

$$Z_{out} = \frac{\frac{1}{C_a} \cdot s + \frac{R_a}{L_a \cdot C_a}}{s^2 + \frac{R_a}{L_a} \cdot s + \frac{1}{L_a \cdot C_a}}$$

$$\text{b) } Z_{in} = \frac{1}{C_b \cdot s} + \frac{1}{R_b} + \frac{1}{L_b \cdot s}$$

$$\text{b) } Z_{out} = \frac{s^2 + \frac{1}{R_b \cdot C_b} \cdot s + \frac{1}{L_b \cdot C_b}}{s^2 + \frac{1}{R_b \cdot C_b} \cdot s + \frac{1}{L_b \cdot C_b}}$$

$$2. \quad Z_{in} = \frac{1}{C_a \cdot s} + \frac{1}{R_a + L_a \cdot s} + \frac{1}{\frac{1}{C_b \cdot s} + \frac{1}{R_b} + \frac{1}{L_b \cdot s}}$$

$$Z_{out} = \frac{1}{\frac{1}{C_a \cdot s + \frac{1}{R_a + L_a \cdot s}} + \frac{1}{\frac{1}{C_b \cdot s} + \frac{1}{R_b} + \frac{1}{L_b \cdot s}}}$$

$$3. \quad Z_{in} = R_a + L_a \cdot s + \frac{K^2}{B_m + J_m \cdot s}$$

$$Z_{out} = \frac{1}{\frac{K^2}{R_a + L_a \cdot s} + B_m + J_m \cdot s}$$