




PLC Fundamentals – Ladder Logic Fundamentals

MET 382
Controls & Instrumentation
for Automation

Spring '08
T.E. Kostek

Topics

- PLC programming languages
- Anatomy of a ladder program
- Logic functions
- Logical continuity vs. electrical continuity
- I/O Mapping
- Mastering examine on and examine off instructions
- The PLC scanning process




2

PLC Programming Languages

- In the United States, **ladder logic** is the most popular method used to program a PLC
- This course will focus primarily on ladder logic programming
- Other programming methods include:
 - Function block diagrams (FBDs)
 - Structured text (ST)
 - Instruction List (IL)
 - Sequential function charts (SFCs)

3

Anatomy of a Ladder Program

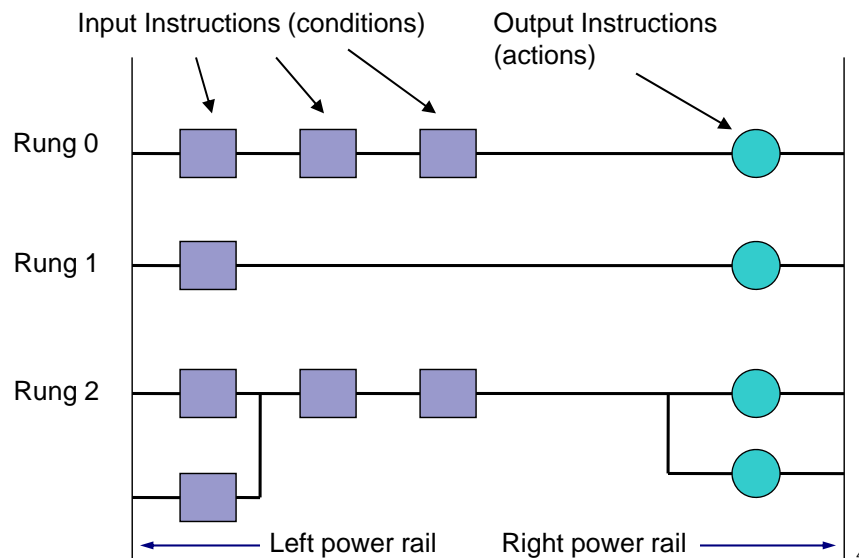

4

Anatomy of a Ladder Program (cont'd)



- Input instructions are entered on the left
- Output instructions are entered on the right
- The power rails simulate the power supply lines
 - L1 and L2 for AC circuits and +24 v and ground for DC circuits
- Most PLCs allow more than one output per rung

5

Anatomy of a Ladder Program (cont'd)

- The processor (or “controller”) scans ladder rungs from top-to-bottom and from left-to-right.
 - The basic sequence is altered whenever jump or subroutine instructions are executed.

6

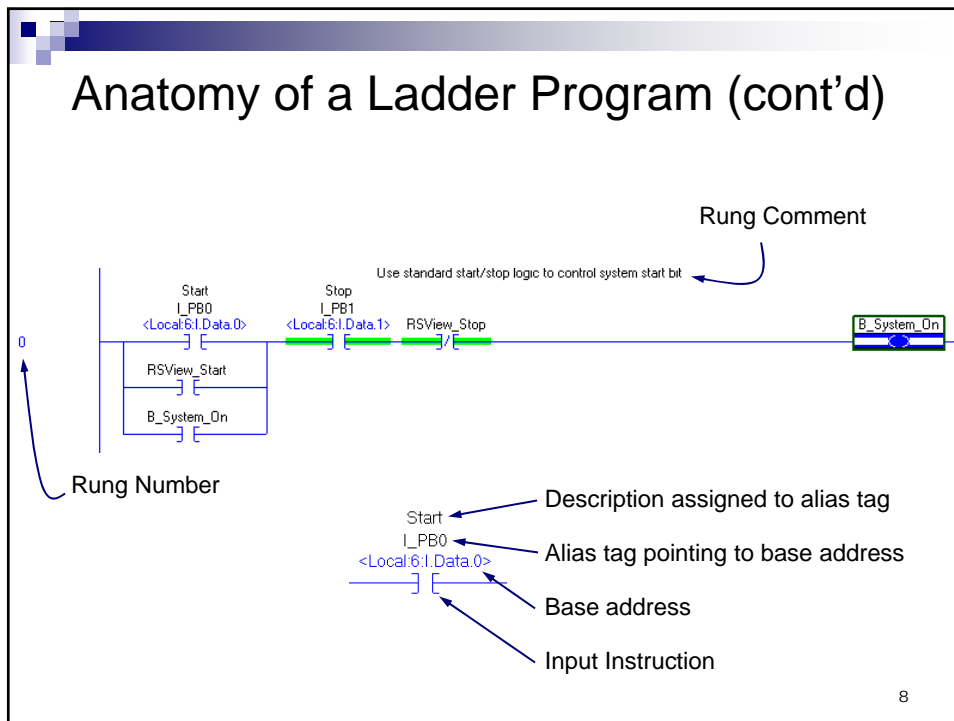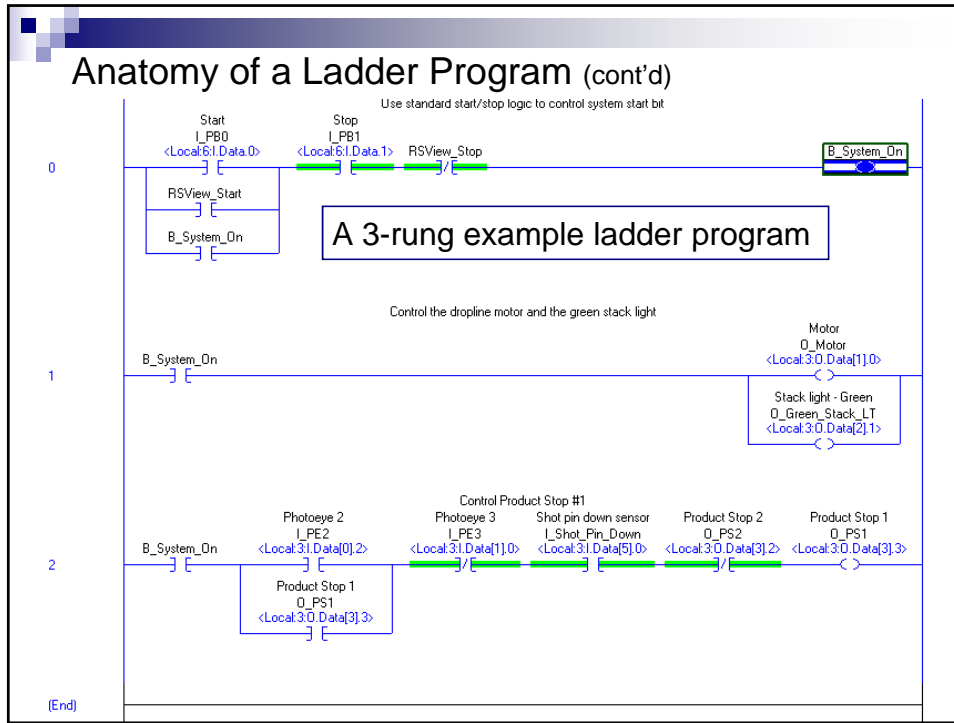

Logic Functions

- PLC programming is a logical procedure
- In a PLC program, “things” (inputs and rungs) are either TRUE or FALSE
- If the proper input conditions are TRUE:
 - The rung becomes TRUE and an output action occurs (for example, a motor turns on)
- If the proper input conditions are not TRUE:
 - The rung becomes FALSE and an output action does not occur


9

Logic Functions (cont'd)

- Ladder logic is based on the following logic functions:
 - AND
 - OR
 - Sometimes called “inclusive OR”
 - Exclusive OR


10

Logic Functions - AND

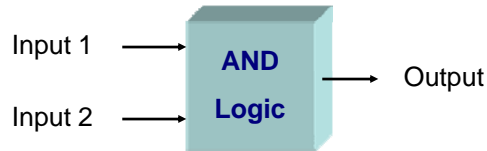


Input 1	Input 2	Output
0	0	0
0	1	0
1	0	0
1	1	1

0 → False
1 → True

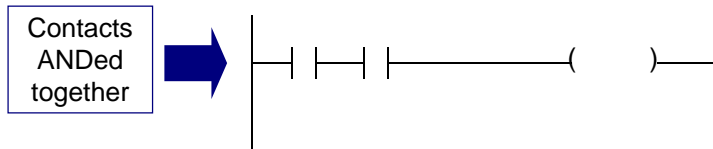


11

Logic Functions - OR

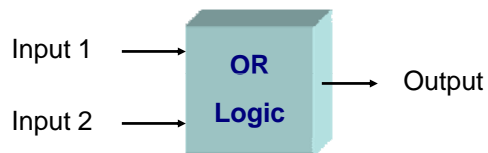

Input 1	Input 2	Output
0	0	0
0	1	1
1	0	1
1	1	1


0 → False
1 → True

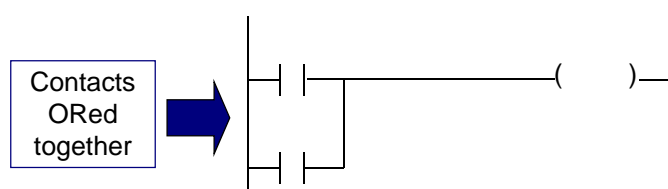

12

Logic Functions - Exclusive OR

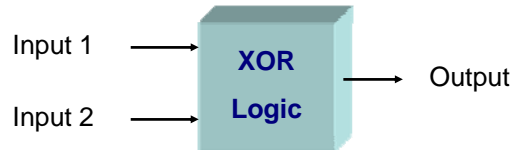In addition to ANDing and ORing, the Exclusive OR (XOR) is also useful. When the inputs are DIFFERENT, the XOR output is true.




Input 1	Input 2	Output
0	0	0
0	1	1
1	0	1
1	1	0

0 → False
1 → True

13

Logic Functions (cont'd)

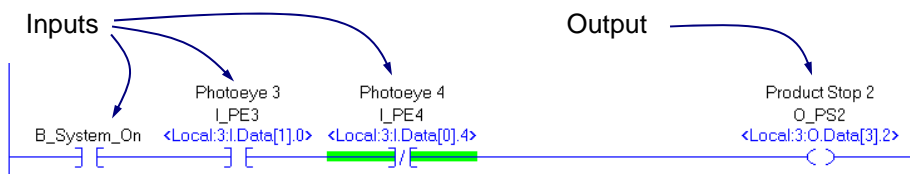■ Example 1 – Inputs ANDed together in series




Three input instructions ANDed together.

All 3 input instructions must be true in order to energize the output

14

Logic Functions (cont'd)

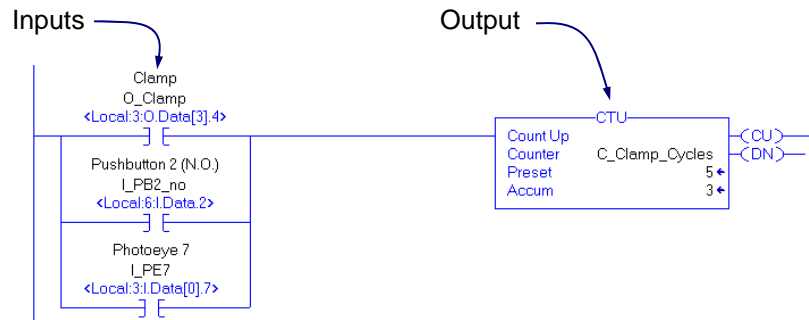- Example 2 – Inputs ORed together in parallel




Three input instructions ORed together.

If any of the 3 input instructions are true the output will be energized

15

Logic Functions (cont'd)

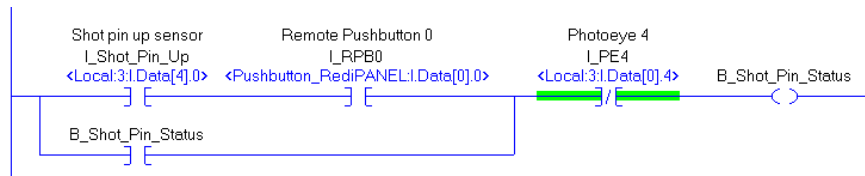- Example 3 – A combination of ANDing and ORing




16

Logical Continuity


- **Logical continuity** in a ladder rung occurs when there is a continuous path of TRUE conditions from the left power rail to the output instruction(s)
- When there is logical continuity, the rung becomes true and the output becomes energized

17

Logical Continuity – Example 1

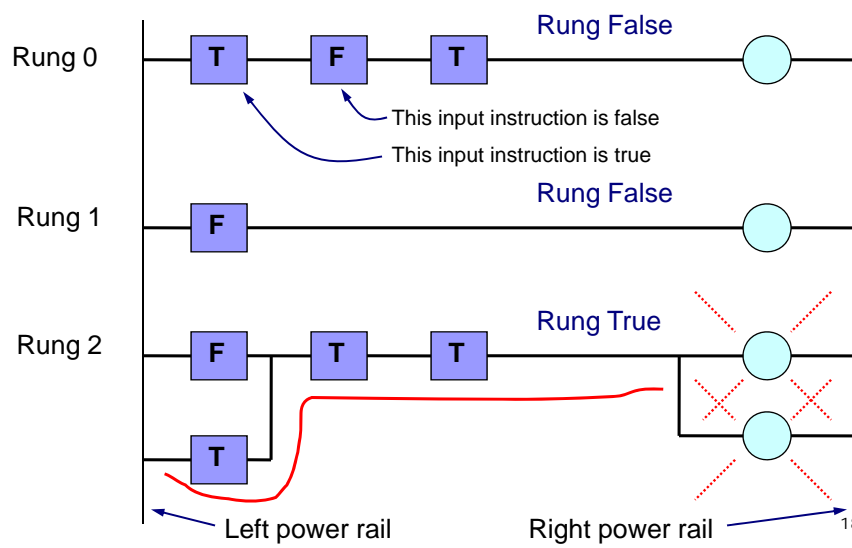

Logical Continuity – Example 2

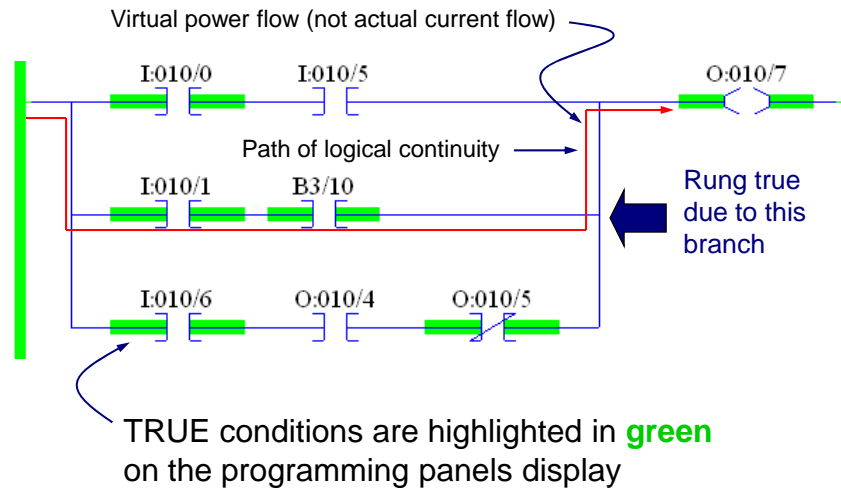



 → PLC-5 Systems

19

Logical Continuity vs. Electrical Continuity

- **Electrical continuity** in an input circuit, occurs when there is a complete path for current to flow.
- A PLC input circuit is a simple series circuit consisting of a:
 - Power supply,
 - Switch, and a
 - Load
- When there is electrical continuity, a bit in the PLCs memory (sometimes called the input image table) is set to a 1.

20

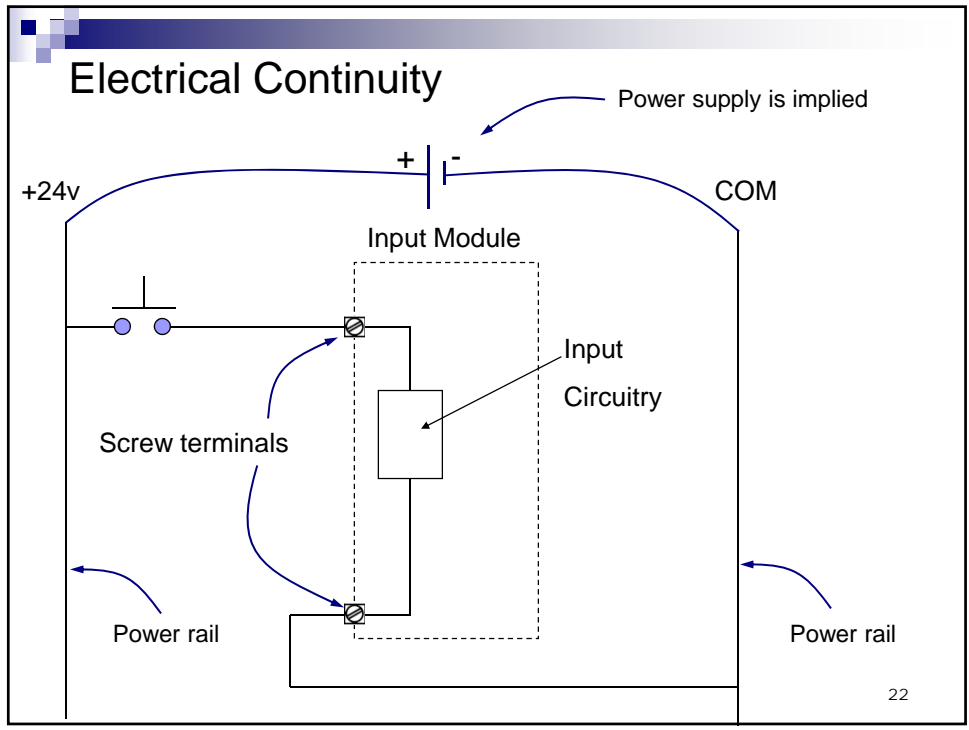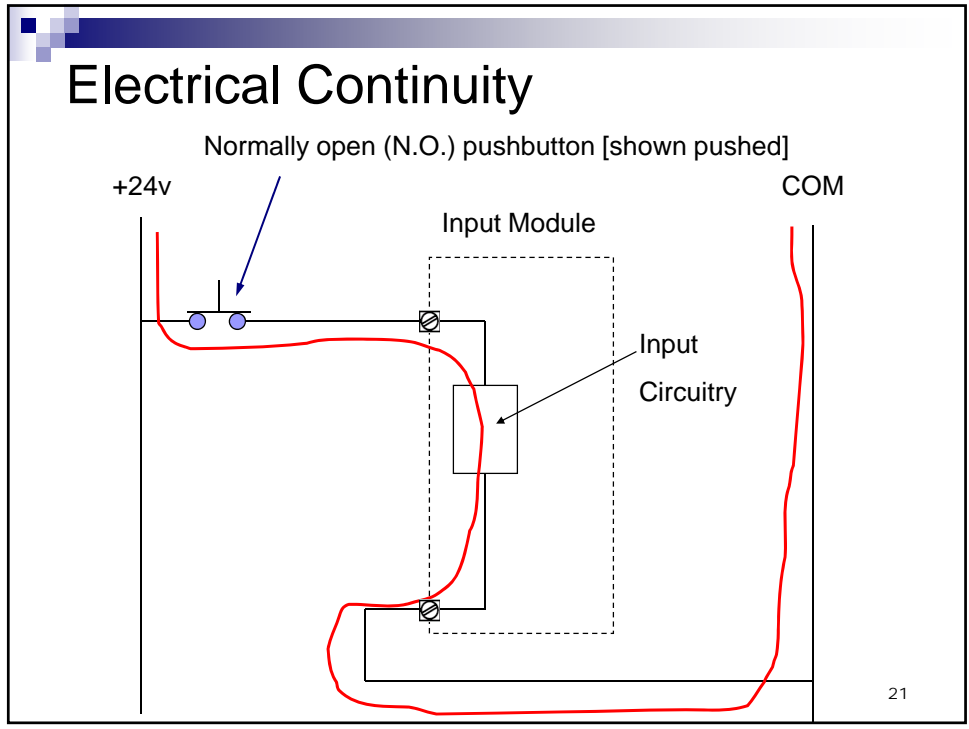

Logical vs. Electrical Continuity

- Note: It's possible to have electrical continuity and not have logical continuity (and vice versa).

Control Wiring Diagram:

Electrical Continuity

Ladder Program:



No Logical Continuity

23

I/O Mapping

- Every discrete input is assigned to a specific bit in the PLC's memory (**input image table**)
 - If there is electrical continuity, the bit is set to a 1
 - If there is no electrical continuity, the bit is reset to a 0
- Every discrete output is assigned to a specific bit in the PLC's memory (**output image table**)
 - In order for an output to turn on, its associated bit must first be set to a 1

24

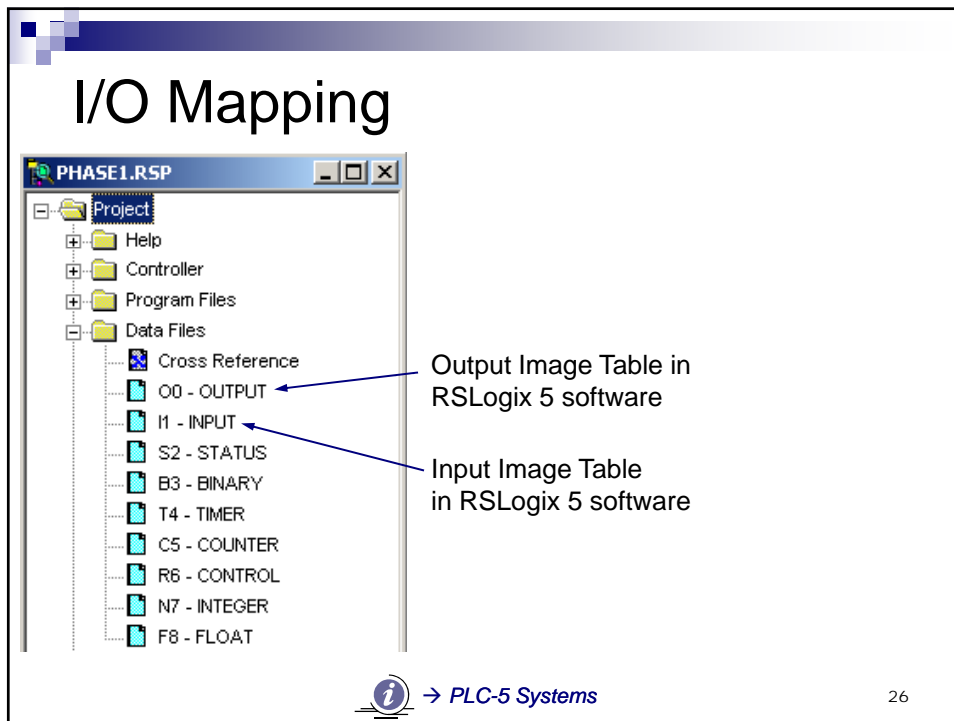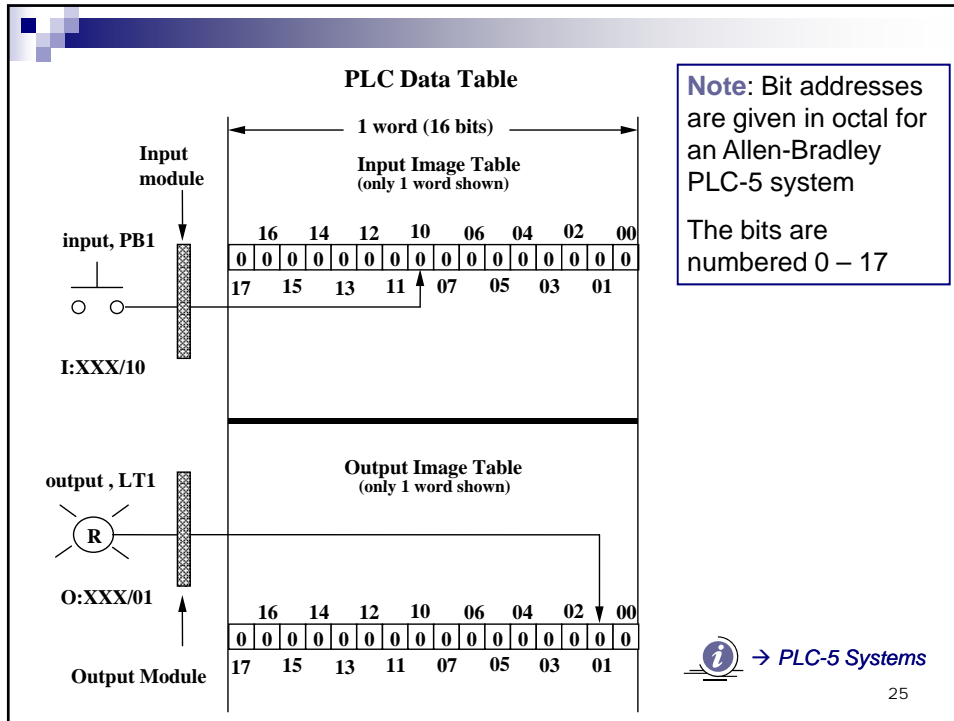

I/O Mapping

Output Image Table in RSLogix 5:

O:005 is a 16 bit word address:

O:005/07 is the address of a bit which resides in the word O:005

Offset	17	16	15	14	13	12	11	10	7	6	5	4	3	2	1	0
O:000	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
O:001	0	1	0	0	0	0	0	0	1	0	0	1	0	0	0	0
O:002	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
O:003	0	0	0	0	0	0	0	1	0	1	0	0	1	1	0	0
O:004	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
O:005	0	0	0	1	0	0	0	0	1	0	0	0	0	0	0	0

I/O Mapping

Input Image Table in RSLogix 5:

1 word = 16 bits (bits are numbered in octal for a PLC-5)

Offset	17	16	15	14	13	12	11	10	7	6	5	4	3	2	1	0
I:000	0	0	0	0	0	0	0	0	0	1	0	0	1	0	0	0
I:001	1	0	0	1	0	0	0	1	0	1	1	0	0	1	1	0
I:002	0	0	1	0	1	0	0	1	0	0	0	1	1	0	1	1
I:003	1	0	0	0	0	1	1	1	0	0	1	0	0	0	0	1
I:004	0	0	0	0	0	0	0	0	0	0	0	0	0	1	1	0

I/O Mapping

ControlLogix tag database:

Controller Tags - Template(controller)					
Scope:	Template	Show...	Show All		
Name	Value	Style	Data Type	Description	Alias For
I_PB0	0	Decimal	BOOL	Start	Local:6:I.Data.0
I_PB1	1	Decimal	BOOL	Stop	Local:6:I.Data.1
I_PB2_nc	1	Decimal	BOOL	Pushbutton 2 (N.C.)	Local:6:I.Data.3
I_PB2_no	0	Decimal	BOOL	Pushbutton 2 (N.O.)	Local:6:I.Data.2
I_PE1	0	Decimal	BOOL	Photoeye 1	Local:3:I.Data[0].1
I_PE2	0	Decimal	BOOL	Photoeye 2	Local:3:I.Data[0].2

Alias tag
(a pointer to a base address)

Current tag
value

Base address
(real address)



29

Mastering Examine On & Examine Off Instructions



- Discrete input devices have normally open (N.O.) and/or normally closed (N.C.) contacts.
 - Example: Pushbuttons can be purchased with either N.O. or N.C. mechanical contacts.
 - “Normally” implies the state of the contacts when you are NOT pushing the button.

30

Mastering Examine On & Examine Off Instructions




- Normally open (N.O.) vs. normally closed (N.C.) contacts:

Contact Type:	Resistance between contacts when NOT pushed:	Resistance between contacts when pushed:
N.O.	Infinite ohms	Zero ohms
N.C.	Zero ohms	Infinite ohms

31


Mastering Examine On & Examine Off Instructions

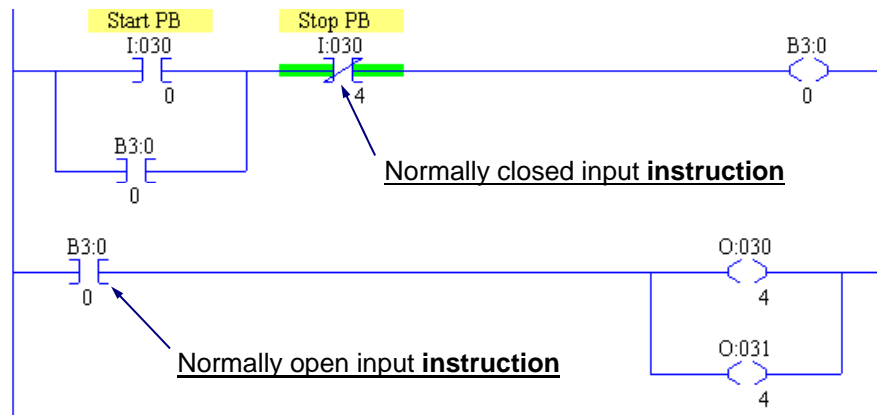- PLC programs have both normally open and normally closed input instructions.



Mastering Examine On & Examine Off Instructions

■ The **Examine On** Instruction

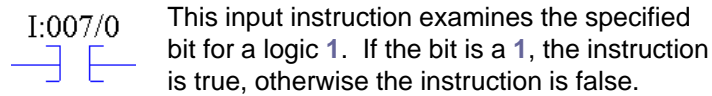


This is generally known as a **normally open** input instruction.

33

Mastering Examine On & Examine Off Instructions


■ The **Examine On** Instruction

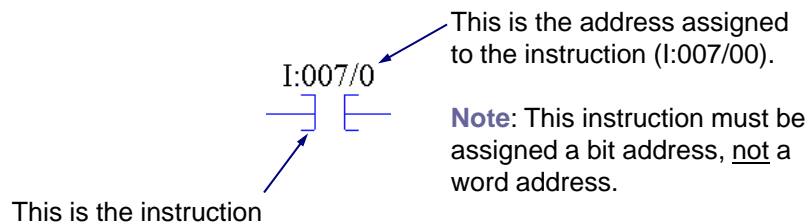

34

Mastering Examine On & Examine Off Instructions

■ The **Examine Off** Instruction

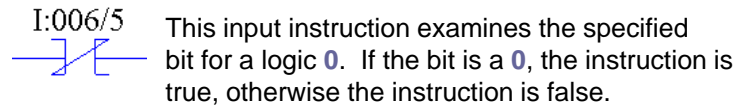

This is generally known as a **normally closed** input instruction.

35

Mastering Examine On & Examine Off Instructions



- Examine On instructions are also called:
 - **XIC**, e**X**amine **I**f **C**losed
- Examine Off instructions are also called:
 - **XIO**, e**X**amine **I**f **O**pen

Note: The terms Examine on, Examine off, Examine if closed (XIC), and Examine if open (XIO) are unique to Allen-Bradley PLCs.

36

Mastering Examine On & Examine Off Instructions

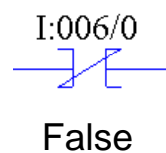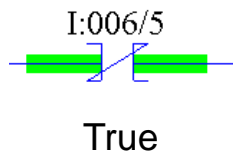
- Examine On and Examine Off Instructions that are **True** are highlighted **green** in the PLC programming software:




37

Mastering Examine On & Examine Off Instructions

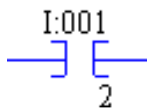
- A program can Examine On (or Examine Off) real inputs, real outputs, internal storage bits, timer done bits, etc.



Examine ON
a real input

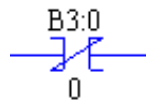

Examine OFF an
internal storage bit

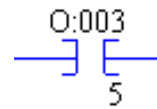

Examine ON
a real output

38

Mastering Examine On & Examine Off Instructions

- Input and output field devices are wired to PLC discrete Input/Output (I/O) modules. How the system functions depends on the program!

(Continued on next slide ...)

Mastering Examine On & Examine Off Instructions





How the system functions depends on the program:

The inputs could be programmed as two inputs **ANDed** together:



Or, the inputs could be programmed as two inputs **ORed** together:

In either case, the wiring is the same!
 The PLC program logically connects the input devices to the output actuators through the PLC program!

Mastering Examine On & Examine Off Instructions

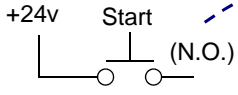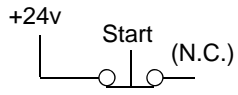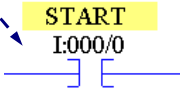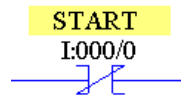
Input field devices wired to the PLC	The PLC Data Table	Instructions in the PLC program
<p><u>Electrical Continuity</u></p>  <p>Current flows if button is pressed</p>  <p>Current flows if button is <u>NOT</u> pressed</p>	<p><u>Input Image Table Bit</u></p> <div style="border: 1px solid black; padding: 5px; width: fit-content; margin: 10px auto;">0 or 1</div> <p>The bit representing the push button is:</p> <p>ON (set to a 1) if there is electrical continuity</p> <p>OFF (reset to a 0) if there is NO electrical continuity</p>	<p><u>Logical Continuity</u></p> <div style="background-color: yellow; padding: 2px; display: inline-block; margin-bottom: 5px;">START</div>  <p>True if the bit is a 1</p> <div style="background-color: yellow; padding: 2px; display: inline-block; margin-bottom: 5px;">START</div>  <p>True if the bit is a 0</p> <p style="text-align: right; font-size: small;">41</p>

Mastering Examine On & Examine Off Instructions

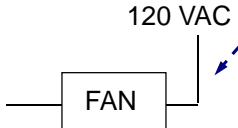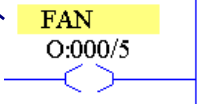Output field devices wired to the PLC	The PLC Data Table	Instructions in the PLC program
<p><u>Electrical Continuity</u></p>  <p>Output turns on when the bit in the output image table is a 1 (voltage is applied across the output terminals and current flows in the output circuit)</p>	<p><u>Output Image Table Bit</u></p> <div style="border: 1px solid black; padding: 5px; width: fit-content; margin: 10px auto;">0 or 1</div> <p>The bit representing the fan output is:</p> <p>ON (set to a 1) if there is logical continuity</p> <p>OFF (reset to a 0) if there is NO logical continuity</p>	<p><u>Logical Continuity</u></p> <div style="background-color: yellow; padding: 2px; display: inline-block; margin-bottom: 5px;">FAN</div>  <p>The output image table bit is set to a 1 when the rung is true or is reset to a 0 when the rung is false</p> <p style="text-align: right; font-size: small;">42</p>

The Scanning Process

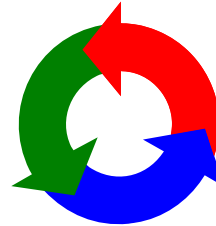- Scan refers to the continuous and sequential process of:
 - Reading the PLC inputs
 - Executing the ladder program (rung-by-rung)
 - Updating the PLC outputs



43

The Scanning Process

- The scan sequence can be broken into two functional parts:
 - The **Program Scan**
 - Scan the ladder program
 - The **I/O Update Scan**
 - Write outputs, Read inputs

44

The Scanning Process

■ The Program Scan:

- For each rung executed, the PLC processor will:
 - Examine the status of the input image table bits,
 - Solve the ladder logic in order to determine logical continuity (is the rung true?),
 - Update the appropriate output image table bits, if necessary.

Note: The output will not actually be energized until the I/O update part of the scan.


45

The Scanning Process

■ The I/O Update Scan:


- Copy the output image table status to the ALL of the output terminals (discrete output circuits)
 - Power is applied to the output device if it's output image table bit has been previously set to a 1.
- Copy the status of ALL of the input terminals to the input image table
 - If an input is active (i.e., there is electrical continuity), the corresponding bit in the input image table will be set to a 1.

46

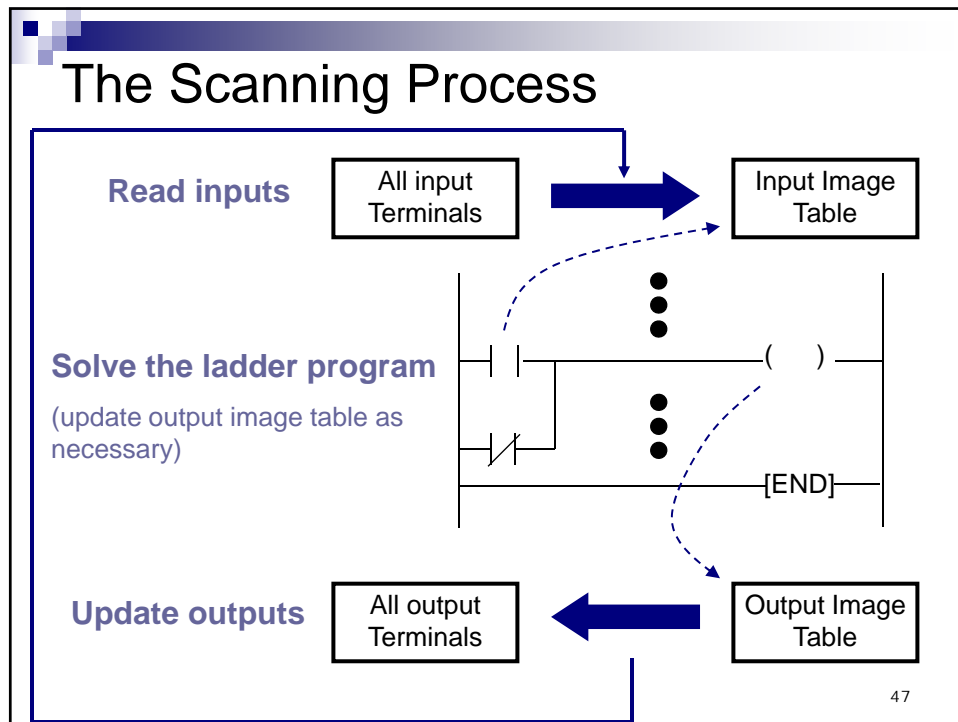


The Scanning Process

- In a ladder program, a specific output address (e.g., O:013/02) should NOT be referenced on more than one rung!
 - This is sometimes called “duplicate coils”
 - Using duplicate coils will cause unpredictable operation and should be avoided
 - When using duplicate coils “the last rung wins”
 - See example on next slide


 Continued on next slide ... 48

Duplicate Coil Example

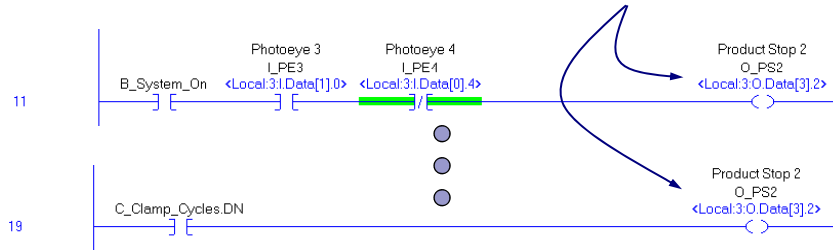Problem: Rungs 11 and 19 both reference the same output address:



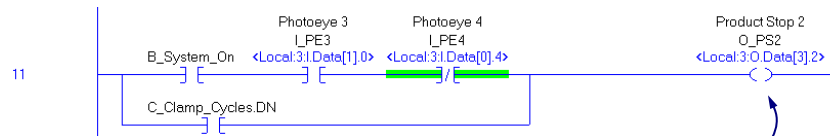Solution: Edit the ladder program as follows:



Problem corrected, this output is only used once in the entire program

49


The Scanning Process

- The actual scan time is a function of:
 - The speed of the processor module
 - The length of the ladder program
 - The type of instructions executed
 - The actual ladder true/false conditions (e.g., jump instructions, subroutines, etc.)

50


The Scanning Process

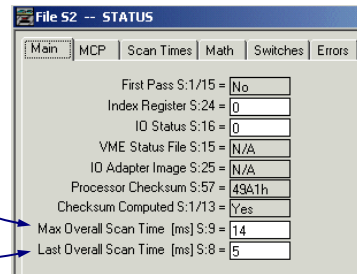- The actual scan time is calculated and stored in the PLCs memory
 - The PLC computes the scan time each time the END instruction is executed
 - Scan time data can be monitored via the PLC programming software (e.g., RSLogix 5)
 - Scan time data is addressable and can therefore be referenced in the PLC program
- Typical scan time data includes:
 - The maximum scan time
 - The last scan time



The Scanning Process

- Allen-Bradley PLCs generally have 3 modes of operation:
 - **Run Mode**
 - When placed in the RUN mode, the processor begins the scanning process as previously described
 - **Program Mode**
 - When placed in the PROGRAM mode, the processor stops scanning the ladder program and (typically) all the outputs are turned off
 - **Test Mode**
 - The TEST mode is identical to the RUN mode, except all outputs are disabled (held in their off state)

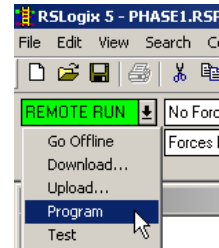

The Scanning Process

- Most Allen-Bradley processors (controllers) have a 3-position keyswitch:
 - **REM (Remote)**
 - In the remote mode, the PLC programming software (e.g., RSLogix5000) can be used to place the controller into the remote program mode or the remote run mode.
 - **RUN**
 - When keyswitch is placed in the RUN mode, the controller is switched into the run mode. The PLC programming software cannot change the controller's mode.
 - **PROG (Program)**
 - When keyswitch is placed in the PROG mode, the controller is switched into the program mode. The PLC programming software cannot change the controller's mode.



53