

# AC Notes

ECE 2210 / 00

A.Stolp  
2/27/00  
rev. 2/22/07

AC = Alternating Current

This term is used for any time-varying voltage or current waveform

Periodic waveforms: Waveshape repeats


T = Period = repeat time

$$f = \text{frequency, cycles / second} \quad f = \frac{1}{T} = \frac{\omega}{2\pi}$$

$\omega$  = radian frequency, radians/sec  $\omega = 2\pi f$

A = amplitude

DC = average

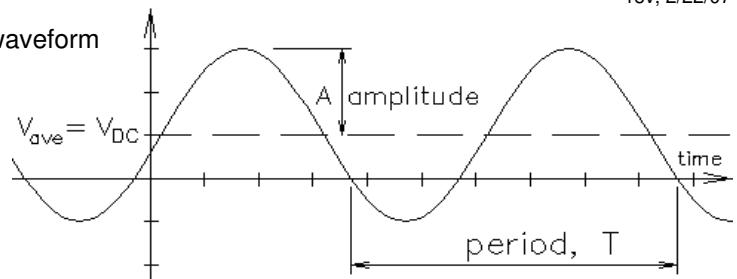

## Sinusoidal AC


### Phasor

$$y(t) = A \cdot \cos(\omega t + \phi)$$

$$\text{voltage: } v(t) = V_p \cdot \cos(\omega t + \phi) \quad V(\omega) = V_p e^{j\phi}$$

$$\text{current: } i(t) = I_p \cdot \cos(\omega t + \phi) \quad I(\omega) = I_p e^{j\phi}$$
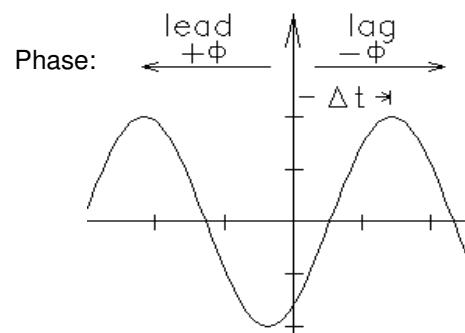
$$\text{Phase: } \phi = -\frac{\Delta t}{T} \cdot 360 \text{-deg} \quad \text{or: } \phi = -\frac{\Delta t}{T} \cdot 2\pi \text{-rad}$$



## Adding and subtracting Sinusoidal AC voltages or currents

Voltages and currents are represented by phasors drawn on a real - imaginary "phasor" diagram. These phasors add and subtract just like vectors.

$$v_1(t) = V_{p1} \cdot \cos(\omega t + \phi) \quad v_2(t) = V_{p2} \cdot \cos(\omega t + \theta)$$


$$\text{The problem: } v_3(t) = v_1(t) + v_2(t) = ?$$

$$\text{Draw phasors as shown, } V_1(j\omega) = V_{p1} / \phi \text{ and } V_2(j\omega) = V_{p2} / \theta$$

$$\text{Add the phasors just as you would vectors to get: } V_3(j\omega) = V_{p3} / \psi$$

$$V_{p3} = \sqrt{(V_{p1} \cdot \cos(\phi) + V_{p2} \cdot \cos(\theta))^2 + (V_{p1} \cdot \sin(\phi) + V_{p2} \cdot \sin(\theta))^2}$$
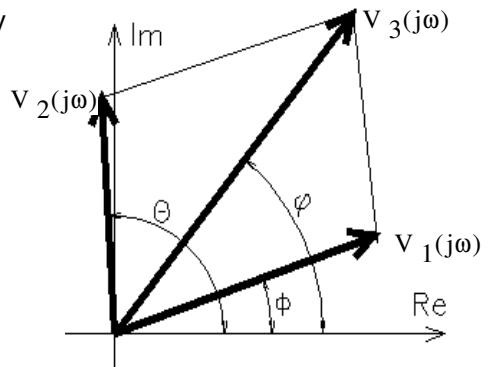
$$\psi = \arctan \left( \frac{V_{p1} \cdot \sin(\phi) + V_{p2} \cdot \sin(\theta)}{V_{p1} \cdot \cos(\phi) + V_{p2} \cdot \cos(\theta)} \right)$$



$$\text{Convert phasor back to time-domain voltage: } v_3(t) = v_1(t) + v_2(t) = V_{p3} \cdot \cos(\omega t + \psi) \quad \text{Done}$$

## Phasor analysis, For steady-state sinusoidal response ONLY

Phasors are used for much more than just adding and subtracting sinusoidal waveforms and are drawn on a complex plane for a very good reason. The math is all based on the Euler's equation:

$$\text{Euler's equation} \quad e^{j\alpha} = \cos(\alpha) + j \cdot \sin(\alpha) \quad \text{OR: } \cos(\alpha) = \frac{e^{j\alpha} + e^{-j\alpha}}{2} \quad \sin(\theta) = \frac{e^{j\alpha} - e^{-j\alpha}}{2j}$$

$$e^{j(\omega t + \theta)} = \cos(\omega t + \theta) + j \cdot \sin(\omega t + \theta)$$

$$\text{Re}[e^{j(\omega t + \theta)}] = \cos(\omega t + \theta)$$

If we freeze this at time  $t=0$ , then we can represent  $\cos(\omega t + \theta)$  by  $e^{j\theta}$  That's the phasor

Capacitors and Inductors in AC circuits cause  $90^\circ$  phase shifts between voltages and currents because they integrate and differentiate. But... integration and differentiation is a piece-of-cake in phasors.

Drop the  $\omega t$  ( $t=0$ ) to get:

$$\text{Calculus} \quad \frac{d}{dt} [A \cdot e^{j(\omega t + \theta)}] = j \cdot \omega \cdot A \cdot e^{j(\omega t + \theta)} = \omega \cdot A \cdot e^{j(\omega t + \theta + 90^\circ)} = \omega \cdot A \cdot e^{j(\theta + 90^\circ)}$$

$$\int A \cdot e^{j(\omega t + \theta)} dt = \frac{1}{j \cdot \omega} \cdot A \cdot e^{j(\omega t + \theta)} = \frac{1}{\omega} \cdot A \cdot e^{j(\omega t + \theta - 90^\circ)} = \frac{1}{\omega} \cdot A \cdot e^{j(\theta - 90^\circ)}$$

# AC Notes

## Phasor analysis with impedances, For steady-state sinusoidal response ONLY

Capacitor



$$i_C = C \cdot \frac{d}{dt} v_C$$


$$v_C = \frac{1}{C} \int i_C(t) dt$$

### AC impedance

$$Z_C = \frac{1}{j \cdot \omega \cdot C} = \frac{-j}{\omega \cdot C}$$

$$V_C(j\omega) = \frac{1}{j \cdot \omega \cdot C} \cdot I(j\omega)$$

Inductor

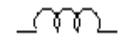

$$v_L = L \cdot \frac{d}{dt} i_L$$

$$i_L = \frac{1}{L} \int v_L(t) dt$$

$$Z_L = j \cdot \omega \cdot L$$

$$V_L(j\omega) = j \cdot \omega \cdot L \cdot I(j\omega)$$

Resistor



$$v_R = i_R \cdot R$$


$$i_R = \frac{v_R}{R}$$

$$Z_R = R$$


$$V_R(j\omega) = R \cdot I(j\omega)$$

You can use impedances just like resistances as long as you deal with the complex arithmetic.  
ALL the DC circuit analysis techniques will work with AC.

**series:**

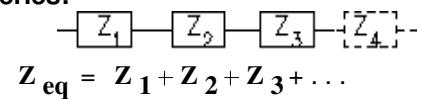

$$Z_{eq} = Z_1 + Z_2 + Z_3 + \dots$$

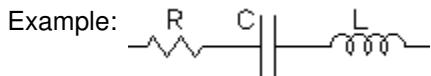


$$Z_{eq} = R + \frac{1}{j \cdot \omega \cdot C} + j \cdot \omega \cdot L$$

$$\text{If: } R := 200 \cdot \Omega \quad C := 2 \cdot \mu F \quad L := 16 \cdot mH \quad \text{and} \quad \omega := 4000 \cdot \frac{\text{rad}}{\text{sec}}$$


$$\text{then } Z_{eq} = R + \frac{1}{j \cdot \omega \cdot C} + j \cdot \omega \cdot L = 200 \cdot \Omega - 125 \cdot j \cdot \Omega + 64 \cdot j \cdot \Omega = 200 - 61j \cdot \Omega$$

**parallel:**

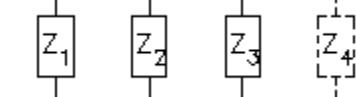

$$Z_{eq} = \frac{1}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} + \dots}$$

Example:

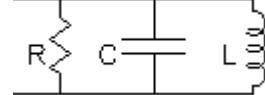

$$Z_{eq} = \frac{1}{\frac{1}{R} + \frac{1}{\left(\frac{1}{j \cdot \omega \cdot C}\right)} + \frac{1}{j \cdot \omega \cdot L}}$$

$$\text{If: } R := 200 \cdot \Omega \quad C := 2 \cdot \mu F \quad L := 16 \cdot mH \quad \text{and} \quad \omega := 4000 \cdot \frac{\text{rad}}{\text{sec}}$$

$$\text{then } Z_{eq} = \frac{1}{\frac{1}{R} + \frac{1}{j \cdot \omega \cdot C} - \frac{j}{\omega \cdot L}} = \frac{1}{\frac{1}{200 \cdot \Omega} + 8 \cdot 10^3 \cdot j \cdot \frac{1}{\Omega} - 0.01563 \cdot j \cdot \frac{1}{\Omega}}$$

$$= 60.1 \cdot \Omega + 91.7 \cdot \Omega = 109.7 \Omega / 56.7^\circ$$

$$\sqrt{(60.1 \cdot \Omega)^2 + (91.7 \cdot \Omega)^2} = 109.6 \cdot \Omega \quad \text{atan}\left(\frac{91.7 \cdot \Omega}{60.1 \cdot \Omega}\right) = 56.76 \cdot \text{deg}$$

### Example

Find  $V_O$  in the circuit shown. Express it as a magnitude and phase angle (the way  $V_S$  is expressed).

$$V_O := \frac{Z_2}{Z_1 + Z_2} \cdot V_S \quad \text{Simple voltage divider}$$

$$|Z_2| \cdot \cos(-60 \cdot \text{deg}) = 40 \cdot \Omega \quad |Z_2| \cdot \sin(-60 \cdot \text{deg}) = -69.282 \cdot \Omega$$

$$Z_2 = 40 - 69.282j \cdot \Omega \quad Z_1 + Z_2 = 25 \cdot \Omega + 35j \cdot \Omega + 40 \cdot \Omega - 69.282 \cdot j \cdot \Omega = 65 - 34.282j \cdot \Omega = 73.486 \cdot \Omega \cdot e^{-j27.81 \cdot \text{deg}}$$

$$V_O := \frac{Z_2}{Z_1 + Z_2} \cdot V_S = \frac{80 \cdot \Omega \cdot e^{-j60 \cdot \text{deg}}}{73.486 \cdot \Omega \cdot e^{-j27.81 \cdot \text{deg}}} \cdot (6 \cdot V \cdot e^{j18 \cdot \text{deg}}) = \frac{80 \cdot \Omega}{73.486 \cdot \Omega} \cdot 6 \cdot V \cdot e^{j(-60 - (-27.81) + 18) \cdot \text{deg}} = 6.53 \cdot V \cdot e^{-j14.2 \cdot \text{deg}}$$

