

This method is based on the method of Linear Graphs. In Linear Graphs, all systems are reduced to a universal symbology peculiar to Linear Graphs (system graph) and then analyzed by methods very similar to those used with electric circuits. Since we, as electrical engineers, are already well versed in the symbology of electric circuits, my variation of linear graphs reduces mechanical systems to electric circuits and leaves them in that symbology for ready analysis by methods, tools and computer programs that we are already familiar with.

Across and Through Variables

	<u>Across Variable</u>	<u>Through Variable</u>
Electrical	V = voltage (volts) or (V)	I = current (Amps) or (A)
Mechanical translational	v = velocity $\left(\frac{\text{m}}{\text{sec}}\right)$	F = force (newtons) or (N) or $\left(\text{Kg} \cdot \frac{\text{m}}{\text{sec}^2}\right)$
Mechanical rotational	ω = angular velocity $\left(\frac{\text{rad}}{\text{sec}}\right)$	T = torque (N·m)
Fluid	P = pressure $\left(\frac{\text{N}}{\text{m}^2}\right)$ or (Pa)	Q = flow $\left(\frac{\text{m}^3}{\text{sec}}\right)$

Elements	<u>Dissipation</u>	<u>Across Variable Energy Storage</u>	<u>Through Variable Energy Storage</u>
Electrical	R = resistance $\left(\frac{\text{V}}{\text{A}}\right)$ or (Ω)	C = capacitance $\left(\frac{\text{A} \cdot \text{sec}}{\text{V}}\right)$ or (F)	L = inductor $\left(\frac{\text{V} \cdot \text{sec}}{\text{A}}\right)$ or (H)
Mechanical translational	B = damping $\left(\frac{\text{N} \cdot \text{sec}}{\text{m}}\right)$	M = mass (Kg) or $\left(\frac{\text{N} \cdot \text{sec}^2}{\text{m}}\right)$	k = Spring constant $\left(\frac{\text{N}}{\text{m}}\right)$
Mechanical rotational	B = damping $\left[\frac{\text{N} \cdot \text{m}}{\left(\frac{\text{rad}}{\text{sec}}\right)}\right]$ (N·m·sec) or $\left[\frac{\text{rad}}{\text{sec}}\right]$	J = moment of inertia $\left(\frac{\text{N} \cdot \text{m}^3}{\text{sec}^2}\right)$ (Kg·m ²) or $\left(\frac{\text{N} \cdot \text{m}^3}{\text{sec}^2}\right)$	k = Spring constant $\left(\frac{\text{N} \cdot \text{m}}{\text{rad}}\right)$
Fluid	R _f = fluid resistance $\left(\frac{\text{N} \cdot \text{sec}}{\text{m}^5}\right)$	C _f = fluid capacitance $\left(\frac{\text{m}^5}{\text{N}}\right)$	I = fluid inertia $\left(\frac{\text{Kg}}{\text{m}^4}\right)$

Basic Electric Circuit Analysis

Element	Parts like resistors, capacitors, inductors & transformers
Wires and connections	Direct the current, but do not affect voltage
Circuit	Wires and elements connected to form loops
Voltage	Measured as a difference across an element
Current	Flows through a wire or element
Kirchhoff's Current Law (KCL)	Current in = current out of all elements, wires & connections
Kirchhoff's Voltage Law (KVL)	Voltage gains = voltage "losses" around any circuit loop
Node	Connected wires and connections which all have the same voltage
Ground	Zero-reference node for all other nodal voltages
Branch	Connected wires and elements which all have the same current
Power P = V·I	Power = Across variable x Through variable

Voltage Source



Constant voltage regardless of current in or out


Current Source



Constant current regardless of voltage + or -

Passive Electrical Elements

Resistors

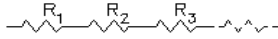


series: $R_{eq} = R_1 + R_2 + R_3 + \dots$

Exactly the **same current** through each resistor

voltage divider:

$$V_{Rn} = V_{total} \cdot \frac{R_n}{R_1 + R_2 + R_3 + \dots}$$

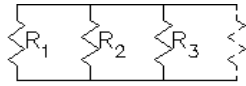parallel: $R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots}$



Exactly the **same voltage** across each resistor

current divider:

$$I_{Rn} = I_{total} \cdot \frac{\frac{1}{R_n}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots}$$

Resistors dissipate power $P = V \cdot I = I^2 \cdot R = \frac{V^2}{R}$

Capacitors


$C = \frac{Q}{V}$ farad = $\frac{\text{coul}}{\text{volt}} = \frac{\text{amp} \cdot \text{sec}}{\text{volt}}$

$v_C = \frac{1}{C} \cdot \int_{-\infty}^t i_C dt = \frac{1}{C} \cdot \int_0^t i_C dt + v_C(0)$ initial voltage $i_C = C \cdot \frac{d}{dt} v_C$


Energy stored in electric field: $E_C = \frac{1}{2} \cdot C \cdot V_C^2$

Capacitor voltage **cannot** change instantaneously

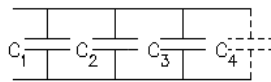parallel: $C_{eq} = C_1 + C_2 + C_3 + \dots$



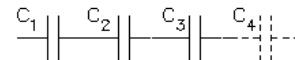series: $C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots}$



Steady-state sinusoids:

Impedance: $Z_C = \frac{1}{j \cdot \omega \cdot C} = \frac{-j}{\omega \cdot C}$

Laplace:

Impedance: $Z_C = \frac{1}{C \cdot s}$

Current leads voltage by 90 deg

Inductors


henry = $\frac{\text{volt} \cdot \text{sec}}{\text{amp}}$

$i_L = \frac{1}{L} \cdot \int_{-\infty}^t v_L dt = \frac{1}{L} \cdot \int_0^t v_L dt + i_L(0)$ initial current $v_L = L \cdot \frac{d}{dt} i_L$


Energy stored in magnetic field: $E_L = \frac{1}{2} \cdot L \cdot I_L^2$

Inductor current **cannot** change instantaneously

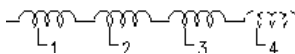series: $L_{eq} = L_1 + L_2 + L_3 + \dots$



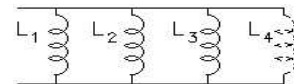parallel: $L_{eq} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots}$



Steady-state sinusoids:

Impedance: $Z_L = j \cdot \omega \cdot L$

Laplace:

Impedance: $Z_L = L \cdot s$

Current lags voltage by 90 deg


Transformers (ideal)

Ideal: $P_1 = P_2$ power in = power out

Turns ratio = $N = \frac{N_1}{N_2} = \frac{V_1}{V_2} = \frac{I_2}{I_1}$

Note: some books define the turns ratio as N_2/N_1

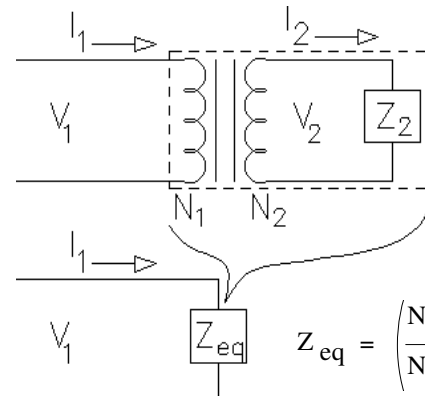Equivalent impedance in primary: $Z_{eq} = N^2 \cdot Z_2 = \left(\frac{N_1}{N_2}\right)^2 \cdot Z_2$



You can replace the entire transformer and load with (Z_{eq}).

This "impedance transformation" can work across systems.

Mechanical system with linear motion (translational)

Through Variable:

Mechanical translational

F = Force (N)

Across Variable:

v = velocity $\left(\frac{\text{m}}{\text{sec}}\right)$

$$\int v \, dt$$

$$\frac{V(s)}{s}$$

x = displacement (m)

$X(s)$ = displacement (m·sec)
(in freq domain)


Electrical

I = current (A)

Source:

V = voltage (V)

Source:

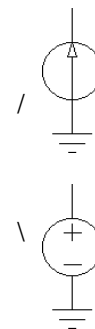

Dissipation element:


power

$$P = v \cdot F = \frac{F^2}{B}$$

$$= v^2 \cdot B$$


Damper or friction

B or f

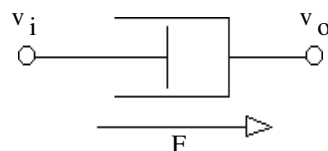

Resistor

$\frac{1}{B}$ or $\frac{1}{f}$

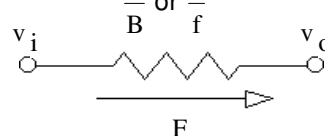

Impedance


$$\frac{1}{B} \text{ or } \frac{1}{f}$$

Through variable
energy storage:

$$E = \frac{1}{2} \cdot \frac{1}{k} \cdot F^2$$


Spring

k

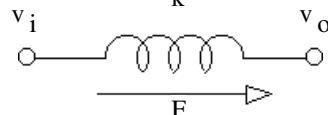


Inductor

$\frac{1}{k}$

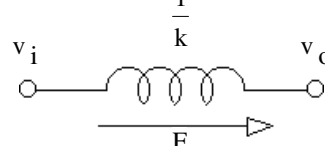

$$\frac{s}{k}$$


Springs are
Sometimes
shown like this:

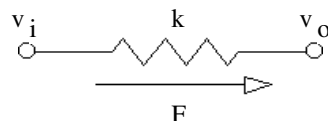


Through variable
energy storage:

$$E = \frac{1}{2} \cdot M \cdot v^2$$

Mass

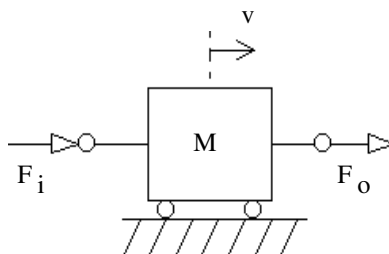


Capacitor hooked to ground

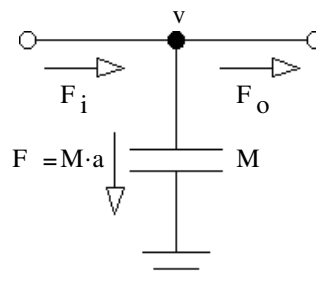


$$\frac{1}{M \cdot s}$$

Mass with friction

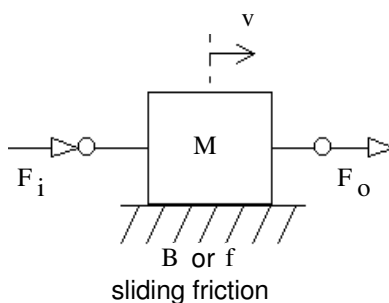

Capacitor and resistor

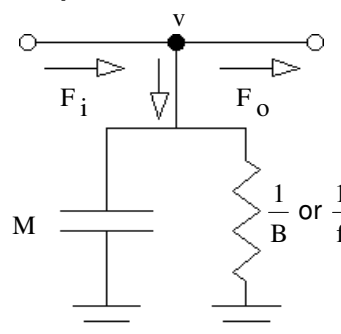

$$\frac{1}{\left(\frac{1}{M \cdot s}\right) + \left(\frac{1}{B}\right)}$$

$$\frac{1}{M \cdot s + B}$$

Mechanical system with circular motion (rotational)

Through Variable:

Mechanical rotational

T = Torque (N·m)

Electrical

I = current (A)

Source:

Across Variable:

ω = angular velocity $\left(\frac{\text{rad}}{\text{sec}}\right)$

V = voltage (V)

Source:

$$\int \omega dt$$

$$\frac{\omega(s)}{s}$$

θ = angular displacement (rad)

$\theta(s)$ = angular displacement (rad·sec)
(in freq domain)

Dissipation element:


power

$$P = v \cdot T = \frac{T^2}{B}$$

$$= \omega^2 \cdot B$$


Damper or friction

B or f

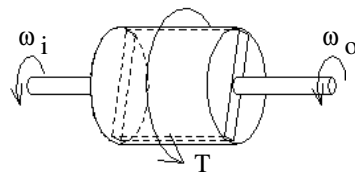

Resistor

$\frac{1}{B}$ or $\frac{1}{f}$

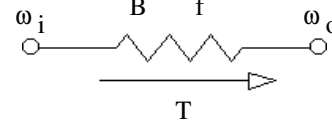

Impedance

$$\frac{1}{B} \text{ or } \frac{1}{f}$$

Through variable
energy storage:

$$E = \frac{1}{2} \cdot \frac{1}{k} \cdot T^2$$


Springs

k







Inductor

$\frac{1}{k}$

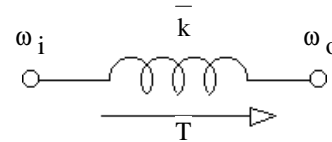


$$\frac{s}{k}$$

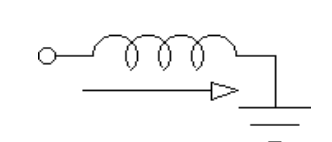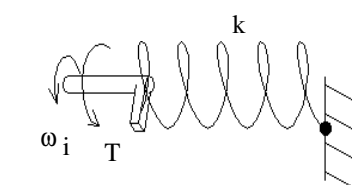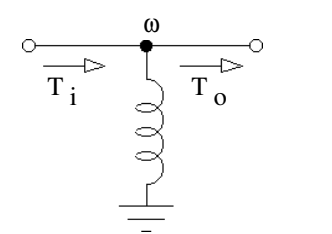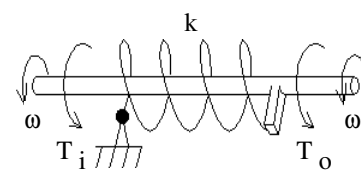


Through variable
energy storage:

$$E = \frac{1}{2} \cdot J \cdot \omega^2$$

Moment of Inertia, J

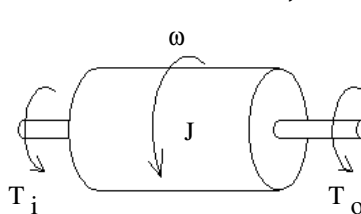


Capacitor hooked to ground

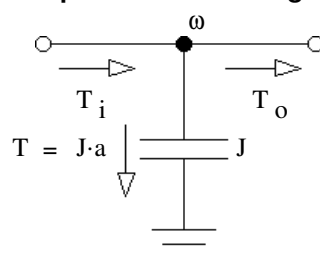


$$\frac{1}{J \cdot s}$$

J with friction

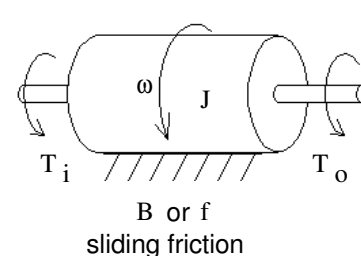

Capacitor and resistor

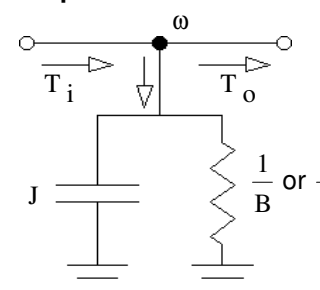

$$\frac{1}{\left(\frac{1}{J \cdot s}\right) + \left(\frac{1}{B}\right)}$$

$$\frac{1}{J \cdot s + B}$$

Fluid (hydraulic) system

Fluid

Through Variable: $Q = \text{volumetric flow rate} \left(\frac{\text{m}^3}{\text{sec}} \right)$


Across Variable: $P = \text{Pressure} \left(\frac{\text{N}}{\text{m}^2} \right) \text{ or } (\text{Pa})$

Dissipation element:
power

$$P = P \cdot Q = \frac{Q^2}{R_f}$$

$$= P^2 \cdot R_f$$


Fluid resistance

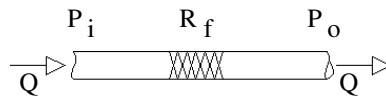

Through variable
energy storage:

$$E = \frac{1}{2} \cdot I \cdot Q^2$$

Fluid Inertia

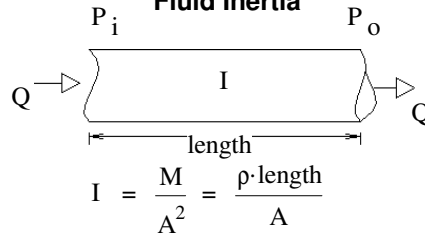


Electrical


$I = \text{current (A)}$

$V = \text{voltage (V)}$

Sources

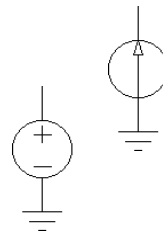


Resistor

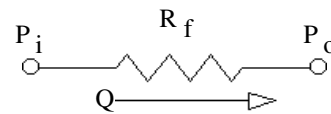

Impedance

R_f

Inductor

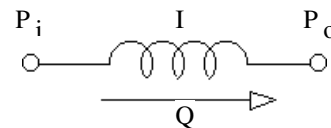


$I \cdot s$


Through variable
energy storage:

$$E = \frac{1}{2} \cdot C_f \cdot P^2$$

Fluid Capacitors

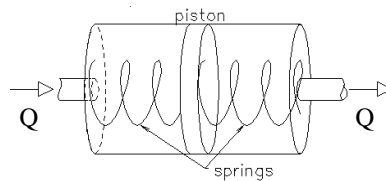


Capacitor

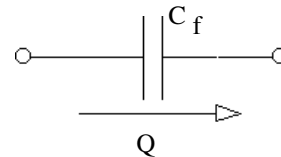


$\frac{1}{C_f s}$


open top tank

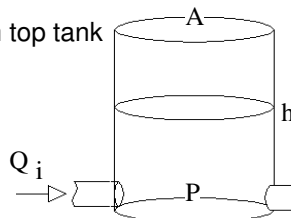

OR

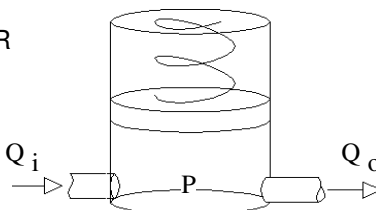


Capacitor hooked to ground

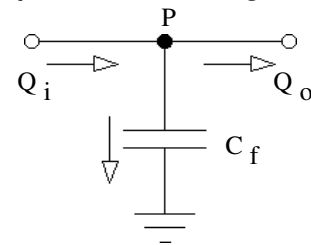

$$C_f = \frac{\Delta \text{volume}}{\Delta \text{pressure}} = \frac{\Delta h \cdot A}{\Delta h \cdot \rho \cdot g} = \frac{A}{\rho \cdot g} \quad \text{For open top tank}$$


Turbine or Pump

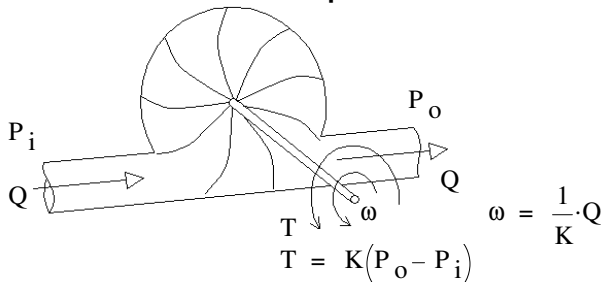

Turbines & pistons convert through variables to across variables & vice versa, so there are no good electrical analogies.

Yet you can still transform an impedance from a mechanical system into the fluid system. But you will find that capacitors become inductors, inductors become capacitors and parallel swaps with series.

Piston & Cylinder


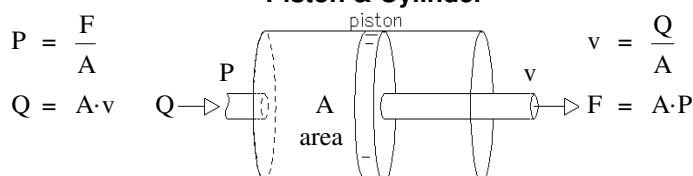


$$Z_{eq} = \frac{\left(\frac{F}{A} \right)}{A \cdot v} = \frac{1}{A^2} \cdot \frac{F}{v} = \frac{1}{A^2} \cdot \frac{1}{Z_2} = \frac{1}{A^2 \cdot Z_2}$$

Transducers and Transformers



A transducer converts power from one type to another. We can model many of them with transformers. Transformers increase the through variable and correspondingly decrease the across variable or vice-versa.

Levers

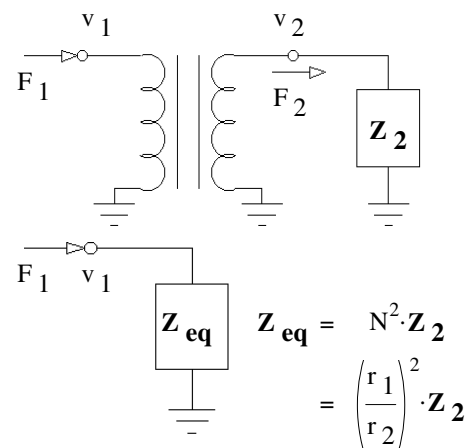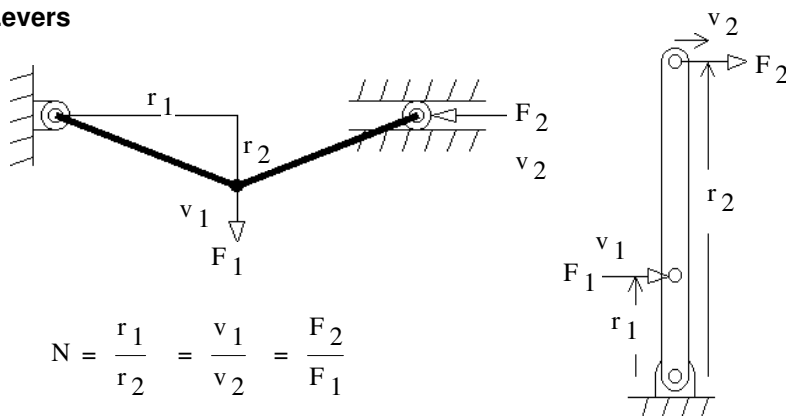



Tires, racks, & conveyors

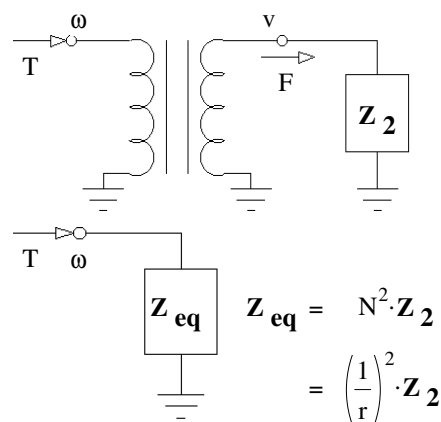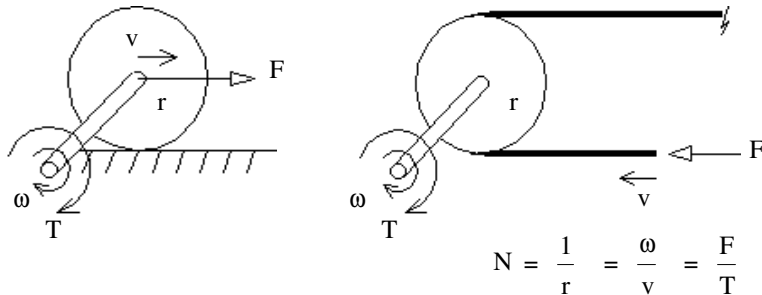r = radius of wheel or pitch radius of pinion gear



Belts, chains, & gears

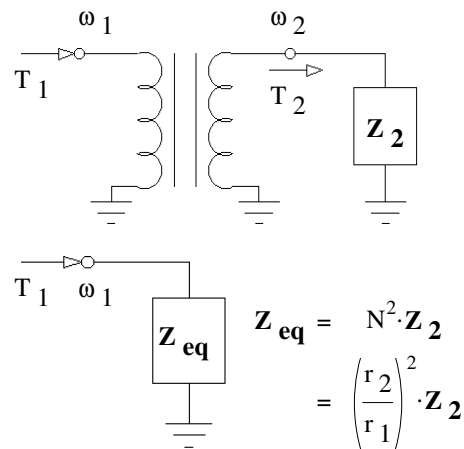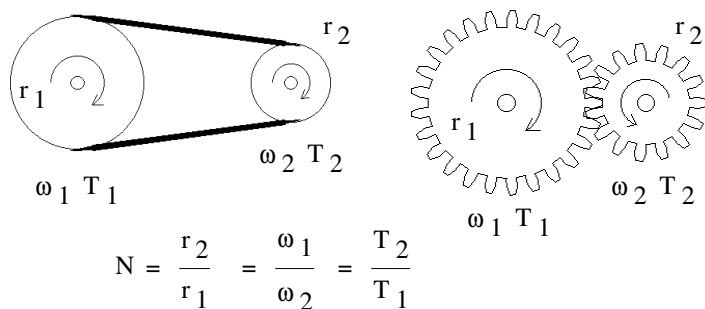r = radius of wheel or pitch radius of gears



DC Motors

