

ECE 3510 Phase-Locked Loops

a

Phase-Locked Loops are a bit of a distraction right here, but we need to cover them for next lab. (6 & 7)

Need parts and breadboard for this lab.


PLL IC is expensive and prone to static & handling damage.

See lab 6 handout

PAY ATTENTION to warnings in the lab.


Modulation

AM = Amplitude Modulation

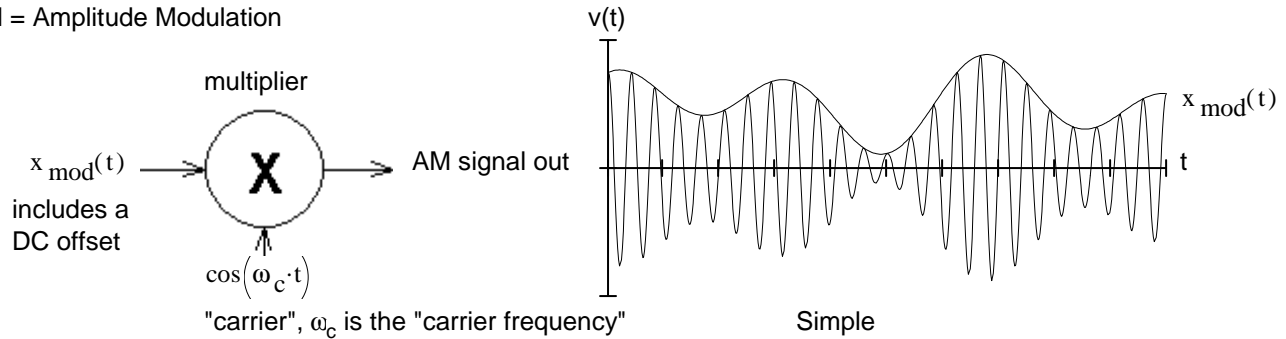


Simple

Demodulation

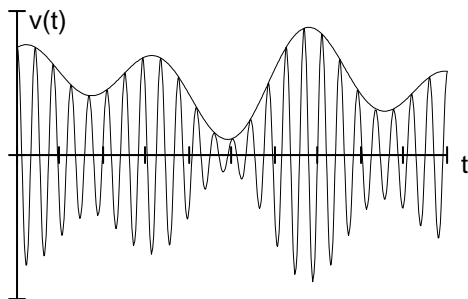


A simple rectifier circuit

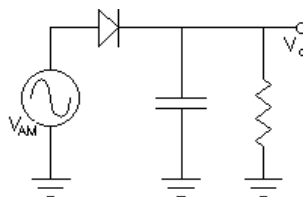


detector

Returns the modulation signal

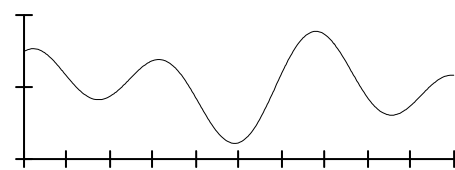

And a coupling capacitor can remove the DC

FM = Frequency Modulation

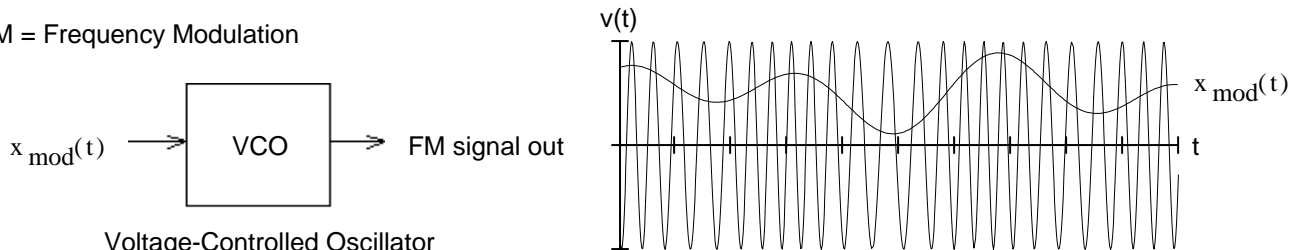

Voltage-Controlled Oscillator

ω_c is the carrier frequency and is the output when $x_{mod} = 0$

$\omega_c + k_{vco} \cdot x_{mod}(t)$ is the output frequency

So if: $\cos(\omega_c \cdot t)$ is the carrier, I guess $\cos[(\omega_c + k_{vco} \cdot x_{mod}(t)) \cdot t]$ must be the output... **WRONG!**

actually: $\cos(\theta(t))$

where: $\theta(t) = \int \omega dt$ is the REAL relationship between θ and ω
 $= \omega t$ for the unmodulated (steady-state sinusoid) case

so if you want to modulate the frequency:


$$\theta(t) = \int (\omega_c + k_{vco} \cdot x_{mod}(t)) dt = \omega_c \cdot t + \int k_{vco} \cdot x_{mod}(t) dt$$

And, the VCO becomes $\frac{k_{vco}}{s}$ if you just care about $\theta(t)$ and not the carrier


PM = Phase Modulation

One way to demodulate FM is with a Phase-Locked-Loop.


Phase-Locked Loops p2

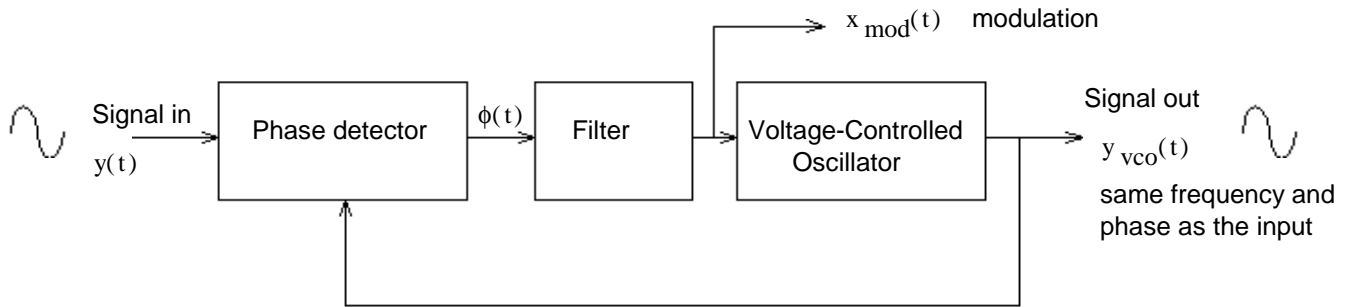

To analyze the Phase-Locked-Loop (PLL).

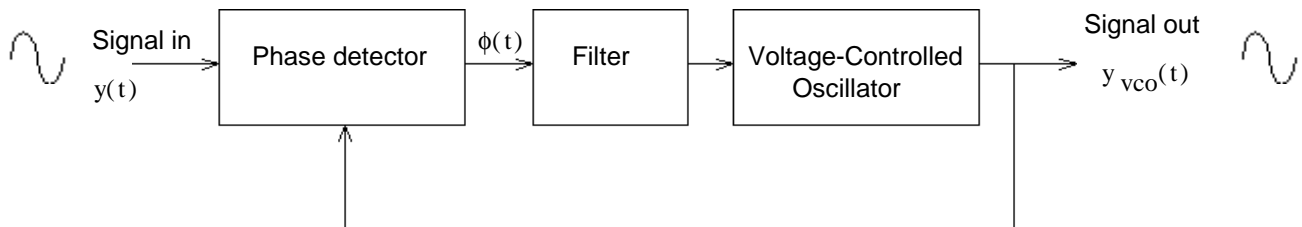

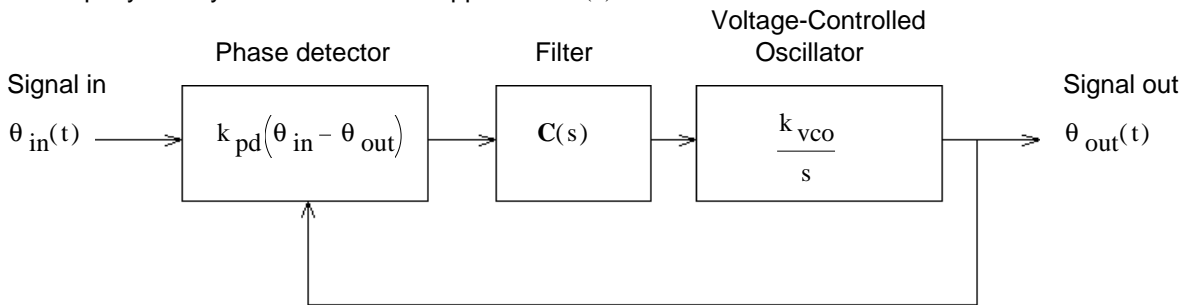The same loop if you only care about what happens to $\theta(t)$




$$G(s) = k_{pd} \cdot \frac{k_{vco}}{s} \cdot C(s) = \frac{k_{pll}}{s} \cdot C(s) \quad \text{where } k_{pll} = k_{pd} \cdot k_{vco}$$

$$\text{Closed-loop: } H(s) = \frac{\frac{k_{pll}}{s} \cdot C(s)}{1 + \frac{k_{pll}}{s} \cdot C(s)} = \frac{k_{pll} \cdot C(s)}{s + k_{pll} \cdot C(s)}$$

At first glance, that filter, $C(s)$, doesn't look necessary, but many phase detectors don't put out a nice DC.

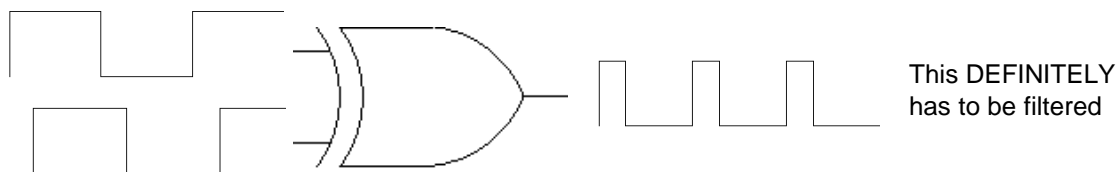Our phase detector in the lab is a good example:



For filter, $C(s)$, design, see Bodson, section 4.5.4 and PLL labs.

Your challenge in the lab will be to get a good demodulation and a stable system.

PLLs can also be used for frequency synthesis and motor speed control, etc..