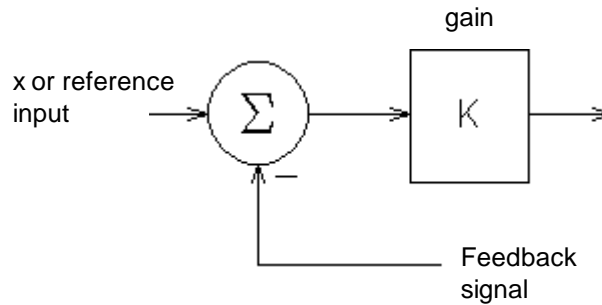



**Implementation (Physical Realization) of Feedback System Components and Compensators**

One way to implement this:




A. Stolp  
2/24/09,  
rev,

Is the **instrumentation amplifier**:

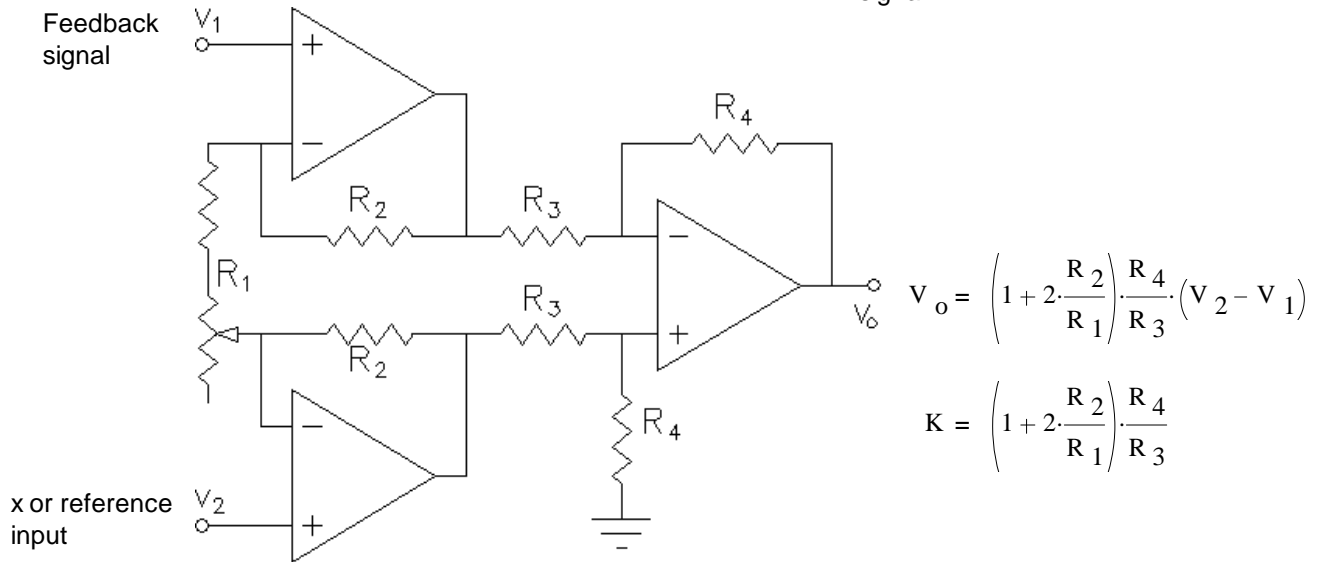

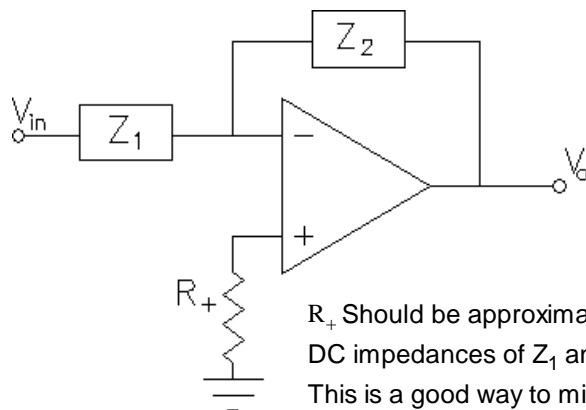To build **active compensators**, use this basic circuit and then consult Table 9.10 (p.555 in 3rd ed. p.504 in 6th) in the Nise textbook.



$R_+$  Should be approximately the parallel combination of the DC impedances of  $Z_1$  and  $Z_2$ .  
This is a good way to minimize the effects of the Op-amp's bias currents.

**Beware!** This is an inverting circuit. You will have to follow it with another inverter.

Or... you could just swap the inputs to the instrumentation amplifier, if you are using one.

The resistors used in Op-amp circuits should be 100Ω to 1MΩ, and preferably 1kΩ to 100kΩ.

These Op-amp circuits require + and - power supplies.

To build **passive compensators**, consult Table 9.11 ( p.558 in 3rd ed. p.506 in 6th) in the Nise textbook.

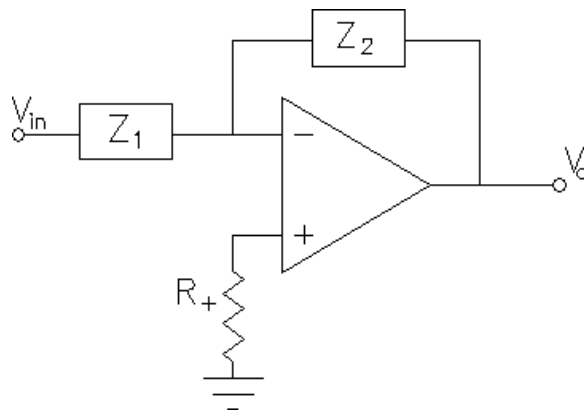


Table similar to table 9.10 ( p.555 in 3rd ed. p.504 in 6th) in the Nise textbook.

Function	$Z_1$	$Z_2$	$C(s)$
Amplifier (Proportional Gain)			$k_p = -\frac{R_1}{R_2}$
Integrator			$\frac{k_i}{s} = -\frac{1}{R \cdot C \cdot s} = -\frac{1}{R \cdot C} \cdot \frac{1}{s}$
Differentiator			$k_d \cdot s = -R \cdot C \cdot s$
PI Controller			$k_p + \frac{k_i}{s} = k_p \cdot \frac{\left(s + \frac{k_i}{k_p}\right)}{s} = -\frac{R_1}{R_2} \cdot \left(s + \frac{1}{R_2 \cdot C}\right)$
PD Controller			$k_p + k_d \cdot s = k_p \cdot \left(1 + \frac{k_d}{k_p} \cdot s\right) = -R_2 \cdot C$
PID Controller			$k_p + \frac{k_i}{s} + s \cdot k_d = -\left[ \left(\frac{R_2}{R_1} + \frac{C_1}{C_2}\right) + \frac{\left(\frac{1}{R_1 \cdot C_2}\right)}{s} + R_2 \cdot C_1 \cdot s \right]$ $\frac{s^2 \cdot k_d + s \cdot k_p + k_i}{s} = -\frac{R_2 \cdot C_1 \cdot s^2 + \left(\frac{R_2}{R_1} + \frac{C_1}{C_2}\right) \cdot s + \frac{1}{R_1 \cdot C_2}}{s}$
Lag or Lead Compensator			$-\left[ \frac{C_1 \cdot \left(s + \frac{1}{R_1 \cdot C_1}\right)}{C_2 \cdot \left(s + \frac{1}{R_2 \cdot C_2}\right)} \right]$ <p>Lag: <math>R_1 \cdot C_1 &lt; R_2 \cdot C_2</math>  Lead: <math>R_1 \cdot C_1 &gt; R_2 \cdot C_2</math></p>


## PID Design Example Implementation p.1

$$C(s) = 0.418 \cdot \frac{(s+0.1) \cdot (s+24.28)}{s} = 0.418 \cdot \frac{s^2 + 24.38s + 2.48}{s} = \frac{0.418 \cdot s^2 + 10.19s + 1.037}{s}$$

$$= \frac{k_d \cdot s^2 + k_p \cdot s + k_i}{s}$$

$k_d := 0.418 \cdot \text{sec}$   
 $k_p := 10.19$   
 $k_i := \frac{1.016}{\text{sec}}$

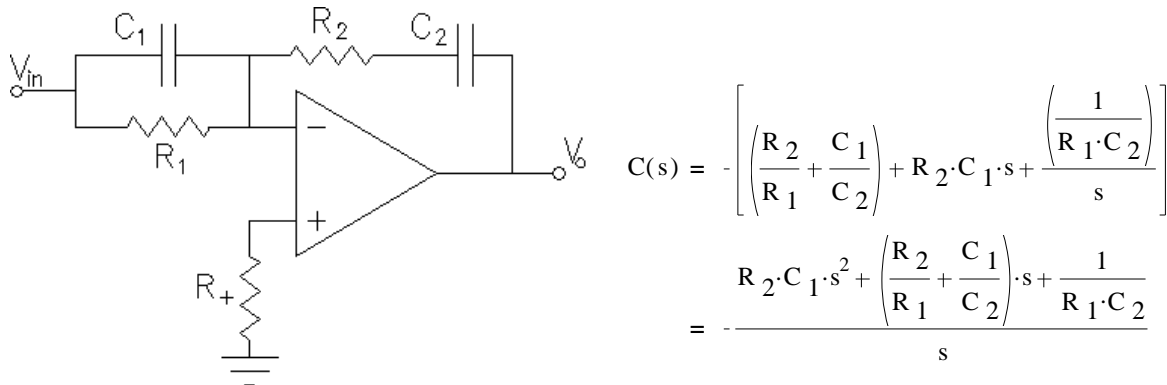Using the PID design from table 9.10 (p.555 in 3rd ed. p.504 in 6th) in Nise:  
 This could be implemented with:



If we use an instrumentation amplifier with a gain of, say 3, and invert the two inputs to "fix" the inversion above, then:

$$R_2 \cdot C_1 = \frac{k_d}{3} = 0.139 \cdot \text{sec} \quad \left( \frac{R_2}{R_1} + \frac{C_1}{C_2} \right) = \frac{10.19}{3} = 3.397 \quad \frac{1}{R_1 \cdot C_2} = \frac{k_i}{3} = 0.339 \cdot \text{sec}^{-1}$$

There are 4 component values to select and only 3 coefficients to match, so arbitrarily select 1 component.

Try  $C_1 := 0.1 \cdot \mu\text{F}$        $R_2 := \frac{0.139 \cdot \text{sec}}{C_1}$        $R_2 = 1.39 \cdot \text{M}\Omega$       too high

Try  $C_1 := 10 \cdot \mu\text{F}$        $R_2 := \frac{0.139 \cdot \text{sec}}{C_1}$        $R_2 = 13.9 \cdot \text{k}\Omega$       Use  $R_2 := 14 \cdot \text{k}\Omega$

Now  $\left( \frac{R_2}{R_1} + \frac{C_1}{C_2} \right) = 3.397$       And  $\frac{1}{R_1 \cdot C_2} = \frac{0.339}{\text{sec}}$       So,  $C_2 = \frac{\text{sec}}{0.339 \cdot R_1}$

Combining:  $= \frac{14 \cdot \text{k}\Omega}{R_1} + \frac{10 \cdot \mu\text{F} \cdot (0.339 \cdot R_1)}{\text{sec}} - 3.397 = 0$

Solve:  $R_1 := \frac{3.397 + \sqrt{3.397^2 - 4 \cdot \frac{C_1 \cdot 0.339 \cdot R_2}{\text{sec}}}}{2 \cdot \frac{C_1 \cdot 0.339}{\text{sec}}}$        $R_1 = 997.927 \cdot \text{k}\Omega$       Use  $R_1 := 1 \cdot \text{M}\Omega$   
 Let  $R_+ = 1\text{M}\Omega$

$C_2 := \frac{\text{sec}}{0.339 \cdot R_1}$        $C_2 = 2.95 \cdot \mu\text{F}$       Use  $C_2 := 3 \cdot \mu\text{F}$

Test:  $R_2 \cdot C_1 = 0.14 \cdot \text{sec}$        $\left( \frac{R_2}{R_1} + \frac{C_1}{C_2} \right) = 3.347$        $\frac{1}{R_1 \cdot C_2} = 0.333 \cdot \text{sec}^{-1}$       Close enough

## PID Design Example Implementation p.2

Instrumentation amp gain:  $K_{inst} := 3$        $k_d := 0.418 \cdot \text{sec}$        $k_p := 10.19$        $k_i := \frac{1.016}{\text{sec}}$

$$R_2 \cdot C_1 = k'_d := \frac{k_d}{3} \qquad \left( \frac{R_2}{R_1} + \frac{C_1}{C_2} \right) = k'_p := \frac{10.19}{3} \qquad \frac{1}{R_1 \cdot C_2} = k'_i := \frac{k_i}{3}$$

$k'_d = 0.139 \cdot \text{sec}$        $k'_p = 3.397$        $k'_i = 0.339 \cdot \text{sec}^{-1}$

For standard capacitor values from  $C_{10} = 0.01 \cdot \mu\text{F}$  to  $C_{32} = 82 \cdot \mu\text{F}$

Combining equations above

$$\left( \frac{R_2}{R_1} + \frac{C_1}{C_2} \right) = k'_p = \left[ \frac{R_2}{R_1} + \frac{C_1}{\left( \frac{1}{k'_i \cdot R_1} \right)} \right] \quad \text{OR} \quad R_2 + C_1 \cdot k'_i \cdot R_1^2 - k'_p \cdot R_1 = 0$$

Rearrange:  $C_1 \cdot k'_i \cdot R_1^2 - k'_p \cdot R_1 + R_2 = 0$

And solve:  $R_{1_i} := \frac{k'_p + \sqrt{k'^p^2 - 4 \cdot (C_{1_i} \cdot k'_i \cdot R_{2_i})}}{2 \cdot (C_{1_i} \cdot k'_i)}$

Finally:  $C_{2_i} := \frac{1}{k'_i \cdot R_{1_i}}$

Possible solutions	$C_{1_i}$ $\mu\text{F}$	$R_{2_i}$ $\text{k}\Omega$	$R_{1_i}$ $\text{k}\Omega$	$C_{2_i}$ $\mu\text{F}$
	0.12	1161.11	83236	0.035
	0.15	928.89	66589	0.044
	0.18	774.07	55491	0.053
	0.22	633.33	45402	0.065
	0.33	422.22	30268	0.098
	0.39	357.26	25611	0.115
	0.47	296.45	21252	0.139
	0.56	248.81	17836	0.166
	0.68	204.9	14689	0.201
	0.82	169.92	12181	0.242
	1	139.33	9988	0.296
	1.2	116.11	8324	0.355
	1.5	92.89	6659	0.443
	1.8	77.41	5549	0.532
	2.2	63.33	4540	0.65
	3.3	42.22	3027	0.976
	3.9	35.73	2561	1.153
	4.7	29.65	2125	1.389
	5.6	24.88	1784	1.655
	6.8	20.49	1469	2.01
	8.2	16.99	1218	2.424
	10	13.93	999	2.956
	12	11.61	832	3.547
	15	9.29	666	4.434
	18	7.74	555	5.321
	22	6.33	454	6.504
	33	4.22	303	9.755
	39	3.57	256	11.529
	47	2.96	213	13.894
	56	2.49	178	16.555
	68	2.05	147	20.102
	82	1.7	122	24.241