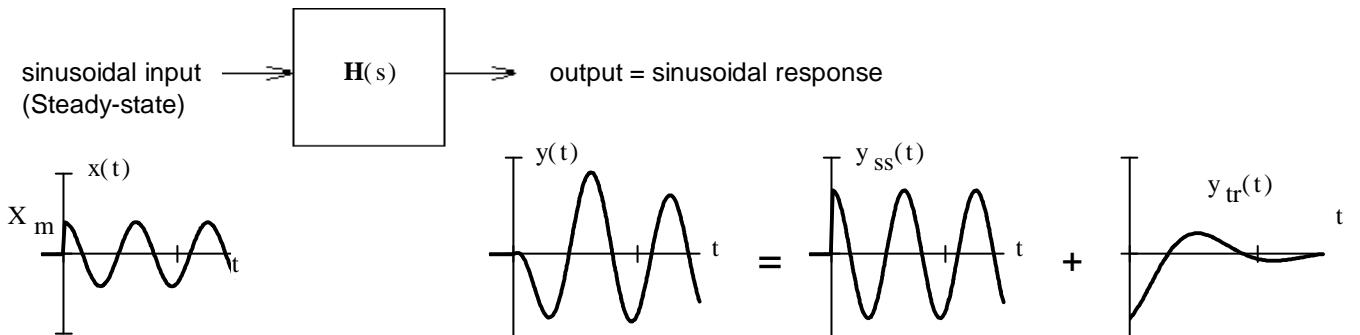


For BIBO Systems

The sinusoidal response of a system is the output when the input is a sinusoidal (which starts at time = 0).

System Sinusoidal Response



Complete step response = steady-state response + transient response

$$Y(s) = X(s) \cdot H(s) = X_m \cdot H(j\omega) \cdot u(t) + Y_{tr}(s)$$

$H(j\omega)$ = phasor-type transfer function

Sinusoidal Input

$$\cos(\omega \cdot t) \cdot u(t) \Leftrightarrow \frac{s}{s^2 + \omega^2}$$

$$\sin(\omega \cdot t) \cdot u(t) \Leftrightarrow \frac{b}{s^2 + \omega^2}$$

$$\text{General sinusoidal input: } [X_{mc} \cdot \cos(\omega \cdot t) + X_{ms} \cdot (\sin(\omega \cdot t) \cdot u(t))] \cdot u(t)$$

$$X(s) = \frac{X_{mc} \cdot s + X_{ms} \cdot \omega}{s^2 + \omega^2}$$

$$\text{OR } X_m \cdot \cos(\omega \cdot t + \theta) \cdot u(t) = [X_{mc} \cdot \cos(\omega \cdot t) + X_{ms} \cdot (\sin(\omega \cdot t) \cdot u(t))] \cdot u(t)$$

$$X_{mc} = X_m \cdot \cos(\theta) \quad X_{ms} = -X_m \cdot \sin(\theta)$$

Steady-State Response & $H(j\omega)$

$$Y(s) = X(s) \cdot H(s) = \frac{X_{mc} \cdot s + X_{ms} \cdot \omega}{s^2 + \omega^2} \cdot H(s) = \text{Complete sinusoidal response}$$

$$= \frac{A \cdot s + B \cdot \omega}{s^2 + \omega^2} + \frac{C}{(s + i\omega)} + \frac{D}{(s - i\omega)} + \dots$$

$$\text{partial fraction expansion: } Y(s) = \frac{X_{mc} \cdot s + X_{ms} \cdot \omega}{s^2 + \omega^2} \cdot H(s) = \frac{A \cdot s + B \cdot \omega}{s^2 + \omega^2} + \left[\frac{C}{(s + i\omega)} + \frac{D}{(s - i\omega)} + \frac{E}{(s^2 + \omega^2)} \right] \cdot s$$

steady-state response + transient response

$$Y_{ss}(s) + Y_{tr}(s)$$

$$\text{multiply both sides by } (s^2 + \omega^2) \quad (X_{mc} \cdot s + X_{ms} \cdot \omega) \cdot H(s) = A \cdot s + B \cdot \omega + \left[\frac{C}{(s + i\omega)} + \frac{D}{(s - i\omega)} + \frac{E}{(s^2 + \omega^2)} \right] \cdot (s^2 + \omega^2)$$

$$\text{set } s := j\omega \quad (X_{mc} \cdot j\omega + X_{ms} \cdot \omega) \cdot H(j\omega) = A \cdot j\omega + B \cdot \omega + \left[\frac{C}{(j\omega + i\omega)} + \frac{D}{(j\omega - i\omega)} + \frac{E}{(j\omega^2 + \omega^2)} \right] \cdot 0$$

$$\text{divide both sides by } j\omega \quad X(j\omega) \cdot H(j\omega) = A - B \cdot j = Y_{ss}(j\omega) = \text{steady-state response in phasor form}$$

(real is cosine, imaginary is -sine)

$X(j\omega)$ = the input expressed in phasor form NOT $X(s)$ with $s := j\omega$, that would be ∞

$H(j\omega)$ = the steady-state sinusoidal transfer function

= phasor-type transfer function

The transient part would be found by finishing the partial-fraction expansion.

Steady-State Response by Phasors

Expression of signals as phasors

T = Period

$$f = \text{frequency, cycles / second} \quad f = \frac{1}{T} = \frac{\omega}{2\pi}$$

$$\omega = \text{radian frequency, radians/sec} \quad \omega = 2\pi f$$

A = amplitude

$$\text{Phase: } \phi = -\frac{\Delta t}{T} \cdot 360 \cdot \text{deg} \quad \text{or: } \phi = -\frac{\Delta t}{T} \cdot 2\pi \cdot \text{rad}$$

$$y(t) = A \cdot \cos(\omega \cdot t + \phi)$$



Phasor

$$\text{voltage: } v(t) = V_p \cdot \cos(\omega \cdot t + \phi)$$

$$V(j\omega) = V_p \cdot e^{j\phi}$$

$$\text{current: } i(t) = I_p \cdot \cos(\omega \cdot t + \phi)$$

$$I(j\omega) = I_p \cdot e^{j\phi}$$

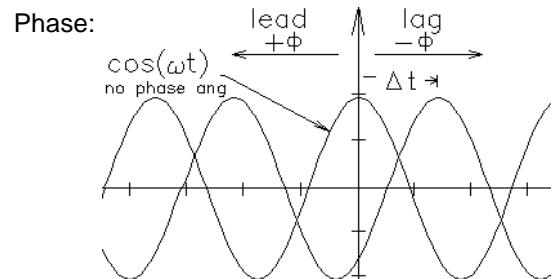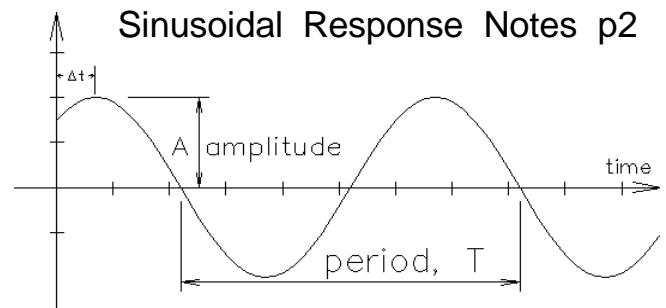

Ex1 Let's assume the input to your system is $v_1(t) = 3.2 \cdot V \cdot \cos(\omega \cdot t + 15^\circ)$ $V_1(j\omega) = 3.2 \cdot V \cdot e^{j15^\circ}$

In rectangular form:

$$3.2 \cdot V \cdot \cos(15^\circ) = 3.091 \cdot V$$

$$3.2 \cdot V \cdot \sin(15^\circ) = 0.828 \cdot V$$

$$V_1(j\omega) = 3.2 \cdot V \cdot e^{j15^\circ}$$

$$\text{or: } V_1(j\omega) = 3.2V \angle 15^\circ$$

$$\text{or: } V_1(j\omega) = (3.091 + 0.828j) \cdot V$$


Ex2 What if a signal is the sum of two sinusoids.

$$v_1(t) = 3.2 \cdot V \cdot \cos(\omega \cdot t + 15^\circ)$$

$$v_2(t) = 4.5 \cdot V \cdot \sin(\omega \cdot t + 60^\circ) \quad v_3(t) = v_1(t) + v_2(t)$$

I'm going to drop the $(j\omega)$ notation from the phasor notation, it gets cumbersome, but remember that phasors are in the frequency domain..
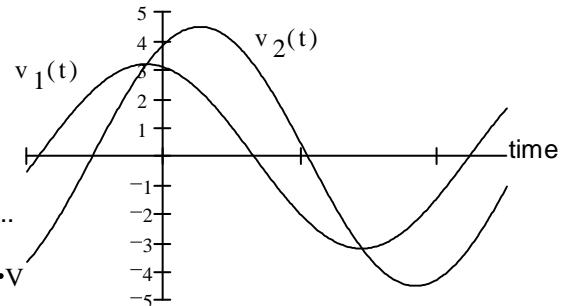
$$\text{From Ex1: } V_1 := 3.2 \cdot V \cdot e^{j15^\circ} = 3.2V \angle 15^\circ \quad V_1 = 3.091 + 0.828j \cdot V$$



Phasors are based on cosines, so express $v_2(t)$ as a cosine. Remember: $\sin(\omega t) = \cos(\omega t - 90^\circ)$

$$\text{So: } v_2(t) = 4.5 \cdot V \cdot \cos(\omega \cdot t + 60^\circ - 90^\circ) = 4.5 \cdot V \cdot \cos(\omega \cdot t - 30^\circ)$$

$$V_2 = 4.5V \angle -30^\circ \quad \text{or: } V_2 = 4.5 \cdot V \cdot e^{-j30^\circ}$$

$$4.5 \cdot V \cdot \cos(-30^\circ) = 3.897 \cdot V$$

$$4.5 \cdot V \cdot \sin(-30^\circ) = -2.25 \cdot V$$

$$V_2 = 3.897 - 2.25j \cdot V$$

$$V_1 = 3.091 + 0.828j \cdot V \quad \} \text{ add}$$

$$V_3 := V_1 + V_2$$

$$V_3 = 6.988 - 1.422j \cdot V \quad \text{sum}$$

$$\text{Add real parts: } 3.897 + 3.091 = 6.988$$

$$\text{Add imaginary parts: } -2.25 + 0.828 = -1.422$$

Change V_3 back to polar coordinates:

$$\sqrt{6.988^2 + 1.422^2} = 7.131 \quad \text{atan}\left(\frac{-1.422}{6.988}\right) = -11.502^\circ$$


OR, in Mathcad notation (you'll see these in future solutions):

$$|V_3| = 7.131 \cdot V \quad \arg(V_3) = -11.5^\circ$$

$$V_3(j\omega) = 7.131V \angle -11.5^\circ \quad \text{or: } V_3(j\omega) = 7.131 \cdot V \cdot e^{-j11.5^\circ}$$

V_3 may also be converted back to the time domain:
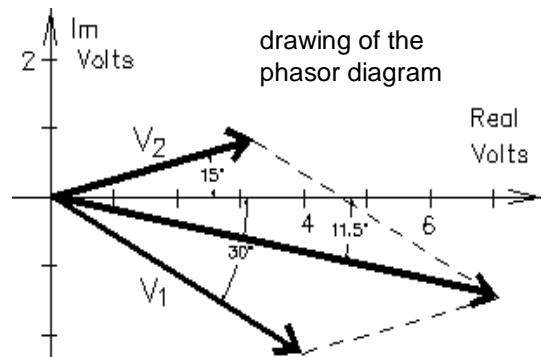
$$v_3(t) = v_1(t) + v_2(t) = 7.13 \cdot \cos(\omega \cdot t - 11.5^\circ) \cdot V$$



Magnitude and Phase of transfer functions With steady-state sinusoidal inputs

Ex3 a) Find the magnitude and phase of the following transfer function at this frequency: $\omega := 2 \frac{\text{rad}}{\text{sec}}$

$$H(s) = \frac{2 \cdot s^2 + 5 \cdot s + 20}{s^2 + 1 \cdot s + 10} = \frac{2 \cdot \frac{s^2}{\text{sec}} + 5 \cdot \frac{s}{\text{sec}} + \frac{20}{\text{sec}^2}}{\frac{s^2}{\text{sec}} + \frac{1}{\text{sec}} \cdot \frac{s}{\text{sec}} + \frac{10}{\text{sec}^2}}$$

Expressed with proper units

$$s := j \cdot \omega$$

$$H(j \cdot \omega) = \frac{2 \cdot (j \cdot \omega)^2 + 5 \cdot (j \cdot \omega) + 20}{(j \cdot \omega)^2 + \frac{1}{\text{sec}} \cdot (j \cdot \omega) + \frac{10}{\text{sec}^2}} = \frac{(20 - 2 \cdot \omega^2) + (5 \cdot \omega) \cdot j}{(10 - \omega^2) + (1 \cdot \omega) \cdot j} = \frac{(20 - 2 \cdot 2^2) + (5 \cdot 2) \cdot j}{(10 - 2^2) + (1 \cdot 2) \cdot j} = \frac{12 + 10 \cdot j}{6 + 2 \cdot j}$$

without units

$$|H(j \cdot \omega)| = M = \sqrt{12^2 + 10^2} = 2.47$$

$$\angle H(j\omega) = \arctan\left(\frac{10}{12}\right) - \arctan\left(\frac{2}{6}\right) = 21.37^\circ$$

b) Find the steady-state sinusoidal output if the input is: $3.2 \cdot V \cdot \cos(2 \cdot t + 15^\circ)$ $V_{in} := 3.2 \cdot V \cdot e^{j \cdot 15^\circ} = 3.2V \angle 15^\circ$

$$V_{outss}(j\omega) = V_{in}(j\omega) \cdot H(j\omega) = (3.2 \cdot V \cdot e^{j \cdot 15^\circ}) \cdot (2.47 \cdot e^{j \cdot 21.37^\circ}) = 3.2 \cdot V \cdot 2.47 \cdot e^{j \cdot (15^\circ + 21.37^\circ)} = 7.904 \cdot V \cdot e^{j \cdot 36.37^\circ} = 6.364 + 4.687j \text{ V}$$

$$v_{outss}(t) = 7.904 \cdot V \cdot \cos(2 \cdot t + 36.37^\circ)$$

Ex4 a) Find the magnitude and phase of the following transfer function at this frequency: $f := 5 \text{ Hz}$ $\omega := 2 \cdot \pi \cdot f$

$$H(s) = \frac{s^2 + \frac{20}{\text{sec}} \cdot s + \frac{1000}{\text{sec}^2}}{s^2 + \frac{10}{\text{sec}} \cdot s + \frac{800}{\text{sec}^2}}$$

$\omega = 31.42 \frac{\text{rad}}{\text{sec}}$

$$s := j \cdot \omega = j \cdot 31.42 \frac{\text{rad}}{\text{sec}} \quad H(j \cdot \omega) = \frac{(j \cdot \omega)^2 + \frac{20}{\text{sec}} \cdot (j \cdot \omega) + \frac{1000}{\text{sec}^2}}{(j \cdot \omega)^2 + \frac{10}{\text{sec}} \cdot (j \cdot \omega) + \frac{800}{\text{sec}^2}} = \frac{(j \cdot 31.42)^2 + 20 \cdot (j \cdot 31.42) + 1000}{(j \cdot 31.42)^2 + 10 \cdot (j \cdot 31.42) + 800}$$

without units

$$= \frac{13.04 + 628.319 \cdot j}{-186.96 + 314.159 \cdot j} = 1.459 - 0.91j$$

$$|H(j \cdot \omega)| = M = \sqrt{1.459^2 + 0.91^2} = 1.72 \quad \angle H(j\omega) = \arctan\left(\frac{-0.91}{1.459}\right) = -31.95^\circ$$

b) Find the steady-state sinusoidal output if the input is: $x(t) = 4 \cdot \cos(2 \cdot \pi \cdot 5 \text{ Hz} \cdot t)$

$$X(\omega) = 4 + 0j \quad \text{and then} \quad Y(\omega) = 4 \cdot (1.459 - 0.91j) = 5.836 - 3.64j$$

Note that you can use the rectangular form of $H(j \cdot \omega)$

$$y(t) = 5.836 \cdot \cos\left(31.42 \frac{\text{rad}}{\text{sec}} \cdot t\right) + 3.64 \cdot \sin\left(31.42 \frac{\text{rad}}{\text{sec}} \cdot t\right) \quad \text{note that the sine carries the opposite sign as the imaginary part.}$$



$$\sqrt{5.836^2 + 3.64^2} = 6.878$$

$$\arctan\left(\frac{-3.64}{5.836}\right) = -31.95^\circ$$

$$y(t) = 6.88 \cdot \cos\left(31.42 \frac{\text{rad}}{\text{sec}} \cdot t - 32^\circ\right)$$


Impedances

series:

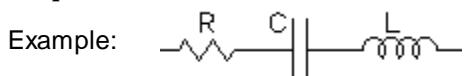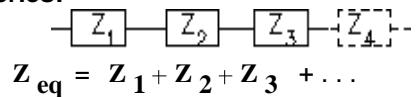

$$Z_{\text{eq}} = R + \frac{1}{C \cdot s} + L \cdot s$$

parallel:

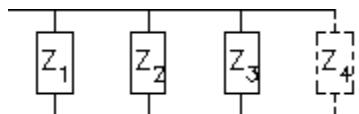

$$Z_{\text{eq}} = \frac{1}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} + \dots}$$

Example:

Voltage divider:


$$V_{Zn} = V_{\text{total}} \cdot \frac{Z_n}{Z_1 + Z_2 + Z_3 + \dots}$$

Current divider:

$$I_{Zn} = I_{\text{total}} \cdot \frac{\frac{1}{Z_n}}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} + \dots}$$

$$Z_{\text{eq}} = \frac{1}{\frac{1}{R} + \frac{1}{C \cdot s} + \frac{1}{L \cdot s}} = \frac{1}{\frac{1}{R} + C \cdot s + \frac{1}{L \cdot s}}$$

Ex5

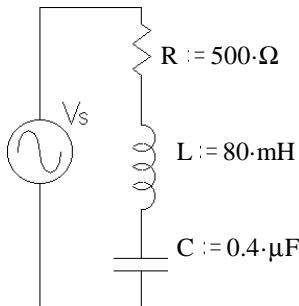

a) Find the steady-state V_R and $v_R(t)$ given $v_S(t)$ is a 12 Vpp cosine wave at: $f = 2\text{-kHz}$

$$V_S(j\omega) = 6 \cdot V \cdot e^{j0} \quad \omega := 2 \cdot \pi \cdot f \quad \omega = 12566 \cdot \frac{\text{rad}}{\text{sec}}$$

$$\text{Transfer function for } V_R \text{ as the output: } H(s) = \frac{V_R(s)}{V_S(s)} = \frac{R}{R + L \cdot s + \frac{1}{C \cdot s}}$$

$$V_R(j\omega) = 6 \cdot V \cdot \frac{R}{R + L \cdot (j \cdot \omega) + \frac{1}{C \cdot (j \cdot \omega)}} = 1.666 - 2.687j \cdot V \quad V_R = 3.163V \underline{-58.2^\circ}$$

$$v_R(t) = 3.163 \cdot V \cdot \cos \left(12566 \cdot \frac{\text{rad}}{\text{sec}} \cdot t - 58.2 \cdot \text{deg} \right)$$

b) Find the current: $\frac{I(s)}{V(s)} = \frac{1}{Z(s)}$ $I(s) = \frac{V(s)}{Z(s)}$ $s := j \cdot \omega = j \cdot 12566 \cdot \frac{\text{rad}}{\text{sec}}$

$$I := \frac{6 \cdot V \cdot e^{j0}}{R + L \cdot (j \cdot \omega) + \frac{1}{C \cdot (j \cdot \omega)}} = \frac{6 \cdot V}{500 + 0.080 \cdot (j \cdot 12566) + \frac{1}{0.4 \cdot 10^{-6} \cdot (j \cdot 12566)}} = \frac{6 \cdot V}{500 + 1005.3 \cdot j - 198.95 \cdot j} = \frac{6 \cdot V}{500 + 806.366 \cdot j}$$

$$\sqrt{500^2 + 806.366^2} = 948.802$$

$$\text{magnitude: } \frac{6 \cdot V}{948.8 \cdot \Omega} = 6.324 \cdot \text{mA}$$

$$\text{angle: } 0 \cdot \text{deg} - 58.2 \cdot \text{deg} = -58.2 \cdot \text{deg}$$

$$I = 6.324 \text{mA} \underline{-58.2^\circ}$$

$$\text{atan} \left(\frac{806.366}{500} \right) = 58.198 \cdot \text{deg}$$

c) Draw a phasor diagram of all the voltages.

$$V_L = I \cdot Z_L \quad 6.324 \cdot \text{mA} \cdot 1005 \cdot \Omega = 6.356 \cdot V$$


$$-58.2 \cdot \text{deg} + 90 \cdot \text{deg} = 31.8 \cdot \text{deg}$$

$$V_L = 6.356V \underline{31.8^\circ}$$

$$V_C = I \cdot Z_C \quad 6.324 \cdot \text{mA} \cdot (-199) \cdot \Omega = -1.258 \cdot V$$

$$-58.2 \cdot \text{deg} + (90) \cdot \text{deg} = 31.8 \cdot \text{deg}$$
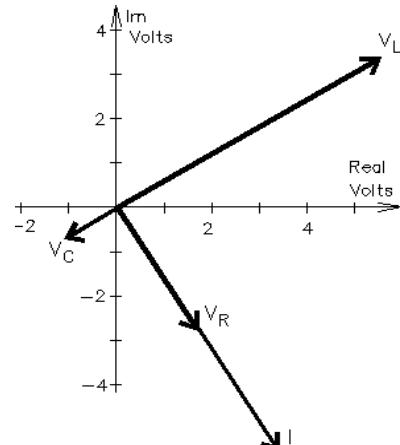
$$V_C = -1.258V \underline{31.8^\circ} = 1.258V \underline{-148.2^\circ}$$




Sinusoidal Response Notes p5

Ex6 a) Find the steady-state \mathbf{V}_C and $v_C(t)$ given $v_{in}(t)$ is a 12 Vp cosine wave at: $f := 2.5 \cdot \text{kHz}$ with a 20° leading phase angle.

Transfer function for \mathbf{V}_C as the output: $H(s) = \frac{\mathbf{V}_C(s)}{\mathbf{V}_{in}(s)}$
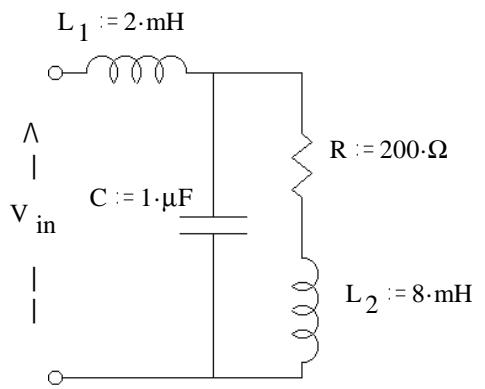
$$H(s) = \frac{\frac{1}{R + L_2 \cdot s}}{L_1 \cdot s + \frac{1}{R + L_2 \cdot s} + C \cdot s} = \frac{\left(\frac{1}{R + L_2 \cdot s} + C \cdot s \right)}{\left(\frac{1}{R + L_2 \cdot s} + C \cdot s \right) + L_1 \cdot s} = \frac{1}{L_1 \cdot s \cdot \left(\frac{1}{R + L_2 \cdot s} + C \cdot s \right) + 1}$$



$$V_{in} := 12 \cdot V \cdot e^{j \cdot 20^\circ \text{deg}} \quad \omega := 2 \cdot \pi \cdot f \quad \omega = 15708 \cdot \frac{\text{rad}}{\text{sec}}$$

$$\begin{aligned} H(j\omega) &= \frac{1}{L_1 \cdot (j\omega) \cdot \left[\frac{1}{R + L_2 \cdot (j\omega)} + C \cdot (j\omega) \right] + 1} = \frac{1}{0.002 \cdot (j \cdot 15708) \cdot \left[\frac{1}{200 + 0.008 \cdot (j \cdot 15708)} + 10^{-6} \cdot (j \cdot 15708) \right] + 1} \\ &= \frac{1}{31.416 \cdot j \cdot [3.585 \cdot 10^{-3} - 2.252 \cdot 10^{-3} \cdot j + (j \cdot 0.015708)] + 1} = \frac{1}{1 - 0.423 + 0.113 \cdot j} = \frac{1}{0.588 \cdot e^{j \cdot 11.039^\circ \text{deg}}} \\ &= 1.7 \cdot e^{-j \cdot 11.039^\circ \text{deg}} \end{aligned}$$

$$V_C = V_{in}(j\omega) \cdot H(j\omega) = 12 \cdot V \cdot e^{j \cdot 20^\circ \text{deg}} \cdot 1.7 \cdot e^{-j \cdot 11.039^\circ \text{deg}} = 12 \cdot V \cdot 1.7 / 20 - 11.039^\circ = 20.4 \text{V} / 8.96^\circ$$

$$v_C(t) = 20.4 \cdot V \cdot \cos \left(15708 \cdot \frac{\text{rad}}{\text{sec}} \cdot t + 8.96^\circ \text{deg} \right)$$

a) Find the steady-state I_{L2} and $i_{L2}(t)$.

Transfer function for I_{L2} as the output: $H(s) = \frac{I_{L2}(s)}{\mathbf{V}_{in}(s)} = \frac{\left(\frac{\mathbf{V}_C(s)}{R + L_2 \cdot s} \right)}{\mathbf{V}_{in}(s)} = \frac{\mathbf{V}_C(s)}{\mathbf{V}_{in}(s)} \cdot \frac{1}{R + L_2 \cdot s}$

$$H(s) = \frac{1}{L_1 \cdot s \cdot \left(\frac{1}{R + L_2 \cdot s} + C \cdot s \right) + 1} \cdot \frac{1}{(R + L_2 \cdot s)} = \frac{1}{L_1 \cdot s + L_1 \cdot s \cdot C \cdot s \cdot (R + L_2 \cdot s) + (R + L_2 \cdot s)}$$

$$H(j\omega) = \frac{1}{L_1 \cdot (j\omega) + L_1 \cdot C \cdot (j\omega)^2 \cdot [R + L_2 \cdot (j\omega)] + [R + L_2 \cdot (j\omega)]} = 5.249 \cdot 10^{-3} - 4.926 \cdot 10^{-3} j \cdot \frac{1}{\Omega} = \frac{7.198}{k\Omega} \cdot e^{-j \cdot 43.181^\circ \text{deg}}$$

$$I_{L2} = V_{in}(j\omega) \cdot H(j\omega) = 12 \cdot V \cdot e^{j \cdot 20^\circ \text{deg}} \cdot \left(\frac{7.198}{k\Omega} \cdot e^{-j \cdot 43.181^\circ \text{deg}} \right) = 12 \cdot V \cdot \frac{7.198}{k\Omega} / 20 - 43.181^\circ = 86.38 \text{mA} / -23.18^\circ$$

$$i_{L2}(t) = 86.38 \cdot \text{mA} \cdot \cos \left(15708 \cdot \frac{\text{rad}}{\text{sec}} \cdot t - 23.18^\circ \text{deg} \right)$$

Sinusoidal Response Notes p5

Sinusoidal Response Notes p6

Ex7 This system: $H(s) = \frac{s+20}{s+5}$ Has this input: $x(t) = 4 \cdot \sin(12 \cdot t - 40 \cdot \text{deg}) \cdot u(t)$

a) Use steady-state AC analysis to find the steady-state output. $y_{ss}(t) = ?$

$$\text{AC steady-state } H(j\omega) = H(j \cdot 12) = \frac{j \cdot 12 + 20}{j \cdot 12 + 5} = \frac{\sqrt{12^2 + 20^2} \cdot e^{j \cdot \tan^{-1}\left(\frac{12}{20}\right)}}{\sqrt{12^2 + 5^2} \cdot e^{j \cdot \tan^{-1}\left(\frac{12}{5}\right)}} = \frac{23.324 \cdot e^{j \cdot 30.964 \cdot \text{deg}}}{13 \cdot e^{j \cdot 67.38 \cdot \text{deg}}} = 1.794 / \angle -36.416 \cdot \text{deg}$$

$$X(j\omega) = 4 \cdot e^{-j \cdot 130 \cdot \text{deg}} \quad \text{Note } 90^\circ \text{ phase-lag because it's given as a sine wave}$$

$$\begin{aligned} Y_{ss}(j\omega) &= 4 \cdot 1.794 = 7.176 / \angle -130 - 36.416 = -166.416 \\ &= 7.176 / \angle -166.416 \cdot \text{deg} \end{aligned}$$

$$y_{ss}(t) = 7.176 \cdot \cos(12 \cdot t - 166.416 \cdot \text{deg})$$

b) Express the output, and separate into 3 partial fractions that you can find in the laplace transform table without using complex numbers. Show what they are, but don't find the coefficients.

Find the input as a sum of a pure sine and cosine $-4 \cdot \sin(-130 \cdot \text{deg}) = 3.064 \quad 4 \cdot \cos(-130 \cdot \text{deg}) = -2.571$

$$\text{so: } 4 \cdot \sin(12 \cdot t - 40 \cdot \text{deg}) \cdot u(t) = (3.064 \cdot \sin(12 \cdot t) - 2.571 \cdot \cos(12 \cdot t)) \cdot u(t)$$

$$Y(s) = \frac{3.064 \cdot 12 - 2.571 \cdot s}{s^2 + 144} \cdot \frac{(s+20)}{(s+5)} = \frac{A}{s+5} + \frac{B \cdot s}{(s^2 + 144)} + \frac{C \cdot 12}{(s^2 + 144)}$$

c) Continue with the partial fraction expansion just far enough to find the **transient** coefficient as a number.

$$(3.064 \cdot 12 - 2.571 \cdot s) \cdot (s+20) = A \cdot (s^2 + 144) + B \cdot s \cdot (s+5) + C \cdot 12 \cdot (s+5)$$

let $s := -5$

$$(3.064 \cdot 12 - 2.571 \cdot (-5)) \cdot (-5+20) = A \cdot (5^2 + 144) + 0 + 0$$

$$A := \frac{(s+20) \cdot (3.064 \cdot 12 - 2.571 \cdot s)}{25 + 144} \quad A = 4.404$$

d) Express the complete (both transient and steady-state) output as a function of time. $y(t) = ?$

$$y(t) = (4.404 \cdot e^{-5t} + 7.176 \cdot \cos(12 \cdot t - 166.416 \cdot \text{deg})) \cdot u(t)$$

$$7.176 \cdot \cos(-166.416 \cdot \text{deg}) = -6.975$$

Either answer

$$-7.176 \cdot \sin(-166.416 \cdot \text{deg}) = 1.685$$

$$y(t) = (4.404 \cdot e^{-5t} - 6.975 \cdot \cos(12 \cdot t) + 1.685 \cdot \sin(12 \cdot t)) \cdot u(t)$$

e) What is the time constant of the transient part this expression? $\tau = ? = \frac{1}{5}$

Sinusoidal Response Notes p6