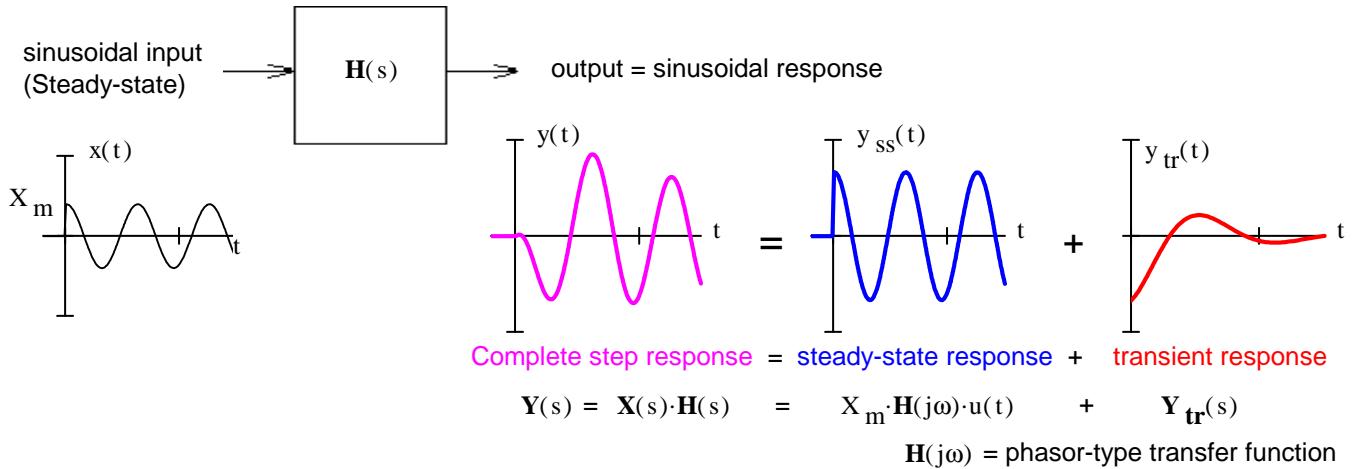


The sinusoidal response of a system is the output when the input is a sinusoidal (which starts at time = 0).

System Sinusoidal Response



Sinusoidal Input

$$\cos(\omega t) \cdot u(t) \Leftrightarrow \frac{s}{s^2 + \omega^2}$$

$$\sin(\omega t) \cdot u(t) \Leftrightarrow \frac{\omega}{s^2 + \omega^2}$$

General sinusoidal input: $[X_{mc} \cdot \cos(\omega t) + X_{ms} \cdot (\sin(\omega t) \cdot u(t))] \cdot u(t)$

$$X(s) = \frac{X_{mc} \cdot s + X_{ms} \cdot \omega}{s^2 + \omega^2}$$

OR $X_m \cdot \cos(\omega t + \theta) \cdot u(t) = [X_{mc} \cdot \cos(\omega t) + X_{ms} \cdot (\sin(\omega t) \cdot u(t))] \cdot u(t)$

$$X_{mc} = X_m \cdot \cos(\theta) \quad X_{ms} = -X_m \cdot \sin(\theta) \quad \text{note that the sine carries the opposite sign as you might expect.}$$

Steady-State Response & $H(j\omega)$

$$Y(s) = X(s) \cdot H(s) = \frac{X_{mc} \cdot s + X_{ms} \cdot \omega}{s^2 + \omega^2} \cdot H(s) = \text{Complete sinusoidal response}$$

$$= \frac{A \cdot s + B \cdot \omega}{s^2 + \omega^2} + \frac{C}{(s + i\omega)} + \frac{D}{(s - i\omega)} + \frac{E}{(s^2 + \omega^2)}$$

partial fraction expansion: $Y(s) = \frac{X_{mc} \cdot s + X_{ms} \cdot \omega}{s^2 + \omega^2} \cdot H(s) = \frac{A \cdot s + B \cdot \omega}{s^2 + \omega^2} + \left[\frac{C}{(s + i\omega)} + \frac{D}{(s - i\omega)} + \frac{E}{(s^2 + \omega^2)} \right] \cdot s$

steady-state response + transient response

multiply both sides by $(s^2 + \omega^2)$ $(X_{mc} \cdot s + X_{ms} \cdot \omega) \cdot H(s) = A \cdot s + B \cdot \omega + \left[\frac{C}{(s + i\omega)} + \frac{D}{(s - i\omega)} + \frac{E}{(s^2 + \omega^2)} \right] \cdot (s^2 + \omega^2)$

set $s := j\omega$ $(X_{mc} \cdot j\omega + X_{ms} \cdot \omega) \cdot H(j\omega) = A \cdot j\omega + B \cdot \omega + \left[\frac{C}{(j\omega + i\omega)} + \frac{D}{(j\omega - i\omega)} + \frac{E}{(j\omega^2 + \omega^2)} \right] \cdot 0$

divide both sides by $j\omega$ $(X_{mc} - X_{ms} \cdot j) \cdot H(j\omega)$

$$X(\omega) \cdot H(j\omega) = A - B \cdot j = Y_{ss}(\omega) = \text{steady-state response in phasor form}$$

(real is cosine, imaginary is -sine)

$X(\omega)$ = the input expressed in phasor form NOT $X(s)$ with $s := \omega$ or $s := j\omega$
 $H(j\omega)$ = the steady-state sinusoidal transfer function (that would be ∞)
= phasor-type transfer function

Steady-State Response by Phasors

Time-domain sinusoids

T = Period



$$f = \text{frequency, cycles / second} \quad f = \frac{1}{T} = \frac{\omega}{2\pi}$$

$$\omega = \text{radian frequency, radians/sec} \quad \omega = 2\pi f$$

A = amplitude

$$\text{Phase: } \phi = -\frac{\Delta t}{T} \cdot 360 \cdot \text{deg} \quad \text{or: } \phi = -\frac{\Delta t}{T} \cdot 2\pi \cdot \text{rad}$$

$$y(t) = A \cdot \cos(\omega t + \phi)$$

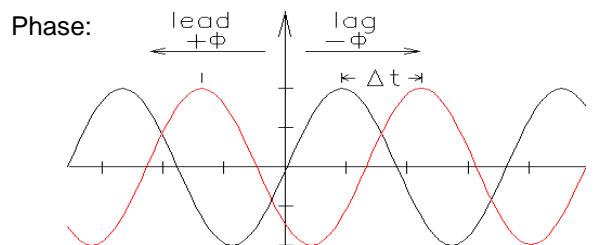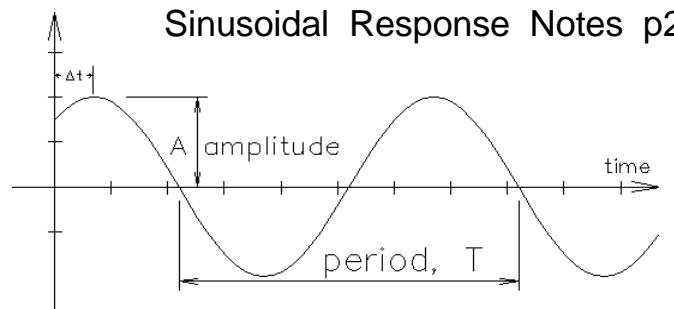

Expression of signals as phasors

Phasor

$$\text{voltage: } v(t) = V_p \cdot \cos(\omega t + \phi)$$

$$V(\omega) = V_p e^{j\phi}$$

$$\text{current: } i(t) = I_p \cdot \cos(\omega t + \phi)$$

$$I(\omega) = I_p e^{j\phi}$$

Ex1 What if a signal is the sum of two sinusoids of the same frequency.

$$v_1(t) = 3.2 \cdot V \cdot \cos(\omega t + 40^\circ)$$

$$v_2(t) = 4.5 \cdot V \cdot \sin(\omega t + 75^\circ)$$


$$v_3(t) = v_1(t) + v_2(t)$$

I'm going to drop the (ω) notation from the phasor notation, it gets cumbersome, but remember that phasors are in the frequency domain.

Express the time-domain voltages as phasors:

$$V_1 := 3.2 \cdot V \cdot e^{j40^\circ} = 3.2V / 40^\circ$$
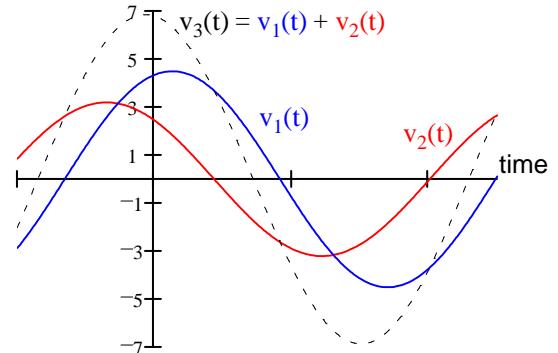
$$\text{Convert to rectangular: } 3.2 \cdot V \cdot \cos(40^\circ) = 2.451 \cdot V \quad 3.2 \cdot V \cdot \sin(40^\circ) = 2.057 \cdot V \quad V_1 = 2.451 + 2.057j \cdot V$$



Phasors are based on cosines, so express $v_2(t)$ as a cosine. Remember: $\sin(\omega t) = \cos(\omega t - 90^\circ)$

$$\text{So: } v_2(t) = 4.5 \cdot V \cdot \cos(\omega t + 75^\circ - 90^\circ) = 4.5 \cdot V \cdot \cos(\omega t - 15^\circ)$$

$$V_2 = 4.5V / -15^\circ \quad \text{or: } V_2 := 4.5 \cdot V \cdot e^{-j15^\circ}$$

$$4.5 \cdot V \cdot \cos(-15^\circ) = 4.347 \cdot V$$

$$4.5 \cdot V \cdot \sin(-15^\circ) = -1.165 \cdot V$$

$$V_2 = 4.347 - 1.165j \cdot V$$

$$V_1 = 2.451 + 2.057j \cdot V \quad \} \text{ add}$$

$$V_3 := V_1 + V_2$$

$$V_3 = 6.798 + 0.892j \cdot V \quad \text{sum}$$

$$\text{Add real parts: } 4.347 + 2.451 = 6.798$$

$$\text{Add imaginary parts: } -1.165 + 2.057 = 0.892$$

Change V_3 back to polar coordinates:

$$\sqrt{6.798^2 + 0.892^2} = 6.856 \quad \text{atan}\left(\frac{0.892}{6.798}\right) = 7.48^\circ$$


OR, in Mathcad notation (which you'll see a lot more):

$$|V_3| = 6.856 \cdot V \quad \arg(V_3) = 7.48^\circ$$

$$V_3(\omega) = 6.856V / 7.48^\circ \quad \text{or: } V_3(\omega) = 6.856 \cdot V \cdot e^{-j7.48^\circ}$$

V_3 may also be converted back to the time domain:
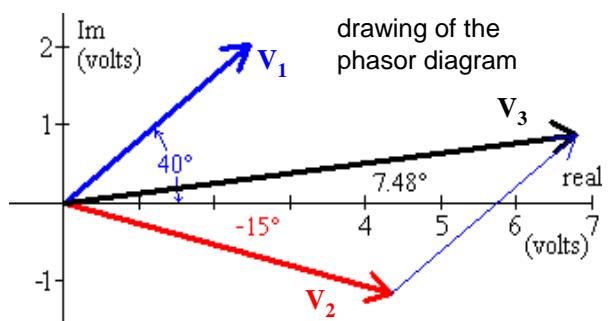
$$v_3(t) = v_1(t) + v_2(t) = 6.856 \cdot \cos(\omega t + 7.48^\circ) \cdot V$$



Impedances


Resistor

$$v_R = i_R \cdot R$$


$$V_R(s) = R \cdot I(s)$$

$$Z_R = R$$

series:

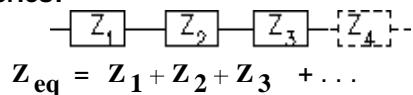

Example:

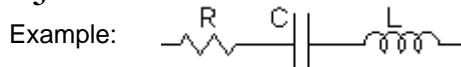

Inductor

$$v_L(t) = L \cdot \frac{d}{dt} i_L(t)$$

$$V_L(s) = s \cdot L \cdot I_L(s)$$

$$Z_L = L \cdot s$$

Capacitor

$$i_C(t) = C \cdot \frac{d}{dt} v_C(t)$$

$$I_C(s) = C \cdot s \cdot V_C(s)$$

$$V_C(\omega) = \frac{1}{C \cdot s} \cdot I(s)$$


$$Z_C = \frac{1}{C \cdot s}$$

Voltage divider:


$$V_{Zn} = V_{total} \cdot \frac{Z_n}{Z_1 + Z_2 + Z_3 + \dots}$$

$$Z_{eq} = R + \frac{1}{C \cdot s} + L \cdot s$$

parallel:

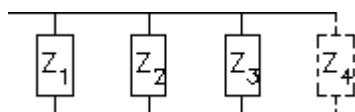

Example:

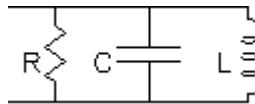


Current divider:

$$I_{Zn} = I_{total} \cdot \frac{\frac{1}{Z_n}}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} + \dots}$$

$$Z_{eq} = \frac{1}{\frac{1}{R} + \frac{1}{C \cdot s} + \frac{1}{L \cdot s}} = \frac{1}{\frac{1}{R} + C \cdot s + \frac{1}{L \cdot s}}$$

For Steady-State Response, replace s with $j\omega$ & $1/s$ with $-j\omega$.

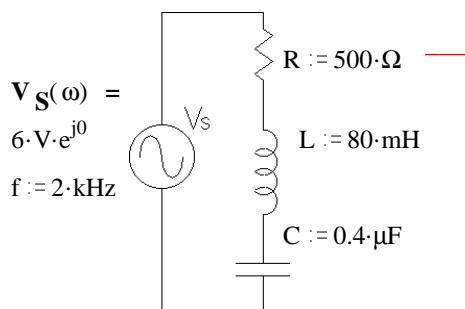Ex2 Find V_R , V_L , and V_C in polar phasor form. $f := 2\text{-kHz}$ Steady-state



$$\omega := 2 \cdot \pi \cdot f$$

$$\omega = 12566 \cdot \frac{\text{rad}}{\text{sec}}$$

$$Z_L := j \cdot \omega L$$

$$Z_L = 1.005j \cdot k\Omega$$

$$= 1005\Omega \angle 90^\circ$$

$$Z_C := \frac{1}{j \cdot \omega C}$$

$$Z_C = -0.199j \cdot k\Omega$$

$$= -199\Omega \angle 90^\circ = 199\Omega \angle -90^\circ$$


$$Z_{eq} := R + j \cdot \omega L + \frac{1}{j \cdot \omega C}$$

$$Z_{eq} = 500 + 806.366j \cdot \Omega$$

$$\sqrt{500^2 + 806^2} = 948.491$$

$$\text{atan}\left(\frac{806}{500}\right) = 58.187 \cdot \text{deg}$$
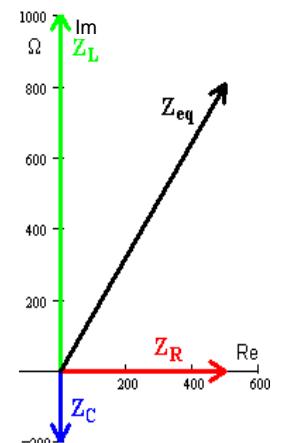
$$Z_{eq} = 948.5\Omega \angle 58.2^\circ$$



b) find the current: $I := \frac{6 \cdot V \cdot e^{j0}}{Z_{eq}}$

magnitude: $\frac{6 \cdot V}{948.5 \cdot \Omega} = 6.326 \cdot \text{mA}$

angle: $0^\circ - 58.2^\circ = -58.2^\circ$

$$I = 6.326 \text{mA} \angle -58.2^\circ$$

c) Draw a phasor diagram of V_s , V_R , V_L , and V_C

$$V_R := I \cdot R$$

magnitude $6.326 \cdot \text{mA} \cdot 500 \cdot \Omega = 3.163 \cdot \text{V}$

angle $-58.2^\circ + 0^\circ = -58.2^\circ$

$$V_R = 3.163 \text{V} \angle -58.2^\circ$$

$$V_L := I \cdot Z_L$$

$6.326 \cdot \text{mA} \cdot 1005 \cdot \Omega = 6.358 \cdot \text{V}$

$-58.2^\circ + 90^\circ = 31.8^\circ$



$$V_L = 6.358 \text{V} \angle 31.8^\circ$$

$$V_C := I \cdot Z_C$$

$6.326 \cdot \text{mA} \cdot (199) \cdot \Omega = 1.259 \cdot \text{V}$

$-58.2^\circ + (-90^\circ) = -148.2^\circ$
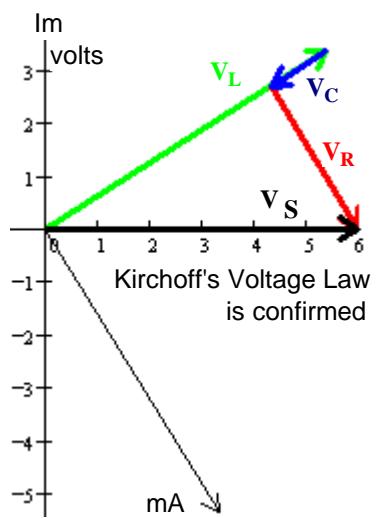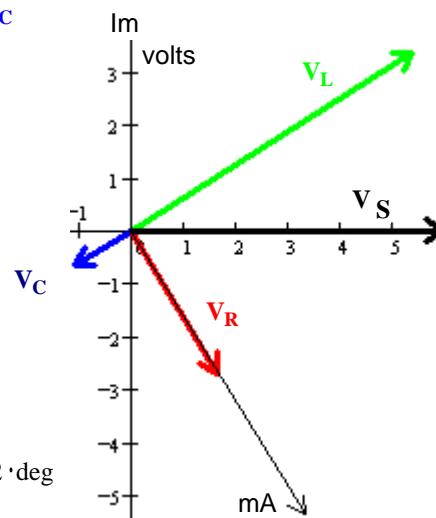
$$V_C = 1.259 \text{V} \angle -148.2^\circ$$



Sinusoidal Response Notes p4

Ex3 a) Find the steady-state V_C and $v_C(t)$


given $v_{in}(t)$ is a 12-V cosine wave at: $f := 2.5 \text{ kHz}$

with a 20° leading phase angle. $V_{in} := 12 \cdot V \cdot e^{j \cdot 20^\circ \text{ deg}}$

Transfer function for V_C as the output: $H(s) = \frac{V_C(s)}{V_{in}(s)}$

$$H(s) = \frac{\frac{1}{R + L_2 \cdot s}}{L_1 \cdot s + \frac{1}{R + L_2 \cdot s} + C \cdot s} = \frac{\left(\frac{1}{R + L_2 \cdot s} + C \cdot s \right)}{\left(\frac{1}{R + L_2 \cdot s} + C \cdot s \right)}$$
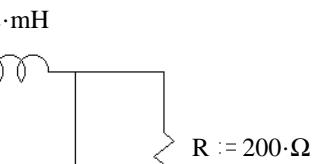
$$= \frac{1}{L_1 \cdot s \cdot \left(\frac{1}{R + L_2 \cdot s} + C \cdot s \right) + 1} = \frac{1}{L_1 \cdot (j \cdot \omega) \cdot \left[\frac{1}{R + L_2 \cdot (j \cdot \omega)} + C \cdot (j \cdot \omega) \right] + 1}$$



$$\begin{aligned} & L_1 := 2 \cdot mH \\ & C := 1 \cdot \mu F \\ & R := 200 \cdot \Omega \\ & L_2 := 8 \cdot mH \end{aligned}$$

$$\begin{aligned} f &= 2.5 \cdot \text{kHz} \\ \omega &:= 2 \cdot \pi \cdot f \\ \omega &= 15708 \cdot \frac{\text{rad}}{\text{sec}} \end{aligned}$$

$$H(j\omega) = \frac{1}{0.002 \cdot (j \cdot 15708) \cdot \left[\frac{1}{200 + 0.008 \cdot (j \cdot 15708)} + 10^{-6} \cdot (j \cdot 15708) \right] + 1}$$

$$= \frac{1}{31.416 \cdot j \cdot [3.585 \cdot 10^{-3} - 2.252 \cdot 10^{-3} \cdot j + (j \cdot 0.015708)] + 1} = \frac{1}{1 - 0.423 + 0.113 \cdot j} = \frac{1}{0.588 \cdot e^{-j \cdot 11.039 \cdot \text{deg}}}$$

$$= 1.7 \cdot e^{-j \cdot 11.039 \cdot \text{deg}}$$

$$V_C = V_{in}(\omega) \cdot H(j\omega) = 12 \cdot V \cdot e^{j \cdot 20^\circ \text{ deg}} \cdot 1.7 \cdot e^{-j \cdot 11.039 \cdot \text{deg}} = 12 \cdot V \cdot 1.7 / 20 - 11.039^\circ = 20.4 \text{ V} / 8.96^\circ$$

$$v_C(t) = 20.4 \cdot V \cdot \cos \left(15708 \cdot \frac{\text{rad}}{\text{sec}} \cdot t + 8.96^\circ \right)$$

a) Find the steady-state I_{L2} and $i_{L2}(t)$.

Transfer function for I_{L2} as the output: $H(s) = \frac{I_{L2}(s)}{V_{in}(s)} = \frac{\left(\frac{V_C(s)}{R + L_2 \cdot s} \right)}{V_{in}(s)} = \frac{V_C(s)}{V_{in}(s)} \cdot \frac{1}{R + L_2 \cdot s}$

$$H(s) = \frac{1}{L_1 \cdot s \cdot \left(\frac{1}{R + L_2 \cdot s} + C \cdot s \right) + 1} \cdot \frac{1}{(R + L_2 \cdot s)} = \frac{1}{L_1 \cdot s + L_1 \cdot s \cdot C \cdot s \cdot (R + L_2 \cdot s) + (R + L_2 \cdot s)}$$

$$H(j\omega) = \frac{1}{L_1 \cdot (j \cdot \omega) + L_1 \cdot C \cdot (j \cdot \omega)^2 \cdot [R + L_2 \cdot (j \cdot \omega)] + [R + L_2 \cdot (j \cdot \omega)]} = 5.249 \cdot 10^{-3} - 4.926 \cdot 10^{-3} j \cdot \frac{1}{\Omega} = \frac{7.198}{k\Omega} \cdot e^{-j \cdot 43.181 \cdot \text{deg}}$$

$$I_{L2} = V_{in}(\omega) \cdot H(j\omega) = 12 \cdot V \cdot e^{j \cdot 20^\circ \text{ deg}} \cdot \left(\frac{7.198}{k\Omega} \cdot e^{-j \cdot 43.181 \cdot \text{deg}} \right) = 12 \cdot V \cdot \frac{7.198}{k\Omega} / 20 - 43.181^\circ = 86.38 \text{ mA} / -23.18^\circ$$

$$i_{L2}(t) = 86.38 \cdot \text{mA} \cdot \cos \left(15708 \cdot \frac{\text{rad}}{\text{sec}} \cdot t - 23.18^\circ \right)$$

Sinusoidal Response Notes p4

Magnitude and Phase of transfer functions

With steady-state sinusoidal inputs which start at $t = 0$

Ex4 a) Find the magnitude and phase of the following transfer function at this frequency: $f := 5 \cdot \text{Hz}$ $\omega := 2 \cdot \pi \cdot f$

$$\mathbf{H}(s) = \frac{s^2 + \frac{20}{\text{sec}} \cdot s + \frac{1000}{\text{sec}^2}}{s^2 + \frac{8}{\text{sec}} \cdot s + \frac{800}{\text{sec}^2}}$$

$$s := j \cdot \omega = j \cdot 31.42 \frac{\text{rad}}{\text{sec}} \quad \mathbf{H}(j \cdot \omega) = \frac{(j \cdot \omega)^2 + \frac{20}{\text{sec}} \cdot (j \cdot \omega) + \frac{1000}{\text{sec}^2}}{(j \cdot \omega)^2 + \frac{8}{\text{sec}} \cdot (j \cdot \omega) + \frac{800}{\text{sec}^2}} = \frac{(j \cdot 31.42)^2 + 20 \cdot (j \cdot 31.42) + 1000}{(j \cdot 31.42)^2 + 8 \cdot (j \cdot 31.42) + 800} \quad \text{without units}$$

$$= \frac{13.04 + 628.319 \cdot j}{-187.2164 + 251.36 \cdot j} = 1.583 - 1.231j$$

$$|\mathbf{H}(j \cdot \omega)| = M = \sqrt{(1.583)^2 + (1.231)^2} = 2.005 \quad \underline{\mathbf{H}(j \omega)} = \text{atan}\left(\frac{-1.231}{1.583}\right) = -37.87 \cdot \text{deg} \quad \mathbf{H}(j \cdot \omega) = 2.005 \angle -37.87^\circ$$

b) Find the **steady-state** sinusoidal output if the input is: $x(t) = 4 \cdot \cos(2 \cdot \pi \cdot 5 \cdot \text{Hz} \cdot t)$ $\mathbf{X}(\omega) = 4 + 0j$

$$\text{and then } \mathbf{Y}(\omega) = \mathbf{X}(\omega) \cdot \mathbf{H}(j \cdot \omega) = 4 \cdot (1.583 - 1.231j) = 6.332 - 4.924j$$

Note that you can use the rectangular form of $\mathbf{H}(j \cdot \omega)$

$$y_{ss}(t) = \left(6.332 \cdot \cos\left(31.42 \frac{\text{rad}}{\text{sec}} \cdot t\right) + 4.924 \cdot \sin\left(31.42 \frac{\text{rad}}{\text{sec}} \cdot t\right) \right) \cdot u(t) \quad \text{note that the sine carries the opposite sign as the imaginary part of phasor.}$$

$$\sqrt{6.332^2 + 4.924^2} = 8.021 \quad \text{atan}\left(\frac{-4.924}{6.332}\right) = -37.87 \cdot \text{deg} \quad y_{ss}(t) := 8.021 \cdot \cos(31.42 \cdot t - 37.87 \cdot \text{deg}) \cdot u(t)$$

c) Find the **transient response** for the same input. $x(t) = 4 \cdot \cos(2 \cdot \pi \cdot 5 \cdot \text{Hz} \cdot t)$ $\mathbf{X}(s) = 4 \cdot \frac{s}{s^2 + 31.42^2}$

$$\mathbf{Y}_{tr}(s) = \frac{4 \cdot s}{s^2 + 31.42^2} \cdot \frac{s^2 + 20 \cdot s + 1000}{s^2 + 8 \cdot s + 800} \quad a := -4 \quad b := \sqrt{800 - 4^2} \quad b = 28$$

$$= A \cdot \frac{s + 4}{s^2 + 8 \cdot s + 800} + B \cdot \frac{28}{s^2 + 8 \cdot s + 800} + C \cdot \frac{s}{s^2 + 31.42^2} + D \cdot \frac{31.42}{s^2 + 31.42^2}$$

multiply both sides by $(s^2 + 8 \cdot s + 800)$ and let $s := -4 + 28 \cdot j$


$$\frac{4 \cdot (-4 + 28j) \cdot [(-4 + 28j)^2 + 20 \cdot (-4 + 28j) + 1000]}{(-4 + 28j)^2 + 31.42^2} = -115.969 - 65.365j = A((-4 + 28j) - 4) + B \cdot 28$$

$$\frac{-115.969 - 65.365j}{28} = -4.142 - 2.334j = A \cdot j + B \quad A := -2.334 \quad B := -4.142$$

$$y_{tr}(t) := (-2.334 \cdot e^{-4t} \cdot \cos(28t) - 4.142 \cdot e^{-4t} \cdot \sin(28t)) \cdot u(t)$$

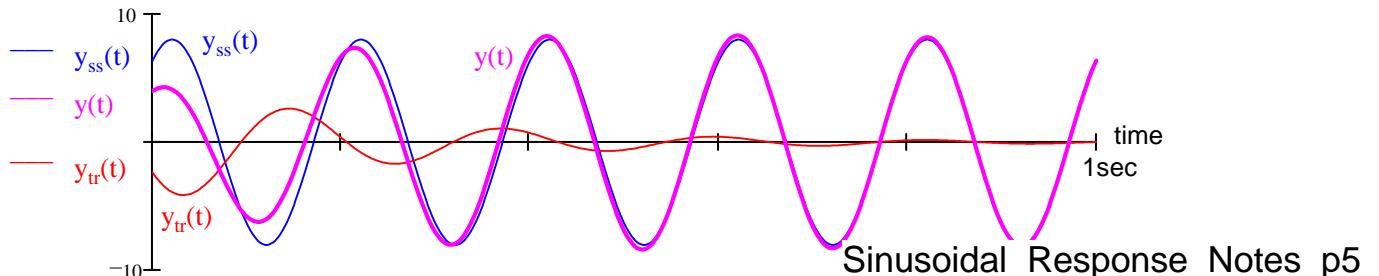d) Find the **total response** for the same input.

$$y(t) := (-2.334 \cdot e^{-4t} \cdot \cos(28t) - 4.142 \cdot e^{-4t} \cdot \sin(28t) + 8.021 \cdot \cos(31.42t - 37.87 \cdot \text{deg})) \cdot u(t)$$



Sinusoidal Response Notes p6

Ex4 a) Find the magnitude and phase of the following transfer function at this frequency: $\omega := 2 \cdot \frac{\text{rad}}{\text{sec}}$

$$H(s) = \frac{2 \cdot s^2 + 5 \cdot s + 20}{s^2 + 2 \cdot s + 10} = \frac{2 \cdot s^2 + \frac{5}{\text{sec}} \cdot s + \frac{20}{\text{sec}^2} \cdot V}{s^2 + \frac{2}{\text{sec}} \cdot s + \frac{10}{\text{sec}^2} \cdot V}$$

Expressed with proper units.
In this case the transfer function is for a circuit where both the input and output are voltages.

$$s := j \cdot \omega$$

$$H(j \cdot \omega) = \frac{2 \cdot (j \cdot \omega)^2 + 5 \cdot (j \cdot \omega) + 20}{(j \cdot \omega)^2 + \frac{2}{\text{sec}} \cdot (j \cdot \omega) + \frac{10}{\text{sec}^2}} = \frac{(20 - 2 \cdot \omega^2) + (5 \cdot \omega) \cdot j}{(10 - \omega^2) + (2 \cdot \omega) \cdot j} = \frac{(20 - 2 \cdot 2^2) + (5 \cdot 2) \cdot j}{(10 - 2^2) + (2 \cdot 2) \cdot j} = \frac{12 + 10 \cdot j}{6 + 4 \cdot j}$$

without units

$$|H(j \cdot \omega)| = M = \sqrt{12^2 + 10^2} = 2.166 \quad \angle H(j \omega) = \arctan\left(\frac{10}{12}\right) - \arctan\left(\frac{4}{6}\right) = 6.12^\circ \quad H(j \cdot \omega) = 2.166 \angle 6.12^\circ$$

b) Find the **steady-state response** if the input is: $v_{in}(t) = 3.2 \cdot \cos(2 \cdot t + 15^\circ)$ $V_{in} := 3.2 \cdot V \cdot e^{j \cdot 15^\circ} = 3.2V \angle 15^\circ$

$$V_{out_ss}(\omega) = V_{in}(\omega) \cdot H(j \cdot \omega) = (3.2 \cdot V \cdot e^{j \cdot 15^\circ}) \cdot (2.166 \cdot e^{j \cdot 6.12^\circ}) = 3.2 \cdot V \cdot 2.166 \cdot e^{j \cdot (15^\circ + 6.12^\circ)} = 6.931 \cdot V \cdot e^{j \cdot 21.12^\circ} = 6.465 + 2.497j \cdot V$$

$$v_{out_ss}(t) = 6.931 \cdot V \cdot \cos(2 \cdot t + 21.12^\circ) \cdot u(t) = (6.465 \cdot \cos(2 \cdot t) - 2.497 \cdot \sin(2 \cdot t)) \cdot u(t)$$

Note that the sine carries the opposite sign as the imaginary part of phasor.

c) Find the **transient response** for the same input.

$$\text{Phasor: } V_{in} = 3.091 + 0.828j \cdot V \quad V_{in}(s) = 3.091 \cdot \frac{s}{s^2 + 2^2} - 0.828 \cdot \frac{2}{s^2 + 2^2} = \frac{3.091 \cdot s - 0.828 \cdot 2}{s^2 + 2^2} \quad \text{Note the sign change for the sine.}$$

$$V_{out_tr}(s) = \frac{(3.091 \cdot s - 0.828 \cdot 2) \cdot (2 \cdot s^2 + 5 \cdot s + 20)}{s^2 + 2^2} = \frac{6.182 \cdot s^3 + 12.143 \cdot s^2 + 53.54 \cdot s - 33.12}{(s^2 + 4) \cdot (s^2 + 2 \cdot s + 10)}$$

$$= A \cdot \frac{s+1}{s^2 + 2 \cdot s + 10} + B \cdot \frac{3}{s^2 + 2 \cdot s + 10} + C \cdot \frac{s}{s^2 + 4} + D \cdot \frac{2}{s^2 + 4}$$

Multiply both sides by $(s^2 + 2 \cdot s + 10)$ and let $s := -1 + 3 \cdot j$

$$\frac{6.182 \cdot s^3 + 12.143 \cdot s^2 + 53.54 \cdot s - 33.12}{(s^2 + 4)} = A \cdot ((-1 + 3 \cdot j) + 1) + B \cdot 3$$

$$\frac{6.182 \cdot (-1 + 3 \cdot j)^3 + 12.143 \cdot (-1 + 3 \cdot j)^2 + 53.54 \cdot (-1 + 3 \cdot j) - 33.12}{[(-1 + 3 \cdot j)^2 + 4]} = \frac{-23.072 - 23.514 \cdot j}{-4 - 6 \cdot j} = 4.488 - 0.853j = A \cdot 3 \cdot j + B \cdot 3$$

$$\frac{4.488 - 0.853 \cdot j}{3} = 1.496 - 0.284j \quad A := -0.284 \quad B := 1.496$$

$$v_{out_tr}(t) = (-0.281 \cdot V \cdot e^{-1 \cdot t} \cdot \cos(3 \cdot t) + 1.496 \cdot V \cdot e^{-1 \cdot t} \cdot \sin(3 \cdot t)) \cdot u(t)$$

d) Find the **total response** for the same input.

$$v_{out}(t) = (-0.281 \cdot V \cdot e^{-1 \cdot t} \cdot \cos(3 \cdot t) + 1.496 \cdot V \cdot e^{-1 \cdot t} \cdot \sin(3 \cdot t) + 6.931 \cdot V \cdot \cos(2 \cdot t + 21.12^\circ)) \cdot u(t)$$