

## ECE 3600 3-Phase Examples

A. Stolp  
9/9/09  
rev 9/10/14

**Ex. 1** A Y-connected load is connected to 208-V 3-phase.  
It draws 1.2kW of power at a power factor of 75%, leading.

$$P_{3\phi} := 1.2 \cdot \text{kW} \quad \text{pf} := 0.75$$

a) Find the apparent power and the reactive power.

$$S_{3\phi} := \frac{P_{3\phi}}{\text{pf}} \quad S_{3\phi} = 1.6 \cdot \text{kVA} \quad Q_{3\phi} := -\sqrt{S_{3\phi}^2 - P_{3\phi}^2} \quad Q_{3\phi} = -1.058 \cdot \text{kVAR}$$

Negative because the power factor is leading.

b) Find the line current.

$$I_L = I_\phi = \frac{S_\phi}{V_\phi}$$

$$S_\phi := \frac{S_{3\phi}}{3} \quad V_\phi := \frac{208 \cdot \text{V}}{\sqrt{3}} \quad V_\phi = 120.089 \cdot \text{V} \quad I_L := \frac{S_\phi}{V_\phi} \quad I_L = 4.441 \cdot \text{A}$$

c) Find the values of the load components, assuming they are connected in series.

The components must be a resistor and a capacitor because there is some real power and the power factor is leading.

$$P_\phi := \frac{P_{3\phi}}{3} \quad R_L := \frac{P_\phi}{I_\phi^2} = \frac{P_\phi}{I_L^2} = 20.28 \cdot \Omega$$

$$Q_\phi := \frac{Q_{3\phi}}{3} \quad Z_{CL} := \frac{Q_\phi}{I_L^2} \quad Z_{CL} = -17.885 \cdot \Omega = -\frac{1}{\omega \cdot C}$$

$$\text{assume } \omega = 377 \cdot \frac{\text{rad}}{\text{sec}} \quad C := -\frac{1}{\omega \cdot Z_{CL}} \quad C = 148.3 \cdot \mu\text{F}$$

d) Find the values of the load components, assuming they are connected in parallel.  
Still a resistor and a capacitor.

$$R_L := \frac{V_\phi^2}{P_\phi} \quad R_L = 36.053 \cdot \Omega$$

$$Z_{CL} := \frac{V_\phi^2}{Q_\phi} \quad Z_{CL} = -40.881 \cdot \Omega = -\frac{1}{\omega \cdot C}$$

$$\text{assume } \omega = 377 \cdot \frac{\text{rad}}{\text{sec}} \quad C := -\frac{1}{\omega \cdot Z_{CL}} \quad C = 64.9 \cdot \mu\text{F}$$

e) Correct the power factor with Y-connected components.

Need inductors

$$Q_{\phi\text{Ind}} := -Q_\phi = \frac{V_\phi^2}{\omega \cdot L_Y} \quad L_Y := \frac{V_\phi^2}{\omega \cdot Q_\phi} \quad L_Y = 108.4 \cdot \text{mH}$$

f) Correct the power factor with  $\Delta$ -connected components.

$$\omega \cdot L_\Delta = Z_\Delta = 3 \cdot Z_Y = 3 \cdot \omega \cdot L_Y$$

$$3 \cdot L_Y = 325.3 \cdot \text{mH}$$

# ECE 3600 3-Phase Examples p2


**Ex. 2** From F08, exam 1, Find the following:

a) The line current that would be measured by an ammeter.

$$V_{LL} := 480\text{-V} \quad Z_{\Delta} := (30 + 12j)\cdot\Omega$$

$$I_{AB} := \left| \frac{V_{LL}}{Z_{\Delta}} \right| \quad I_{AB} = 14.856\text{-A}$$
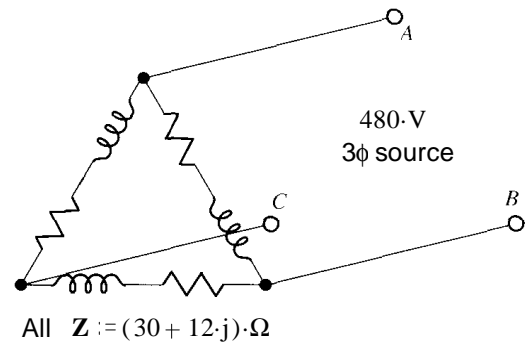
$$I_A := \sqrt{3} \cdot I_{AB} \quad I_A = 25.73\text{-A}$$



b) The power consumed by the three-phase load.

$$\theta := \text{atan}\left(\frac{12}{30}\right) \quad \theta = 21.801\text{-deg} \quad \text{pf} := \cos(\theta) \quad \text{pf} = 0.928$$

$$S_{3\phi} := 3 \cdot V_{LL} \cdot I_{AB} \quad S_{3\phi} = 21.39\text{-kVA}$$

$$P_{3\phi} := S_{3\phi} \cdot \text{pf} = 3 \cdot I_{AB}^2 \cdot 30\cdot\Omega = 19.86\text{-kW}$$

alternate way

c) The value of Y-connected impedances that would result in exactly the same line currents and same pf.

$$Z_Y = \frac{Z_{\Delta}}{3} = 10 + 4j \cdot\Omega$$

d) The value of Y-connected capacitors that would correct the pf.

$$Q_{1\phi} := \frac{1}{3} \cdot \sqrt{S_{3\phi}^2 - P_{3\phi}^2} \quad Q_{1\phi} = 2.648\text{-kVAR}$$

so we need:  $Q_C := -Q_{1\phi}$

$$Q_C = -2.648\text{-kVAR} = -\frac{V_{LN}^2}{\left(\frac{1}{\omega \cdot C}\right)} = -V_{LN}^2 \cdot \omega \cdot C$$

$$C := \frac{Q_C}{-\left(\frac{V_{LL}}{\sqrt{3}}\right)^2 \cdot \omega} \quad C = 91.47\text{-}\mu\text{F}$$

**Ex. 3** For the three-phase delta-connected load in fig P1.7, The line-to-line voltage and line current are:

$$V_{AB} := 480\text{-V} \angle 0^\circ \quad I_A = 10\text{A} \angle -40^\circ$$

a) What is  $V_{CA}$ ?

$$V_{CA} := 480\text{-V} \angle 120^\circ = 480\text{-V} \angle -240^\circ$$

b) What is the phase current in the load? (As always, give the rms value.)

$$\frac{10\text{-A}}{\sqrt{3}} = 5.774\text{-A}$$

c) What is the time-average power into the load?

$$V_{AN} := \frac{480\text{-V}}{\sqrt{3}} \angle -30^\circ \quad \text{Since } I_A = 10\text{A} \angle -40^\circ$$


$I$  lags  $V$  by  $10^\circ$

$$\theta := 10\text{-deg}$$


$$P_{3\phi} = 3 \cdot \left( 480\text{-V} \cdot \frac{10\text{-A}}{\sqrt{3}} \right) \cdot \cos(\theta) = 8.188\text{-kW}$$

d) What is the phase impedance?  $Z_{\Delta} := \frac{(480\text{-V})}{\left(\frac{10\text{-A}}{\sqrt{3}}\right)}$

$$Z_{\Delta} = 83.14\cdot\Omega \angle 10^\circ$$

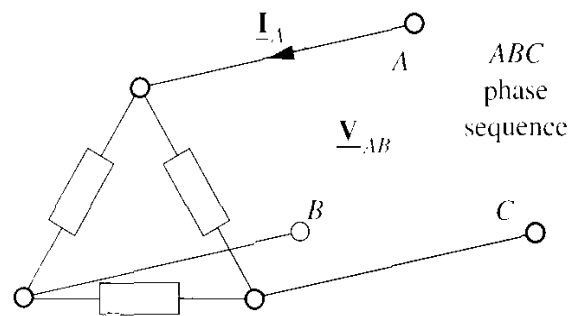

**Figure P1.7**

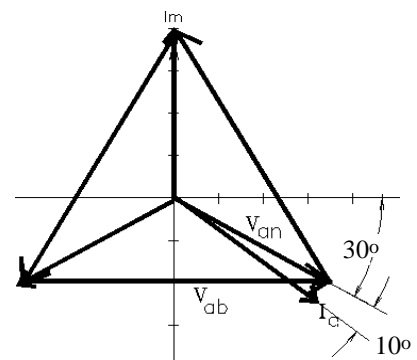

# ECE 3600 3-Phase Examples p3


**Ex. 4** In the three-phase circuit shown in Fig. P1.9. find the following:

a) The line current that would be measured by an ammeter.

$$V_{LL} := 600 \cdot V \quad Z_{\Delta} := (20 + 11j) \cdot \Omega$$

$$I_{AB} := \left| \frac{V_{LL}}{Z_{\Delta}} \right| \quad I_{AB} = 26.286 \cdot A$$

$$I_A := \sqrt{3} \cdot I_{AB} \quad I_A = 45.53 \cdot A$$

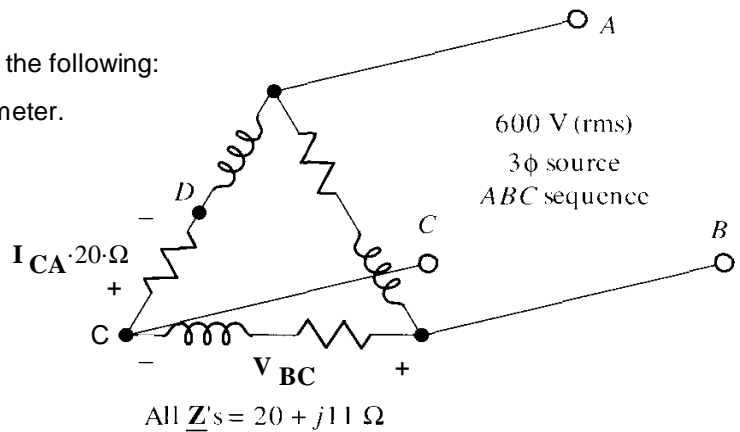

**Figure P1.9**

b) The power factor of the three-phase load.

$$\phi := \text{atan}\left(\frac{11}{20}\right) \quad \phi = 28.811 \cdot \text{deg} \quad \text{pf} = \cos(\phi) = 0.876$$

c) The voltage that would be measured between B and D by a voltmeter.

Using  $V_A$  as reference ( $0^\circ$ ):

$$V_{BC} := 600 \cdot V \cdot e^{-j \cdot 90 \cdot \text{deg}}$$


$$I_{CA} := 26.286 \cdot A \cdot e^{j \cdot (150 - 28.811) \cdot \text{deg}}$$

$$V_{CD} := I_{CA} \cdot 20 \cdot \Omega$$

$$V_{CD} = -272.251 + 449.734j \cdot V$$


$$V_{BD} := V_{BC} + V_{CD} \quad V_{BD} = -272.251 - 150.266j \cdot V \quad |V_{BD}| = 311 \cdot V$$

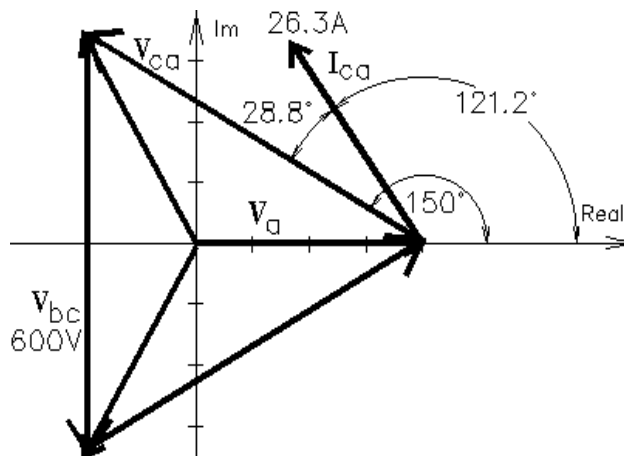(must be the sum, NOT the difference, see the + and - signs on the drawing.)



**Ex. 5** Textbook problem 2-2

Figure P2-1 shows a three-phase power system with two loads. The  $\Delta$ -connected generator is producing a line voltage of 480 V, and the line impedance is  $0.09 + j0.16 \Omega$ . Load 1 is Y-connected, with a phase impedance of  $2.5 \angle 36.87^\circ \Omega$  and load 2 is  $\Delta$ -connected, with a phase impedance of  $5 \angle -20^\circ \Omega$ .

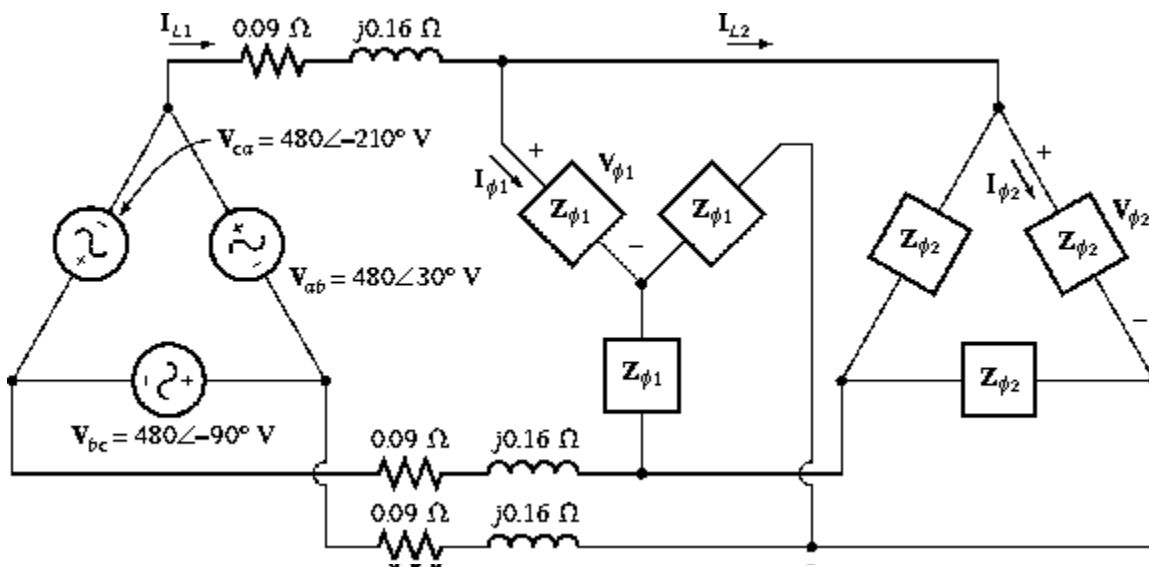


$$Z_{\phi 1} := 2.5 \cdot e^{j \cdot 36.87 \cdot \text{deg}} \cdot \Omega$$

$$Z_{\phi 2} := 5 \cdot e^{-j \cdot 20 \cdot \text{deg}} \cdot \Omega$$

a) What is the line voltage at the two loads?

Find an equivalent Y-only circuit:

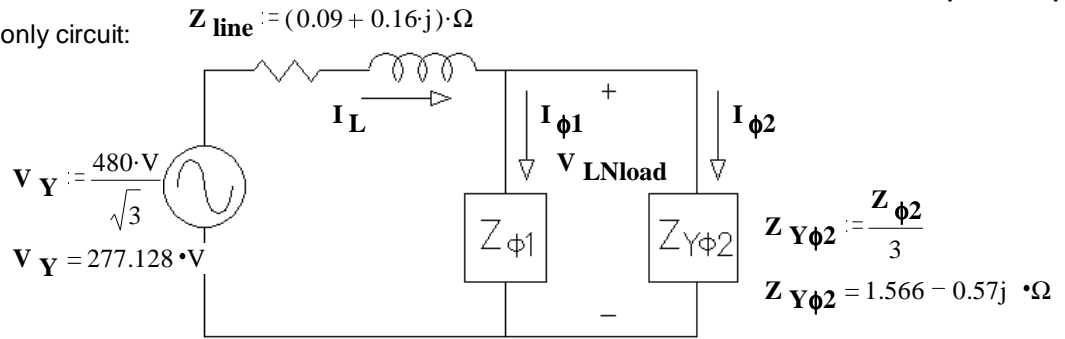

$$Z_{Yloads} := \frac{1}{\frac{1}{Z_{\phi1}} + \frac{1}{Z_{Y\phi2}}}$$

$$Z_{Yloads} = 1.13 + 0.044j \cdot \Omega$$

$$|Z_{Yloads}| = 1.131 \cdot \Omega$$

$$\arg(Z_{Yloads}) = 2.254 \cdot \text{deg}$$

$$Z_{Ytot} := Z_{line} + Z_{Yloads}$$

$$Z_{Ytot} = 1.22 + 0.204j \cdot \Omega$$

$$|Z_{Ytot}| = 1.237 \cdot \Omega$$

$$\arg(Z_{Ytot}) = 9.516 \cdot \text{deg}$$

$$I_L := \frac{V_Y}{Z_{Ytot}}$$

$$I_L = 220.998 - 37.047j \cdot A$$

$$|I_L| = 224.082 \cdot A$$

$$\arg(I_L) = -9.516 \cdot \text{deg}$$

$$V_{line} := I_L \cdot Z_{line}$$

$$V_{line} = 25.817 + 32.025j \cdot V$$

$$|V_{line}| = 41.136 \cdot V$$

$$\arg(V_{line}) = 51.126 \cdot \text{deg}$$

$$V_{LNload} := I_L \cdot Z_{Yloads}$$

$$V_{LNload} = 251.311 - 32.025j \cdot V$$

$$|V_{LNload}| = 253.343 \cdot V$$

$$\arg(V_{LNload}) = -7.262 \cdot \text{deg}$$

$$V_{Lload} := V_{LNload} \cdot \sqrt{3}$$

$$V_{Lload} = 435.283 - 55.47j \cdot V$$

$$|V_{Lload}| = 438.803 \cdot V$$

$$\arg(V_{Lload}) = -7.262 \cdot \text{deg}$$

b) What is the voltage drop on the transmission lines?

$$V_{line} := I_L \cdot Z_{line}$$

$$V_{line} = 25.817 + 32.025j \cdot V$$

$$|V_{line}| = 41.136 \cdot V$$

$$\arg(V_{line}) = 51.126 \cdot \text{deg}$$

c) Find the real and reactive powers supplied to each load.

$$I_{\phi1} := \frac{|V_{LNload}|}{|Z_{\phi1}|}$$

$$I_{\phi1} = 101.337 \cdot A$$

$$I_{\phi2} := \frac{|V_{LNload}|}{|Z_{Y\phi2}|}$$

$$I_{\phi2} = 152.006 \cdot A$$

$$P_{3\phi1} := 3 \cdot I_{\phi1}^2 \cdot \text{Re}(Z_{\phi1})$$

$$P_{3\phi1} = 61.615 \cdot \text{kW}$$

$$P_{3\phi2} := 3 \cdot I_{\phi2}^2 \cdot \text{Re}(Z_{Y\phi2})$$

$$P_{3\phi2} = 108.562 \cdot \text{kW}$$

$$Q_{3\phi1} := 3 \cdot I_{\phi1}^2 \cdot \text{Im}(Z_{\phi1})$$

$$Q_{3\phi1} = 46.212 \cdot \text{kVAR}$$

$$Q_{3\phi2} := 3 \cdot I_{\phi2}^2 \cdot \text{Im}(Z_{Y\phi2})$$

$$Q_{3\phi2} = -39.513 \cdot \text{kVAR}$$

d) Find the real and reactive power losses in the transmission line.

$$P_{3\phi L} := 3 \cdot (|I_L|)^2 \cdot \text{Re}(Z_{line})$$

$$P_{3\phi L} = 13.557 \cdot \text{kW}$$

$$Q_{3\phi L} := 3 \cdot (|I_L|)^2 \cdot \text{Im}(Z_{line})$$

$$Q_{3\phi L} = 24.102 \cdot \text{kVAR}$$

e) Find the real power, reactive power, and power factor supplied by the generator.

$$P_{3\phi gen} := P_{3\phi L} + P_{3\phi1} + P_{3\phi2}$$

$$P_{3\phi gen} = 183.734 \cdot \text{kW}$$

$$Q_{3\phi gen} := Q_{3\phi L} + Q_{3\phi1} + Q_{3\phi2}$$

$$Q_{3\phi gen} = 30.801 \cdot \text{kVAR}$$

$$pf = \frac{P_{3\phi gen}}{3 \cdot |V_Y| \cdot |I_L|} = 0.986$$

lagging

f) What is the efficiency of this system?

$$\eta = \frac{P_{3\phi1} + P_{3\phi2}}{P_{3\phi gen}} = 92.621 \cdot \%$$