

Name: \_\_\_\_\_

ECE 3600 homework # 1 Due: Fri, 8/28/20

a

Base your answers on class lecture & discussion, books and/or internet research. Some possible sources:

<http://www.nerc.com/>

[http://en.wikipedia.org/wiki/Electricity\\_generation](http://en.wikipedia.org/wiki/Electricity_generation)

<http://www.energy.gov/energysources/electricpower.htm>

[http://en.wikipedia.org/wiki/Relative\\_cost\\_of\\_electricity\\_generated\\_by\\_different\\_sources](http://en.wikipedia.org/wiki/Relative_cost_of_electricity_generated_by_different_sources)

1. What is the name of the organization which ensures the reliability of power in North America?

2. Electric Utilities have been forced to break up into two separate companies responsible for:

a.

b.

3. What does deregulation provide for independent power producers (IPPs)?

4. The current bottleneck to overall system capacity.

5. What are the advantages of a highly interconnected system? (List at least 2)

6. Rank the sources of electrical energy in the US (highest to lowest %) 1.

2.

3.

4.

5.

7. List 3 of the "Other" sources. 1.

2.

3.

8. Rank the sources of electrical energy in the US by environmental and social negatives

(worst to best). Assume "Other" is all the 3 you listed above. Consider petroleum just a little worse than natural gas (due to the danger of spills). Also give (in your opinion) the worst environment or social negative of each. Your answers here may be subjective.

1.

2.

3.

4.

9. Rank the sources of electrical energy in the US cost per kWh.

ECE 3600 Hw 1 p2

List Nat gas twice, once for single cycle and once for combined-cycle. Choose one of the "Other" that you listed above. Initial costs are amortized over the life of the generation facility. You will have to make some guesses and may qualify your answers.

1. (cheapest)

2.

3.

4.

5.

6. (most expensive).

10. Give the approximate efficiencies of each type of power plant:

a. Hydroelectric

b. Rankin-cycle steam turbine plants, regardless of the source of heat.  
(coal, oil, gas-steam, nuclear, solar-steam, geothermal)

c. Single-cycle gas turbine

d. Combined-cycle gas turbine

11. In nuclear fission reactions, what is particle is crucial to the chain reaction and is used to control the reaction rate?

12. a) Why can't a wind turbine's coefficient of performance (conversion of wind energy to rotational mechanical energy) be 100%?

b) What two things can be controlled to maximize the coefficient of performance?

c) What is the biggest single problem of wind power?

13. a) Do photovoltaic cells produce AC or DC power?

b) What is the biggest single problem of photovoltaic cells?

14. What is cogeneration?

15. Some power sources are used to supply base loads and some are used to supply peak loads. Give some reasons to differentiate the sources in this way.

Base loads

Peak loads

ECE 3600 Hw 1 p2

# Complex Numbers

ECE 3600

$$j = \sqrt{-1} \quad \text{the imaginary number}$$

**Rectangular Form**  $A = a + b \cdot j$

$$\operatorname{Re}(A) = a \quad \operatorname{Im}(A) = b$$

**Polar Form**  $A = A \cdot e^{j\theta}$

$$\operatorname{Re}(A) = A \cdot \cos(\theta) \quad \operatorname{Im}(A) = A \cdot \sin(\theta)$$

**Conversions**  $A = |A| = \sqrt{a^2 + b^2}$   $\theta = \arg(A) = \tan^{-1}\left(\frac{b}{a}\right)$

$$a = A \cdot \cos(\theta) \quad b = A \cdot \sin(\theta)$$

$$A = A \cdot e^{j\theta} = A \cdot \cos(\theta) + A \cdot \sin(\theta) \cdot j \quad A = a + b \cdot j = \left(\sqrt{a^2 + b^2}\right) \cdot e^{j \cdot \tan^{-1}\left(\frac{b}{a}\right)}$$

**Special Cases**  $j := \sqrt{-1} = e^{j \cdot 90^\circ}$   $\frac{1}{j} = -j = e^{-j \cdot 90^\circ}$   $e^{j \cdot 0^\circ} = 1$   $e^{-j \cdot 180^\circ} = e^{-j \cdot 180^\circ} = -1$   
 $j \cdot e^{j\theta} = e^{j \cdot (\theta + 90^\circ)}$

Define a 2<sup>nd</sup> number: rect:  $D = c + d \cdot j$  polar:  $D = D \cdot e^{j\phi}$

**Equality**  $A = D$  if and only if  $a = c$  and  $b = d$  OR  $A = D$  and  $\theta = \phi$

**Addition and Subtraction**  $A + D = (a + b \cdot j) + (c + d \cdot j) = (a + c) + (b + d) \cdot j$

$$A - D = (a + b \cdot j) - (c + d \cdot j) = (a - c) + (b - d) \cdot j$$

Convert polars to rectangular form first

**Multiplication and Division**  $A \cdot D = (a + b \cdot j) \cdot (c + d \cdot j) = (a \cdot c - b \cdot d) + (b \cdot c + a \cdot d) \cdot j$

$$\text{Rectangular: } \frac{A}{D} = \frac{a + b \cdot j}{c + d \cdot j} = \frac{a + b \cdot j \cdot c - d \cdot j}{c + d \cdot j \cdot c - d \cdot j} = \frac{a \cdot c + b \cdot d}{c^2 + d^2} + \frac{b \cdot c - a \cdot d}{c^2 + d^2} \cdot j$$

$$\text{Polar: } A \cdot D = A \cdot e^{j\theta} \cdot D \cdot e^{j\phi} = A \cdot D \cdot e^{j(\theta + \phi)}$$

$$\frac{A}{D} = \frac{A \cdot e^{j\theta}}{D \cdot e^{j\phi}} = \frac{A}{D} \cdot e^{j(\theta - \phi)}$$

**Powers**  $A^n = A^n \cdot e^{j \cdot n \cdot \theta} = A^n \cdot \cos(n \cdot \theta) + A^n \cdot \sin(n \cdot \theta) \cdot j$  Convert rectangulairs first, usually

**Conjugates** complex number

$$A = a + b \cdot j$$

$$A = A \cdot e^{j\theta}$$

$$F = \frac{3 + 5 \cdot j}{(2 - 6 \cdot j) \cdot e^{j \cdot 40^\circ}}$$

Conjugate

$$\bar{A} = a - b \cdot j$$

$$\bar{A} = A \cdot e^{-j\theta}$$

$$\bar{F} = \frac{3 - 5 \cdot j}{(2 + 6 \cdot j) \cdot e^{-j \cdot 40^\circ}}$$

$$\bar{\bar{A}} = A$$

**Euler's equation**

$$e^{j\alpha} = \cos(\alpha) + j \cdot \sin(\alpha)$$

$$\text{OR: } \cos(\alpha) = \frac{e^{j\alpha} + e^{-j\alpha}}{2}$$

$$\sin(\alpha) = \frac{e^{j\alpha} - e^{-j\alpha}}{2j}$$

$$e^{j(\omega t + \theta)} = \cos(\omega t + \theta) + j \cdot \sin(\omega t + \theta)$$



$$\operatorname{Re}[e^{j(\omega t + \theta)}] = \cos(\omega t + \theta)$$

If we freeze this at time  $t=0$ , then we can represent  $\cos(\omega t + \theta)$  by  $e^{j\theta}$

**Calculus** Remember, when we write  $e^{j\theta}$ , we really mean  $e^{j(\omega t + \theta)}$

$$\frac{d}{dt} A = \frac{d}{dt} (A \cdot e^{j\theta}) = j \cdot \omega \cdot A \cdot e^{j\theta} = \omega \cdot A \cdot e^{j(\theta + 90^\circ)}$$
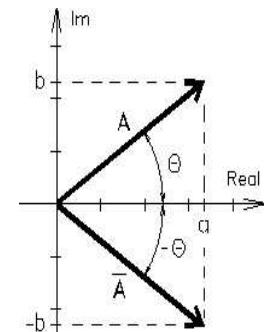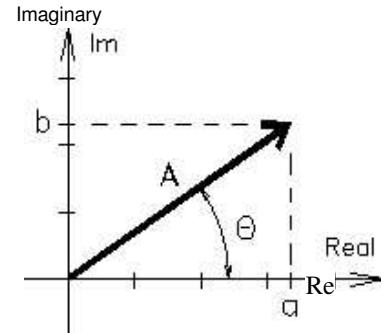
$$\int A dt = \int A \cdot e^{j\theta} dt = \frac{1}{j \cdot \omega} \cdot A \cdot e^{j\theta} = \frac{1}{\omega} \cdot A \cdot e^{j(\theta - 90^\circ)}$$





# Review of Phasors

ECE 3600

A.Stolp  
9/3/08  
rev,

For steady-state sinusoidal response ONLY


## Phasors

### Time domain

$$v(t) = \sqrt{2} \cdot V_1 \cdot \cos(377t + \theta)$$
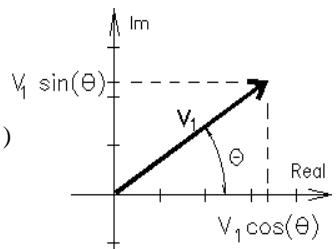
### Phasor, frequency domain (RMS)

$$V_1 = V_1 e^{j\theta} = V_1 / \underline{\theta} = V_1 \cos(\theta) + j \cdot V_1 \sin(\theta)$$



## Impedances,

Inductor

$$\text{---\textcircled{M}} \quad v_L = L \frac{d}{dt} i_L = L \frac{d}{dt} I_p e^{j(\omega t + \theta)} = j \cdot \omega \cdot L [I_p e^{j(\omega t + \theta)}]$$

$$V_L(\omega) = j \cdot \omega \cdot L I(\omega)$$

### AC impedance

$$Z_L = j \cdot \omega \cdot L$$

Capacitor

$$\text{---||---} \quad i_C = C \frac{d}{dt} v_C = C \frac{d}{dt} V_p e^{j(\omega t + \theta)} = j \cdot \omega \cdot C [V_p e^{j(\omega t + \theta)}]$$

$$I_C(\omega) = j \cdot \omega \cdot C V(\omega) \quad V_C(\omega) = \frac{1}{j \cdot \omega \cdot C} \cdot I(\omega)$$

$$Z_C = \frac{1}{j \cdot \omega \cdot C} = \frac{-j}{\omega \cdot C}$$

Resistor


$$\text{~\textwedge\textbackslash\textwedge\textbackslash\textwedge} \quad v_R = i_R \cdot R$$

$$V_R(\omega) = R \cdot I(\omega)$$

$$Z_R = R$$


You can use impedances just like resistances as long as you deal with the complex arithmetic.  
ALL the DC circuit analysis techniques will work with AC.

## series:

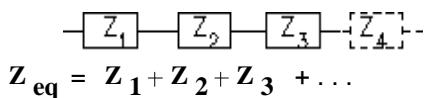

$$f := 60 \cdot \text{Hz} \quad \omega := 2 \cdot \pi \cdot f \quad \omega = 377 \cdot \frac{\text{rad}}{\text{sec}}$$

Example:

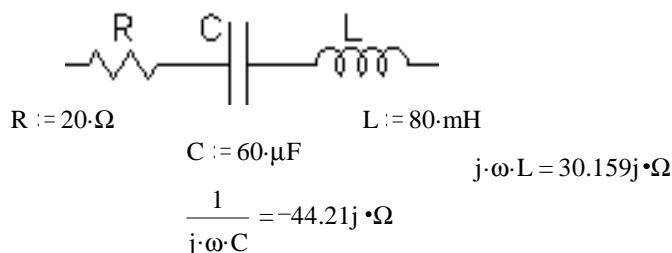

$$Z_{eq} := R + \frac{1}{j \cdot \omega \cdot C} + j \cdot \omega \cdot L = 20 \cdot \Omega - 44.21 \cdot j \cdot \Omega + 30.16 \cdot j \cdot \Omega = 20 - 14.05j \cdot \Omega$$

$$\sqrt{(20 \cdot \Omega)^2 + (14.05 \cdot \Omega)^2} = 24.44 \cdot \Omega \quad \text{atan}\left(\frac{-14.05 \cdot \Omega}{20 \cdot \Omega}\right) = -35.09 \cdot \text{deg}$$

$$Z_{eq} = 24.44 \Omega / -35.1^\circ$$

$$\text{If: } V := 120 \cdot V \cdot e^{j \cdot 0 \cdot \text{deg}} \quad I := \frac{V}{Z_{eq}} = \frac{120 \cdot V}{24.44 \cdot \Omega} = 4.91 \cdot A \quad \underline{\quad} \quad 0 - - 35.1 = 35.1 \quad \text{deg}$$

$$4.91 \cdot \cos(35.1 \cdot \text{deg}) = 4.017 \quad 4.91 \cdot \sin(35.1 \cdot \text{deg}) = 2.823 \quad \mathbf{I} = 4.017 + 2.822j \cdot A$$

slight roundoff error

**Voltage divider:**


$$V_{Zn} = V_{\text{total}} \cdot \frac{Z_n}{Z_1 + Z_2 + Z_3 + \dots}$$

Eg:  $V_C := V \cdot \frac{1}{Z_{\text{eq}}} = 120 \cdot V \cdot e^{j \cdot 0 \cdot \text{deg}} \cdot \frac{44.21 \cdot e^{-j \cdot 90 \cdot \text{deg}} \cdot \Omega}{24.44 \cdot e^{-j \cdot 35.1 \cdot \text{deg}} \cdot \Omega}$

$$120 \cdot V \cdot \frac{44.21 \cdot \Omega}{24.44 \cdot \Omega} = 217.07 \cdot V \quad \angle 0^\circ - 90^\circ - 35.1^\circ = -54.9^\circ \text{ deg}$$

$$V_C = 217.1 \text{ V } / -54.9^\circ \quad V_C = 124.771 - 177.604j \text{ V}$$


$$217.1 \cdot \cos(-54.9^\circ) = 124.8 \quad 217.1 \cdot \sin(-54.9^\circ) = -177.6$$

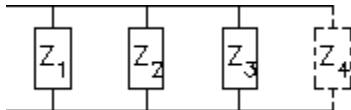**parallel:**


$$Z_{\text{eq}} = \frac{1}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} + \dots}$$

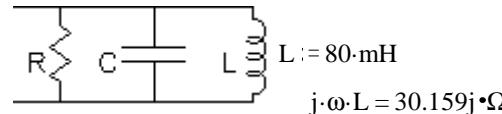**Example:**

$$f := 60 \cdot \text{Hz} \quad \omega := 2 \cdot \pi \cdot f \quad \omega = 377 \cdot \frac{\text{rad}}{\text{sec}}$$



$$j \cdot \omega \cdot L = 30.159j \cdot \Omega$$

$$R := 20 \cdot \Omega \quad C := 60 \cdot \mu\text{F} \quad \frac{1}{\omega \cdot L} = 3.316 \cdot 10^{-2} \cdot \frac{1}{\Omega}$$

$$\frac{1}{j \cdot \omega \cdot C} = -44.21j \cdot \Omega \quad \omega \cdot C = 2.262 \cdot 10^{-2} \cdot \frac{1}{\Omega}$$

$$Z_{\text{eq}} := \frac{1}{\frac{1}{R} + \frac{1}{\left(\frac{1}{j \cdot \omega \cdot C}\right)} + \frac{1}{j \cdot \omega \cdot L}} = \frac{1}{\frac{1}{R} + j \cdot \omega \cdot C - \frac{j}{\omega \cdot L}} = \frac{1}{20 \cdot \Omega + 2.262 \cdot 10^{-2} \cdot j \cdot \frac{1}{\Omega} - 3.316 \cdot 10^{-2} \cdot j \cdot \frac{1}{\Omega}}$$

$$= \frac{1}{\left(5 \cdot 10^{-2} - 1.054 \cdot 10^{-2} \cdot j\right) \cdot \frac{1}{\Omega} \cdot \left(5 \cdot 10^{-2} + 1.054 \cdot 10^{-2} \cdot j\right)} = 19.149 + 4.037j \cdot \Omega$$

$$\sqrt{\left(5 \cdot 10^{-2} \cdot \frac{1}{\Omega}\right)^2 + \left(1.054 \cdot 10^{-2} \cdot \frac{1}{\Omega}\right)^2} = 5.11 \cdot 10^{-2} \cdot \frac{1}{\Omega} \quad \text{atan}\left(\frac{1.054 \cdot 10^{-2} \cdot \Omega}{5 \cdot 10^{-2} \cdot \Omega}\right) = 11.9^\circ \text{ deg}$$

$$\frac{1}{5.11 \cdot 10^{-2} \cdot \frac{1}{\Omega}} = 19.569 \cdot \Omega$$

$$Z_{\text{eq}} = 19.57 \Omega / 11.9^\circ$$

If:  $V := 120 \cdot V \cdot e^{j \cdot 0 \cdot \text{deg}}$        $I := \frac{V}{Z_{\text{eq}}} = \frac{120 \cdot V}{19.57 \cdot \Omega} = 6.132 \cdot A \quad \angle 0^\circ - 11.9^\circ = -11.9^\circ \text{ deg}$

$$6.132 \cdot \cos(-11.9^\circ) = 6 \quad 6.132 \cdot \sin(-11.9^\circ) = -1.264 \quad I = 6 - 1.265j \cdot A$$

slight roundoff error

**Current divider:**

$$I_{Zn} = I_{\text{total}} \cdot \frac{1}{Z_n} = I_{\text{total}} \cdot \frac{1}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} + \dots}$$

Eg:  $I_L := I \cdot \frac{\frac{1}{j \cdot \omega \cdot L}}{\frac{1}{R} + j \cdot \omega \cdot C + \frac{1}{j \cdot \omega \cdot L}} = I \cdot \frac{Z_{\text{eq}}}{j \cdot \omega \cdot L}$

$$= 6.132 \cdot A \cdot e^{j \cdot 11.9 \cdot \text{deg}} \cdot \frac{19.57 \cdot e^{-j \cdot 11.9 \cdot \text{deg}} \cdot \Omega}{30.159 \cdot e^{-j \cdot 90 \cdot \text{deg}} \cdot \Omega}$$


$$I_L = 6.132 \cdot A \cdot \frac{19.57 \cdot \Omega}{30.159 \cdot \Omega} = 3.979 \cdot A \quad \angle 11.9^\circ + 11.9^\circ - 90^\circ = -90^\circ \text{ deg} \quad I_L = -3.979 \cdot 10^3 j \cdot \text{mA}$$

Duh...  $\frac{V}{j \cdot \omega \cdot L} = -3.979 \cdot 10^3 j \cdot \text{mA}$
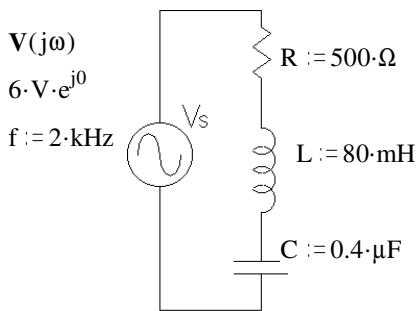
# ECE 3600 Phasor Examples

A.Stolp  
9/3/08  
rev

Ex 1. Find  $\mathbf{V}_R$ ,  $\mathbf{V}_L$ , and  $\mathbf{V}_C$  in polar phasor form.  $f := 2\text{ kHz}$




$$\omega := 2\pi f \quad \omega = 1.257 \cdot 10^4 \frac{\text{rad}}{\text{sec}}$$

$$Z_L := j\omega L \quad Z_L = 1.005j \text{ k}\Omega$$

$$Z_C := \frac{1}{j\omega C} \quad Z_C = -0.199j \text{ k}\Omega$$

$$Z_{\text{eq}} := R + j\omega L + \frac{1}{j\omega C} \quad Z_{\text{eq}} = 500 + 806.366j \text{ } \Omega$$
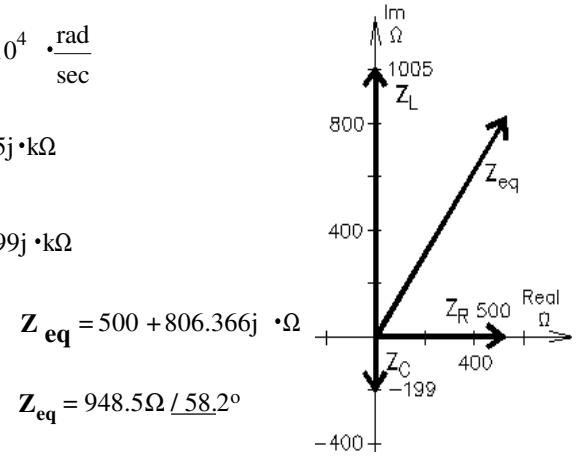
$$\sqrt{500^2 + 806^2} = 948.491 \quad \text{atan}\left(\frac{806}{500}\right) = 58.187^\circ$$



$$\text{find the current: } I := \frac{6 \cdot V \cdot e^{j0}}{Z_{\text{eq}}}$$

$$\text{magnitude: } \frac{6 \cdot V}{948.5 \cdot \Omega} = 6.326 \text{ mA}$$

$$\text{angle: } 0^\circ - 58.2^\circ = -58.2^\circ$$

$$I = 6.326 \text{ mA } / -58.2^\circ$$

find the magnitude

$$\mathbf{V}_R := I \cdot R \quad 6.326 \text{ mA} \cdot 500 \cdot \Omega = 3.163 \text{ V}$$

$$-58.2^\circ \text{ deg} + 0^\circ \text{ deg} = -58.2^\circ$$

$$\mathbf{V}_R = 3.163 \text{ V } / -58.2^\circ$$

$$\mathbf{V}_L := I \cdot Z_L \quad 6.326 \text{ mA} \cdot 1005 \cdot \Omega = 6.358 \text{ V}$$

$$-58.2^\circ \text{ deg} + 90^\circ \text{ deg} = 31.8^\circ$$

$$\mathbf{V}_L = 6.358 \text{ V } / 31.8^\circ$$

$$\mathbf{V}_C := I \cdot Z_C \quad 6.326 \text{ mA} \cdot (-199) \cdot \Omega = -1.259 \text{ V}$$

$$-58.2^\circ \text{ deg} + (90^\circ) \text{ deg} = 31.8^\circ$$

$$\mathbf{V}_C = -1.259 \text{ V } / 31.8^\circ$$

$$\text{OR: } 6.326 \text{ mA} \cdot (199) \cdot \Omega = 1.259 \text{ V} \quad -58.2^\circ \text{ deg} + (-90^\circ) \text{ deg} = -148.2^\circ$$

$$\mathbf{V}_C = 1.259 \text{ V } / -148.2^\circ$$

OR, you can also find these voltages directly, using a voltage divider. I.E. to find  $\mathbf{V}_C$  directly:

$$\mathbf{V}_C := \frac{\frac{1}{j\omega C}}{R + j\omega L + \frac{1}{j\omega C}} \cdot 6 \text{ V} = \frac{1}{R(j\omega C) + j\omega L(j\omega C) + 1} \cdot 6 \text{ V} = \frac{1}{R(j\omega C) - \omega^2 L C + 1} \cdot 6 \text{ V}$$

$$= \frac{1}{(1 - \omega^2 L C) + j\omega R C} \cdot 6 \text{ V} \quad (1 - \omega^2 L C) = -4.053 \quad j\omega R C = 2.513j$$

$$= \frac{6 \cdot V}{-4.053 + 2.513j} \cdot \frac{(-4.053 - 2.513j)}{(-4.053 - 2.513j)} = \frac{6 \cdot V \cdot (-4.053 - 2.513j)}{(-4.053)^2 + 2.513^2}$$

$$6 \cdot V \cdot (-4.053 - 2.513j) = -24.318 - 15.078j \text{ V}$$

$$(-4.053)^2 + 2.513^2 = 22.742$$

$$= \left( \frac{-24.318}{22.742} - \frac{15.078j}{22.742} \right) \cdot V = -1.069 - 0.663j \text{ V}$$


$$\text{magnitude: } \sqrt{1.069^2 + 0.663^2} = 1.258$$

$$\text{angle: } \text{atan}\left(\frac{-0.663}{-1.069}\right) = 31.81^\circ$$

but this is actually in the third quadrant,  
so modify your calculator's results:

$$31.81^\circ \text{ deg} - 180^\circ \text{ deg} = -148.19^\circ$$

$$= 1.258 \text{ V } / -148.2^\circ$$

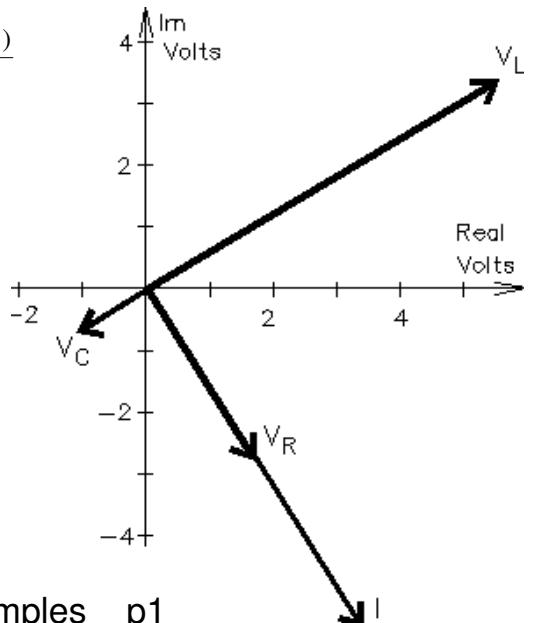

## ECE 3600 Phasor Examples p2

Ex 2. a) Find  $Z_{eq}$ .  $f := 2.5 \cdot kHz$   $\omega := 2 \cdot \pi \cdot f$   $\omega = 1.571 \cdot 10^4 \frac{rad}{sec}$

Left branch

$$Z_L := \frac{1}{j \cdot \omega \cdot C}$$

$$Z_L = -63.662j \Omega$$

Right branch

$$Z_R := j \cdot \omega \cdot L_2 + R$$

$$Z_R = 200 + 125.664j \Omega$$

$$\begin{aligned} Z_{eq} &:= j \cdot \omega \cdot L_1 + \frac{1}{\frac{1}{R + j \cdot \omega \cdot L_2} + \frac{1}{\frac{1}{j \cdot \omega \cdot C}}} = j \cdot \omega \cdot L_1 + \frac{1}{\frac{1}{R + j \cdot \omega \cdot L_2} + j \cdot \omega \cdot C} \\ &= j \cdot \omega \cdot L_1 + \frac{R + j \cdot \omega \cdot L_2}{1 + j \cdot \omega \cdot C \cdot (R + j \cdot \omega \cdot L_2)} \\ &= j \cdot \omega \cdot L_1 + \frac{R + j \cdot \omega \cdot L_2}{1 - \omega^2 \cdot C \cdot L_2 + j \cdot \omega \cdot C \cdot R} \end{aligned}$$

Sometimes it's worth simplifying a little before putting in numbers.

$$\begin{aligned} Z_{eq} &= 31.416 \cdot j \Omega + \frac{(200 + 125.664 \cdot j) \cdot \Omega}{-0.974 + 3.142 \cdot j} \cdot \frac{(-0.974 - 3.142 \cdot j)}{-0.974 - 3.142 \cdot j} = 31.416 \cdot j \Omega + \frac{(200 + 125.664 \cdot j) \cdot (-0.974 - 3.142 \cdot j)}{0.974^2 + 3.142^2} \\ &= 31.416 \cdot j \Omega + \frac{((200 \cdot (-0.974) - 125.664 \cdot (-3.142)) + (125.664 \cdot (-0.974) - 200 \cdot 3.142) \cdot j) \cdot \Omega}{0.974^2 + 3.142^2} \\ &= 31.416 \cdot j \Omega + \frac{(200.036288 - 750.796736 \cdot j) \cdot \Omega}{10.82084} = 31.416 \cdot j \Omega + 18.486 \cdot \Omega - 69.384 \cdot j \Omega = 18.486 - 37.968j \Omega \end{aligned}$$

$$\sqrt{18.49^2 + 37.97^2} = 42.233 \quad \text{atan}\left(\frac{-37.97}{18.49}\right) = -64.036 \cdot \text{deg} \quad Z_{eq} = 42.24 \Omega / -64.04^\circ$$

b)  $V_{in} := 12 \cdot V \cdot e^{j20\text{deg}}$  Find  $I_{L1}$ ,  $V_C$   $I_{L1} := \frac{V_{in}}{Z_{eq}}$   $\frac{12 \cdot V}{42.24 \cdot \Omega} = 284.091 \cdot \text{mA}$   $20\text{deg} - (-64.04)\cdot \text{deg} = 84.04\text{deg}$

$$I_{L1} = 284 \cdot \text{mA} / 84.04^\circ = 284 \cdot \text{mA} \cdot e^{j84.04\text{deg}} \quad I_{L1} = 29.485 + 282.569j \cdot \text{mA}$$

$$V_C := I_{L1} \cdot (18.486 - 69.384 \cdot j) \cdot \Omega = 284 \cdot \text{mA} \cdot \sqrt{18.486^2 + 69.384^2} \cdot \Omega = 20.392 \cdot V$$

$$84.04\text{deg} + \text{atan}\left(\frac{-69.384}{18.486}\right) = 8.959 \cdot \text{deg} \quad V_C = 20.4V / 8.96^\circ$$

To find  $V_C$  directly:  $\frac{1}{\frac{1}{R + j \cdot \omega \cdot L_2} + j \cdot \omega \cdot C}$

You could then use another voltage divider to find  $V_R$  or  $V_{L2}$ .

$$\begin{aligned} V_C &:= \frac{\frac{1}{j \cdot \omega \cdot L_1 + \frac{1}{\frac{1}{R + j \cdot \omega \cdot L_2} + j \cdot \omega \cdot C}} \cdot V_{in}}{\frac{1}{R + j \cdot \omega \cdot L_2}} = \frac{1}{j \cdot \omega \cdot L_1 \cdot \left( \frac{1}{R + j \cdot \omega \cdot L_2} + j \cdot \omega \cdot C \right) + 1} \cdot V_{in} = \frac{1}{\frac{j \cdot \omega \cdot L_1}{R + j \cdot \omega \cdot L_2} - \frac{\omega^2 \cdot L_1 \cdot C + 1}{R + j \cdot \omega \cdot L_2}} \cdot V_{in} \\ &= \frac{1}{\frac{j \cdot \omega \cdot L_1}{R + j \cdot \omega \cdot L_2} - \frac{\omega^2 \cdot L_1 \cdot C + 1}{R + j \cdot \omega \cdot L_2}} \cdot V_{in} = \frac{1}{\frac{j \cdot \omega \cdot L_1 \cdot (R - j \cdot \omega \cdot L_2)}{R^2 + (\omega \cdot L_2)^2} - \frac{\omega^2 \cdot L_1 \cdot C + 1}{R^2 + (\omega \cdot L_2)^2}} \cdot V_{in} \\ &= \frac{1}{\left[ \frac{\omega^2 \cdot L_1 \cdot L_2}{R^2 + (\omega \cdot L_2)^2} - \frac{\omega^2 \cdot L_1 \cdot C + 1}{R^2 + (\omega \cdot L_2)^2} \right] + j \cdot \frac{\omega \cdot L_1 \cdot R}{R^2 + (\omega \cdot L_2)^2}} \cdot V_{in} = \frac{12 \cdot V \cdot e^{j20\text{deg}}}{0.58816 \cdot e^{j11.039\text{deg}}} = \frac{12 \cdot V}{0.58816} / 20 - 11.039^\circ \\ &= 20.4V / 8.96^\circ \quad \text{Same} \end{aligned}$$

## ECE 3600 Phasor Examples p3

Ex 2. Continued Find  $I_{L2}$ .

$$Z_r := R + j\omega L_2 \\ Z_r = 200 + 125.664j \cdot \Omega \quad \sqrt{200^2 + 125.664^2} = 236.202 \quad \text{atan}\left(\frac{125.664}{200}\right) = 32.142^\circ$$

$$I_{L2} = \frac{20.4 \cdot V \cdot e^{j8.96\text{-deg}}}{236.202 \cdot \Omega \cdot e^{j32.142\text{-deg}}} = \frac{20.4 \cdot V}{236.202 \cdot \Omega} / 8.96 - 32.142^\circ = 86.4 \text{mA } /-23.18$$

Or, directly by  
Current divider:

$$I_{L2} := \frac{\frac{1}{R + j\omega L_2}}{\frac{1}{j\omega C + \frac{1}{R + j\omega L_2}}} \cdot I_{L1} = \frac{1}{j\omega C \cdot (R + j\omega L_2) + 1} \cdot I_{L1} = \frac{I_{L1}}{1 - \omega^2 C \cdot L_2 + j\omega C \cdot R}$$

denominator:  $\sqrt{(1 - \omega^2 C \cdot L_2)^2 + (\omega C \cdot R)^2} = 3.289 \quad \text{atan}\left(\frac{\omega C \cdot R}{1 - \omega^2 C \cdot L_2}\right) + 180^\circ = 107.224^\circ$

$$I_{L2} = \frac{284 \cdot \text{mA} \cdot e^{j84.04\text{-deg}}}{3.289 \cdot e^{j107.224\text{-deg}}} = \frac{284 \cdot \text{mA}}{3.289} / 84.04 - 107.224^\circ = 86.4 \text{mA } /-23.18$$

$$I_{L2} = 79.404 - 34.001j \cdot \text{mA}$$

How about  $I_C$ ?  $I_C := \frac{V_C}{\left(\frac{1}{j\omega C}\right)} = V_C \cdot j\omega C = 20.4 \text{V } / 8.96^\circ \cdot 0.015708 / 90^\circ \cdot \frac{1}{\Omega} = 320 \text{mA } / 98.96^\circ$

Or, directly by  
Current divider:

$$I_C := \frac{j\omega C}{j\omega C + \frac{1}{R + j\omega L_2}} \cdot I_{L1} = \frac{j\omega C \cdot (R + j\omega L_2)}{j\omega C \cdot (R + j\omega L_2) + 1} \cdot I_{L1} = \frac{-\omega^2 C \cdot L_2 + j\omega C \cdot R}{1 - \omega^2 C \cdot L_2 + j\omega C \cdot R} \cdot I_{L1}$$

numerator:  $\sqrt{(\omega^2 C \cdot L_2)^2 + (\omega C \cdot R)^2} = 3.71 \quad \text{atan}\left(\frac{\omega C \cdot R}{-\omega^2 C \cdot L_2}\right) + 180^\circ = 122.142^\circ$   
Second quadrant

denominator is the same as above.

$$I_C = \frac{3.71 \cdot e^{j122.14\text{-deg}}}{3.289 \cdot e^{j107.224\text{-deg}}} \cdot 284 \cdot \text{mA} \cdot e^{j84.04\text{-deg}} = \frac{3.71}{3.289} \cdot 284 \cdot \text{mA} / 122.14 - 107.224 + 84.04^\circ = 320 \text{mA } / 98.96^\circ$$

This current is greater than the input current. What's going on?

The angle between  $I_C$  &  $I_{L2}$  is big enough that they somewhat cancel each other out.

Check Kirchoff's Current Law:  $I_C + I_{L2} = 29.485 + 282.569j \cdot \text{mA} = I_{L1} = 29.485 + 282.569j \cdot \text{mA}$


Ex 3. a) Find  $Z_2$ .

$$I := 25 \cdot \text{mA} \cdot e^{j10\text{-deg}}$$

$$V_{in} := 10 \cdot \text{V} \cdot e^{-j20\text{-deg}}$$

$$Z_T := \frac{V_{in}}{I} = \frac{10 \cdot \text{V}}{25 \cdot \text{mA}} / -20 - 10^\circ = 400 \Omega / -30^\circ$$

$$Z_T = 346.41 - 200j \cdot \Omega$$

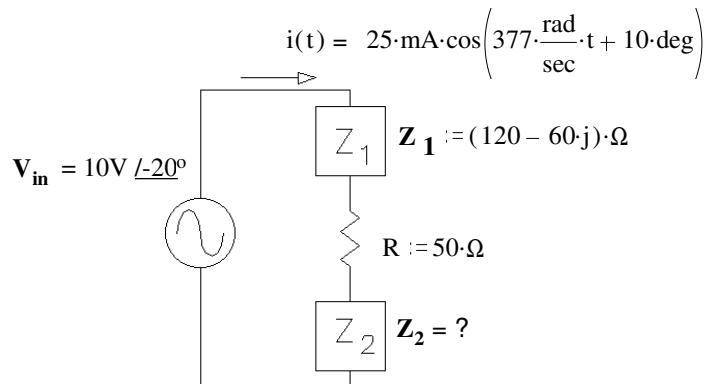

$$Z_2 := Z_T - R - Z_1 = (346.41 - 200j) \cdot \Omega - 50 \cdot \Omega - (120 - 60j) \cdot \Omega = 176.41 - 140j \cdot \Omega$$

- b) Circle 1:  
i) The source current leads the source voltage  
ii) The source voltage leads the source current

<--- answer, because  $10^\circ > -20^\circ$ .

## ECE 3600 Phasor Examples p4

Ex 4. a) Find  $V_{in}$  in polar form.


$$I_Z := 100 \text{ mA} \quad Z := (80 - 60j) \Omega$$

$$V_{in} := I_Z \cdot Z \quad V_{in} = 8 - 6j \text{ V}$$

$$\sqrt{8^2 + 6^2} = 10 \quad \text{atan}\left(\frac{-6}{8}\right) = -36.87 \text{ deg}$$

$$V_{in} = 10V \angle -36.9^\circ$$
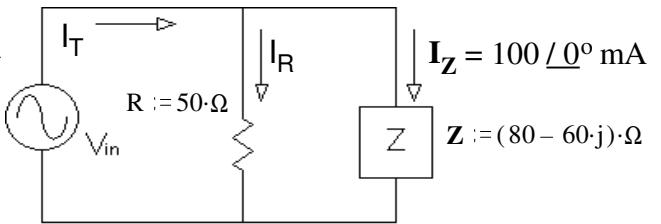
$$\omega := 1000 \frac{\text{rad}}{\text{sec}} \quad R := 50 \Omega$$



b) Find  $I_T$  in polar form.  $I_R := \frac{V_{in}}{R} = \frac{10 \text{ V}}{50 \Omega} \angle -36.9^\circ = \frac{10 \text{ V}}{50 \Omega} \cdot \cos(-36.9^\circ) + j \cdot \frac{10 \text{ V}}{50 \Omega} \cdot \sin(-36.9^\circ) = 160 - 120j \text{ mA}$

$$I_T := I_R + I_Z = (160 - 120j) \text{ mA} + 100 \text{ mA} = 260 - 120j \text{ mA}$$

$$\sqrt{260^2 + 120^2} = 286.356 \quad \text{atan}\left(\frac{-120}{260}\right) = -24.78 \text{ deg} \quad I_T = 286 \text{ mA } \angle -24.8^\circ$$


- c) Circle 1: i) The source current leads the source voltage ii) The source voltage leads the source current  
answer i),  $-24.8^\circ > -36.9^\circ$

Ex 5. a) The impedance  $Z$  (above) is made of two components in series. What are they and what are their values?

$$Z = 80 - 60j \Omega$$

Must have a resistor because there is a real part.

$$R := \text{Re}(Z)$$

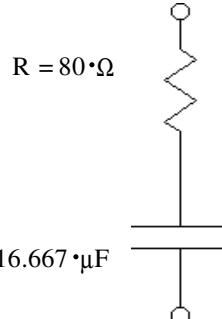

Must have a capacitor because the imaginary part is negative.

$$\text{Im}(Z) = -60 \Omega = \frac{-1}{\omega C} \quad C := \frac{-1}{\omega \cdot \text{Im}(Z)}$$

$$C = 16.667 \mu\text{F}$$

- b) The impedance  $Z$  is made of two components in parallel. What are they and what are their values?

$$Z = 80 - 60j \Omega$$

Must have a resistor because there is a real part.

Must have a capacitor because the imaginary part is negative.

$$Z = \frac{1}{\frac{1}{R} + j \cdot \omega C} \quad \frac{1}{Z} = \frac{1}{(80 - 60j) \Omega} \cdot \frac{(80 + 60j)}{(80 + 60j)} = \frac{80 + 60j}{80^2 + 60^2} = \frac{80 + 60j}{10,000} \Omega$$


$$\frac{1}{Z} = 8 \cdot 10^{-3} + 6 \cdot 10^{-3}j \cdot \Omega^{-1} = \frac{1}{R} + j \cdot \omega C$$

$$\frac{1}{R} = .008 \cdot \frac{1}{\Omega}$$

$$R = 125 \Omega$$

$$\omega C = .006 \cdot \frac{1}{\Omega}$$


$$C = 6 \mu\text{F}$$

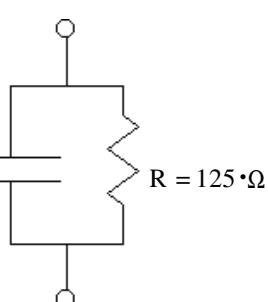


1. Express the impedance of a 5.2mH inductor at 60 Hz in polar form.
2. A capacitor impedance has a magnitude of  $240\Omega$  at a frequency of 1.8kHz. What is the value of capacitor?

3. Find  $Z_{eq}$  in each case.


a)

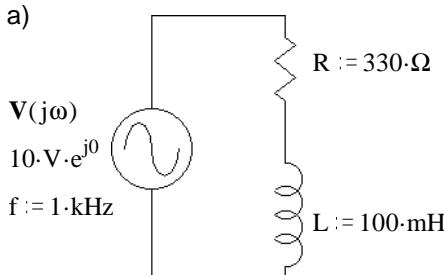

b)

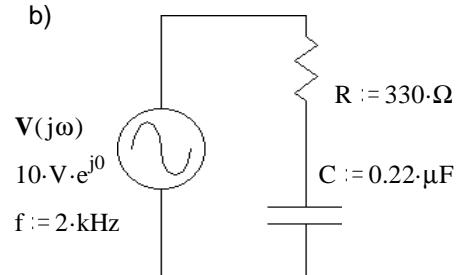

c)

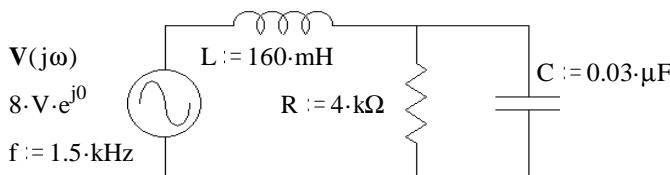


4. Find the current  $I(j\omega)$  in each case above.

5. a) Find  $Z$ . Hint: Find the total impedance ( $R+Z$ ) first.


- b) Which leads, current or voltage?

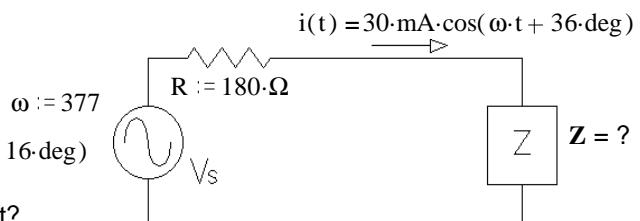- c) By how much?

I.E. what is the phase angle between the voltage and current?




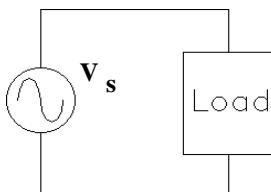6. The phasor diagram at right shows the voltage and current in the circuit below



Assume the load consists of a resistor in series with a reactive component and the frequency is 60 Hz.

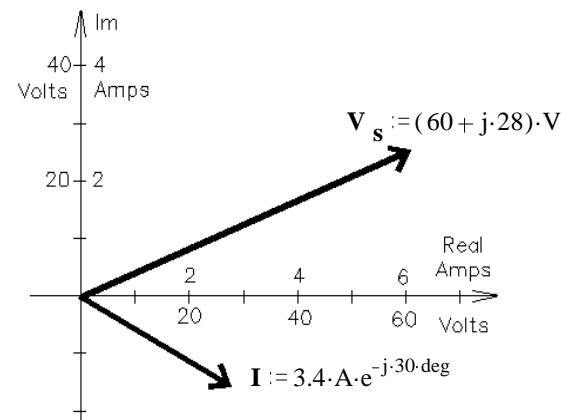- a) What is the magnitude of the impedance?
- b) What is the value of the resistor?
- c) What is the reactive component (type and value)?




7. a) Find the AC current source,  $I_{in}$  in polar form.

- b) Find  $V_T$ .

- c) Choose one:

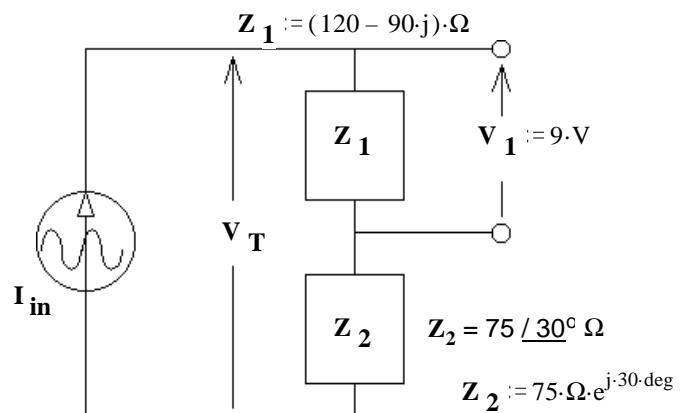
- i) The source current leads the source voltage.  
ii) The source current lags the source voltage.



# ECE 3600 homework # 2 p.2

8. a) Find  $Z_1$ .

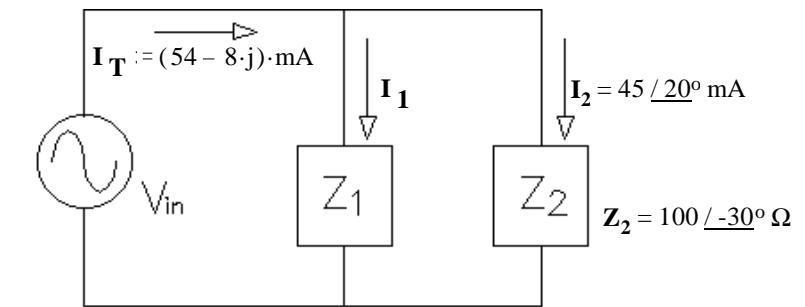
- b) To make  $Z_1$  in the simplest way, what part(s) would you need? Just determine the needed part(s) from the list below and state why you made that choice, don't find the values.



resistor	capacitor	inductor	power supply	current source
Thevenin resistor	Ideal transformer	voltmeter	ammeter	scope

- c) Choose one: i)  $I_2$  leads the source voltage ( $V_{in}$ ) ii)  $I_2$  lags the source voltage ( $V_{in}$ )  
d) Choose one: i)  $I_1$  leads  $I_2$  ii)  $I_1$  lags  $I_2$

9. Find  $Z$ .

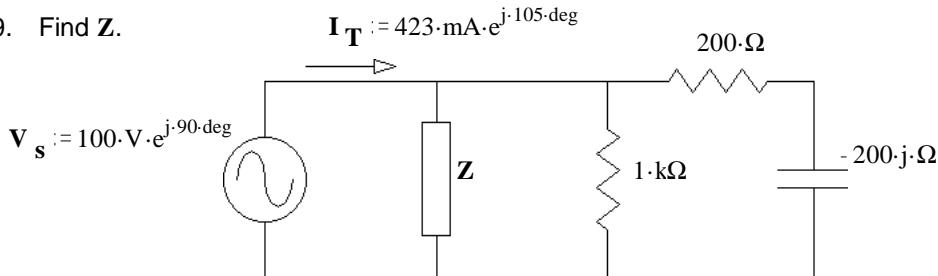

## Answers

1.  $1.96 \Omega / 90^\circ$
2.  $0.368 \cdot \mu F$
3. a)  $(330 + 628.3 \cdot j) \cdot \Omega = 709.7 \Omega / 62.29^\circ$       b)  $(330 - 361.7 \cdot j) \cdot \Omega = 489.6 \Omega / -47.63^\circ$       c)  $1.82 k\Omega / -15.2^\circ$
4. a)  $(6.6 - 12.5 \cdot j) \cdot \text{mA} = 14.1 \text{mA} / -62.29^\circ$       b)  $(13.8 + 15.1 \cdot j) \cdot \text{mA} = 20.4 \text{mA} / 47.63^\circ$       c)  $4.4 \text{mA} / 15.2^\circ$
5. a)  $259 - 160 \cdot j$       b) The current leads the voltage      c)  $20^\circ$
6. a)  $19.5 \cdot \Omega$       b)  $11.2 \cdot \Omega$       c) inductor  $42.3 \cdot \text{mH}$
7. a)  $60 / 36.87^\circ \text{ mA}$       b)  $11.54 / 21^\circ \text{ V}$       c) i)
8. a)  $172 / 53.4^\circ \Omega$       b) phase angle  $> 0$ , resistor and inductor      c) i)      d) ii)
9.  $657 \Omega / 67.4^\circ$