
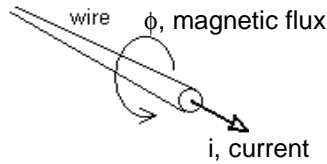


Electromagnetics basics

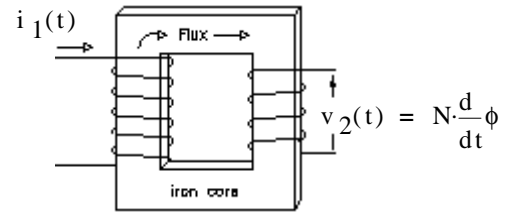1. Electric currents produce magnetic fields.




Right-hand-rule



2. A fluctuating magnetic field passing through a coil of wire will induce a voltage in that coil. Basis of transformer secondary, and primary too (back EMF).

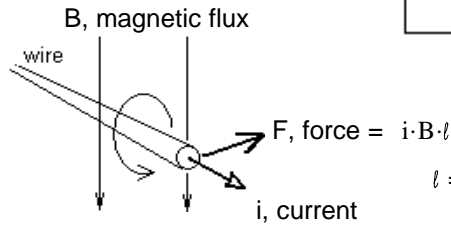
3. A wire with a current in the presence of another magnetic field feels a force.

(Basis of electric motors, also explains why generators resist the mechanical input)




$l = \text{length of the wire}$

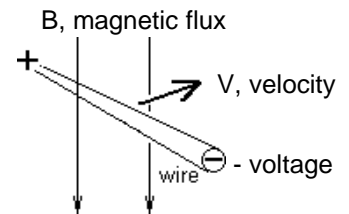4. A voltage will be induced on wires moving in the presence of a magnetic field. This is very similar to 2. (Basis of electric generators)



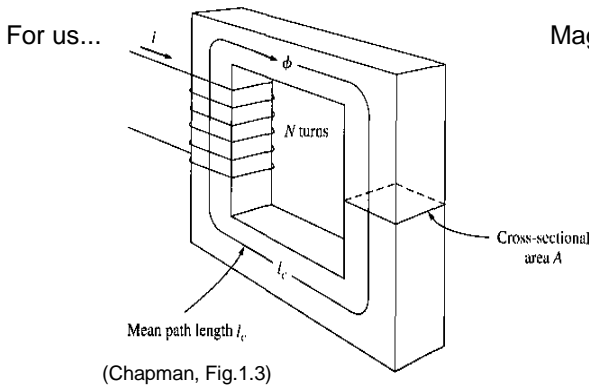1. Magnetic field from a current

Ampere's law: $\oint \mathbf{H} \cdot d\mathbf{l} = I_{\text{net}}$



(Chapman, Fig.1.3)

Magnetic field intensity: $H = \frac{N \cdot i}{l_c} \left(\frac{\text{A} \cdot \text{turns}}{\text{meter}} \right)$

Ampere-turns: $= N \cdot i$ (like voltage)

Flux density: $B = \mu \cdot H = \frac{\mu \cdot N \cdot i}{l_c}$ (tesla, T)

Flux: $\phi = B \cdot A$ (weber) (Wb) (like current)

Permeability of free space: $\mu_0 := 4 \cdot \pi \cdot 10^{-7} \cdot \frac{\text{henry}}{\text{m}}$

Relative permeability: μ_r

Permeability: $\mu = \mu_r \cdot \mu_0$


Reluctance of core: $\mathcal{R}_c = \frac{l_c}{\mu \cdot A_c} \left(\frac{\text{A} \cdot \text{turns}}{\text{Wb}} \right)$ (like resistance)

Flux: $\phi = \frac{N \cdot i}{\mathcal{R}_c}$ (weber, Wb)


Inductance: $L = \frac{N^2}{\mathcal{R}_c} = N^2 \cdot \left(\frac{\mu_r \cdot \mu_0 \cdot A_c}{l_c} \right)$ (henry, H)

material	relative permeability μ_r
Mu-metal	20000
Permalloy	8000
Electrical steel	4000
ferrite (nickel zinc)	16 - 640
ferrite (manganese zinc)	> 640
Steel	700
Nickel	100



Magnetic "Circuits"

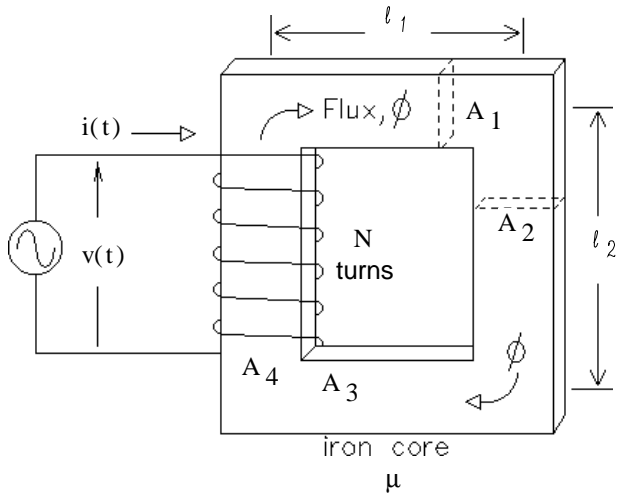

Similar to this electric circuit

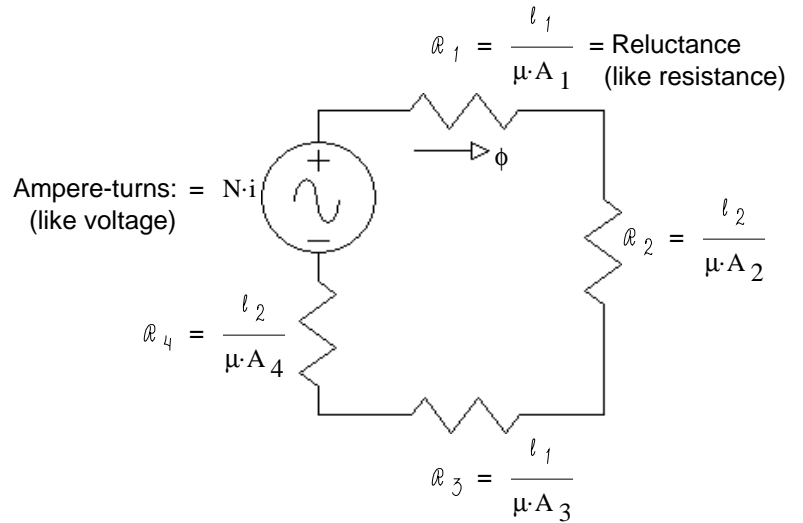

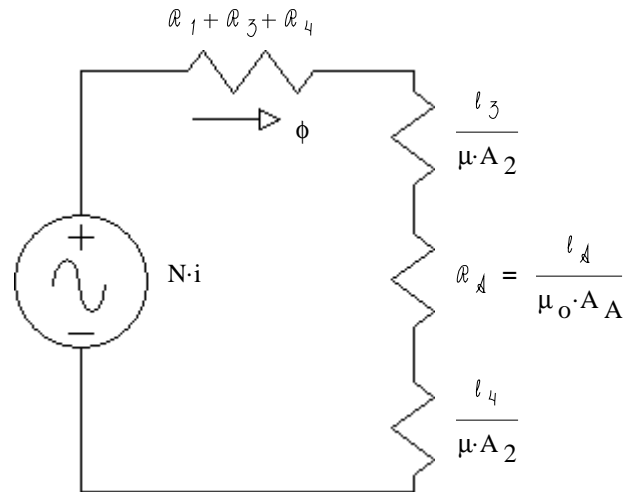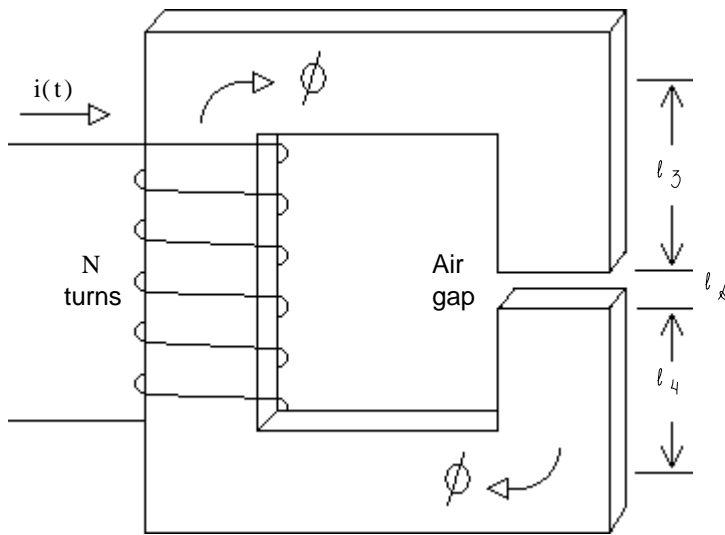magnetic flux = $\phi = \frac{N \cdot i}{r_1 + r_2 + r_3 + r_4}$ (weber) (like current) (Wb)



$\phi = \frac{N \cdot i}{r_1 + r_3 + r_4 + \frac{l_3 + l_4}{\mu \cdot A_2} + r_A}$ (weber) (Wb)

Flux density: $B = \frac{\phi}{A} = \mu \cdot H$ (tesla, T)

Magnetic field intensity: $H = \frac{B}{\mu} = \frac{\phi}{A \cdot \mu}$ (A·turns / meter)

$v(t) = N \cdot \frac{d}{dt} \phi = N \cdot \frac{d}{dt} B \cdot A$

$= -N \cdot \frac{d}{dt} \phi = -N \cdot \frac{d}{dt} B \cdot A$ often shown with a negative sign



- indicates that this voltage tries to produce a current to oppose the change.

Non-ideal Ferrromagnetic materials (B-H curve)

Magnetics are not really linear

The B-H or Hystereses curve
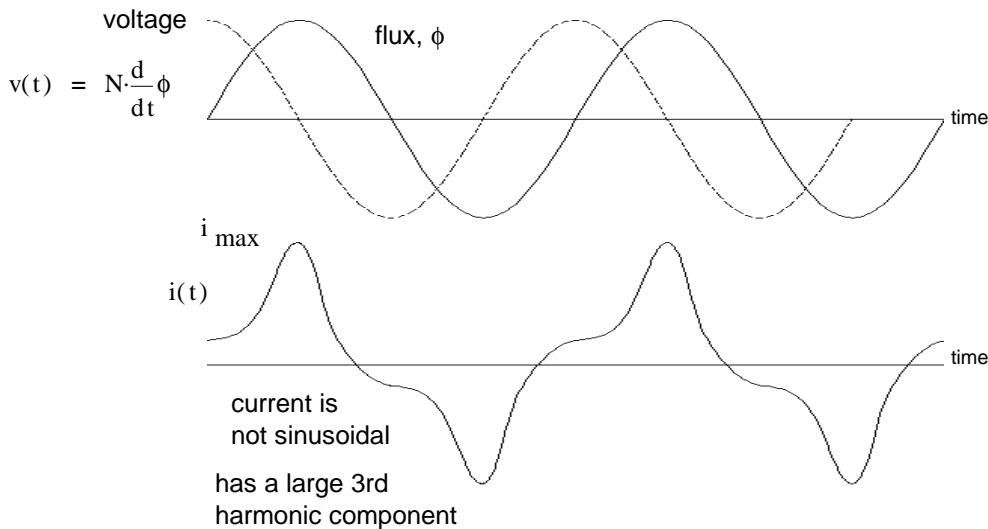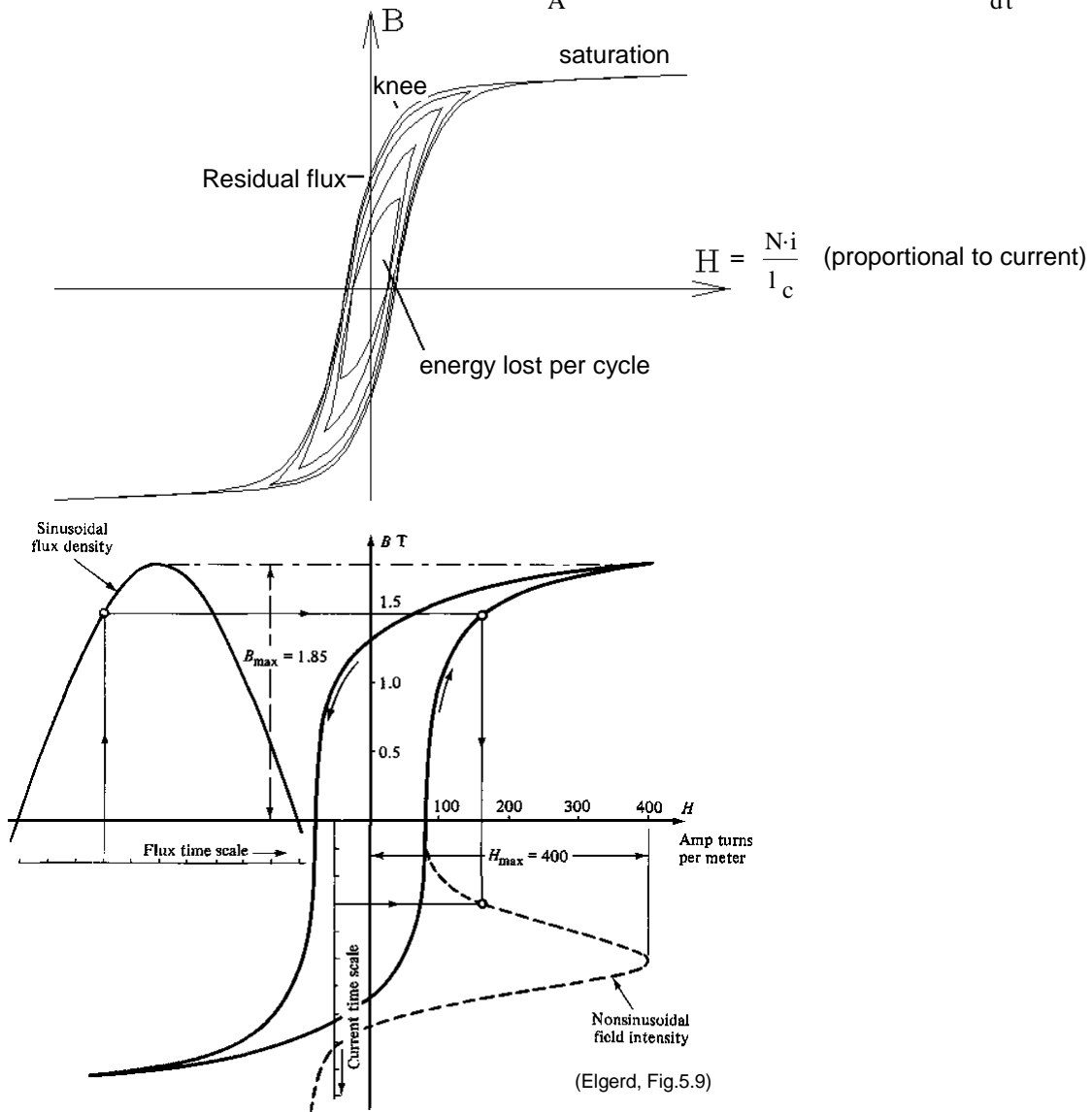
$$B = \mu \cdot H = \frac{\phi}{A} \quad (\text{proportional to voltage}) \quad v(t) = N \cdot \frac{d}{dt} \phi = -N \cdot \frac{d}{dt} B \cdot A$$



Sources: [Electric Machinery and Power System Fundamentals](#), Stephen J. Chapman
[Basic Electric Power Engineering](#), Ollie I. Elgerd

Transformer basics and ratings

A Transformer is two coils of wire that are magnetically coupled.

Transformers are only useful for AC, which is one of the big reasons electrical power is generated and distributed as AC.

Transformer turns and turns ratios are rarely given, V_p/V_s is much more common where V_p/V_s is the rated primary voltage over rated secondary voltage. Ideally, you may take this to be the same as N_1/N_2 although in reality N_2 is usually a little bit bigger to make up for losses. Another common way to show the same thing: $V_p : V_s$.


Transformers are rated in VA Transformer Rating (VA) = (rated V) x (rated I) , on either side.

Don't allow voltages over the rated V, regardless of the actual current.


Don't allow steady-state currents over the rated I, regardless of the actual voltage.

Short-term inrush and startup currents may be higher as long as there's no overheating.

Ideal Transformers

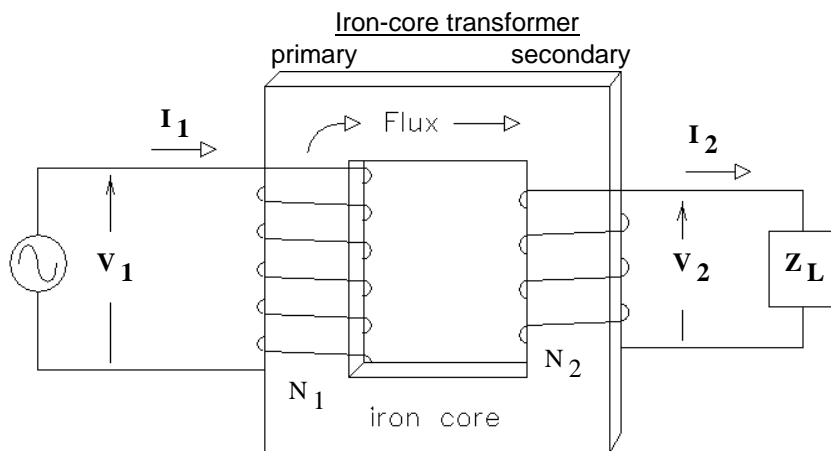

Ideal: $P_1 = P_2$
power in = power out

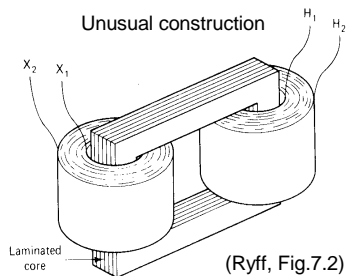

Transformation of voltage and current

$$\frac{N_1}{N_2} = \frac{V_1}{V_2} = \frac{I_2}{I_1}$$


Turns ratio

Turns ratio as defined in Chapman text: $a = \frac{N_1}{N_2}$, same as $N = \frac{N_1}{N_2}$

Note: some other texts define the turns ratio as: $\frac{N_2}{N_1}$

Be careful how you and others use this term

Transformation of impedance

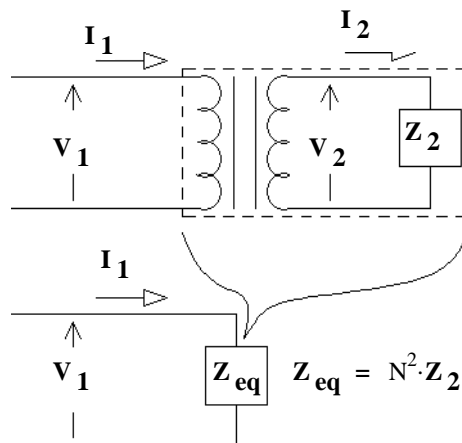


You can replace the entire transformer and load with (Z_{eq}). This "impedance transformation" can be very handy.

Transformers can be used for "impedance matching"

This also works the opposite way, to move an impedance from the primary to the secondary, multiply by:



$$\left(\frac{N_2}{N_1}\right)^2$$

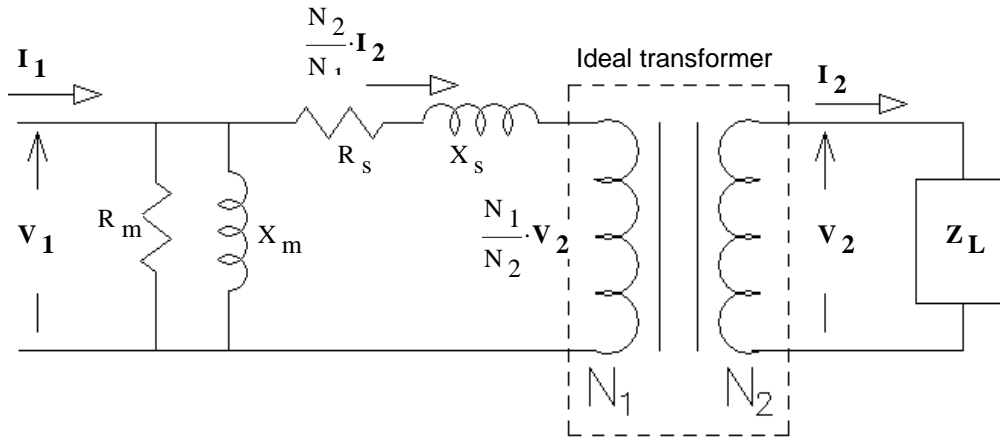

R_m - Core losses

Eddy-current losses - minimized by laminating the core and adding silicon to raise the resistivity

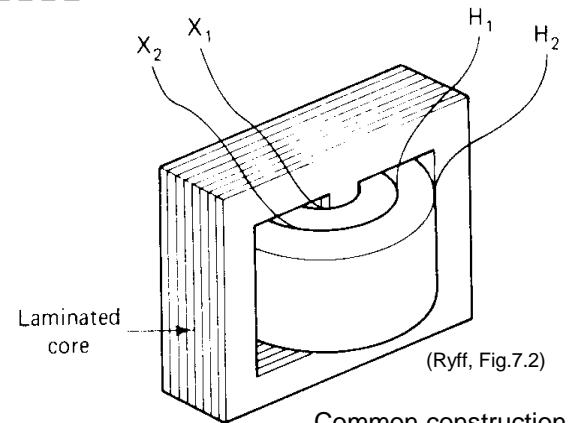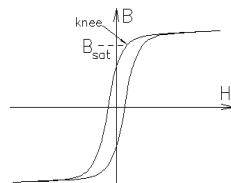Hysteresis losses - caused by the B-H hysteresis curve



Common construction

X_m - basic inductance caused by the need to magnetize the core

R_s - Winding resistance (copper) losses


X_s - Reactance caused by flux leakage (leakage reactance)

Actually, a more accurate model would have R_m and X_m to the right of R_s and X_s because the magnetization current still has to pass through the windings, but this model is simpler to work with and accurate enough.



Move the load impedance to further simplify the math.

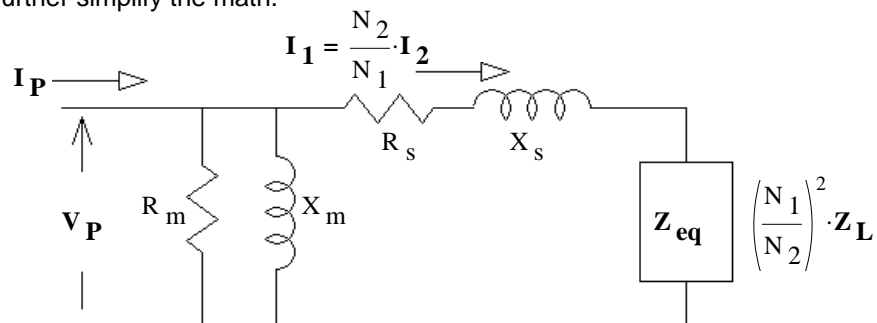Note:
 I_P can be slightly larger than the rated current to makeup for losses.



Typical calculations


$$\text{Voltage regulation } \%VR = \frac{V_{no_load} - V_{full_load}}{V_{full_load}} \cdot 100\%$$

Note: A low %VR is good and a high %VR is bad, counter-intuitive.


$$\text{Efficiency } \eta = \frac{P_{out}}{P_{in}} \cdot 100\%$$

Tests to find parameters

Open-Circuit test

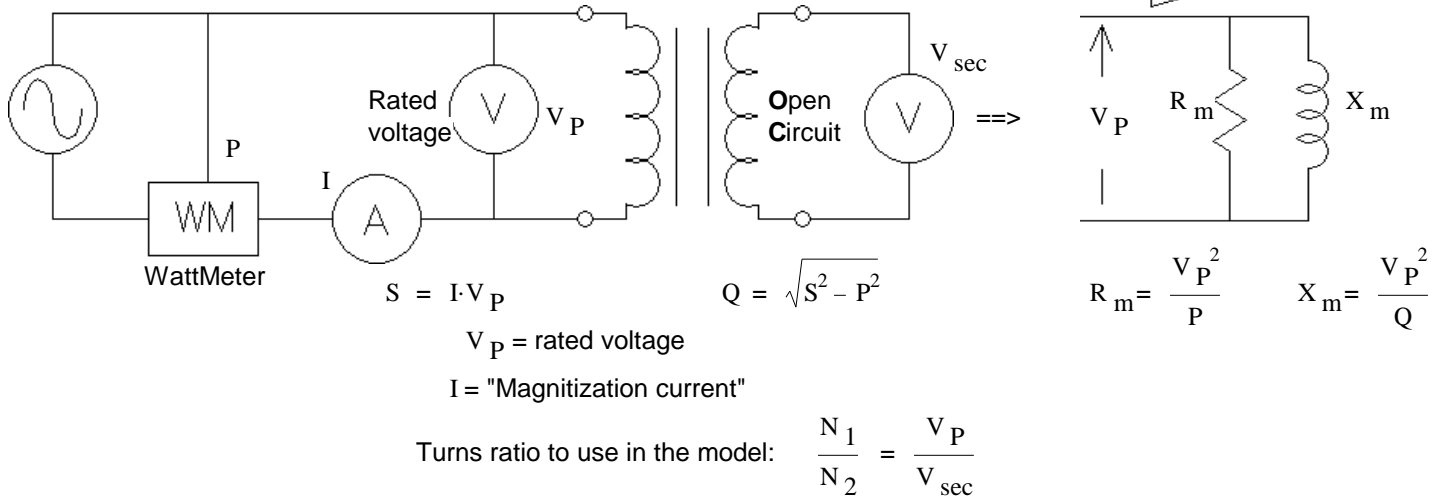

Short-Circuit test

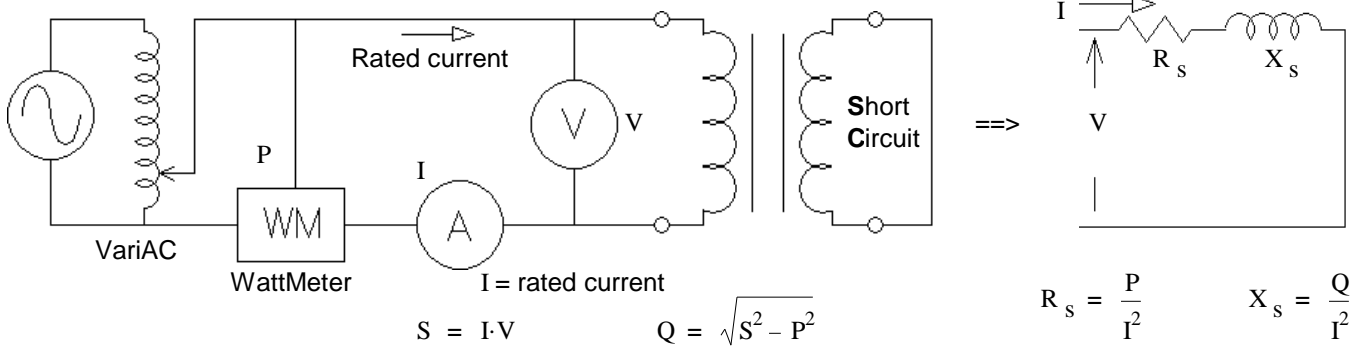

Determining $\frac{N_1}{N_2}$ if you're working from transformer ratings and parameters.

Manufacturers of transformers are well aware of R_s and X_s and how they reduce the output voltage, so they add a few windings (1 - 5%) to the secondary in order to make up for the loss. This lowers the effective turns ratio of the ideal transformer in the model by the same 1 - 5%.

If you're given transformer ratings as V_{Prated}/V_{Srated} , S_{rated} along with R_s and X_s , what turn ratio (N) would the manufacturer actually use for the transformer?

The following calculations are based on: $V_P = V_{Prated}$ $V_S = V_{Srated}$ $P_{out} = S_{rated}$ and $pf = 1$


Then: $R_L = \frac{V_{Srated}^2}{S_{rated}}$ define: $R_x = \frac{V_{Prated}^2}{S_{rated}} - 2 \cdot R_s$ for ease of calculation below

$$R_L, \text{ referred to primary side} = R_{eq} = \frac{R_x + \sqrt{R_x^2 - 4 \cdot (R_s^2 + X_s^2)}}{2} \quad \text{and,} \quad N = \sqrt{\frac{R_{eq}}{R_L}}$$

Finding R_{eq} required lots of messy algebra, which I'm skipping here.

Just use the calculations above as formulas if you're not given a value for N along with the other parameters.

The model becomes:

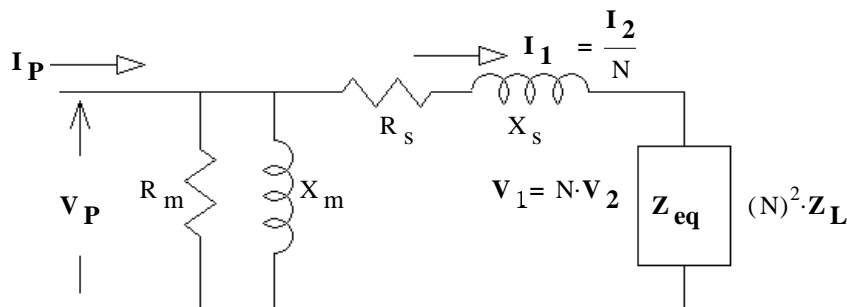


Special Sensing Transformers




(IET Wiley)

CT

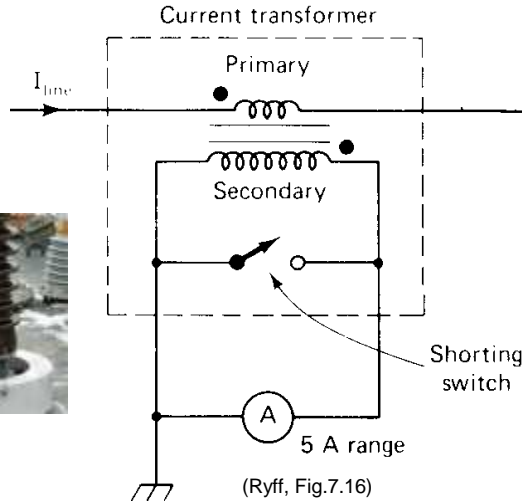

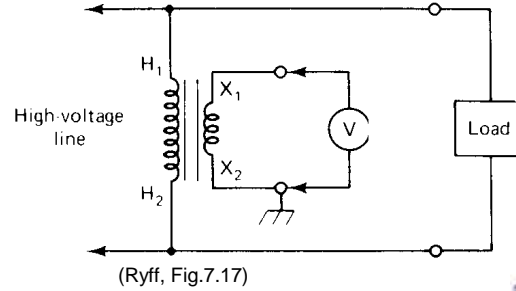The secondary **must** always be shorted or nearly shorted!



"Potential" transformer, for voltage monitoring

VT or PT



base grounded (powerlinedelhi)


Many newer PTs are actually voltage dividers, not transformers.

Other Transformers

Multi-tap transformers



Many transformers have more than two connections to primary and/or the secondary. The extra connections are called "taps" and may allow you to select from several different voltages or get more than one voltage at the same time.

A center tap is very common.

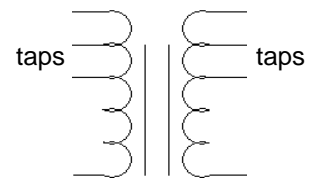


(Wikipedia)

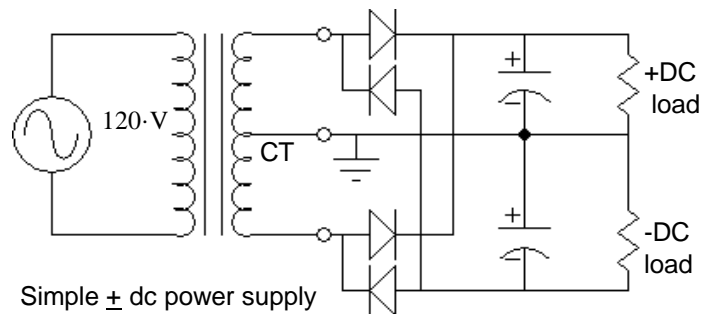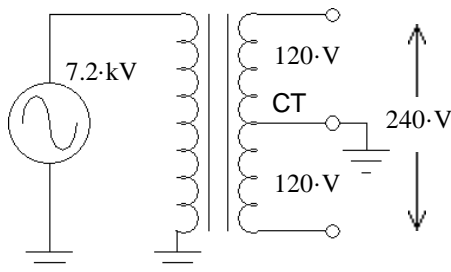Typical transformer for residential distribution



Simple ± dc power supply

Autotransformers

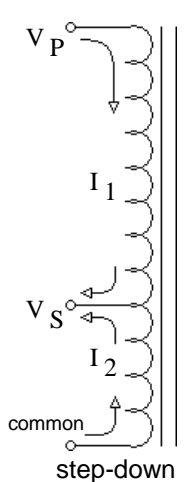

Single-winding transformers where the primary and secondary share windings. For step-down, the secondary is some fraction of the primary. For step-up, the primary is some fraction of the secondary.

Because of the way the currents flow within the windings, the current of the low-voltage side is greater than any current within the windings. Less current means that autotransformers can be economical.


A variAC is an adjustable autotransformer.

Normal transformers can also be wired as autotransformers. More info to come.

Load tap changing

Multiple taps near the top of the transformer can be used to boost or buck (reduce) the voltage a bit. Transformers like this are often used in substations for voltage regulation. Typically, they can adjust the voltage ± 10% in 33 steps (0.625% per step). Those that can change taps while under load are called "Load tap changing". They can either be regular transformers or autotransformers, the latter are usually just called "voltage regulators". Most can be set up to work automatically.

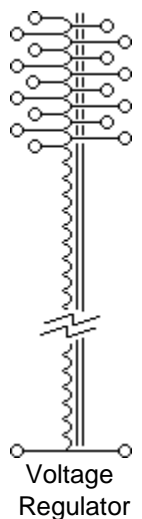The tap changing circuitry is not shown at right. It can be rather tricky in that it can not short two taps together nor can it open the circuit during switching.





Voltage Regulator

Isolation Transformers


All transformers (except autotransformers) isolate the primary from the secondary. An Isolation transformer has a 1:1 turns ratio and is just for isolation.

VariAC-type Autotransformer

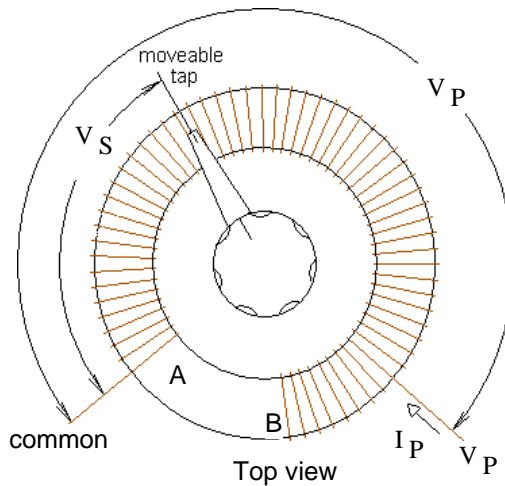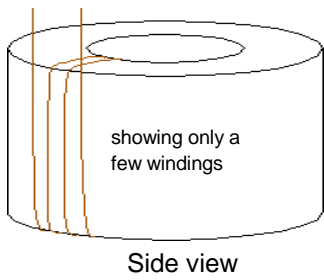
This adjustable autotransformer is wound on a toroidal core.



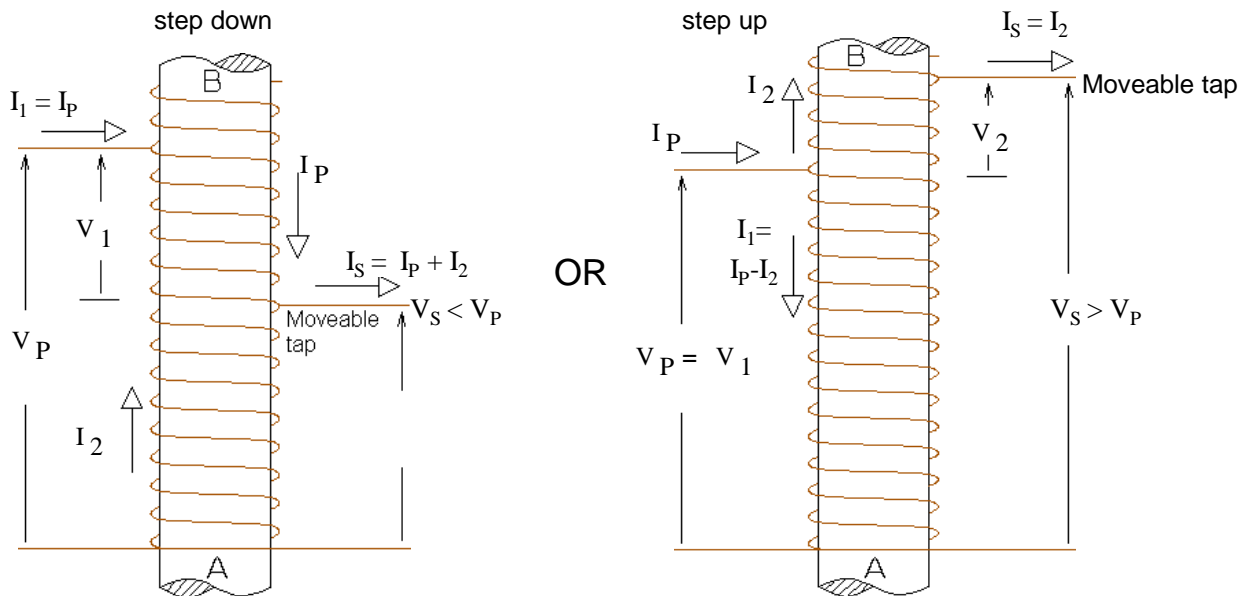
If you cut the toroid open and straightened it out, you would get the views below.



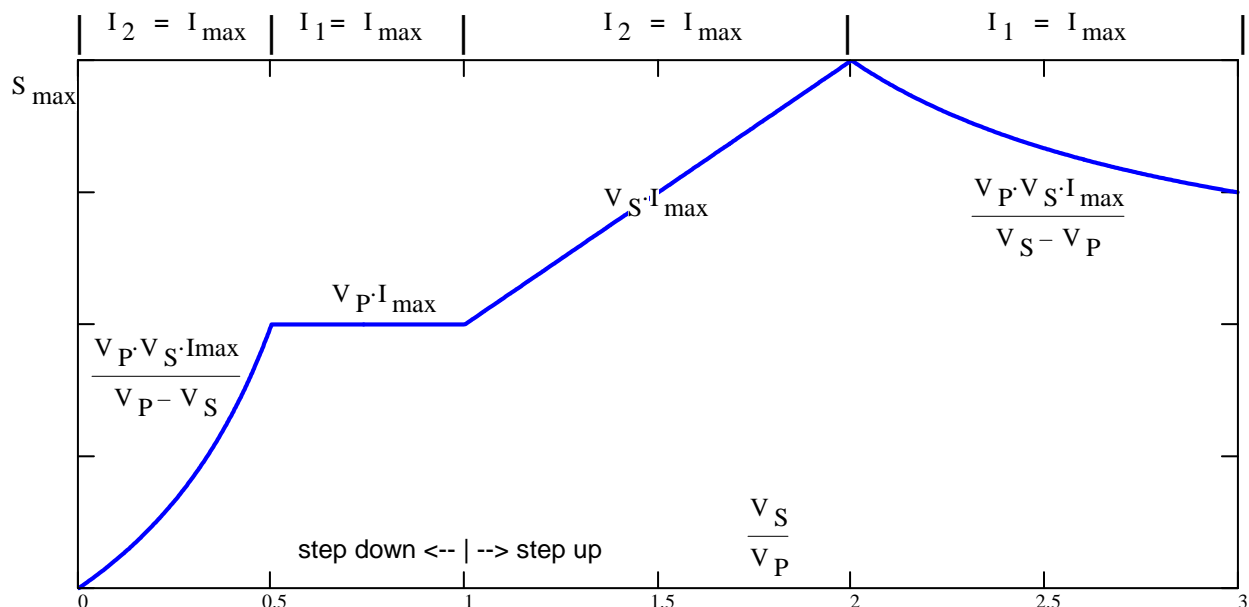Vari-AC type autotransformer "Rating", Based on the maximum winding current: I_{max}





Regular winding connections

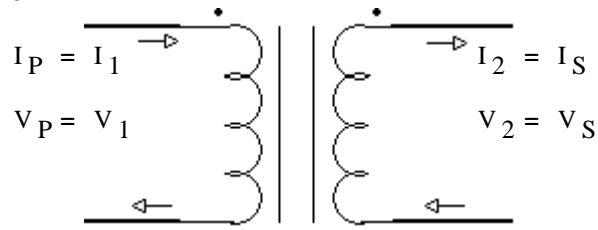


Auto Transformer Connections

4 basic possibilities



Addition connections

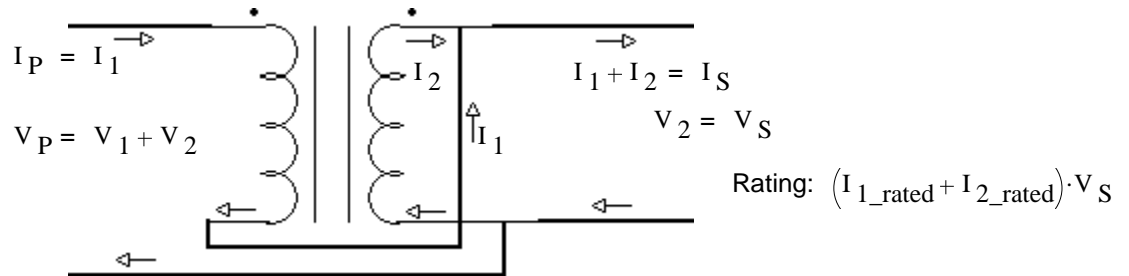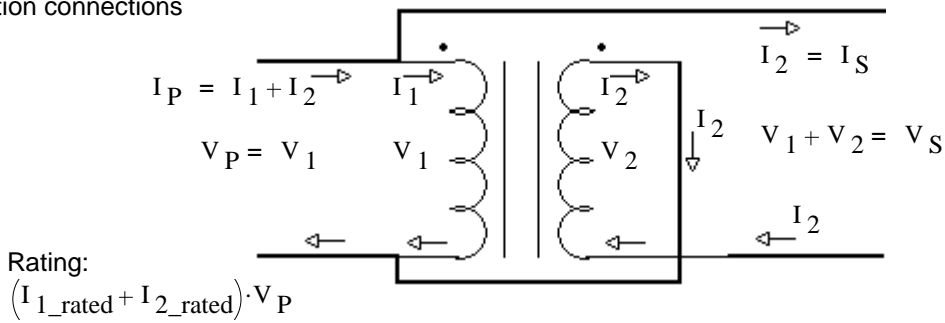

Subtraction connections

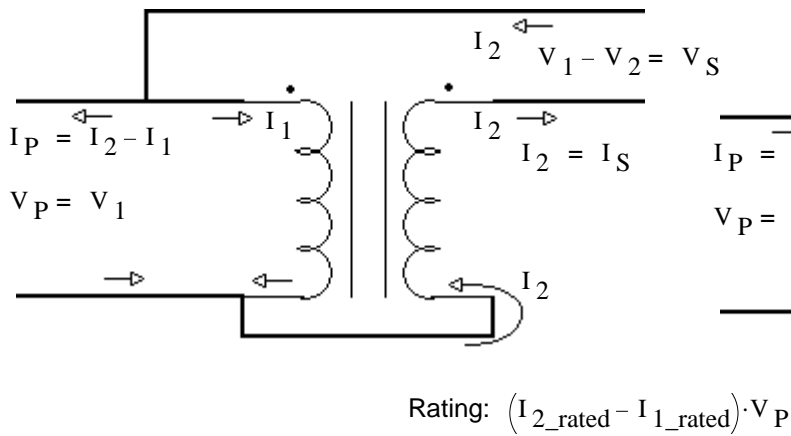

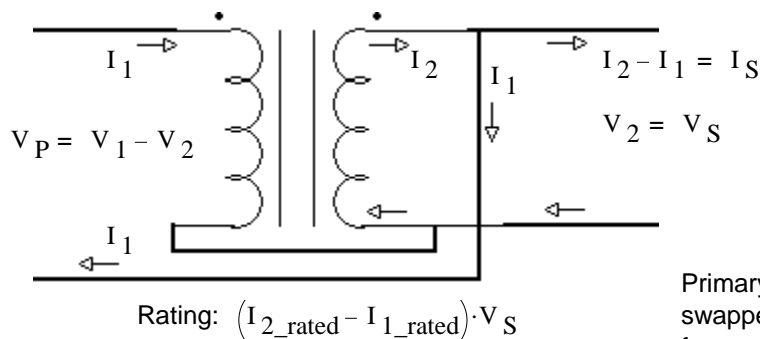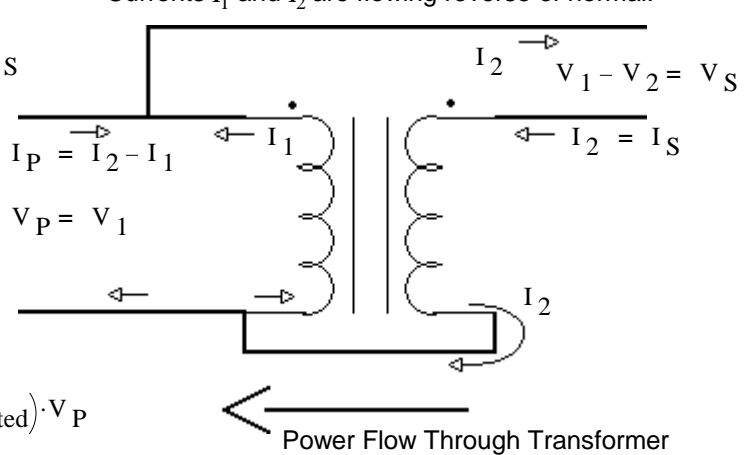
Currents I_1 and I_2 are flowing reverse of normal.



Primary and Secondary could be swapped on any of these connections for an additional 4 possibilities

Inrush current

When a transformer is de-energized (switched off) its core may remain partially magnetized. When it is then re-energized (switched on) it may take several cycles before the B and the H re-center around the 0,0 point of the B-H plot. That can result in pushing the core far into saturation with large peaks of magnetic field intensity (H). H is directly proportional to current, so there are correspondingly large peaks of current. This inrush current is not sinusoidal and usually has a large DC component. Since it is dependent on where in the voltage cycle the transformer was de-energized it will be different each time the transformer is re-energized.

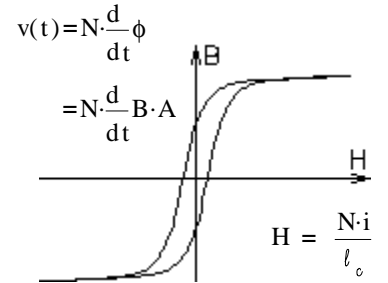

Normal inrush currents can be just as large as abnormal short-circuit currents, yet protection devices (breakers and fuses) should not trip or blow-- a difficult protection problem.

Any device with a magnetic core will experience similar inrush currents.

Cooling and Oil-Immersion

High-voltage transformers are almost universally immersed in oil. That is, the core and windings are in a big enclosure filled with oil. Oil is a much better electrical insulator than air and also has much better thermal conductivity. Typically, it's mineral oil, but other, more expensive, oils and chemicals are also used to reduce fire and/or environmental hazards. PCBs are no longer used. Although PCB reduced the fire risk, it's highly toxic and stays in the environment a long time.


Core losses in a transformer will cause it to heat up even if it's not loaded. I²R losses increase the heating under loaded conditions. Small transformers may just be air-cooled, but larger transformers require more cooling. Large oil-filled transformers typically cool that oil in radiators with fins next to the transformer. Those fins often have fans for forced-air cooling and the oil may be pumped through the transformer for forced-oil cooling. Transformers often have a tank to accommodate the thermal expansion of the oil. A bladder or inert gas inside the tank prevents contact with air.

- Cooling Types: AA Dry-type, Air cooled
- AFA Dry-type, Forced-Air cooled
- OA Oil Immersed, Air-cooled
- OA/FA Oil Immersed, Air / Forced-Air cooled
- OA/FA/FOA Oil Immersed, Air / Forced-Air / Forced-Oil and air cooled

Dissolved Gas Analysis

Analysis of the oil can reveal information about the health of the transformer. The simple version: Oxygen and Nitrogen indicate the oil has had contact with air. Carbon monoxide and dioxide indicate insulation degradation. Hydrogen indicates corona discharge. Methane, ethane, ethylene, and acetylene all indicate increasing levels of electrical faults and/or overheating with acetylene being the worst, indicating arcing. The oil is also checked for water, even a little of which is very bad. Regular maintenance includes filtering and drying the oil.

Large 3-phase Substation Transformer

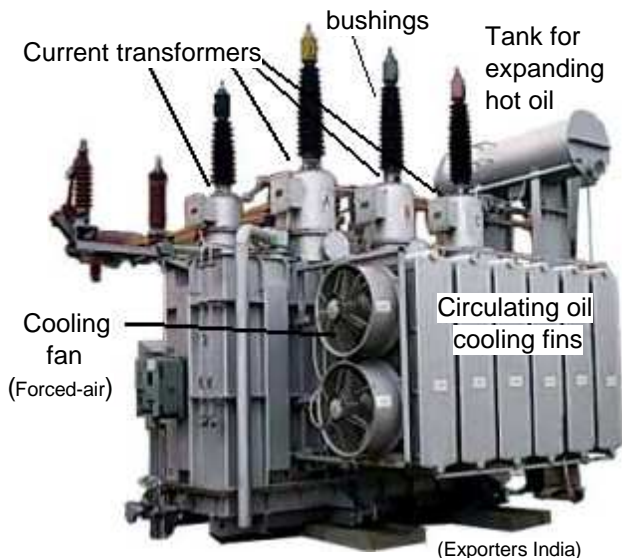


Mineral Oil is Flammable (or is that inflammable?)



(cbn.co.za)


3-phase Transformer Connections

Multiple cores

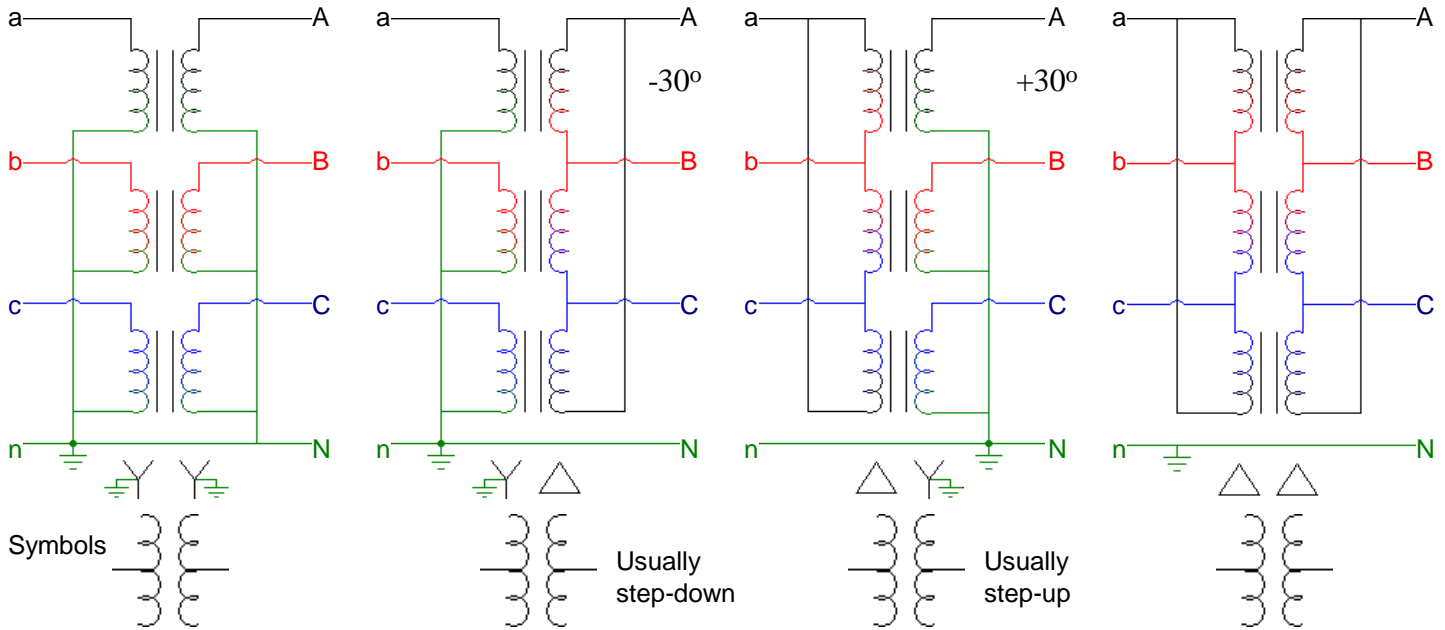


Y-Y transformers usually have a tertiary winding for the 3rd harmonic current, see below.

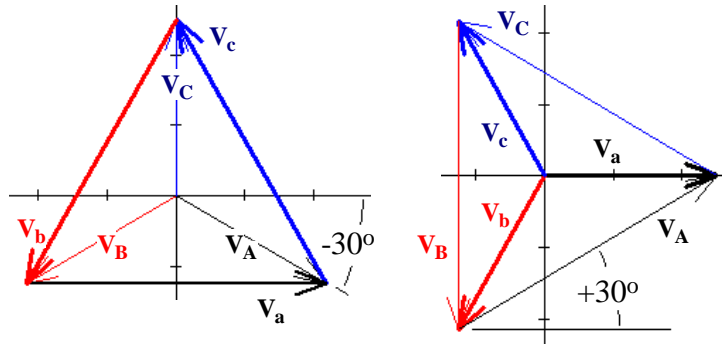The Δ-Δ configuration can get by with just 2 transformers, at 58% VA.



Thick lines are the inputs
Thin lines are the outputs

Other Phase Shifts

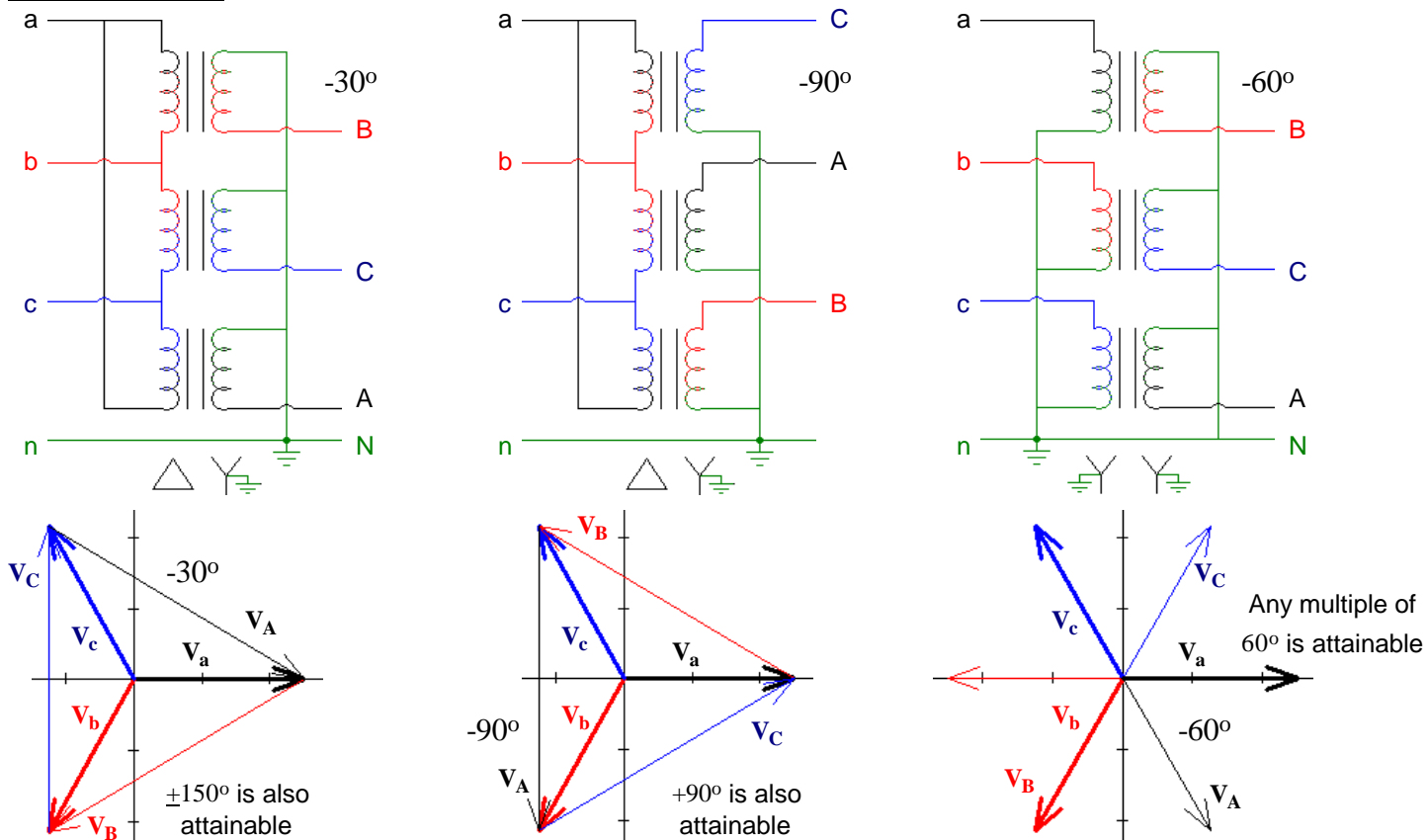

±150° is also attainable



+90° is also attainable

Any multiple of 60° is attainable

These can also be wired Y-Δ

Single-Core 3-phase Transformers

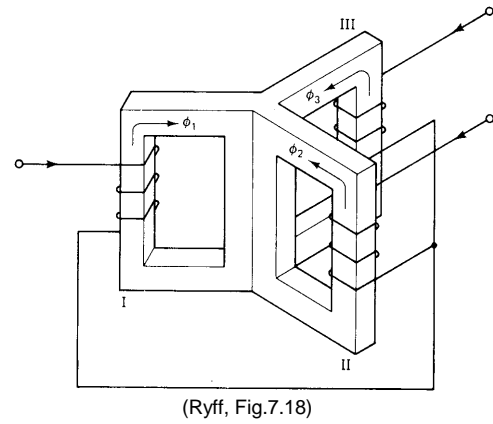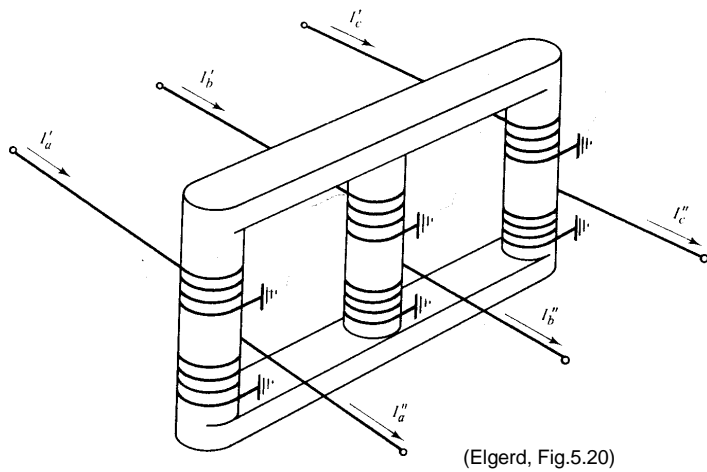
Cheaper and have less core loss than using individual cores or transformers.



Single-core transformers can also create all phase shifts shown on the previous page.

Third-Harmonic Currents

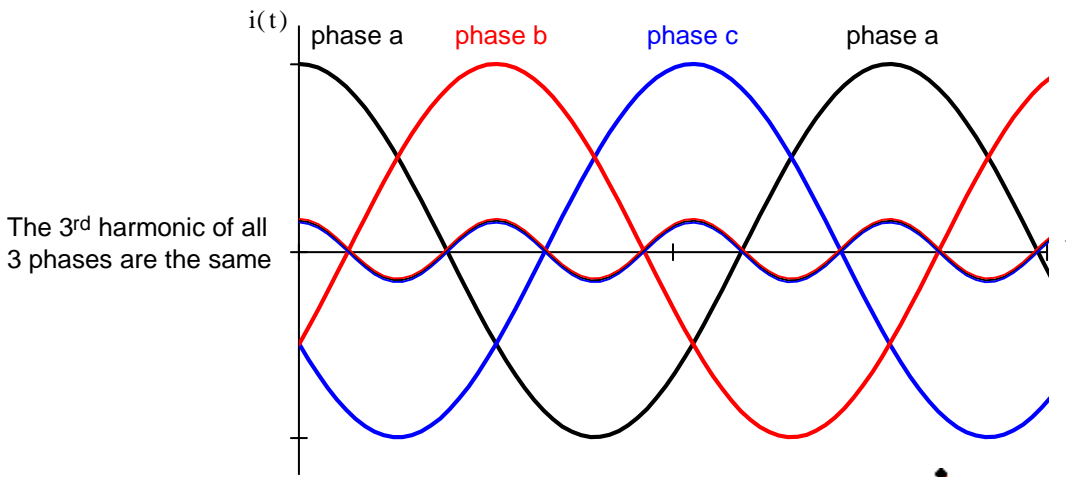Third-harmonic currents (due to B-H non-linearity) add up to a significant neutral current.




Any Δ -connected winding will allow the third-harmonic current to flow in a loop.





3-phase autotransformers

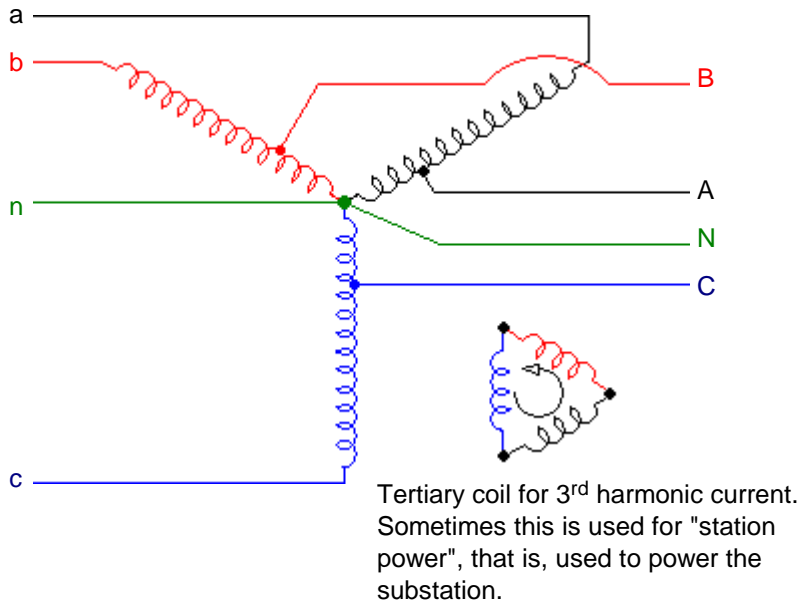Becoming more popular because they're cheaper for a given VA.



345kV/138kV Autotransformer at Terminal Substation in Salt Lake City. Note oil tank and cooling fins. (Am)


Phase-Shifting Transformers

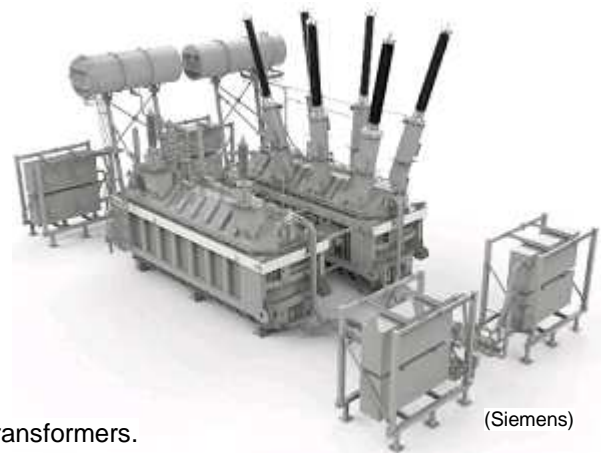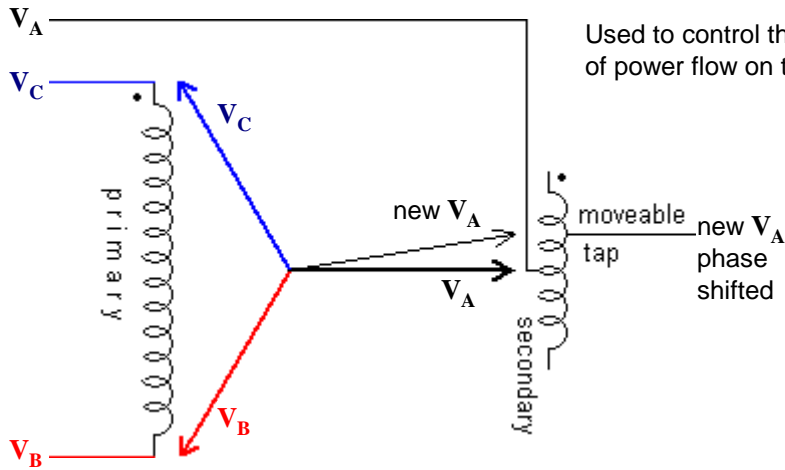

Phases B and C are shifted in exactly the same way, with two other transformers.

Off-Nominal Turns Ratio

Note the weird I_2 direction

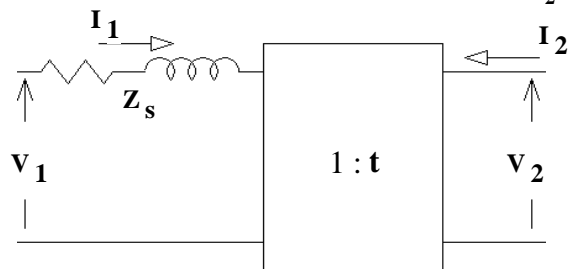

$$Z_s = \frac{1}{Y_s} \quad \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{bmatrix} Y_s & -\frac{Y_s}{t} \\ -\frac{Y_s}{\bar{t}} & Y_s \end{bmatrix} \begin{pmatrix} V_1 \\ V_2 \end{pmatrix}$$

If there is a phase shift, t will be complex

\bar{t} = complex conjugate of t

Transformer Examples

b


Ex.1 a) An ideal transformer has 360 turns on the primary winding and 36 turns on the secondary. If the primary is connected across a 120 V (rms) generator, what is the rms output voltage?

$$120 \cdot \text{volt} \cdot \frac{36}{360} = 12 \cdot \text{volt}$$

b) If you used a full-wave rectifier and a capacitor to make a DC power supply with this transformer, what DC voltage should you get?

$$12 \cdot \text{V} \cdot \sqrt{2} - 2 \cdot 0.7 \cdot \text{V} = 15.6 \cdot \text{V} \quad \text{less under load}$$


peak 2 diodes

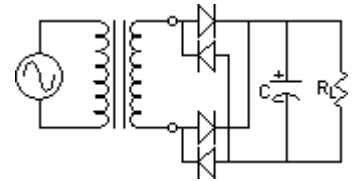

Ex.2 A transformer has $N_1 = 320$ turns and $N_2 = 1000$ turns. If the input voltage is $v(t) = (255 \text{ V})\cos(\omega t)$, what rms voltage is developed across the secondary coil?

$$\frac{255 \cdot \text{volt} \cdot 1000}{\sqrt{2} \cdot 320} = 563 \cdot \text{volt}$$

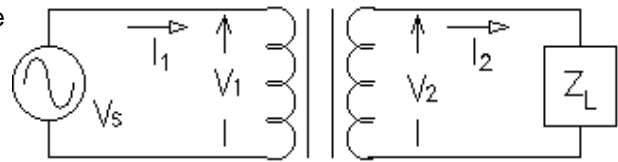Ex.3 A transformer is rated at 480V / 120V, 1.2kVA. Assume the transformer is ideal and all voltages and currents are RMS.



a) What is the current rating of the primary?

$$\frac{1.2 \cdot \text{kVA}}{480 \cdot \text{V}} = 2.5 \cdot \text{A}$$

$$|Z_L| = 20 \cdot \Omega$$

pf := 75% lagging

b) What is the current rating of the secondary? $\frac{1.2 \cdot \text{kVA}}{120 \cdot \text{V}} = 10 \cdot \text{A}$

$$V_L := 110 \cdot \text{V}$$

c) The secondary has 100 turns of wire. How many turns does the primary have?

$$N_2 := 100 \quad N_1 := \frac{480 \cdot \text{V}}{120 \cdot \text{V}} \cdot N_2 \quad N_1 = 400 \text{ turns}$$

d) $V_L := 110 \cdot \text{V}$ How big is the source voltage ($|V_S|$)?

$$V_S := \frac{N_1}{N_2} \cdot V_L \quad V_S = 440 \cdot \text{V}$$

e) The secondary load (Z_L) has a magnitude of 20Ω at a power factor of 75%. Find the secondary current, I_2 (magnitude **and angle**).

pf := 75%

$$I_2 = \frac{V_L}{20 \cdot \Omega} = 5.5 \cdot \text{A} \quad \text{pf} = 0.75 \quad \text{acos}(\text{pf}) = 41.4 \cdot \text{deg} \quad I_2 = 5.5 \text{A} \angle -41.4^\circ$$

f) Find the primary current, I_1 (magnitude **and angle**).

$$I_1 = \frac{100}{400} \cdot 5.5 \cdot \text{A} = 1.375 \cdot \text{A} \quad \text{acos}(\text{pf}) = 41.4 \cdot \text{deg} \quad I_1 = 1.375 \text{A} \angle -41.4^\circ$$

Transformer is ideal, so angle is exactly the same as the load.

g) How much average power does the load dissipate?

$$P_L = |V_2| \cdot |I_2| \cdot \text{pf} = 110 \cdot \text{V} \cdot 5.5 \cdot \text{A} \cdot 75\% = 453.8 \cdot \text{watt}$$

h) How much average power does the power source (V_S) supply?

$$P_S = P_L = 454 \cdot \text{watt}$$


i) What is the load as seen by V_S ? (magnitude **and angle**)

$$\left(\frac{400}{100}\right)^2 \cdot 20 \cdot \Omega = 320 \cdot \Omega \quad \text{acos}(\text{pf}) = 41.4 \cdot \text{deg} \quad Z_{\text{eq}} = 320 \Omega \angle 41.4^\circ$$

$$\text{OR: } \frac{440 \cdot \text{V}}{1.375 \cdot \text{A}} = 320 \cdot \Omega \angle 0 - -41.4^\circ$$

Transformer Examples p2

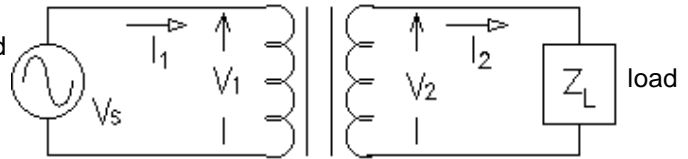Ex.4 A transformer is rated at 480V/240V, 1.2kVA.
Assume the transformer is ideal and all voltages and currents are RMS.



How much power does the load consume?

$$V_L := V_S \cdot \left(\frac{240}{480}\right) \quad |V_L| = 220 \cdot V \quad |V_S| = 440 \cdot V \quad |Z_L| = 16 \cdot \Omega$$

$$I_2 := \frac{|V_L|}{|Z_L|} \quad P_L := |V_L| \cdot I_2 \cdot \text{pf} \quad P_L = 2.42 \cdot \text{kW}$$



pf := 80% lagging

Ex.5 The transformer shown in the circuit below is ideal. It is rated at 220/110 V, 200 VA, 60 Hz

Find the following:

a) The primary current (magnitude).

$$|I_1| = ?$$

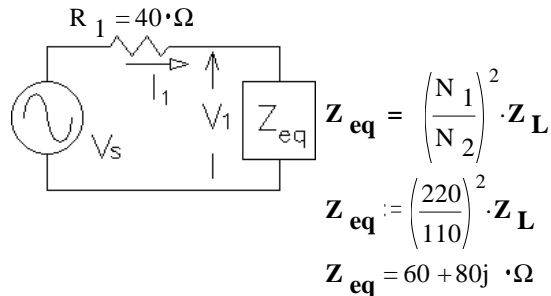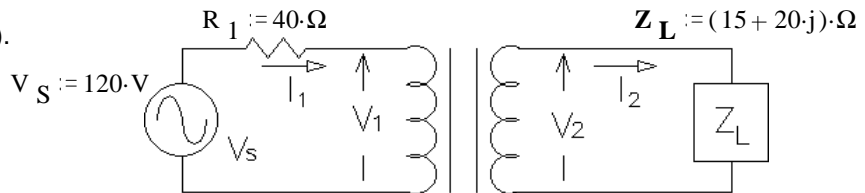

$$R_1 + Z_{eq} = 100 + 80j \cdot \Omega$$

$$I_1 := \frac{V_S}{\sqrt{100^2 + 80^2 \cdot \Omega}} \quad I_1 = 0.937 \cdot A$$

b) The primary voltage (magnitude).

$$|V_1| = ?$$

$$V_1 := I_1 \cdot \sqrt{60^2 + 80^2 \cdot \Omega} \quad V_1 = 93.7 \cdot V$$

c) The secondary voltage (magnitude).

$$|V_2| = ?$$

$$V_2 = \frac{110}{220} \cdot V_1 = 46.85 \cdot V$$

d) The power supplied by the source.

$$P_S = ?$$

$$P_S = I_1^2 \cdot 100 \cdot \Omega = 87.8 \cdot W$$

e) Is this transformer operating within its ratings? Show your evidence.

$$I_{1\text{max}} = \frac{200 \cdot \text{VA}}{220 \cdot V} = 0.909 \cdot A < I_1 = 0.937 \cdot A$$


NO

ALWAYS CHECK CURRENT

Transformer Examples p3

Ex.6 Repeat Ex.5 with a non-ideal transformer whose characteristics are shown below.
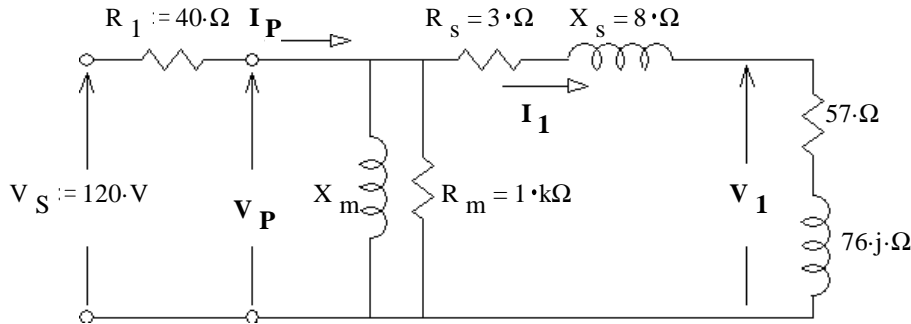
$$R_m := 1 \cdot \text{k}\Omega \quad X_m := 400 \cdot \Omega \quad R_s := 3 \cdot \Omega \quad X_s := 8 \cdot \Omega \quad N := 1.95$$



$$Z_{eq} := (1.95)^2 \cdot (15 + 20j) \cdot \Omega$$

$$Z_{eq} = 57.037 + 76.05j \cdot \Omega$$

Find the following:

a) The primary current (magnitude).

$$|I_P| = ?$$

$$R_s + X_s \cdot j + Z_{eq} = 60.037 + 84.05j \cdot \Omega$$

$$\frac{1}{\frac{1}{X_m \cdot j} + \frac{1}{R_m} + \frac{1}{(60 + 84j) \cdot \Omega}} = 43.689 + 68.412j \cdot \Omega$$

$$R_1 + (43.689 + 68.412j) \cdot \Omega = 83.689 + 68.412j \cdot \Omega$$

$$I_P := \frac{120 \cdot V}{(83.689 + 68.412j) \cdot \Omega}$$

$$I_P = 0.86 - 0.703j \cdot A$$

$$|I_P| = 1.11 \cdot A$$

b) The primary voltage (magnitude).

$$|V_P| = ?$$

$$V_P := I_P \cdot (43.689 + 68.412j) \cdot \Omega$$

$$V_P = 85.619 + 28.105j \cdot V$$

$$|V_P| = 90.114 \cdot V$$

c) The secondary voltage (magnitude).

$$|V_2| = ?$$

$$I_1 := \frac{V_P}{(60 + 84j) \cdot \Omega}$$

$$I_1 = 0.704 - 0.517j \cdot A$$

$$V_1 := I_1 \cdot (57 + 76j) \cdot \Omega$$

$$V_1 = 79.375 + 24.026j \cdot V$$

$$|V_1| = 82.931 \cdot V$$

$$|V_2| = \frac{1}{N} \cdot 82.931 \cdot V = 42.529 \cdot V$$

OR, simply:

$$I_1 := \frac{90.114 \cdot V}{\sqrt{60^2 + 84^2} \cdot \Omega}$$

$$I_1 = 0.873 \cdot A$$

$$V_2 = \frac{I_1 \cdot \sqrt{57^2 + 76^2} \cdot \Omega}{1.95} = 42.529 \cdot V$$

d) The power supplied by the source.

$$P_S = ?$$

$$P_S = 120 \cdot V \cdot \text{Re}(I_P) = 103.14 \cdot W$$

e) Is this transformer operating within its ratings? Show your evidence.

$$I_{2max} = \frac{200 \cdot VA}{110 \cdot V} = 1.818 \cdot A > |I_1| \cdot N = 1.702 \cdot A$$

YES

f) Find the efficiency, assuming that the only useful output is from Z_L .


$$\eta = \frac{(|I_1|)^2 \cdot 57 \cdot \Omega}{103.14 \cdot W} \cdot 100\% = 42.12\%$$

Ex.7 Find the voltage regulation and full-load efficiency of the transformer with the following ratings and characteristics.

Transformer Examples p4

Rated at 480/120 V, 2 kVA, 60 Hz $R_m := 8.4 \cdot k\Omega$ $X_m := 2 \cdot k\Omega$ $R_s := 5 \cdot \Omega$ $X_s := 15 \cdot \Omega$
 $V_{Prated} := 480 \cdot V$ $V_{Srated} := 120 \cdot V$ $S_{rated} := 2000 \cdot VA$

No load:

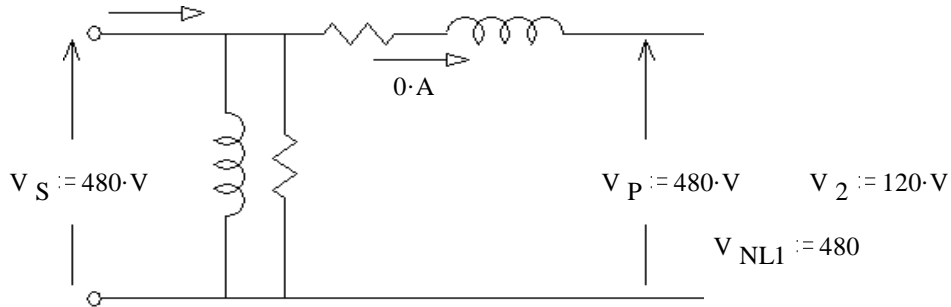


Full load:

$$R_L := \frac{(120 \cdot V)^2}{2000 \cdot W} \quad R_L = 7.2 \cdot \Omega$$

Find the actual turns ratio: (See page 3 of notes)
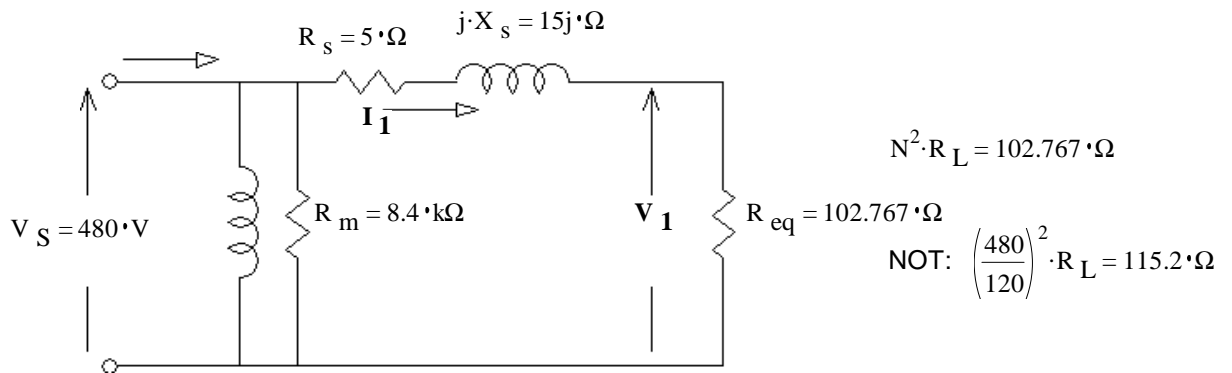
$$R_x := \frac{V_{Prated}^2}{S_{rated}} - 2 \cdot R_s \quad R_{eq} := \frac{R_x + \sqrt{R_x^2 - 4 \cdot (R_s^2 + X_s^2)}}{2} \quad \text{Turns ratio } N := \sqrt{\frac{R_{eq}}{R_L}} \quad N = 3.778$$



$$I_1 := \frac{V_S}{R_{eq} + R_s + 15j \cdot \Omega} \quad I_1 = 4.369 - 0.608j \cdot A$$

$$V_1 := I_1 \cdot R_{eq} \quad V_1 = 449.031 - 62.5j \cdot V$$

$$V_{FL1} := |V_1| \quad V_{FL1} = 453.359 \cdot V$$

OR, simply:

$$I_1 := \frac{V_S}{\sqrt{(R_{eq} + R_s)^2 + X_s^2}} \quad I_1 = 4.412 \cdot A$$

$$V_{FL1} = I_1 \cdot R_{eq} = 453.359 \cdot V$$

Voltage regulation: $\%VR = \frac{V_{no_load} - V_{full_load}}{V_{full_load}} \cdot 100\% = \frac{V_S - V_{FL1}}{V_{FL1}} \cdot 100\% = 5.876\%$

Efficiency $\eta = \frac{P_{out}}{P_{in}} \cdot 100\% = \frac{P_{out}}{P_{out} + P_{losses}} \cdot 100\%$

$$P_{out} := I_1^2 \cdot R_{eq} \quad P_{out} = 2 \cdot kW$$

$$P_{losses} := I_1^2 \cdot 5 \cdot \Omega + \frac{(480 \cdot V)^2}{8400 \cdot \Omega} \quad P_{losses} = 0.125 \cdot kW$$

$$\eta = \frac{P_{out}}{P_{out} + P_{losses}} \cdot 100\% = 94.129\%$$

Transformer Examples p5

Ex.8 A 500/100-V, 2.5-kVA transformer is subjected to an OC test and a SC test with the results below.

a) Draw a model of this transformer and find the values of all the elements of the model, including the turns ratio.

During the open-circuit test: $I_{OC} := 0.5 \cdot A$ $P_{OC} := 150 \cdot W$ $V_{sec} := 108 \cdot V$

During the short-circuit test: $V_{SC} := 22 \cdot V$ $P_{SC} := 70 \cdot W$

$S_{rated} := 2.5 \cdot kVA$ $V_{Prated} := 500 \cdot V$ $I_{Prated} := \frac{S_{rated}}{V_{Prated}}$ $I_{Prated} = 5 \cdot A$

Open-circuit test used to find R_m and X_m and turns ratio.

$V_{OC} := V_{Prated}$

$R_m := \frac{V_{OC}^2}{P_{OC}}$ $R_m = 1.667 \cdot k\Omega$

$Q_{OC} := \sqrt{(V_{OC} \cdot I_{OC})^2 - P_{OC}^2}$ $Q_{OC} = 200 \cdot VAR$

$X_m := \frac{V_{OC}^2}{Q_{OC}}$ $X_m = 1.25 \cdot k\Omega$


Turns ratio: $N := \frac{V_{Prated}}{V_{sec}}$ $N = 4.63$

Short-circuit test used to find R_s and X_s $I_{SC} := I_{Prated}$

$R_s := \frac{P_{SC}}{I_{SC}^2}$ $R_s = 2.8 \cdot \Omega$


$Q_{SC} := \sqrt{(V_{SC} \cdot I_{SC})^2 - P_{SC}^2}$ $Q_{SC} = 0.085 \cdot kVAR$

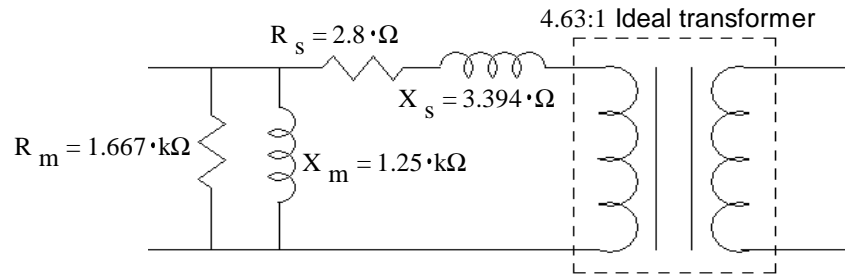$X_s := \frac{Q_{SC}}{I_{SC}^2}$ $X_s = 3.394 \cdot \Omega$



b) The transformer is connected to a primary source voltage of 360V and loaded with $Z_L := (2 + 1 \cdot j) \cdot \Omega$

Find the secondary voltage. Magnitude only. $|V_2| = ?$

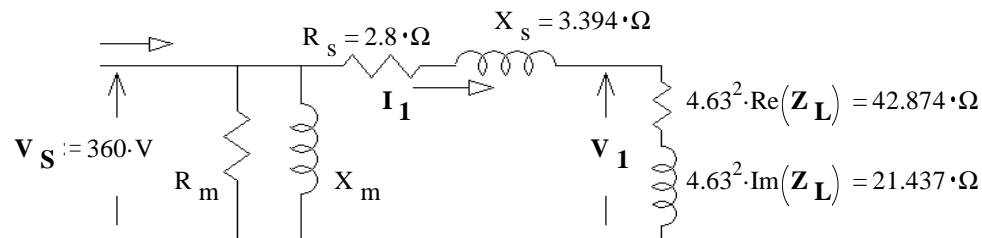

$|V_1| = V_1 := V_S \cdot \frac{\sqrt{(42.874 \cdot \Omega)^2 + (21.437 \cdot \Omega)^2}}{\sqrt{(R_s + 42.874 \cdot \Omega)^2 + (X_s + 21.437 \cdot \Omega)^2}}$ $V_1 = 331.935 \cdot V$

$|V_2| = V_2 = \frac{V_1}{4.63} = 71.69 \cdot V$

c) Is this transformer operating within its ratings? Show all evidence and calculate needed to to determine this.

$|I_2| = I_2 := \frac{V_S}{\sqrt{(R_s + 42.874 \cdot \Omega)^2 + (X_s + 21.437 \cdot \Omega)^2}} \cdot N$ $I_2 = 32.059 \cdot A > I_{Srated} = \frac{S_{rated}}{100 \cdot V} = 25 \cdot A$

NO!

Transformer Examples p6


Ex.9 You have a 250/100-V, 500-VA transformer.

- Show the necessary connections to use this transformer to transform 350 V to 250 V. Also show the 350-V source and the load.
- Connected this way, determine the maximum power that could be converted from 350 V to 250 V without overloading the transformer.

$$\text{ratings: } \frac{500 \cdot \text{VA}}{250 \cdot \text{V}} = 2 \cdot \text{A} \quad \frac{500 \cdot \text{VA}}{100 \cdot \text{V}} = 5 \cdot \text{A}$$

$$\text{new VA rating and maximum power: } 5 \cdot \text{A} \cdot 350 \cdot \text{V} = 1.75 \cdot \text{kVA}$$
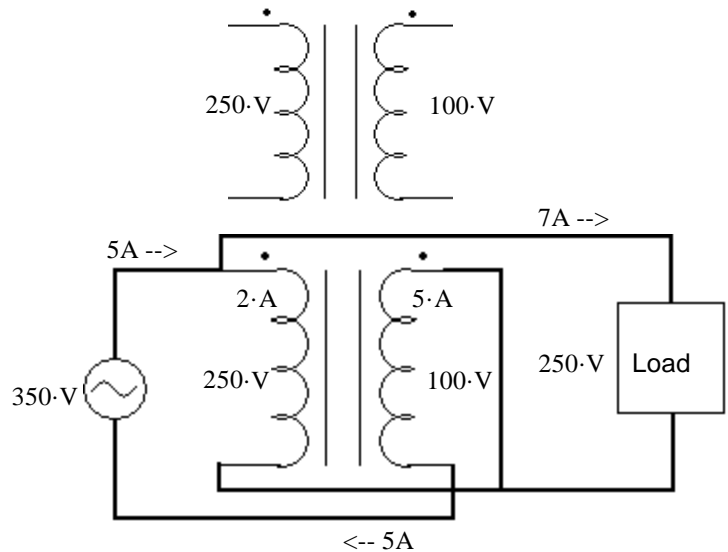
$$\text{OR: } 7 \cdot \text{A} \cdot 250 \cdot \text{V} = 1.75 \cdot \text{kVA} \\ 1.75 \cdot \text{kW}$$



- Besides the right impedance magnitude, what other characteristic must the load possess in order to actually use this much power?

Load must be purely resistive (power factor is 1).

- Could this transformer also be used to transform 280 V to 200 V ? If yes, what is the maximum power that could be transformed?

$$\text{Same connections as above} \quad \text{Maximum power: } 5 \cdot \text{A} \cdot 280 \cdot \text{V} = 1.4 \cdot \text{kW}$$

Ex.10 A 345kV/138kV, 750-MVA transformer is shown.


- What is the purpose of the tertiary winding?

To allow 3rd harmonic currents to flow without affecting currents outside the transformer.

- Find the maximum I_{Lp} and I_{Ls} .

$$I_{Lp.\text{rated}} := \frac{\left(\frac{750 \cdot \text{MVA}}{3} \right)}{\left(\frac{345 \cdot \text{kV}}{\sqrt{3}} \right)} \quad I_{Lp.\text{rated}} = 1255 \cdot \text{A}$$
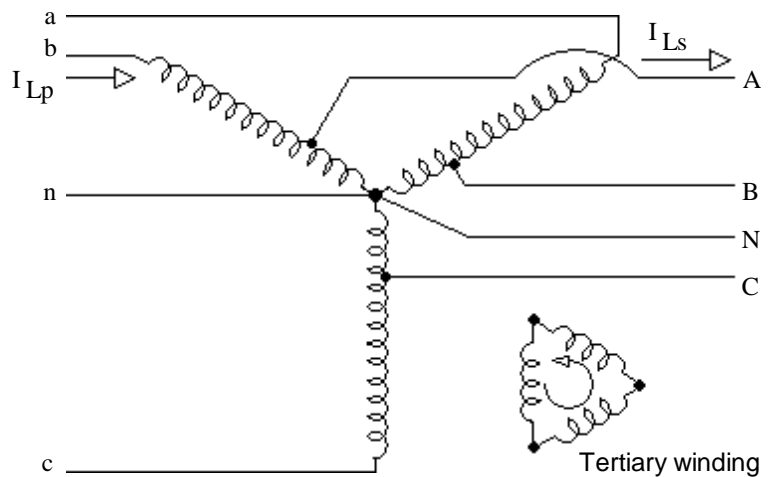
$$I_{Ls.\text{rated}} := \frac{345}{138} \cdot I_{Lp.\text{rated}} \quad I_{Ls.\text{rated}} = 3138 \cdot \text{A}$$



- Find the currents flowing in the transformer when operated at rated capacity.


$$\text{Current from primary terminal to the tap: } I_p = I_{Lp.\text{rated}} = 1255 \cdot \text{A}$$

$$\text{Current from neutral to the tap: } I_p = I_{Ls.\text{rated}} - I_{Lp.\text{rated}} = 1883 \cdot \text{A}$$

$$\text{Current from tap to secondary output of the transformer: } I_s = I_{Ls.\text{rated}} = 3138 \cdot \text{A}$$

- At what fraction of the total turns is the tap located? $\frac{138}{345} = 0.4 = \frac{4}{10}$ OR at 40%

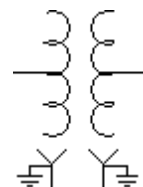- What one-line symbol would be used for this transformer?



Transformer Examples p6