

ECE 3600 Final Exam Information


You may write more on this sheet.
 You may also use Exam 1, 2 & 3 Information sheets

Power Flow

Admittance Matrix

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} & Y_{13} \\ Y_{21} & Y_{22} & Y_{23} \\ Y_{31} & Y_{32} & Y_{33} \end{bmatrix} \cdot \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

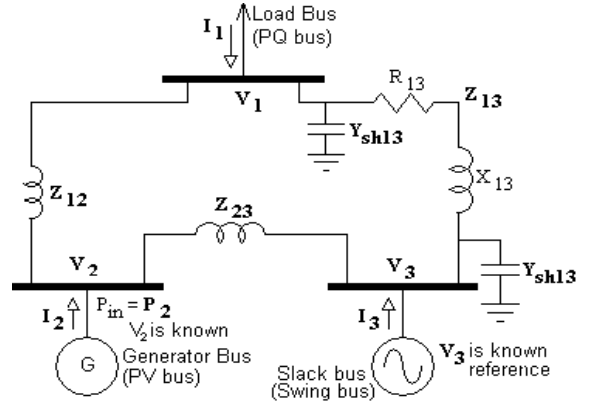$Y_{nn} = \sum$ of all admittances connected to bus n
 $Y_{mn} = -$ admittance connected between busses n & m
 $m \neq n$




Faults

Symmetrical faults Just analyze on a normal per-phase basis

Unsymmetrical Faults

$$\begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \cdot \begin{bmatrix} V_{A0} \\ V_{A1} \\ V_{A2} \end{bmatrix} \quad \begin{bmatrix} V_{A0} \\ V_{A1} \\ V_{A2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \cdot \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix}$$
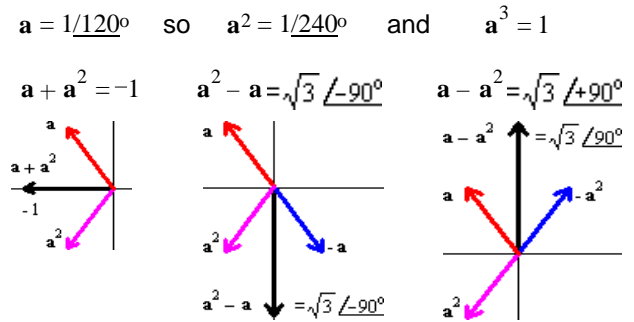
$$\begin{bmatrix} I_A \\ I_B \\ I_C \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \cdot \begin{bmatrix} I_{A0} \\ I_{A1} \\ I_{A2} \end{bmatrix} \quad \begin{bmatrix} I_{A0} \\ I_{A1} \\ I_{A2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \cdot \begin{bmatrix} I_A \\ I_B \\ I_C \end{bmatrix}$$




Pre-Fault Setup Find pre-fault V_T and I_{gen} . $E''_A = V_T + I_{gen} \cdot Z''_g$

Circuits are on the back of this sheet

It can be helpful to find E_{ThA} and all the Thevenin impedances

Zero-Sequence Impedances

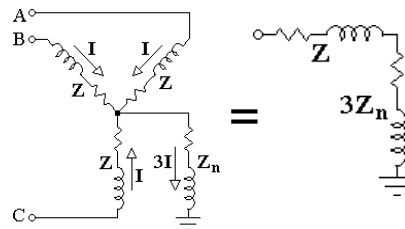Anything connected Δ looks like and open.
 Anything connected Y without a center-to-neutral or ground connection also looks like and open, otherwise:



Transformers are all open from both sides except:

