

1. The parameters of a step-down transformer are shown below.

Due: Sat, 2/1/25

The transformer is loaded with $\mathbf{Z_L} := (2.5 + 0.8 \cdot j) \cdot \Omega$ and the secondary voltage is $V_2 := 36 \cdot V$

$$R_m := 2 \cdot k\Omega$$

$$R_s := 2 \cdot \Omega$$

$$X_m := 800 \cdot \Omega$$

$$X_s := 5 \cdot \Omega$$

$$N := 5$$

a) Draw the model with the load connected. Label parts, voltages and currents as needed for the rest of the problem.

b) Find the primary, source voltage. Magnitude only. $|\mathbf{V_S}| = ?$

c) Find the total complex power supplied the primary, source voltage. $\mathbf{S_S} = P_S + j \cdot Q_S = ?$

d) Find the magnitude of the current flowing from the primary, source voltage. $|\mathbf{I_S}| = ?$

1. continued e) Find the efficiency of the transformer.

- f) The transformer would be fully loaded if $V_S := 208 \cdot V$ and $Z_L := 2 \cdot \Omega$ all real
Find the voltage regulation as defined in your notes. $\%VR = ?$

2. The parameters of a step-down transformer are shown below. The primary voltage is $V_S := 120 \cdot V$
The transformer is loaded with $Z_L = R_L + jX_L$ and the secondary current is $I_2 := 3.2 \cdot A$

$$R_m := 1.5 \cdot k\Omega \quad R_s := 5 \cdot \Omega \quad X_m := 1 \cdot k\Omega \quad X_s := 7 \cdot \Omega \quad N := 4$$


- a) The primary, source voltage provides 40 VARs $Q_S := 40 \cdot VAR$ Find X_L
Hint: draw the model with the load.

- b) Find R_L


c) Find the efficiency of this transformer.

Answers

1. a)

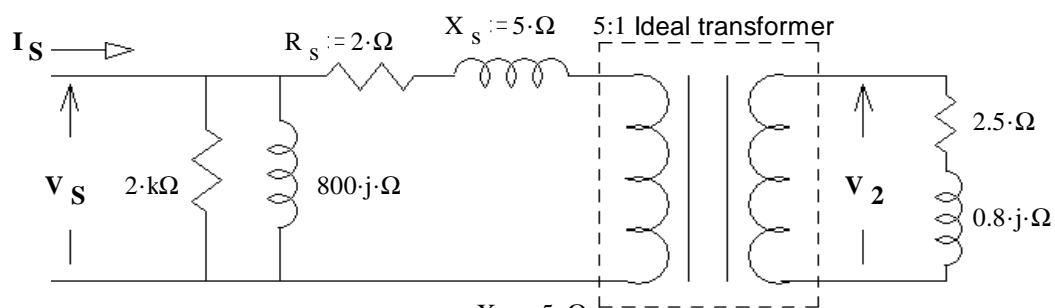

and/or

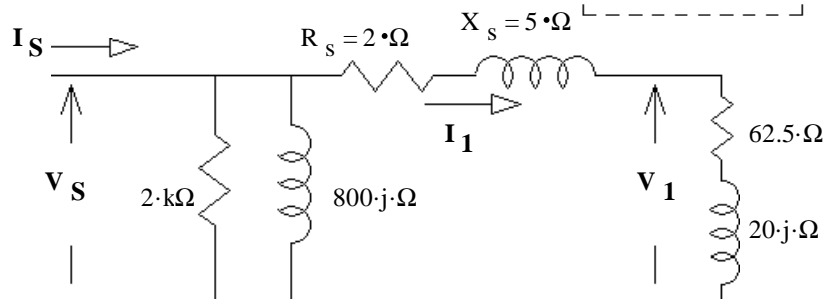

b) 189.7-V

c) $503.3 + 233.1\text{-j VA}$

d) 2.923-A

e) 93.4%

f) 4.48%

2. a) $2.062\cdot\Omega$

b) $8.723\cdot\Omega$

c) 87.5%