

Synchronous Generators

e

Name _____ ECE 3600 Homework SG2 Due: Wed, 10/16/24

1. A 60 Hz, 4-pole, Y-connected, 3-phase synchronous generator supplies 60 kW of power to a 3.6-kV bus. The synchronous reactance is $40 \Omega/\text{phase}$. The generator emf is 2.2 kV. Find the following.
- a) The power angle, δ .

b) The total reactive power generated.

c) Find a new magnitude of the generator emf so that $Q := 18 \text{ kVAR}$

ECE 3600 homework SG2 p2

2. A 3-phase synchronous generator operates onto a grid bus of voltage 12 kV (line value). The synchronous reactance is $5 \Omega/\text{phase}$. The magnitude of the generator emf equals the magnitude of the bus voltage.

The machine delivers 18 MW to the grid. Find:

a) The power angle, δ .

b) The complex phase current, (Assume the bus voltage phase angle is 0°).

c) The magnitude and direction of reactive power.

3. A 60 Hz, 2-pole, 3-phase synchronous generator supplies power to a 12.5 kV bus. The synchronous reactance is $4 \Omega/\text{phase}$. The generator emf is $7 \text{ kV} \angle 20^\circ$ (the angle is referenced to the terminal voltage). Find the following.

a) The total power generated.

b) The total reactive power generated.