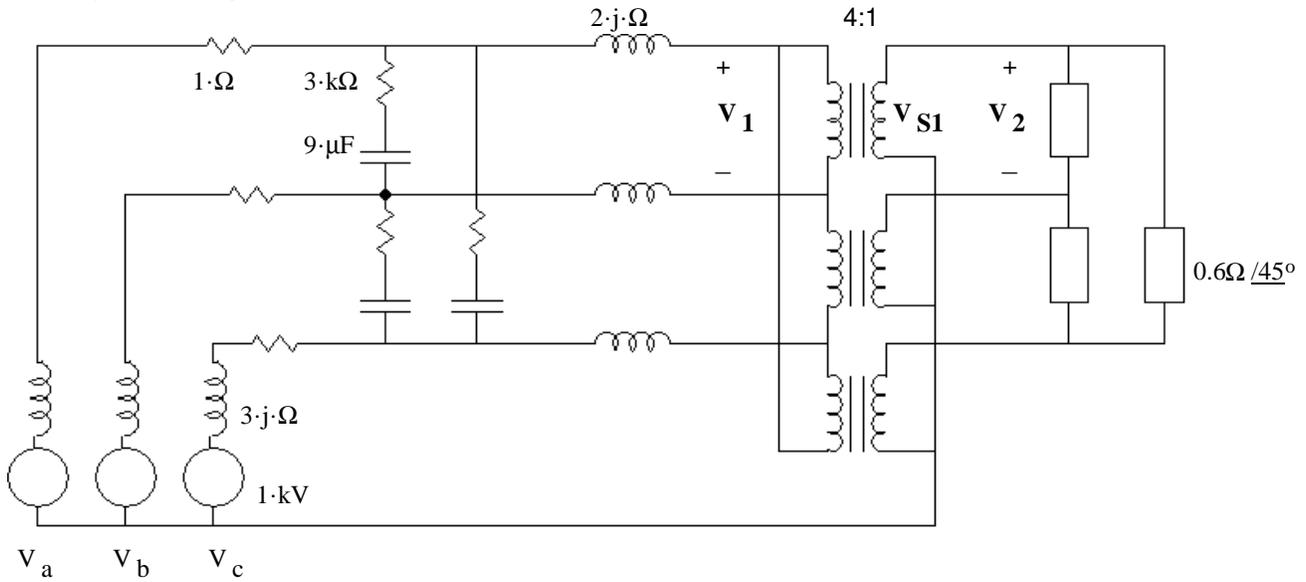


Name _____

1. a) Draw a per-phase drawing of for the balanced 3-phase, 60-Hz system shown. You may neglect phase issues introduced by Y- Δ and Δ -Y connections. You may need to modify the turns ratio of the transformer to reflect Y- Δ and Δ -Y connections. Be sure to show values of the source, passive components and turns ratio on your drawing.




- b) Find $\frac{V_1}{V_2}$ including phase angle

Modify turns ratio to reflect Δ -Y transformer connection


2. The configuration shown is called the "open-delta" or "V" connection, for obvious reasons. Identical 2:1 transformers are used.

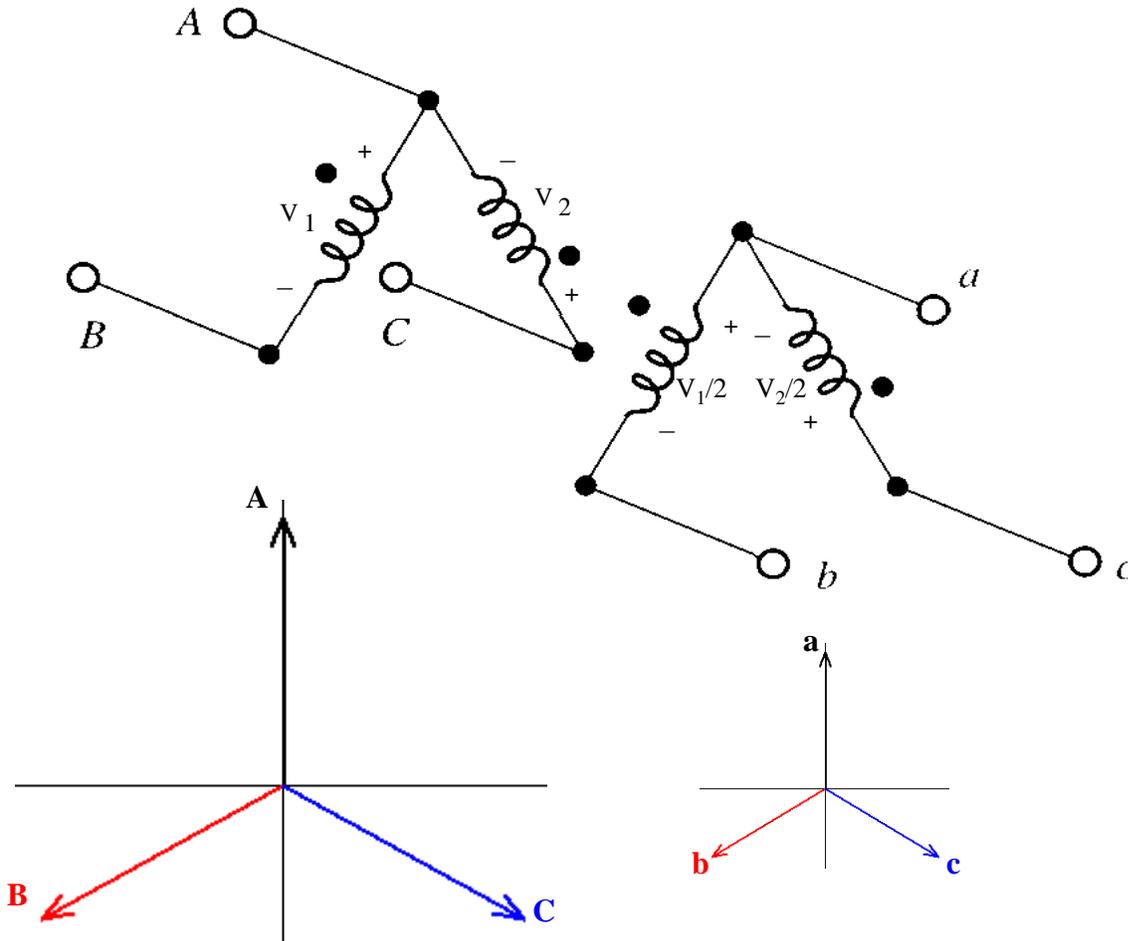a) Show that if ABC is 480-V balanced three phase, abc is 240-V balanced three-phase. Consider the ABC voltages to be a three-phase set and prove the abc set is three-phase.



b) If the load is 30 kVA, find the required kVA rating of the transformers to avoid overload.
 [You can solve this independent of part a)]

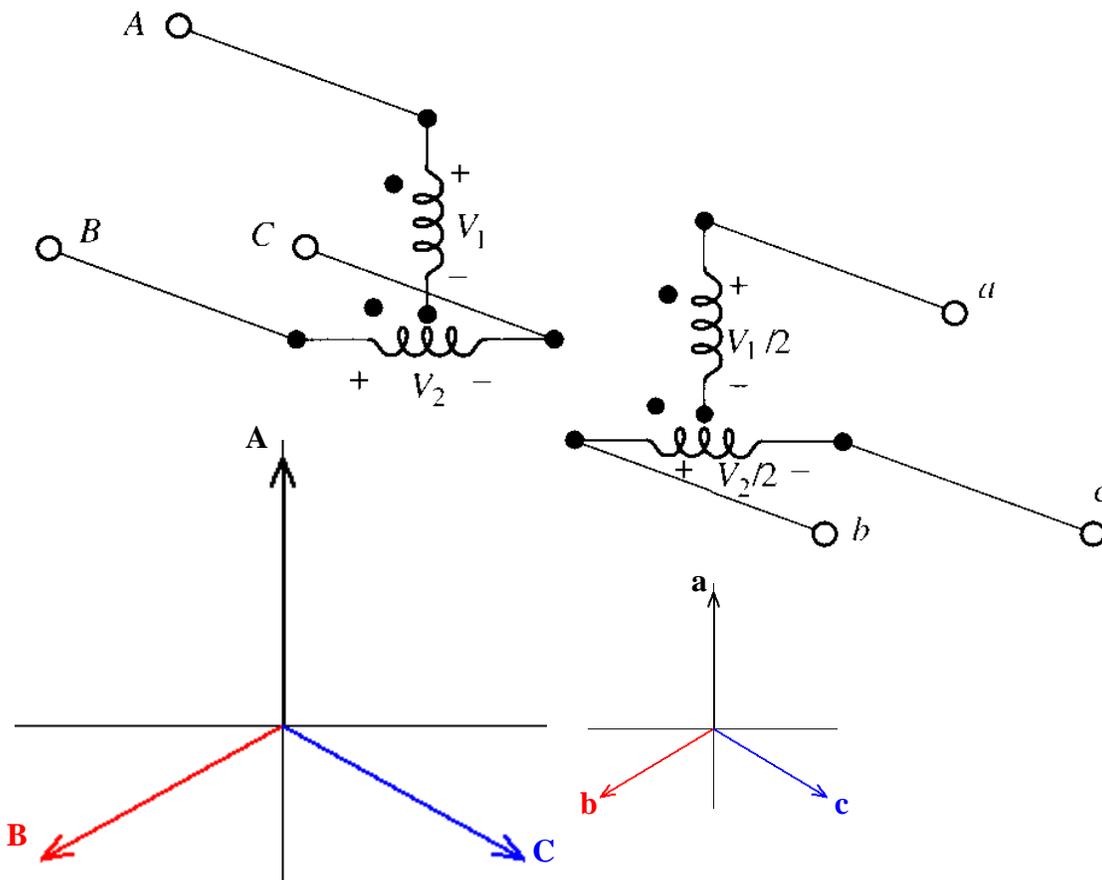3. The configuration shown is called the "T" connection. For this connection, the 2:1 transformers are not identical but have different voltage and kVA ratings. The bottom transformer is center-tapped so as to have equal, in-phase voltages for each half.
- a) Show that if ABC is 480-V balanced three phase, abc is 240-V balanced three-phase. Consider the ABC voltages to be a three-phase set and prove the abc set is three-phase.



- b) If the load is 30 kVA, find the required kVA rating of each transformer to avoid overload.


ECE 3600 homework 9B p4

4. A phase-shifting transformer has a complex turns ratio of $t := 4 \cdot e^{j \cdot 20 \cdot \text{deg}} = 4 / 20^\circ$

It has a series impedance of $Z_S := (0.05 + j \cdot 0.6) \cdot \Omega$
 Find the admittance matrix of this transformer $Y_S := \frac{1}{Z_S} =$
 (see the last page of the transformer notes).

$$\begin{bmatrix} Y_S & -\frac{Y_S}{t} \\ -\frac{Y_S}{t} & \frac{Y_S}{(|t|)^2} \end{bmatrix} = \begin{bmatrix} & \\ & \frac{1}{\Omega} \end{bmatrix}$$

Answers

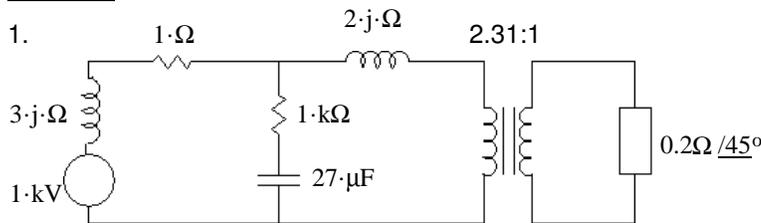

b) $2.309 / -30^\circ$

2. a) Calculate V_{bc} from the other two voltages and show that it has the correct magnitude and correct phase angle.

b) 17.3-kVA per transformer, 34.6-kVA for both

3. a) 415.7-V 480-V b) 15-kVA 17.3-kVA 32.3-kVA for both

4. $\begin{pmatrix} 0.138 - 1.655 \cdot j & 0.109 + 0.401 \cdot j \\ -0.174 + 0.377 \cdot j & 8.621 \cdot 10^{-3} - 0.103 \cdot j \end{pmatrix} \cdot \frac{1}{\Omega}$