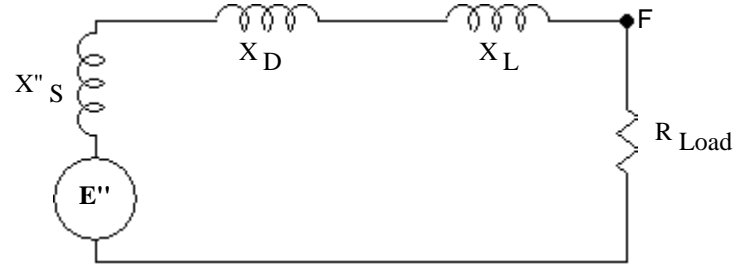


May be submitted Sat., 12/9 for full credit


1. One phase of a balanced 3-phase system is shown here.

A fault occurs point F. It is a short between lines b and c with an impedance of Z_f .

- a) Draw the circuit you would have to analyze to find the fault current. Identify the parts and Include the component voltages and currents at the fault.
- b) Set up a mathematical expression (or expressions) to find the fault current. (don't forget j & that the fault current is NOT I_{A1})



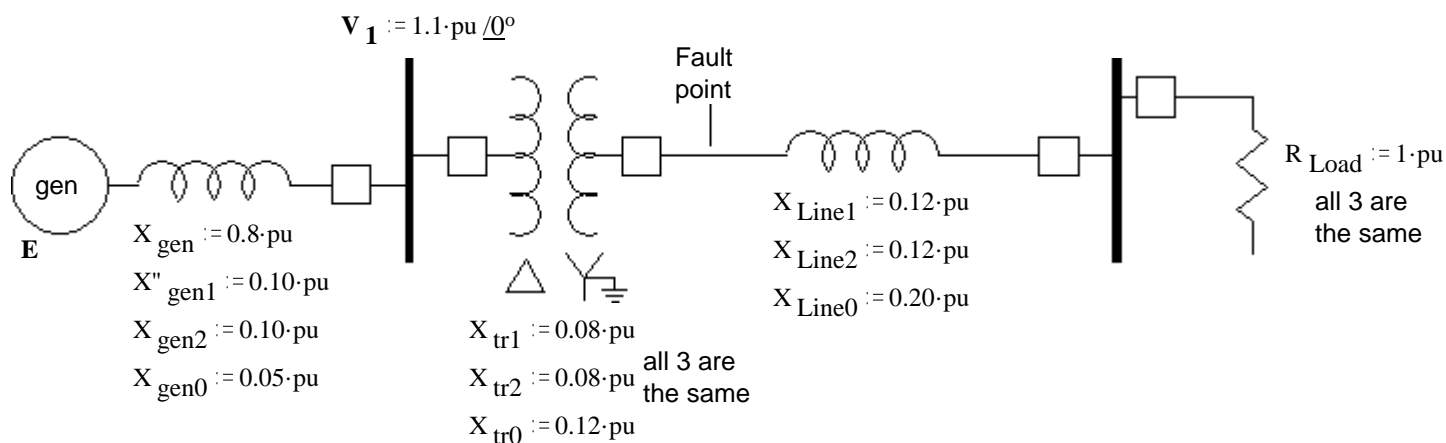2. Consider this power system. Same as the example in the notes, except for V_1 and X_{tr0} .




There is a phase-A single-line to ground (SLG) fault with a fault impedance of $Z_f := 0.15 \cdot \text{pu} \angle 0^\circ$

Find the fault current. You may be able to use some numbers already calculated in the example

Answers

1. a)

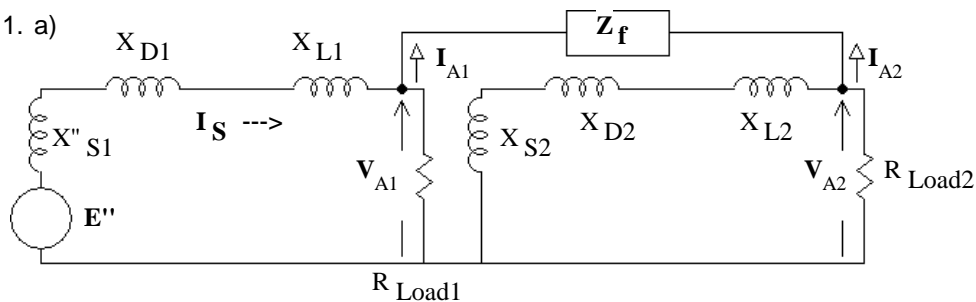

- 2. $4.69 \cdot \text{pu} \angle -45.7^\circ$
- 3. $5.016 \cdot \text{pu} \angle -46.85^\circ$

b) define
$$\mathbf{Z}_X = \mathbf{Z}_f + \frac{1}{\frac{1}{(X_{S2} + X_{D2} + X_{L2}) \cdot j} + \frac{1}{R_{\text{Load2}}}}$$

$$\mathbf{I}_S = \frac{\mathbf{E}''}{(X''_{S1} + X_{D1} + X_{L1}) \cdot j + \left(\frac{1}{R_{\text{Load1}}} + \frac{1}{\mathbf{Z}_X} \right)}$$

$$\mathbf{V}_{A1} = \mathbf{I}_S \cdot \frac{1}{\left(\frac{1}{R_{\text{Load1}}} + \frac{1}{\mathbf{Z}_X} \right)}$$

$$\mathbf{I}_{A1} = \frac{\mathbf{V}_{A1}}{\mathbf{Z}_X}$$

$$\mathbf{I}_{\text{fault}} = \mathbf{I}_B = \mathbf{a}^2 \cdot \mathbf{I}_{A1} + \mathbf{a} \cdot \mathbf{I}_{A2} = (\mathbf{a}^2 - \mathbf{a}) \cdot \mathbf{I}_{A1} = \sqrt{3} \angle -90^\circ \mathbf{I}_{A1}$$

ECE 3600 homework LF2 p4

3. Repeat problem 2 if before the fault, the load was zero, that is, $\mathbf{P}_{\text{Load}} = 0$ and $R_{\text{Load}} := \infty$

hint: this problem is considerably easier now