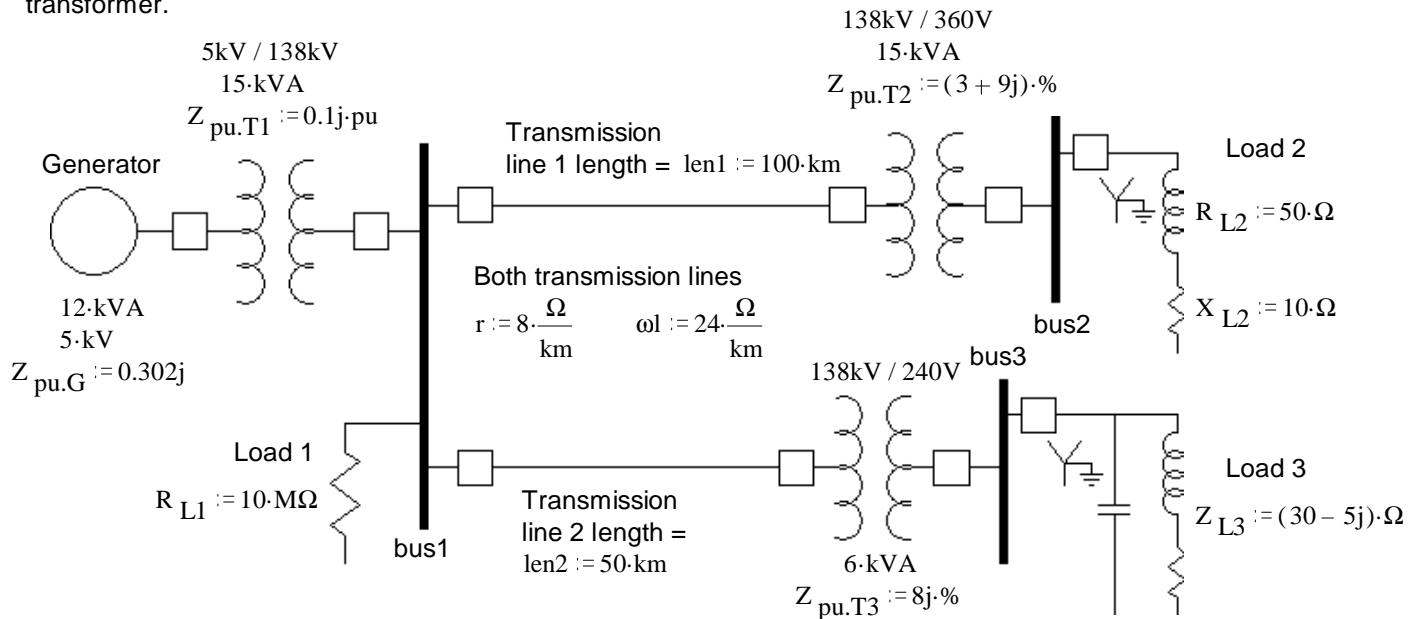


Like problem 4 on homework

Zoom Example

4. A one-line diagram of a 3 ϕ system is shown below. Manufacturer's information is shown for the generator and each transformer.



a) Choose an S_{base} to minimize the per-unit base conversions. Then choose regions and a V_{base} for each region.

$S_{base} := 15 \cdot \text{kVA}$	Region 1	The generator	$V_{base1} := 5 \cdot \text{kV}$
	Region 2	Bus1, Load 1 and the transmission lines	$V_{base2} := 138 \cdot \text{kV}$
	Region 3	Bus2 and Load 2	$V_{base3} := 360 \cdot \text{V}$
	Region 4	Bus2 and Load 3	$V_{base4} := 240 \cdot \text{V}$

b) Find I_{base} and Z_{base} in each of the regions.

Region 1	$I_{base1} := \frac{S_{base}}{\sqrt{3} \cdot V_{base1}}$	$I_{base1} = 1.732 \cdot \text{A}$	$Z_{base1} := \frac{V_{base1}^2}{S_{base}}$	$Z_{base1} = 1.667 \cdot \text{k}\Omega$
Region 2	$I_{base2} := \frac{S_{base}}{\sqrt{3} \cdot V_{base2}}$	$I_{base2} = 0.063 \cdot \text{A}$	$Z_{base2} := \frac{V_{base2}^2}{S_{base}}$	$Z_{base2} = 1.27 \cdot 10^3 \cdot \text{k}\Omega$
Region 3	$I_{base3} := \frac{S_{base}}{\sqrt{3} \cdot V_{base3}}$	$I_{base3} = 24.056 \cdot \text{A}$	$Z_{base3} := \frac{V_{base3}^2}{S_{base}}$	$Z_{base3} = 8.64 \cdot \Omega$
Region 4	$I_{base4} := \frac{S_{base}}{\sqrt{3} \cdot V_{base4}}$	$I_{base4} = 36.084 \cdot \text{A}$	$Z_{base4} := \frac{V_{base4}^2}{S_{base}}$	$Z_{base4} = 3.84 \cdot \Omega$

c) Make the necessary per-unit S_{base} conversions.


$$Z_{pu.G} := Z_{pu.G} \cdot \frac{S_{base}}{12 \cdot \text{kVA}} \quad Z_{pu.G} = 0.378j \cdot \text{pu} \quad Z_{pu.T3} := Z_{pu.T3} \cdot \frac{S_{base}}{6 \cdot \text{kVA}} \quad Z_{pu.T3} = 0.2j \cdot \text{pu}$$

d) Find the impedances of the two transmission lines and convert to pu.

$$Z_{TL1} := (8 + 24j) \cdot \frac{\Omega}{\text{km}} \cdot \text{len1} \quad Z_{TL1} = 800 + 2400j \cdot \Omega \quad Z_{TL2} := (8 + 24j) \cdot \frac{\Omega}{\text{km}} \cdot \text{len2} \quad Z_{TL2} = 400 + 1.2 \cdot 10^3 j \cdot \Omega$$

$$Z_{pu.TL1} := \frac{Z_{TL1}}{Z_{base2}} \quad Z_{pu.TL1} = 0.063 + 0.189j \cdot \% \quad Z_{pu.TL2} := \frac{Z_{TL2}}{Z_{base2}} \quad Z_{pu.TL2} = 0.032 + 0.095j \cdot \%$$

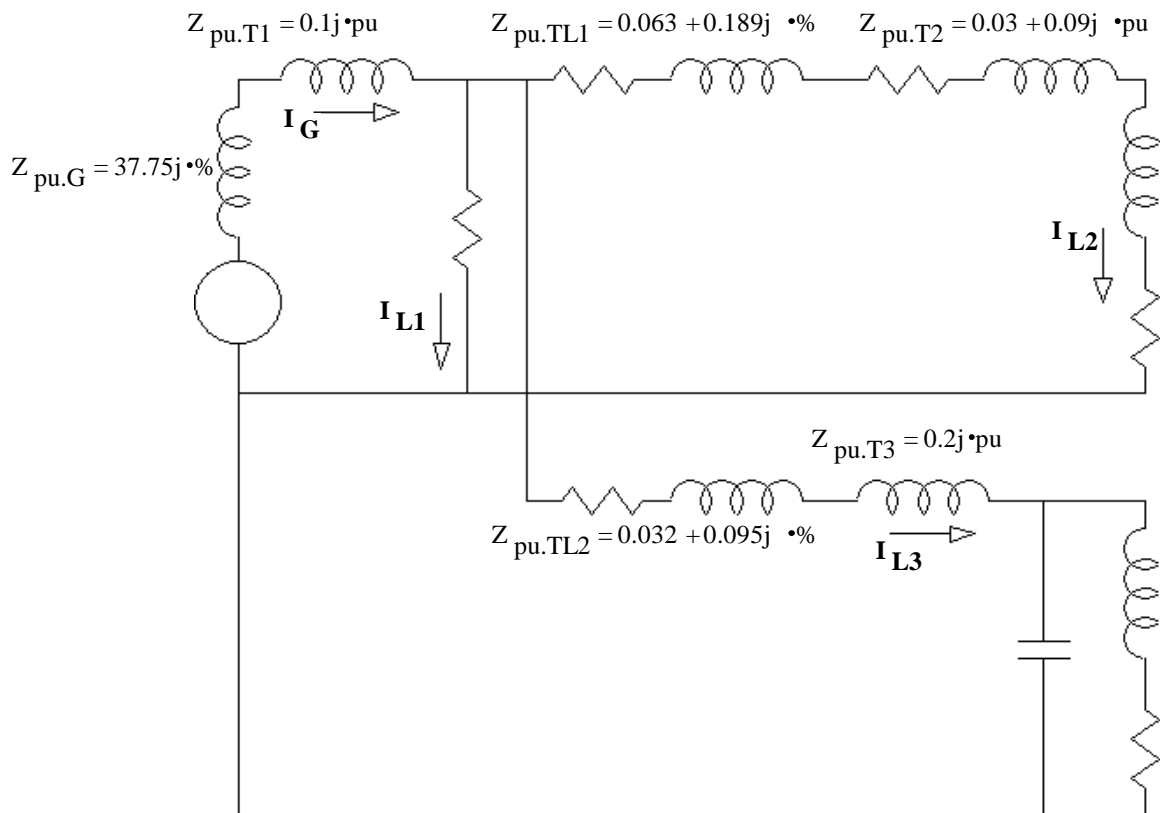e) Draw the per-phase diagram showing all the per-unit numbers found or given so far.




ALL calculations made to this point **ONLY need to be made ONCE** for this system and S_{base} !!

f) Find the pu values of the 3 loads and add that information to the per-phase diagram.

$$R_{pu.L1} := \frac{R_{L1}}{Z_{base2}} \quad R_{pu.L1} = 7.876 \cdot pu$$

$$R_{pu.L2} := \frac{R_{L2}}{Z_{base3}} \quad R_{pu.L2} = 5.787 \cdot pu \quad X_{pu.L2} := \frac{X_{L2}}{Z_{base3}} \quad X_{pu.L2} = 1.157 \cdot pu$$
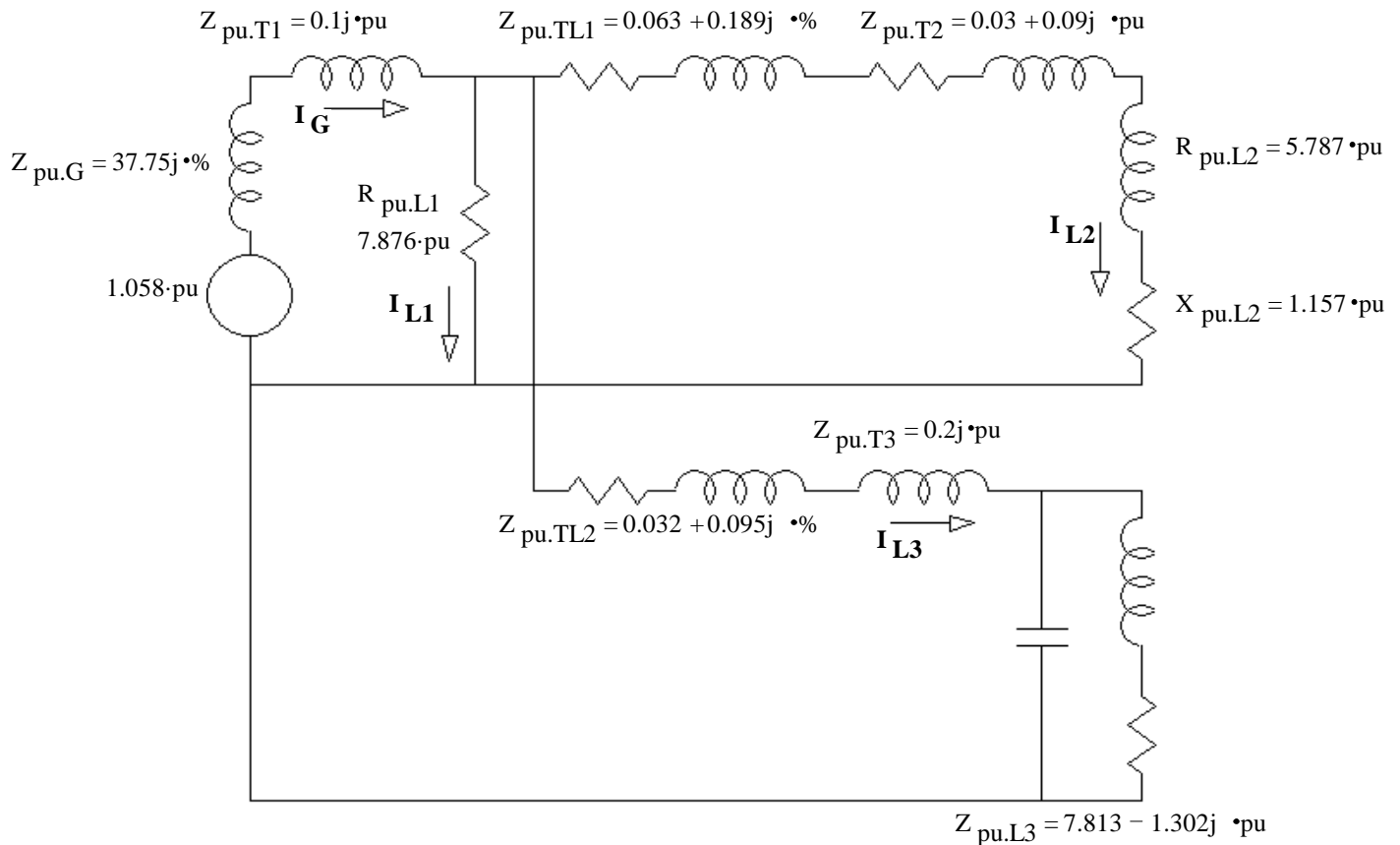
$$Z_{pu.L3} := \frac{Z_{L3}}{Z_{base4}} \quad Z_{pu.L3} = 7.813 - 1.302j \cdot pu$$



g) The line voltage at bus1 is measured and found to be $V_{bus1} := 146 \cdot kV$ Assume the phase angle is 0° .

Find all 3 load line-current magnitudes and the magnitude of the generator line-current. Please remember that you can't add magnitudes, so may need some complex values.

$$V_{pu.bus1} := \frac{146 \cdot kV}{V_{base2}} \quad V_{pu.bus1} = 1.058 \cdot pu$$

$$I_{pu.L1} := \frac{1 \cdot pu}{R_{pu.L1}} \quad I_{pu.L1} = 0.127 \cdot pu \quad |I_{pu.L1}| \cdot I_{base2} = 7.967 \cdot mA$$

$$I_{pu.L2} := \frac{V_{pu.bus1}}{Z_{pu.TL1} + Z_{pu.TL2} + (R_{pu.L2} + X_{pu.L2} \cdot j)} \quad I_{pu.L2} = 0.174 - 0.037j \cdot pu \quad |I_{pu.L2}| \cdot I_{base3} = 4.277 \cdot A$$

$$I_{pu.L3} := \frac{V_{pu.bus1} \cdot pu}{Z_{pu.TL2} + Z_{pu.TL3} + Z_{pu.L3}} \quad I_{pu.L3} = 0.133 + 0.019j \cdot pu \quad |I_{pu.L3}| \cdot I_{base4} = 4.839 \cdot A$$

$$I_{pu.G} := I_{pu.L1} + I_{pu.L2} + I_{pu.L3} \quad I_{pu.G} = 43.358 - 1.862j \cdot pu \quad |I_{pu.G}| \cdot I_{base1} = 0.752 \cdot A$$

h) Find the power delivered to Load 2, both in pu and in kW.

$$P_{\text{pu.L2}} := \left(|I_{\text{pu.L2}}| \right)^2 \cdot R_{\text{pu.L2}} \quad P_{\text{pu.L2}} = 0.183 \cdot \text{pu} \quad P_{\text{L2}} := P_{\text{pu.L2}} \cdot S_{\text{base}} \quad P_{\text{L2}} = 2.744 \cdot \text{kW}$$

i) Find the line voltage at Load 2 (magnitude).

$$V_{\text{Load2}} := |I_{\text{pu.L2}}| \cdot \sqrt{R_{\text{pu.L2}}^2 + X_{\text{pu.L2}}^2} \cdot V_{\text{base3}} \quad V_{\text{Load2}} = 377.8 \cdot \text{V}$$

j) Find the line voltage at the generator (magnitude).

$$V_{\text{pu.G}} := 1 \cdot \text{pu} + I_{\text{pu.G}} \cdot (Z_{\text{pu.G}} + Z_{\text{pu.T1}}) \quad V_{\text{pu.G}} = 100.889 + 20.703j \cdot \% \quad |V_{\text{pu.G}}| \cdot V_{\text{base1}} = 5.15 \cdot \text{kV}$$

k) The line voltage at the generator drops by 8% to: $146 \cdot \text{kV} \cdot 0.92 = 134.32 \cdot \text{kV}$

Find the magnitude of Load-3 line current and repeat parts h) and i) for this new generator voltage.

Note: It may be helpful to realize that if one voltage in the system drops by 8%, so do all the rest, and so do all the currents. Drop by 8% means multiply by 0.92. All powers drop too, but use $(0.92)^2$ as the factor.

$$|I_{\text{pu.L3}}| \cdot I_{\text{base4}} \cdot 0.92 = 4.5 \cdot \text{A} = \text{new } I_{\text{Load3}}$$

$$P_{\text{L2}} \cdot 0.92^2 = 2.323 \cdot \text{kW} = \text{new } P_{\text{L2}}$$

$$V_{\text{Load2}} \cdot 0.92 = 347.5 \cdot \text{V} = \text{new } V_{\text{Load2}}$$