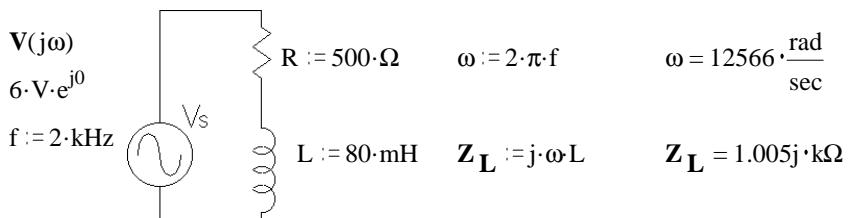


ECE 3600 Phasor Examples

Ex. 1 Find V_R , V_L , and V_C in polar phasor form. $f := 2\text{ kHz}$



$$Z_{\text{eq}} := R + j \cdot \omega L + \frac{1}{j \cdot \omega C} \quad Z_{\text{eq}} = 500 + 806.366j \cdot \Omega$$

$$\sqrt{500^2 + 806^2} = 948.491 \quad \text{atan}\left(\frac{806}{500}\right) = 58.187 \cdot \text{deg} \quad Z_{\text{eq}} = 948.5 \Omega / 58.2^\circ$$

$$\text{find the current: } I := \frac{6 \cdot V \cdot e^{j0}}{Z_{\text{eq}}}$$

$$\text{magnitude: } \frac{6 \cdot V}{948.5 \cdot \Omega} = 6.326 \cdot \text{mA}$$

$$\text{angle: } 0 \cdot \text{deg} - 58.2 \cdot \text{deg} = -58.2 \cdot \text{deg}$$

$$I = 6.326 \text{mA} / -58.2^\circ$$

find the magnitude

$$V_R := I \cdot R \quad 6.326 \cdot \text{mA} \cdot 500 \cdot \Omega = 3.163 \cdot \text{V}$$

$$-58.2 \cdot \text{deg} + 0 \cdot \text{deg} = -58.2 \cdot \text{deg}$$

$$V_R = 3.163 \text{V} / -58.2^\circ$$

$$V_L := I \cdot Z_L \quad 6.326 \cdot \text{mA} \cdot 1005 \cdot \Omega = 6.358 \cdot \text{V}$$

$$-58.2 \cdot \text{deg} + 90 \cdot \text{deg} = 31.8 \cdot \text{deg}$$

$$V_L = 6.358 \text{V} / 31.8^\circ$$

$$V_C := I \cdot Z_C \quad 6.326 \cdot \text{mA} \cdot (-199) \cdot \Omega = -1.259 \cdot \text{V}$$

$$-58.2 \cdot \text{deg} + (90) \cdot \text{deg} = 31.8 \cdot \text{deg}$$

$$V_C = -1.259 \text{V} / 31.8^\circ$$

$$\text{OR: } 6.326 \cdot \text{mA} \cdot (199) \cdot \Omega = 1.259 \cdot \text{V}$$

$$-58.2 \cdot \text{deg} + (-90) \cdot \text{deg} = -148.2 \cdot \text{deg}$$

$$V_C = 1.259 \text{V} / -148.2^\circ$$

OR, you can also find these voltages directly, using a voltage divider. I.E. to find V_C directly:

$$V_C := \frac{\frac{1}{j \cdot \omega C}}{R + j \cdot \omega L + \frac{1}{j \cdot \omega C}} \cdot 6 \cdot V = \frac{1}{R \cdot (j \cdot \omega C) + j \cdot \omega L \cdot (j \cdot \omega C) + 1} \cdot 6 \cdot V = \frac{1}{R \cdot (j \cdot \omega C) - \omega^2 \cdot L \cdot C + 1} \cdot 6 \cdot V$$

$$= \frac{1}{(1 - \omega^2 \cdot L \cdot C) + j \cdot \omega R \cdot C} \cdot 6 \cdot V \quad (1 - \omega^2 \cdot L \cdot C) = -4.053 \quad j \cdot \omega R \cdot C = 2.513j$$

$$= \frac{6 \cdot V}{-4.053 + 2.513j} \cdot \frac{(-4.053 - 2.513j)}{(-4.053 - 2.513j)} = \frac{6 \cdot V \cdot (-4.053 - 2.513j)}{(-4.053)^2 + 2.513^2}$$

$$6 \cdot V \cdot (-4.053 - 2.513j) = -24.318 - 15.078j \cdot \text{V}$$

$$(-4.053)^2 + 2.513^2 = 22.742$$

$$= \left(\frac{-24.318}{22.742} - \frac{15.078j}{22.742} \right) \cdot V = -1.069 - 0.663j \cdot \text{V}$$



$$\text{magnitude: } \sqrt{1.069^2 + 0.663^2} = 1.258$$

$$\text{angle: } \text{atan}\left(\frac{-0.663}{-1.069}\right) = 31.81 \cdot \text{deg}$$

but this is actually in the third quadrant,
so modify your calculator's results:

$$31.81 \cdot \text{deg} - 180 \cdot \text{deg} = -148.19 \cdot \text{deg}$$

$$= 1.258 \text{V} / -148.2^\circ$$

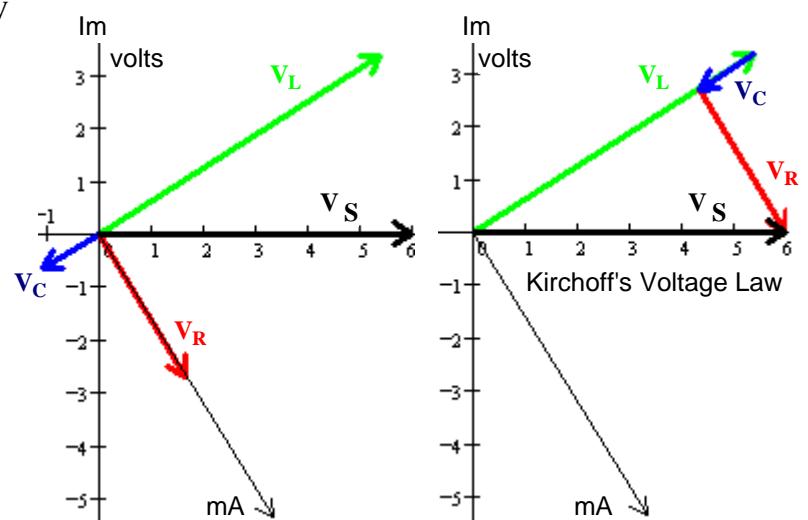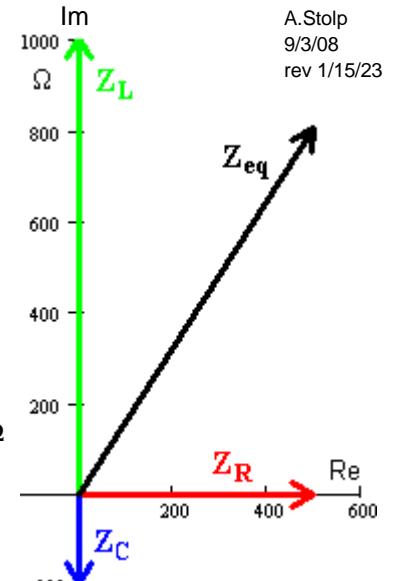


ECE 3600 Phasor Examples p2

Ex. 2 a) Find Z_{eq} . $f := 2.5 \cdot kHz$ $\omega := 2\pi f$ $\omega = 15708 \frac{rad}{sec}$

$$Z_{eq} = j\omega L_1 + \frac{1}{\frac{1}{R+j\omega L_2} + \frac{1}{j\omega C}} = j\omega L_1 + \frac{1}{\frac{1}{R+j\omega L_2} + j\omega C}$$

$$j\omega C = 15.708j \cdot mS$$

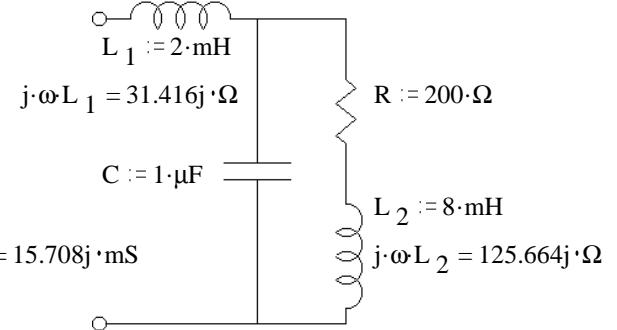

$$Z_{eq} := j\omega L_1 + \frac{1}{\frac{1}{R+j\omega L_2} + j\omega C} = 31.416j \cdot \Omega + \frac{1}{\frac{1}{(200+125.664j)\cdot\Omega} + 15.708j \cdot mS}$$

$$= 31.416j \cdot \Omega + \frac{1}{(3.585 - 2.252j + 15.708j) \cdot mS} = 31.416j \cdot \Omega + (18.487 - 69.391j) \cdot \Omega = 18.487 - 37.975j \cdot \Omega$$

$$|Z_{eq}| = 42.238 \cdot \Omega \quad \arg(Z_{eq}) = -64.043 \cdot deg$$

b) $V_{in} := 12 \cdot V \cdot e^{j \cdot 20 \cdot deg}$ Find I_{L1}, V_C $I_{L1} := \frac{V_{in}}{Z_{eq}}$ $\frac{12 \cdot V}{42.238 \cdot \Omega} = 284.1 \cdot mA$ $20 \cdot deg - (-64.04) \cdot deg = 84.04 \cdot deg$

$$I_{L1} = 284.1 \cdot mA / 84.04^\circ = 284.1 \cdot mA \cdot e^{j \cdot 84.04 \cdot deg} \quad I_{L1} = 29.485 + 282.569j \cdot mA$$

$$V_C := I_{L1} \cdot (18.486 - 69.384j) \cdot \Omega \quad 284.1 \cdot mA \cdot \sqrt{18.486^2 + 69.384^2} \cdot \Omega = 20.4 \cdot V \quad 84.04 \cdot deg + \text{atan}\left(\frac{-69.384}{18.486}\right) = 8.959 \cdot deg$$

To find V_C directly: $V_C = 20.4V / 8.96^\circ$

$$V_C := \frac{\frac{1}{R+j\omega L_2}}{\frac{1}{j\omega L_1} + \frac{1}{R+j\omega L_2}} \cdot V_{in} = \frac{1}{j\omega L_1 \cdot \left(\frac{1}{R+j\omega L_2} + j\omega C \right) + 1} \cdot V_{in} \quad V_C = 20.153 + 3.178j \cdot V$$

You could then use another voltage divider to find V_R or V_{L2} .

c) Find I_{L2} $I_{L2} := \frac{V_C}{R+j\omega L_2} = \frac{20.4 \cdot V \cdot e^{j \cdot 8.96 \cdot deg}}{236.202 \cdot \Omega \cdot e^{j \cdot 32.142 \cdot deg}} = \frac{20.4 \cdot V}{236.202 \cdot \Omega} / 8.96 - 32.142^\circ = 86.4mA / -23.18^\circ$

Or, directly by Current divider: $I_{L2} := \frac{\frac{1}{R+j\omega L_2}}{\frac{1}{j\omega C} + \frac{1}{R+j\omega L_2}} \cdot I_{L1} = \frac{1}{j\omega C \cdot (R + j\omega L_2) + 1} \cdot I_{L1} = 79.404 - 34.001j \cdot mA$

d) How about I_C ? $I_C := \frac{V_C}{\left(\frac{1}{j\omega C}\right)} = V_C \cdot j\omega C = 20.4V / 8.96^\circ \cdot 15.708mS / 90^\circ = 320mA / 98.96^\circ$

Or, directly by Current divider: $I_C := \frac{j\omega C}{j\omega C + \frac{1}{R+j\omega L_2}} \cdot I_{L1}$

This current is greater than the input current. What's going on?

The angle between I_C & I_{L2} is big enough that they somewhat cancel each other out, partial resonance.

Check Kirchoff's Current Law: $I_C + I_{L2} = 29.485 + 282.569j \cdot mA = I_{L1} = 29.485 + 282.569j \cdot mA$

ECE 3600 Phasor Examples p2

ECE 3600 Phasor Examples p3


Ex. 3 a) Find Z_2 .

$$I := 25 \cdot \text{mA} \cdot e^{j \cdot 10^\circ}$$

$$V_{\text{in}} := 10 \cdot \text{V} \cdot e^{-j \cdot 20^\circ}$$

$$Z_T := \frac{V_{\text{in}}}{I} = \frac{10 \cdot \text{V}}{25 \cdot \text{mA}} / -20^\circ = 400 \Omega / -30^\circ$$

$$Z_T = 346.41 - 200j \Omega$$

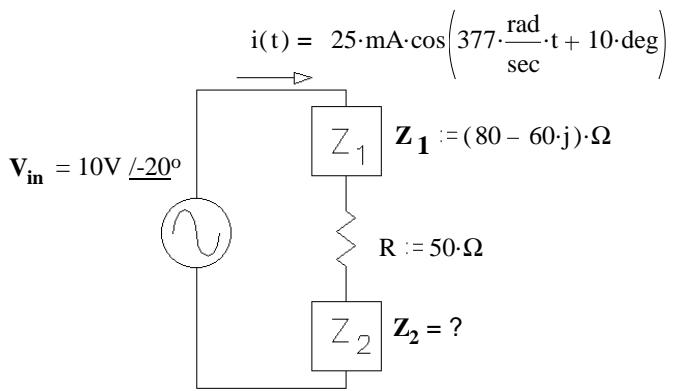

$$Z_2 := Z_T - R - Z_1 = (346.41 - 200j) \cdot \Omega - 50 \cdot \Omega - (80 - 60j) \cdot \Omega = 216.41 - 140j \Omega$$


- b) Circle 1: i) The source current leads the source voltage <--- answer, because $10^\circ > -20^\circ$.
ii) The source voltage leads the source current

Ex. 4 a) The impedance Z_1 (above) is made of two components in series. What are they and what are their values?

$$Z_1 = 80 - 60j \Omega \quad \omega := 377 \cdot \frac{\text{rad}}{\text{sec}}$$


Must have a resistor because there is a real part.

$$R := \text{Re}(Z_1)$$

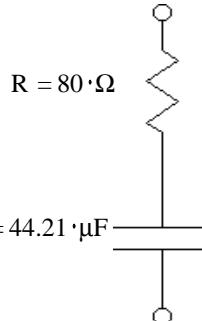

Must have a capacitor because the imaginary part is negative.
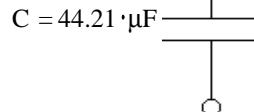
$$\text{Im}(Z_1) = -60 \cdot \Omega = \frac{-1}{\omega C} \quad C := \frac{-1}{\omega \text{Im}(Z_1)}$$



b) The impedance Z_1 is made of two components in parallel. What are they and what are their values?

$$Z_1 = 80 - 60j \Omega$$

Must have a resistor because there is a real part.

Must have a capacitor because the imaginary part is negative.

$$Z_1 = \frac{1}{\frac{1}{R} + j \cdot \omega C} \quad \frac{1}{Z_1} = \frac{1}{(80 - 60j) \cdot \Omega} \cdot \frac{(80 + 60j)}{(80 + 60j)} = \frac{80 + 60j}{80^2 + 60^2} = \frac{80 + 60j}{10,000} \cdot \frac{1}{\Omega}$$

$$80^2 + 60^2 = 10000$$

$$\frac{1}{Z_1} = 8 + 6j \text{ mS} = 0.008 + 0.006j \frac{1}{\Omega} = \frac{1}{R} + j \cdot \omega C$$

$$\frac{1}{R} = 0.008 \cdot \frac{1}{\Omega}$$


$$R := \frac{1}{0.008 \cdot \frac{1}{\Omega}}$$

$$R = 125 \cdot \Omega$$

$$\omega C = 0.006 \cdot \frac{1}{\Omega}$$

$$C := \frac{0.006 \cdot \frac{1}{\Omega}}{\omega}$$

$$C = 15.915 \cdot \mu\text{F}$$

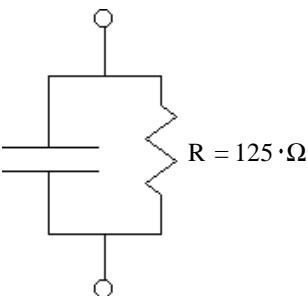


ECE 3600 Phasor Examples p4

Ex. 5 a) Find V_{in} in polar form.

$$I_Z := 100 \cdot \text{mA} \quad Z := (40 + 60 \cdot j) \cdot \Omega$$

$$V_{in} := I_Z \cdot Z \quad V_{in} = 4 + 6j \cdot \text{V}$$
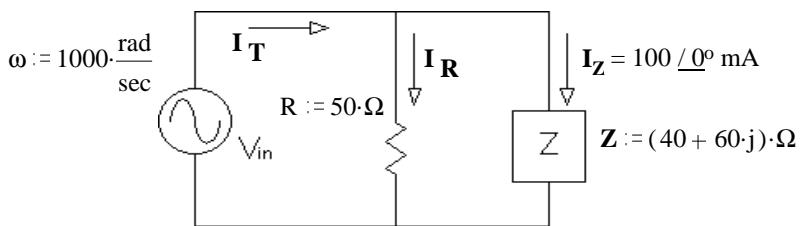
$$\sqrt{4^2 + 6^2} = 7.211 \quad \text{atan}\left(\frac{6}{4}\right) = 56.31^\circ \text{deg} \quad V_{in} = 7.21 \text{V} / -56.3^\circ$$



b) Find I_T in polar form. $I_R := \frac{V_{in}}{R} = \frac{(4 + 6j) \cdot \text{V}}{50 \cdot \Omega} = \frac{4 \cdot \text{V}}{50 \cdot \Omega} + \frac{6j \cdot \text{V}}{50 \cdot \Omega} = 80 + 120j \cdot \text{mA}$

$$I_T := I_R + I_Z = (80 + 120j) \cdot \text{mA} + 100 \cdot \text{mA} = 180 + 120j \cdot \text{mA}$$

$$|I_T| = 216.3 \cdot \text{mA} \quad \arg(I_T) = 33.69^\circ \text{deg} \quad I_T = 216.3 \text{mA} / 33.7^\circ$$


c) Circle 1: i) I_T leads V_{in} ii) V_{in} leads I_T answer ii), $56.3^\circ > 33.7^\circ$

Ex. 6 You need to design a circuit in which the the "output" voltage leads the input voltage ($v_S(t)$) by 30° of phase.

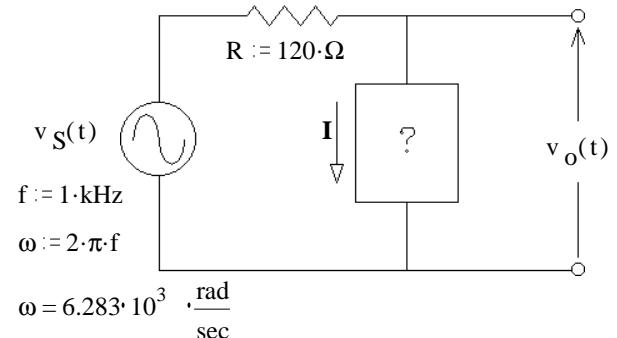a) What should go in the box: R, L, C?

$$V_o = \frac{Z_{\text{box}}}{R + Z_{\text{box}}} \cdot V_S$$

$$\text{angle of } \frac{Z_{\text{box}}}{R + Z_{\text{box}}} \text{ is } 30^\circ.$$



This can only happen if the angle of Z_{box} is positive, so Z_{box} is a inductor

b) Find its value. $V_o = V_o = \frac{j \cdot \omega L}{R + j \cdot \omega L} \cdot V_S \quad \text{angle: } \frac{j \cdot \omega L}{R + j \cdot \omega L} \text{ is } 90^\circ - \text{atan}\left(\frac{\omega L}{R}\right) = 30^\circ \quad \text{so } \text{atan}\left(\frac{\omega L}{R}\right) = 60^\circ.$


$$\frac{\omega L}{R} = \tan(60^\circ \text{deg}) = 1.732 \quad L := \frac{R \cdot 1.732}{\omega} \quad L = 33.1 \cdot \text{mH}$$

Ex. 7 You need to design a circuit in which the the "output" voltage lags the input voltage ($v_S(t)$) by 40° of phase.

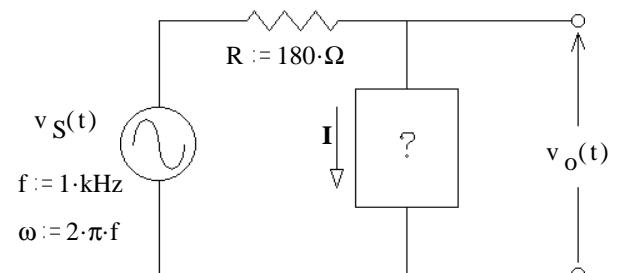a) What should go in the box: R, L, C?

$$V_o = \frac{Z_{\text{box}}}{R + Z_{\text{box}}} \cdot V_S$$

$$\text{angle of } \frac{Z_{\text{box}}}{R + Z_{\text{box}}} \text{ is } -40^\circ.$$



This can only happen if the angle of Z_{box} is negative, so Z_{box} is a capacitor

b) Find its value. $V_o = \frac{1}{j \cdot \omega C} \cdot V_S \quad \text{angle: } \frac{1}{j \cdot \omega C} \text{ is } -90^\circ - \text{atan}\left(\frac{-1}{\omega C}\right) = -90^\circ - \text{atan}\left(-\frac{1}{\omega C \cdot R}\right) \quad \text{so } \text{atan}\left(-\frac{1}{\omega C \cdot R}\right) = -50^\circ$

$$-\frac{1}{\omega C \cdot R} = \tan(-50^\circ \text{deg}) = -1.192 \quad C := \frac{1}{\omega R \cdot 1.192} \quad C = 0.742 \cdot \mu\text{F}$$

ECE 3600 Phasor Examples p5

Ex. 8 The magnitudes of \mathbf{I}_1 and \mathbf{I}_2 are 3A and 2A. They lag the supply voltage by 20° and 30° , respectively.

a) Find the values of R_1 , R_2 , X_1 and X_2 .

$$\mathbf{Z}_1 := \frac{120 \cdot V}{3 \cdot A \cdot e^{-j \cdot 20^\circ \text{deg}}}$$

$$\mathbf{Z}_1 = 37.588 + 13.681j \cdot \Omega$$

$$R_1 := \operatorname{Re}(\mathbf{Z}_1)$$

$$R_1 = 37.588 \cdot \Omega$$

$$X_1 := \operatorname{Im}(\mathbf{Z}_1)$$

$$X_1 = 13.681 \cdot \Omega$$

$$\mathbf{Z}_2 := \frac{120 \cdot V}{2 \cdot A \cdot e^{-j \cdot 30^\circ \text{deg}}}$$

$$\mathbf{Z}_2 = 51.962 + 30j \cdot \Omega$$

$$R_2 := \operatorname{Re}(\mathbf{Z}_2)$$

$$R_2 = 51.962 \cdot \Omega$$

$$X_2 := \operatorname{Im}(\mathbf{Z}_2)$$

$$X_2 = 30 \cdot \Omega$$

b) Add C to the circuit such that \mathbf{I}_{1C} leads \mathbf{I}_2 by 90° . Find the value of C.

$$\omega := 2 \cdot \pi \cdot 60 \cdot \text{Hz}$$


$$\mathbf{I}_{1C} = \frac{120 \cdot V}{R_1 + j \cdot X_1 + j \cdot X_C} \quad \text{needs to be at an angle of } +50^\circ$$

$$\text{So: } \operatorname{atan}\left(\frac{X_1 + X_C}{R_1}\right) = -50^\circ \text{deg}$$

$$\frac{X_1 + X_C}{R_1} = \tan(-50^\circ \text{deg})$$

$$X_C := R_1 \cdot \tan(-50^\circ \text{deg}) - X_1 \quad X_C = -58.476 \cdot \Omega = \frac{-1}{\omega C}$$
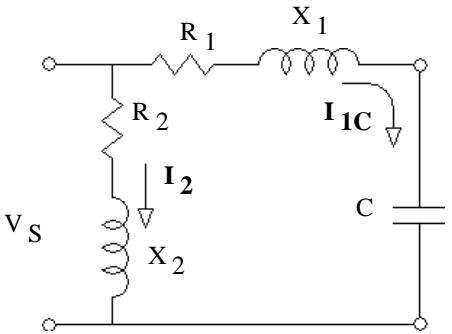
$$C := \frac{-1}{\omega X_C} \quad C = 45.4 \cdot \mu\text{F}$$



c) Change C so that the magnitudes of \mathbf{I}_{1C} and \mathbf{I}_2 are the same. Find the new C.

$$|\mathbf{I}_{1C}| = \left| \frac{120 \cdot V}{R_1 + j \cdot X_1 + j \cdot X_C} \right| \quad \text{needs to be } 2\text{A} \quad \text{So: } |R_1 + j \cdot X_1 + j \cdot X_C| = 60 \cdot \Omega$$

$$\sqrt{R_1^2 + (X_1 + X_C)^2} = 60 \cdot \Omega$$

$$(X_1 + X_C) = \sqrt{(60 \cdot \Omega)^2 - R_1^2} = 46.767 \cdot \Omega$$


$$X_C := \sqrt{(60 \cdot \Omega)^2 - R_1^2} - X_1 \quad X_C = 33.086 \cdot \Omega = \frac{-1}{\omega C} \quad \text{NOT POSSIBLE}$$



$$\text{So: } (X_1 + X_C) = -46.767 \cdot \Omega$$

$$\text{And: } X_C := -\sqrt{(60 \cdot \Omega)^2 - R_1^2} - X_1 \quad X_C = -60.448 \cdot \Omega = \frac{-1}{\omega C} \quad C := \frac{-1}{\omega X_C} \quad C = 43.9 \cdot \mu\text{F}$$


You'll use a very similar method to find start- and run- capacitors for single-phase induction motors.

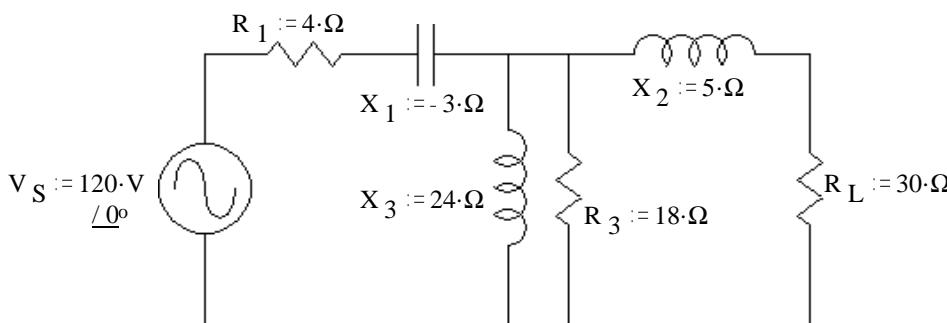Ex. 9 a) In the circuit below R_L is the load resistor. Find and draw the Thevenin equivalent of the rest of the circuit.



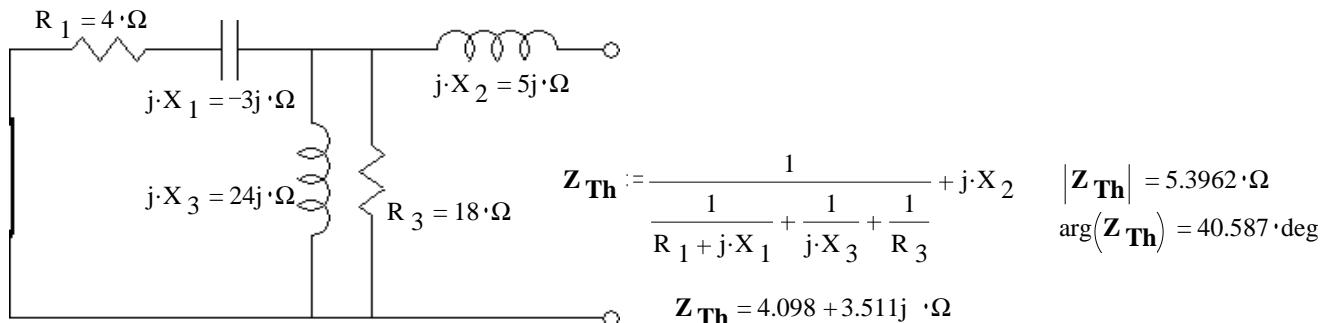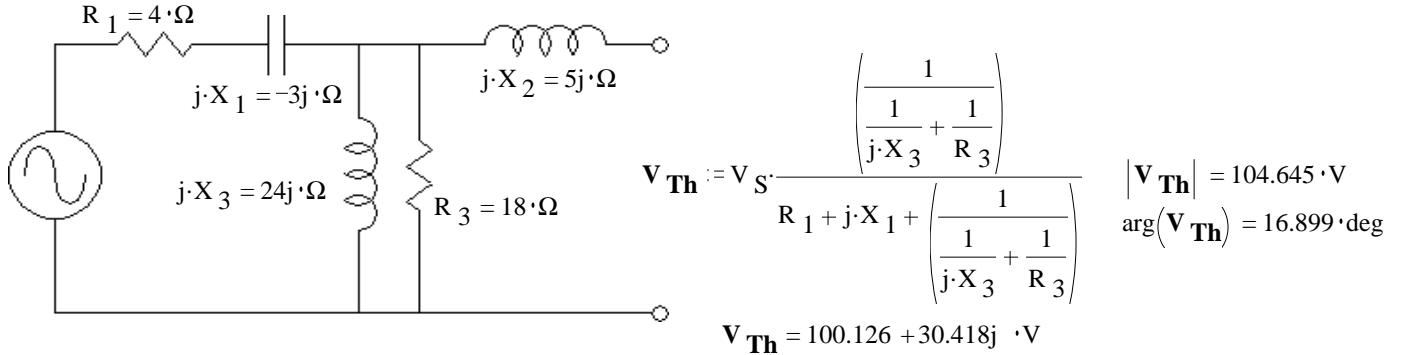

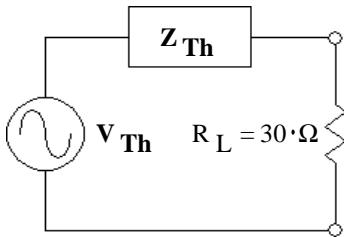- b) Use the Thevenin equivalent to find the current through the load resistor and the voltage across the load resistor.



$$I_{RL} := \frac{V_{Th}}{Z_{Th} + R_L} \quad I_{RL} = 2.997 + 0.584j \cdot A$$

$$|I_{RL}| = 3.053 \cdot A \quad \arg(I_{RL}) = 11.02 \cdot \text{deg}$$

$$V_{RL} := I_{RL} \cdot R_L \quad V_{RL} = 89.895 + 17.507j \cdot V$$

$$|V_{RL}| = 91.584 \cdot V \quad \arg(V_{RL}) = 11.02 \cdot \text{deg}$$

- c) Find a replacement for R_L in order to maximize the power delivered to R_L .

$$R_L := |Z_{Th}| \quad R_L = 5.396 \cdot \Omega$$

- d) Find the new current and voltage for the load resistor.

$$I_{RL} := \frac{V_{Th}}{Z_{Th} + R_L} \quad I_{RL} = 10.32 - 0.612j \cdot A \quad |I_{RL}| = 10.338 \cdot A \quad \arg(I_{RL}) = -3.395 \cdot \text{deg}$$

$$V_{RL} := I_{RL} \cdot R_L \quad V_{RL} = 55.687 - 3.303j \cdot V \quad |V_{RL}| = 55.785 \cdot V \quad \arg(V_{RL}) = -3.395 \cdot \text{deg}$$

You'll use a Thevenin equivalent circuit to analyze induction motors.

Ex. 10 The circuit shown has two sources. The current source is DC and the voltage source is 60Hz.


Using superposition, find the nodal voltage $v_A(t)$. Be sure to redraw the circuit twice as part of your solution.

$$v_A(t) = ?$$

$$\omega := 2 \cdot \pi \cdot 60 \cdot \text{Hz}$$

$$I_S := 200 \cdot \text{mA}$$

DC

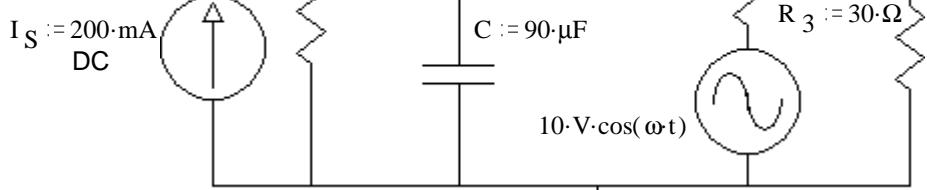

Eliminate voltage source


$$R_{eq} := \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

$$V_{A,Is} := I_S \cdot R_{eq}$$

$$V_{A,Is} = 2 \cdot V$$

$$R_{eq} = 10 \cdot \Omega$$

$$I_S = 200 \cdot mA$$

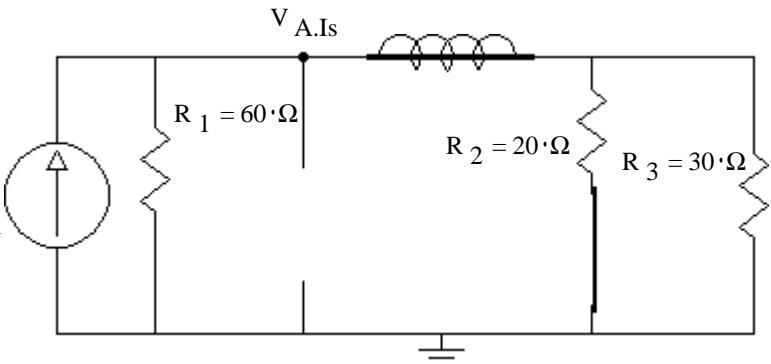

Eliminate current source

Let's use nodal analysis

node A

$$I_L = I_1 + I_C$$

$$\frac{V_B - V_A}{j \cdot \omega L} = \frac{V_A}{R_1} + V_A \cdot j \cdot \omega C$$

$$V_B - V_A = \left(\frac{V_A}{R_1} + V_A \cdot j \cdot \omega C \right) \cdot (j \cdot \omega L) \quad j \cdot \omega L = 11.31j \cdot \Omega$$

$$V_B = \left(\frac{V_A}{R_1} + V_A \cdot j \cdot \omega C \right) \cdot j \cdot \omega L + V_A \quad j \cdot \omega C = 33.929j \cdot mS$$

node B

$$I_2 = I_L + I_3$$

$$\frac{V_S - V_B}{R_2} = \frac{V_B - V_A}{j \cdot \omega L} + \frac{V_B}{R_3}$$

$$\frac{V_S + V_A}{R_2 + j \cdot \omega L} = V_B \cdot \left(\frac{1}{j \cdot \omega L} + \frac{1}{R_3} + \frac{1}{R_2} \right) = V_B \cdot (83.333 - 88.419j) \cdot mS = V_B \cdot 121.5 \cdot mS \cdot e^{-46.696 \cdot \frac{\pi}{180} j}$$

$$V_B = \frac{V_S}{R_2 \left(\frac{1}{j \cdot \omega L} + \frac{1}{R_3} + \frac{1}{R_2} \right)} + \frac{V_A}{j \cdot \omega L \left(\frac{1}{j \cdot \omega L} + \frac{1}{R_3} + \frac{1}{R_2} \right)} = \left(\frac{V_A}{R_1} + V_A \cdot j \cdot \omega C \right) \cdot j \cdot \omega L + V_A$$

Equate to node A equation:

$$\begin{aligned} \frac{V_S}{R_2 \left(\frac{1}{j \cdot \omega L} + \frac{1}{R_3} + \frac{1}{R_2} \right)} &= \left(\frac{V_A}{R_1} + V_A \cdot j \cdot \omega C \right) \cdot j \cdot \omega L + V_A - \frac{V_A}{1 + j \cdot \omega L \left(\frac{1}{R_3} + \frac{1}{R_2} \right)} \\ &= V_A \cdot \left[\left(\frac{1}{R_1} + j \cdot \omega C \right) \cdot j \cdot \omega L + 1 - \frac{1}{1 + j \cdot \omega L \left(\frac{1}{R_3} + \frac{1}{R_2} \right)} \right] \end{aligned}$$

$$1 + j \cdot \omega L \left(\frac{1}{R_3} + \frac{1}{R_2} \right) = 1 + 0.942j$$

$$\left(\frac{1}{R_1} + j \cdot \omega C \right) \cdot j \cdot \omega L = -0.384 + 0.188j$$

$$\begin{aligned} V_A &:= \frac{V_S}{R_2 \left(\frac{1}{j \cdot \omega L} + \frac{1}{R_3} + \frac{1}{R_2} \right)} \cdot \frac{1}{\left[\left(\frac{1}{R_1} + j \cdot \omega C \right) \cdot j \cdot \omega L + 1 - \frac{1}{1 + j \cdot \omega L \left(\frac{1}{R_3} + \frac{1}{R_2} \right)} \right]} \\ &= \frac{V_S}{R_2 \cdot 121.5 \cdot mS \cdot e^{-j \cdot 46.696 \cdot \text{deg}} \cdot \left[(-0.384 + 0.188j) + 1 - \frac{1}{1 + 0.942j} \right]} \end{aligned}$$

$$V_A = 4.796 - 3.5j \cdot V$$

$$|V_A| = 5.938 \cdot V \quad \arg(V_A) = -36.12 \cdot \text{deg}$$

$$V_A \cdot V_S = 5.938 \cdot V \cdot \cos(377 \cdot t - 36.1 \cdot \text{deg})$$


Add the results $v_A(t) = 2 \cdot V + 5.938 \cdot V \cdot \cos(377 \cdot t - 36.1 \cdot \text{deg})$

Ex. 11 The circuit shown has two sources. The frequency of the current source is the third harmonic of the voltage source.

Using superposition, find the voltage across R_4 . Be sure to redraw the circuit twice as part of your solution.

$$v_{R4}(t) = ?$$
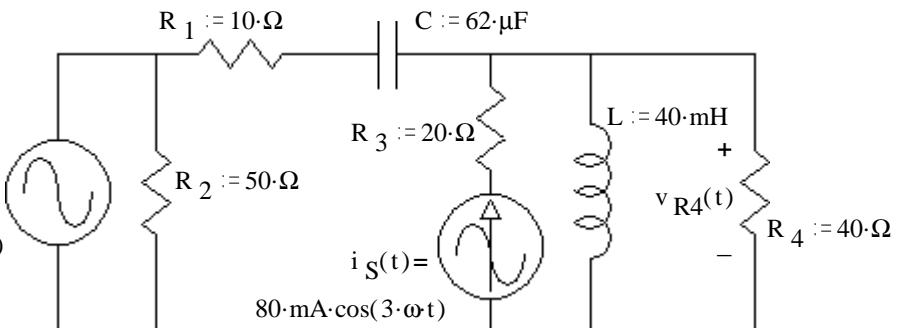
$$\begin{aligned} v_S(t) &:= 10 \cdot V \cdot \cos(\omega t) \\ f &:= 60 \cdot \text{Hz} \\ \omega &:= 2 \cdot \pi \cdot f \end{aligned}$$



Eliminate current source

$$\begin{aligned} R_1 &= 10 \cdot \Omega & Z_C &= \frac{1}{j \cdot \omega C} = -42.784j \cdot \Omega \\ C &= 62 \cdot \mu\text{F} & L &= 40 \cdot \text{mH} \\ v_S &:= 10 \cdot \text{V} & V_{R4.Vs} &:= v_S \cdot \frac{\frac{1}{j \cdot \omega L + R_4}}{R_1 + \frac{1}{j \cdot \omega C} + \frac{1}{j \cdot \omega L + R_4}} \\ Z_L &= j \cdot \omega L = 15.08j \cdot \Omega & V_{R4.Vs} &= -2.875 + 3.138j \cdot \text{V} \\ && |V_{R4.Vs}| &= 4.256 \cdot \text{V} \quad \arg(V_{R4.Vs}) = 132.5^\circ \text{deg} \\ && v_{R4.Vs}(t) &:= 4.256 \cdot \text{V} \cdot \cos(\omega t + 132.5^\circ \text{deg}) \end{aligned}$$


Eliminate voltage source

$$\begin{aligned} R_1 &= 10 \cdot \Omega & Z_C &= \frac{1}{j \cdot 3 \cdot \omega C} = -14.261j \cdot \Omega \\ C &= 62 \cdot \mu\text{F} & L &= 40 \cdot \text{mH} \\ I_S &:= 80 \cdot \text{mA} & R_4 &= 40 \cdot \Omega \\ v_R &:= 10 \cdot \text{V} & V_{R4.Is} &:= I_S \cdot \frac{1}{R_1 + \frac{1}{j \cdot 3 \cdot \omega C} + \frac{1}{j \cdot \omega L + R_4}} \\ Z_L &= j \cdot 3 \cdot \omega L = 45.239j \cdot \Omega & V_{R4.Is} &= 1.165 - 0.501j \cdot \text{V} \\ && |V_{R4.Is}| &= 1.268 \cdot \text{V} \quad \arg(V_{R4.Is}) = -23.25^\circ \text{deg} \\ && v_{R4.Is}(t) &:= 1.268 \cdot \text{V} \cdot \cos(3 \cdot \omega t - 23.25^\circ \text{deg}) \end{aligned}$$

Add the results

$$v_{R4}(t) := 4.256 \cdot \text{V} \cdot \cos(\omega t + 132.5^\circ \text{deg}) + 1.268 \cdot \text{V} \cdot \cos(3 \cdot \omega t - 23.25^\circ \text{deg})$$

$$t := 0, .2..30$$

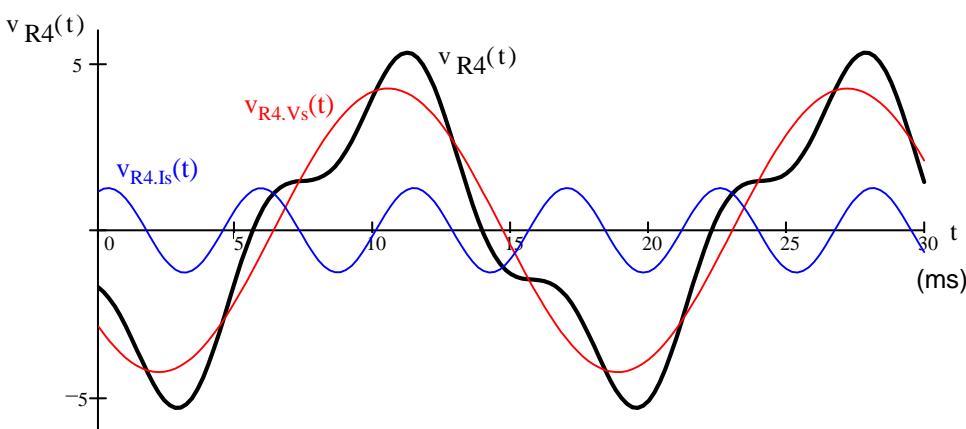

3rd harmonics like this are caused by iron cores used in transformers and motors.

Nodal analysis is used in power flow calculations

A variation of superposition is used to analyze faults on transmission lines.