

Long-length Lines: over 240 km (150 miles)

(over 200 mi in some texts)

Need:

		<u>Units</u>			
line length:	len , d	m or km		stick to the same unit length for all parameters miles may also be used	
Resistance per unit length:	r	$\frac{\Omega}{m}$ or $\frac{\Omega}{km}$			
Inductance per unit length:	l	$\frac{H}{m}$ or $\frac{H}{km}$	OR	Inductive reactance per unit length:	x $\frac{\Omega}{m}$ or $\frac{\Omega}{km}$
Capacitance per unit length:	c	$\frac{F}{m}$ or $\frac{F}{km}$	OR	Capacitance admittance per unit length:	y $\frac{S}{m}$ or $\frac{S}{km}$
Conductance to ground:	g	$\frac{S}{m}$ or $\frac{S}{km}$		Common assumption: g := 0 · $\frac{S}{km}$	S := siemens

Find:

		<u>Units</u>
Surge impedance:	$Z_c = \frac{\sqrt{j \cdot x + r}}{\sqrt{j \cdot y + g}}$	Ω
Propagation constant:	$\gamma = \sqrt{(j \cdot x + r) \cdot (j \cdot y + g)}$	$\frac{1}{m}$ or $\frac{1}{km}$

If your calculator doesn't have hyperbolic trig functions

Series impedance $Z_{series} = Z_c \cdot \sinh(\gamma \cdot len) = Z_c \cdot \frac{e^{\gamma \cdot len} - e^{-\gamma \cdot len}}{2}$ Ω

Shunt admittance: $\frac{Y_{shunt}}{2} = \frac{1}{Z_c} \cdot \tanh\left(\gamma \frac{len}{2}\right) = \frac{1}{Z_c} \cdot \frac{e^{\frac{\gamma \cdot len}{2}} - e^{-\frac{\gamma \cdot len}{2}}}{e^{\frac{\gamma \cdot len}{2}} + e^{-\frac{\gamma \cdot len}{2}}} = \frac{1}{Z_c} \cdot \frac{\sqrt{e^{\gamma \cdot len}} - \sqrt{e^{-(\gamma \cdot len)}}}{\sqrt{e^{\gamma \cdot len}} + \sqrt{e^{-(\gamma \cdot len)}}}$ Ω


OR

Shunt impedance: $2 \cdot Z_{shunt} = \frac{Z_c}{\tanh\left(\gamma \frac{len}{2}\right)}$ S or $\frac{1}{\Omega}$

If your calculator can't handle complex exponents

$$e^{(a+b \cdot j)} = e^a \cdot e^{b \cdot j} = e^a / b \text{ (in radians)}$$

Model:

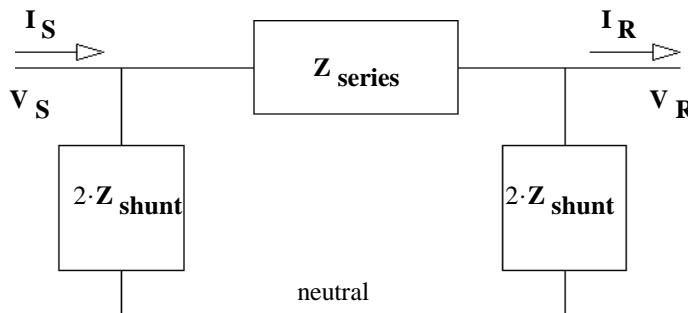

Medium-length Lines: 80 - 240 km (50 to 150 miles)


(100 - 200 mi in some texts)

Need:


		<u>Units</u>		
line length:	len , d	m or km		stick to the same unit length for all parameters miles may also be used
Resistance per unit length:	r	$\frac{\Omega}{m}$ or $\frac{\Omega}{km}$		
Inductance per unit length:	l	$\frac{H}{m}$ or $\frac{H}{km}$	OR	Inductive reactance per unit length: x $\frac{\Omega}{m}$ or $\frac{\Omega}{km}$
Capacitance per unit length:	c	$\frac{F}{m}$ or $\frac{F}{km}$	OR	Capacitance admittance per unit length: y $\frac{S}{m}$ or $\frac{S}{km}$
Conductance to ground:	g	$\frac{S}{m}$ or $\frac{S}{km}$		Common assumption: $g := 0 \cdot \frac{S}{km}$

Find:

		<u>Units</u>
Surge Impedance:	$Z_c = \sqrt{\frac{x}{y}}$	Ω
Series Resistance:	$R_{line} = r \cdot len$	Ω
Series impedance	$Z_{series} = (r + j \cdot x) \cdot len$	Ω
Shunt admittance:	$\frac{Y_{shunt}}{2} = j \cdot y \cdot \frac{len}{2}$	S or $\frac{1}{\Omega}$
OR		
Shunt impedance:	$2 \cdot Z_{shunt} = \frac{2}{j \cdot y \cdot len}$	Ω

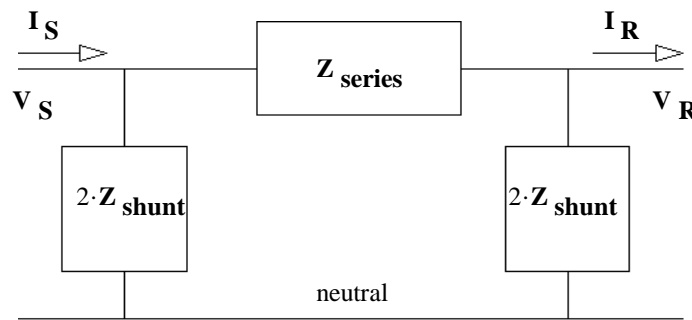


OR:

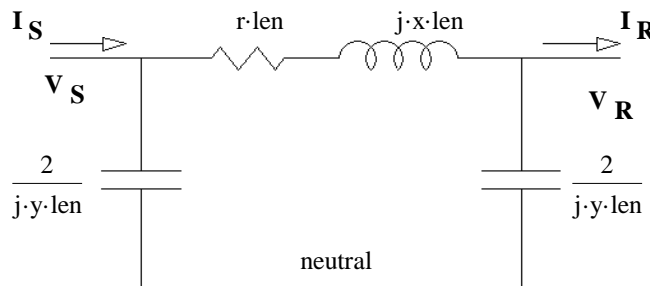

Short-length Lines: less than 80km (50 mi)
(less than 100 mi in some texts)

Same as above but without the capacitors

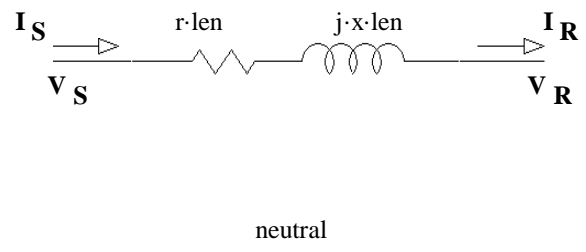

ECE 3600 Transmission Line Examples

b

Ex1. A 500 kV transmission line is 500 km long and has the line parameters shown below. Use the long-length model to find V_S and I_S if the line is loaded to 900 MVA and $|V_{RLL}|$ is 490 kV. Assume the phase angle of V_R is 0° and assume load $pf = 1$.

$$\begin{aligned} \text{len} &:= 500 \cdot \text{km} & V_{RLL} &:= 490 \cdot \text{kV} & V_R &:= \frac{V_{RLL}}{\sqrt{3}} & S_{1\phi} &:= \frac{900 \cdot \text{MVA}}{3} \\ r &:= 0.029 \cdot \frac{\Omega}{\text{km}} & \text{Assume: } g &:= 0 \cdot \frac{\text{S}}{\text{km}} \\ x &:= 0.326 \cdot \frac{\Omega}{\text{km}} & y &:= 5.220 \cdot 10^{-6} \cdot \frac{\text{S}}{\text{km}} \end{aligned}$$

Note: These are typical values for a 500 kV transmission line

Long-length line model:

Surge Impedance: $Z_c := \frac{j \cdot x + r}{j \cdot y + g}$ $Z_c = 250.151 - 11.104j \cdot \Omega$


Propagation constant: $\gamma := \sqrt{(j \cdot x + r) \cdot (j \cdot y + g)}$ $\gamma = 5.797 \cdot 10^{-5} + 1.306 \cdot 10^{-3}j \cdot \frac{1}{\text{km}}$

Series impedance: $Z_{\text{series}} := Z_c \cdot \sinh(\gamma \cdot \text{len})$ $Z_{\text{series}} = 12.508 + 151.772j \cdot \Omega$

Shunt admittance: $Y_{\text{shunt}} := \frac{2}{Z_c} \cdot \tanh\left(\gamma \cdot \frac{\text{len}}{2}\right)$ $\frac{Y_{\text{shunt}}}{2} = 4.49 \cdot 10^{-6} + 1.353 \cdot 10^{-3}j \cdot \text{S}$
 (Not used in my solution)

Shunt impedance: $Z_{\text{shunt}} := \frac{Z_c}{2 \cdot \tanh\left(\gamma \cdot \frac{\text{len}}{2}\right)}$ $2 \cdot Z_{\text{shunt}} = 2.451 - 738.924j \cdot \Omega$

Solve circuit: $I_R := \frac{S_{1\phi}}{|V_R|}$ (Not complex in this case because $pf = 1$ otherwise include a phase angle calculated from the pf or load other information)

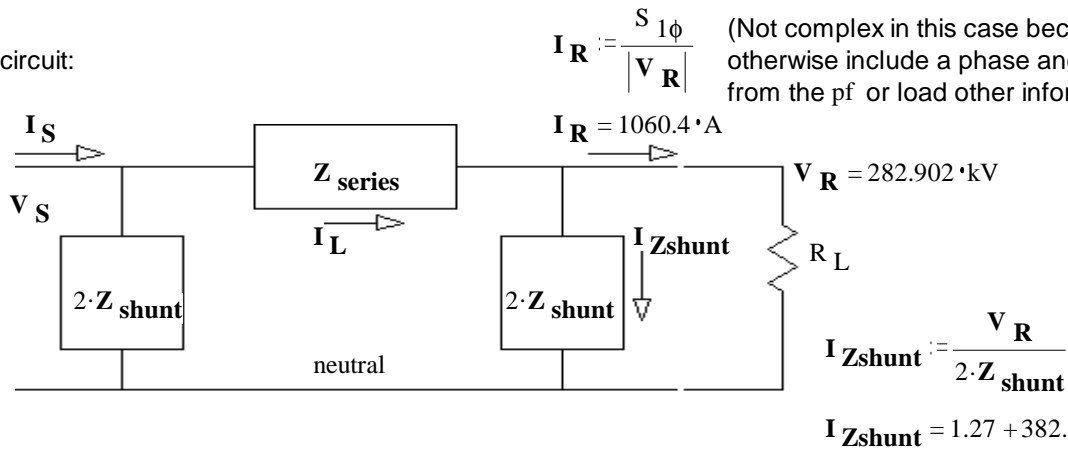

$I_L := I_{Zshunt} + I_R$ $I_L = 1.062 \cdot 10^3 + 382.852j \cdot \text{A}$

$V_S := V_R + I_L \cdot Z_{\text{series}}$ $V_S = 2.381 \cdot 10^5 + 1.659 \cdot 10^5 j \cdot \text{V}$ $|V_S| = 290.192 \cdot \text{kV}$ $\arg(V_S) = 34.874 \cdot \text{deg}$

$I_{ZshuntS} := \frac{V_S}{2 \cdot Z_{shunt}}$ $I_{ZshuntS} = -223.48 + 322.934j \cdot \text{A}$ $|\sqrt{3} \cdot V_S| = 502.628 \cdot \text{kV}$

$I_S := I_{ZshuntS} + I_L$ $I_S = 838.23 + 705.786j \cdot \text{A}$ $|I_S| = 1096 \cdot \text{A}$ $\arg(I_S) = 40.097 \cdot \text{deg}$

ECE 3600 Transmission Line notes p9

Ex 2. A 345 kV transmission line is 220 km long and has the line parameters shown below.

Find V_S and I_S if the line is loaded to 0.9 SIL with $pf = 95\%$ lagging. $|V_{RLL}|$ is 510 kV. $pf := 0.95$

$$\text{len} := 220 \cdot \text{km} \quad V_{RLL} := 510 \cdot \text{kV} \quad V_R := \frac{V_{RLL}}{\sqrt{3}} \quad \text{Assume the phase angle of } V_R \text{ is } 0^\circ \text{ if } V_R \text{ is given}$$

$$r := 0.037 \cdot \frac{\Omega}{\text{km}} \quad \text{Assume: } g := 0 \cdot \frac{\text{S}}{\text{km}} \quad \text{Note: These are typical values for a 345 kV transmission line}$$

$$x := 0.376 \cdot \frac{\Omega}{\text{km}} \quad y := 4.518 \cdot 10^{-6} \cdot \frac{\text{S}}{\text{km}}$$

Medium-length line model:

$$\text{Surge Impedance: } Z_c := \sqrt{\frac{x}{y}} \quad Z_c = 288.5 \cdot \Omega$$

$$\text{Series impedance: } Z_{\text{series}} := (r + j \cdot x) \cdot \text{len} \quad Z_{\text{series}} = 8.14 + 82.72j \cdot \Omega$$

$$\text{Shunt admittance: } Y_{\text{shunt}} := j \cdot y \cdot \text{len} \quad \frac{Y_{\text{shunt}}}{2} = 496.98j \cdot \mu\text{S}$$


$$\text{Not used in my solution}$$

$$\text{Shunt impedance: } Z_{\text{shunt}} := \frac{1}{j \cdot y \cdot \text{len}} \quad 2 \cdot Z_{\text{shunt}} = -2.012 \cdot 10^3 j \cdot \Omega$$

$$\text{Figure out 1 SIL: } \text{SIL} := 3 \cdot \frac{(|V_R|)^2}{|Z_c|} \quad \text{SIL} = 902 \cdot \text{MVA} \quad \text{Actual: } S_{1\phi} := \frac{0.9 \cdot \text{SIL}}{3} \quad (0.9 \text{ SIL loading})$$

Solve circuit:

$$I_R := \frac{S_{1\phi}}{|V_R|} \cdot e^{-j \cdot \arccos(pf)} \quad (\text{Negative phase angle because the pf is lagging})$$

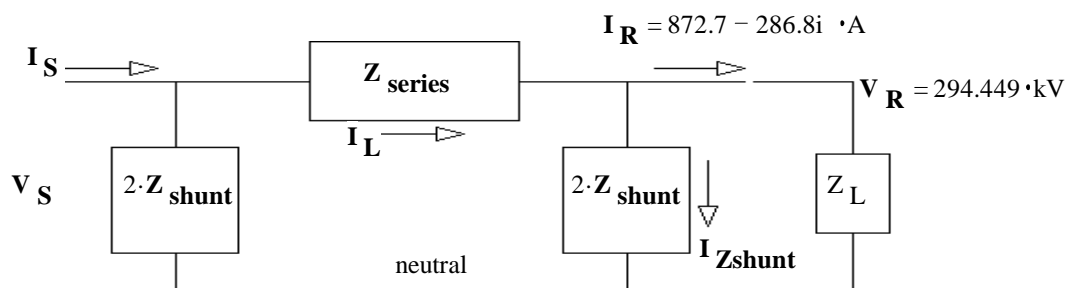

$$I_{Zshunt} := \frac{V_R}{2 \cdot Z_{\text{shunt}}} \quad I_{Zshunt} = 146.335j \cdot \text{A}$$

$$I_L := I_{Zshunt} + I_R \quad I_L = 872.68 - 140.501j \cdot \text{A}$$

$$V_S := V_R + I_L \cdot Z_{\text{series}} \quad V_S = 3.132 \cdot 10^5 + 7.104 \cdot 10^4 j \cdot \text{V} \quad |V_S| = 321.132 \cdot \text{kV} \quad \arg(V_S) = 12.781 \cdot \text{deg}$$

$$I_{ZshuntS} := \frac{V_S}{2 \cdot Z_{\text{shunt}}} \quad I_{ZshuntS} = -35.308 + 155.641j \cdot \text{A}$$

$$\text{Line voltage: } |\sqrt{3} \cdot V_S| = 556.216 \cdot \text{kV}$$

$$I_S := I_{ZshuntS} + I_L \quad I_S = 837.372 + 15.141j \cdot \text{A} \quad |I_S| = 838 \cdot \text{A} \quad \arg(I_S) = 1.036 \cdot \text{deg}$$

Ex3. A 230 kV transmission line has the following length and line parameters.

$$\text{len} := 150 \cdot \text{km} \quad r := 0.06 \cdot \frac{\Omega}{\text{km}} \quad x := 0.5 \cdot \frac{\Omega}{\text{km}} \quad g := 0 \cdot \frac{\text{S}}{\text{km}} \quad y := 4 \cdot 10^{-6} \cdot \frac{\text{S}}{\text{km}}$$


Medium-length line model:

Series impedance: $Z_{\text{series}} := (r + j \cdot x) \cdot \text{len} \quad Z_{\text{series}} = 9 + 75j \cdot \Omega$

Shunt admittance: $Y_{\text{shunt}} := j \cdot y \cdot \text{len} \quad \frac{Y_{\text{shunt}}}{2} = 0.3j \cdot \text{mS}$

Shunt impedance: $Z_{\text{shunt}} := \frac{1}{j \cdot y \cdot \text{len}} \quad 2 \cdot Z_{\text{shunt}} = -3.333j \cdot \text{k}\Omega$

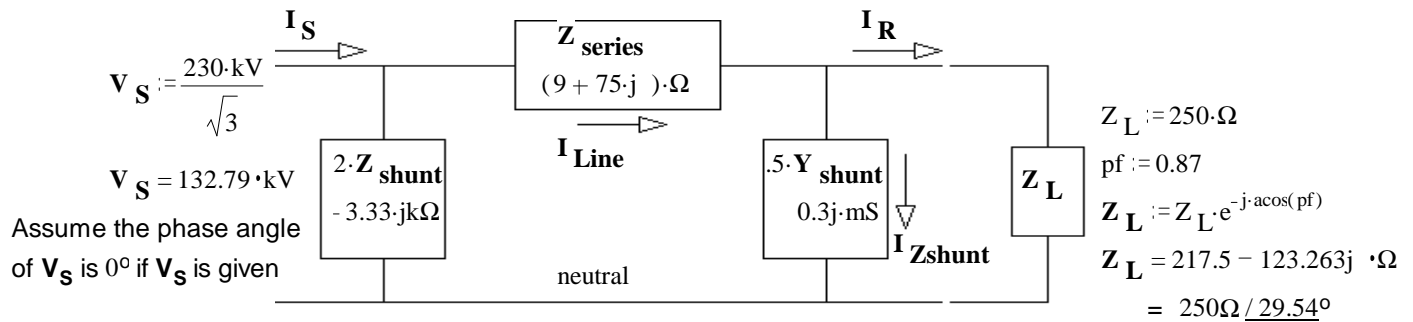a) The load is 250Ω with a power factor of 0.87, leading. Find the line current, I_{Line} .



$$Z := Z_{\text{series}} + \frac{1}{\frac{Y_{\text{shunt}}}{2} + \frac{1}{Z_L}} \quad Z = 210.467 - 56.544j \cdot \Omega = 219.7\Omega / -15.04^\circ$$

$$I_{\text{Line}} := \frac{V_S}{Z} \quad I_{\text{Line}} = 588.459 + 158.096j \cdot \text{A} = 609.3\text{A} / 15.04^\circ$$

b) Find the load line voltage.

$$I_{\text{Line}} \cdot Z_{\text{series}} = -6.561 + 45.557j \cdot \text{kV}$$

$$V_R := V_S - I_{\text{Line}} \cdot Z_{\text{series}} \quad V_R = 139.352 - 45.557j \cdot \text{kV} = 146.6\text{kV} / -18.1^\circ$$

$$\text{Receiving line voltage} = \sqrt{3} \cdot V_R = 253.9 \cdot \text{kV}$$

Notice that $|V_R|$ is bigger than $|V_S|$, this can happen when the receiving-end power factor is leading.

c) What is the "power angle" (δ)?

$$\delta = -\arg(V_R) = 18.104 \cdot \text{deg}$$

d) How much power is delivered to the load?

$$I_R := \frac{V_R}{Z_L} \quad P_L = 3 \cdot |V_R| \cdot |I_R| \cdot \text{pf} = 224.4 \cdot \text{MW}$$

Power estimate for the same $|V_R|$ and $|V_S|$, but neglecting the line resistance:

$$\approx 3 \cdot \frac{|V_S| \cdot |V_R| \cdot \sin(18.1 \cdot \text{deg})}{|Z_{\text{series}}|} = 240 \cdot \text{MW}$$

e) Express this loading in terms of SIL

Surge Impedance: $Z_c := \sqrt{\frac{x}{y}} \quad Z_c = 353.6 \cdot \Omega \quad \frac{Z_c}{Z_L} = 1.414 \quad \text{SIL load}$