

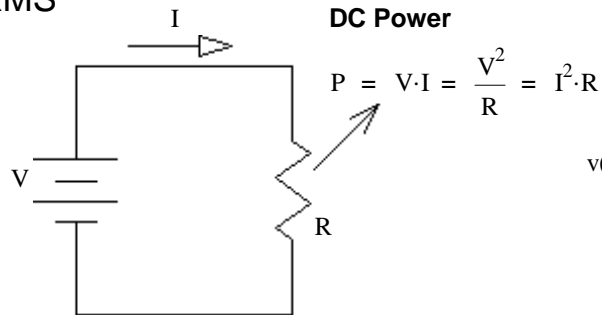
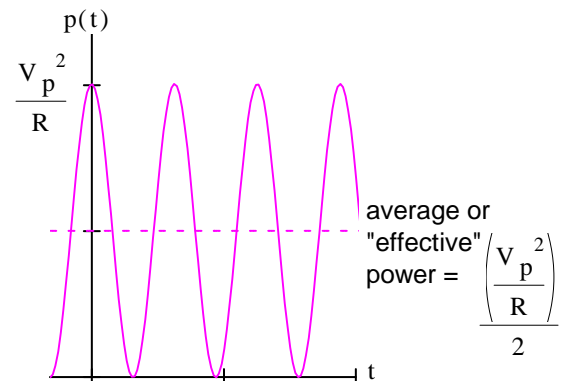


RMS

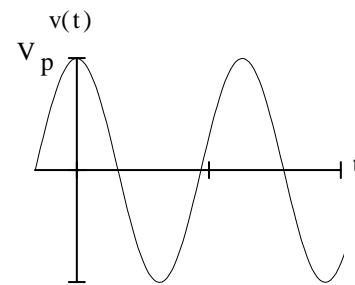

$$v(t) = V_p \cdot \cos(\omega t)$$

AC Power

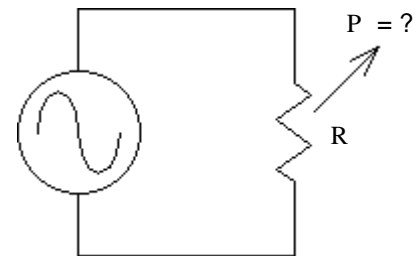


Couldn't we define an "effective" voltage that would allow us to use the same relationships for AC power as used for DC power?

$$P_{\text{ave}} = \frac{\left(\frac{V_p^2}{R}\right)}{2} = \frac{\left(\frac{V_p^2}{2}\right)}{R} = \frac{\left(\frac{V_p}{\sqrt{2}}\right)^2}{R}$$

$$V_{\text{eff}} = \sqrt{\left(\frac{V_p}{\sqrt{2}}\right)^2} = \frac{V_p}{\sqrt{2}} = V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T (v(t))^2 dt}$$

Root Mean (average) Square

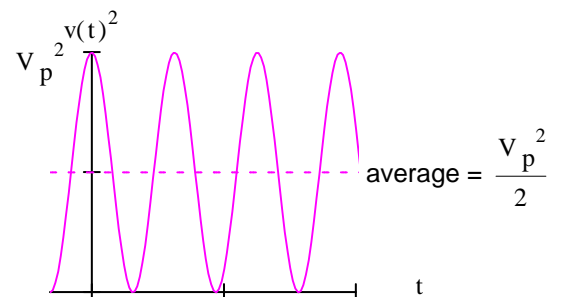

RMS Root of the **M**ean of the **S**quare

Use RMS in power calculations

Sinusoids

$$\begin{aligned} V_{\text{rms}} &= \sqrt{\frac{1}{T} \int_0^T (v(t))^2 dt} = \sqrt{\frac{1}{T} \int_0^T (V_p \cdot \cos(\omega t))^2 dt} = \sqrt{\frac{1}{T} \int_0^T V_p^2 \cdot \left(\frac{1}{2} + \frac{1}{2} \cos(2\omega t)\right) dt} \\ &= \frac{V_p}{\sqrt{2}} \cdot \sqrt{\frac{1}{T} \int_0^T (1) dt + \frac{1}{T} \int_0^T \cos(2\omega t) dt} = \frac{V_p}{\sqrt{2}} \cdot \sqrt{1 + 0} \end{aligned}$$


Common household power

$$f = 60\text{-Hz}$$

$$\omega = 377 \cdot \frac{\text{rad}}{\text{sec}}$$

$$T = 16.67\text{-ms}$$

Neutral, N
white
(also ground)

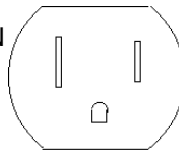

Line, L
black, 120V





Ground, G, green

ECE 3600 Lecture 3 notes p2


$$V_{\text{rms}} := 120\text{-V}$$

$$V_p = V_{\text{rms}} \cdot \sqrt{2} = 170\text{-V}$$

What about other wave shapes??

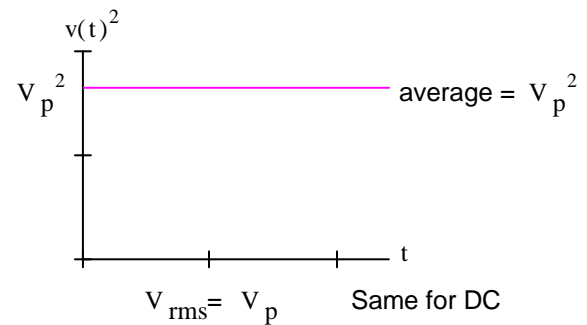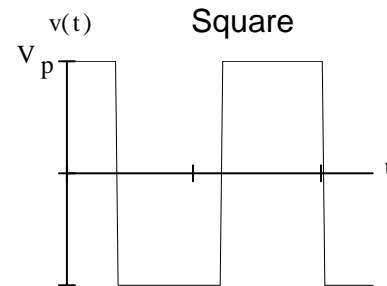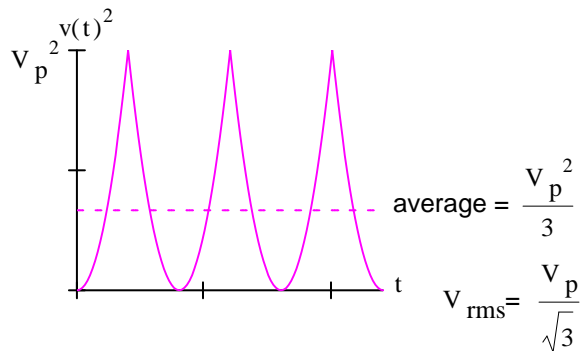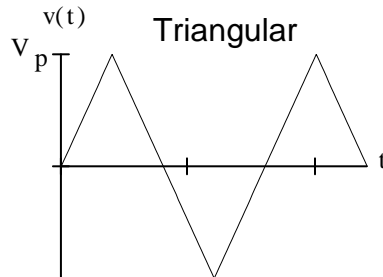


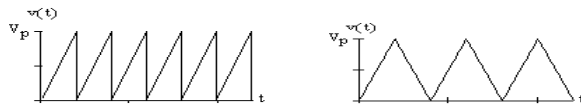Works for all types of triangular and sawtooth waveforms



How about AC + DC ?


$$\begin{aligned}
 V_{\text{rms}} &= \sqrt{\frac{1}{T} \int_0^T (v(t))^2 dt} \\
 &= \sqrt{\frac{1}{T} \int_0^T (V_p \cdot \cos(\omega t) + V_{\text{DC}})^2 dt} \\
 &= \sqrt{\frac{1}{T} \int_0^T \left[(V_p \cdot \cos(\omega t))^2 + 2 \cdot (V_p \cdot \cos(\omega t)) \cdot V_{\text{DC}} + V_{\text{DC}}^2 \right] dt} \\
 &= \sqrt{\frac{1}{T} \int_0^T (V_p \cdot \cos(\omega t))^2 dt + \frac{1}{T} \int_0^T 2 \cdot (V_p \cdot \cos(\omega t)) \cdot V_{\text{DC}} dt + \frac{1}{T} \int_0^T V_{\text{DC}}^2 dt} \\
 &\quad \text{--- zero over one period ---} \\
 &= \sqrt{V_{\text{rmsAC}}^2 + 0 + V_{\text{DC}}^2} = \sqrt{V_{\text{rmsAC}}^2 + V_{\text{DC}}^2}
 \end{aligned}$$

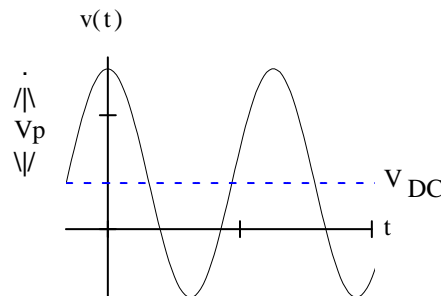



For any sum of waveforms or harmonics:


$$V_{\text{rms}} = \sqrt{V_{\text{rms1}}^2 + V_{\text{rms2}}^2 + V_{\text{rms3}}^2 + V_{\text{rms4}}^2 \dots \text{etc}}$$


ECE 3600 Lecture 3 notes p3


 sinusoid: $V_{rms} = \frac{V_p}{\sqrt{2}}$ $I_{rms} = \frac{I_p}{\sqrt{2}}$

 triangular: $V_{rms} = \frac{V_p}{\sqrt{3}}$ $I_{rms} = \frac{I_p}{\sqrt{3}}$


 square: $V_{rms} = V_p$ $I_{rms} = I_p$

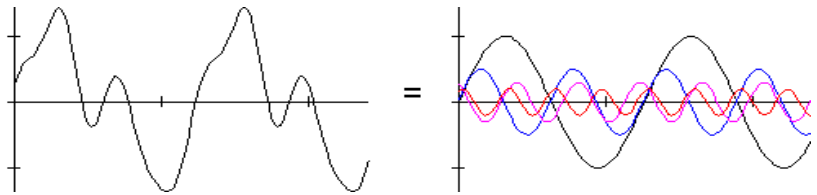 waveform + DC $V_{rms} = \sqrt{V_{rmsAC}^2 + V_{DC}^2}$



rectified average $V_{ra} = \frac{1}{T} \int_0^T |v(t)| dt$
 $V_{ra} = \frac{2}{\pi} \cdot V_p$ $I_{ra} = \frac{2}{\pi} \cdot I_p$

 $V_{ra} = \frac{1}{2} \cdot V_p$ $I_{ra} = \frac{1}{2} \cdot I_p$

 $V_{ra} = V_{rms} = V_p$ $I_{ra} = I_{rms} = I_p$

Most AC meters don't measure true RMS. Instead, they measure V_{ra} , display $1.11 V_{ra}$, and call it RMS. That works for sine waves but not for any other waveform.


$V_{rms} = \sqrt{V_{rms1}^2 + V_{rms2}^2 + V_{rms3}^2 + V_{rms3}^2}$
etc...

Some waveforms don't fall into these forms, then you have to perform the math from scratch

For waveform shown

The average DC (V_{DC}) value
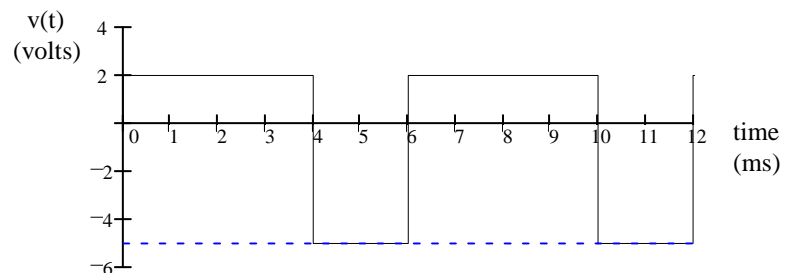
$$\frac{2 \cdot V \cdot (4 \cdot \text{ms}) + (-5 \cdot V) \cdot (2 \cdot \text{ms})}{6 \cdot \text{ms}} = -0.333 \cdot V$$




The RMS (effective) value

Graphical way

$$\frac{4 \cdot V^2 \cdot (4 \cdot \text{ms}) + 25 \cdot V^2 \cdot (2 \cdot \text{ms})}{6 \cdot \text{ms}} = 11 \cdot V^2$$
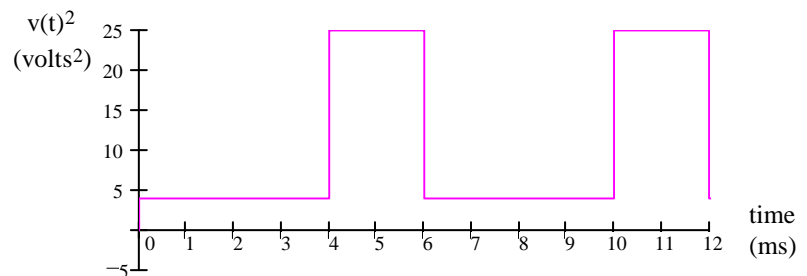
$$V_{RMS} := \sqrt{11 \cdot V^2} \quad V_{RMS} = 3.32 \cdot V$$



OR...

$$V_{RMS} = \sqrt{\frac{1}{T} \int_0^T (v(t))^2 dt}$$


$$= \sqrt{\frac{1}{6 \cdot \text{ms}} \left[\int_{0 \cdot \text{ms}}^{4 \cdot \text{ms}} (2 \cdot V)^2 dt + \int_{4 \cdot \text{ms}}^{6 \cdot \text{ms}} (-5 \cdot V)^2 dt \right]} = \sqrt{\frac{1}{6 \cdot \text{ms}} \cdot [4 \cdot \text{ms} \cdot (2 \cdot V)^2 + 2 \cdot \text{ms} \cdot (-5 \cdot V)^2]} = 3.32 \cdot V$$

The voltage is hooked to a resistor, as shown, for 6 seconds.

The energy is transferred to the resistor during that 6 seconds:

$$P_L := \frac{V_{RMS}^2}{R_L} \quad P_L = 0.22 \cdot \text{W}$$



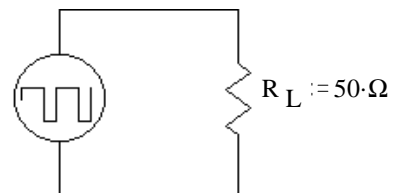
$$W_L := P_L \cdot 6 \cdot \text{sec} \quad W_L = 1.32 \cdot \text{joule} \quad \text{All converted to heat}$$






Use RMS in power calculations

$$P = I_{\text{Rms}}^2 \cdot R = \frac{V_{\text{Rms}}^2}{R} \quad \text{for Resistors ONLY !!}$$

Capacitors and Inductors

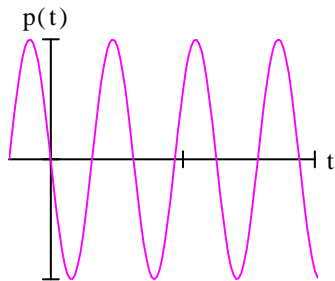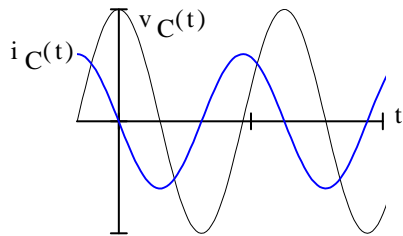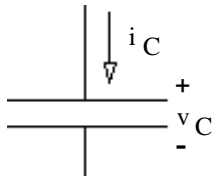

Average power is ZERO $P = 0$

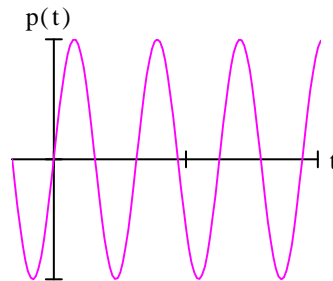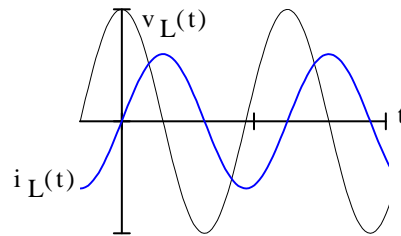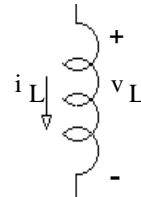

Average power is ZERO $P = 0$

Capacitors and Inductors DO NOT dissipate (real) average power.


Reactive power is negative

$$\begin{aligned} Q_C &= -I_{\text{Crms}} \cdot V_{\text{Crms}} \\ &= -I_{\text{Crms}}^2 \cdot \frac{1}{\omega C} = -V_{\text{Crms}}^2 \cdot \omega C \end{aligned}$$

Reactive power is positive


$$\begin{aligned} Q_L &= I_{\text{Lrms}} \cdot V_{\text{Lrms}} \\ &= I_{\text{Lrms}}^2 \cdot \omega L = \frac{V_{\text{Lrms}}^2}{\omega L} \end{aligned}$$

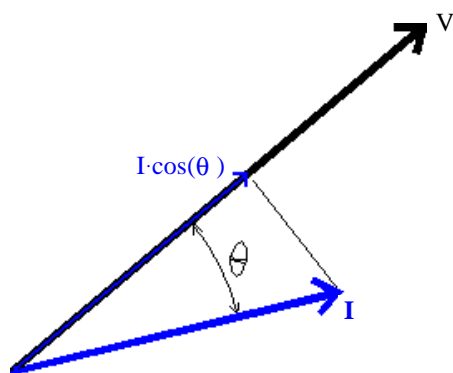If current and voltage are not in phase, only the in-phase part of the current matters for the power-- DOT PRODUCT



"Lagging" power

Inductor dominates

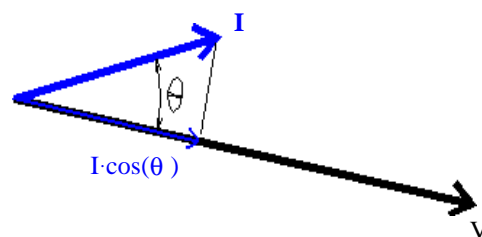

"Leading" Power


Capacitor dominates

Real Power

$$P = V \cdot I \cdot \cos(\theta) = I^2 \cdot |Z| \cdot \cos(\theta) = \frac{V^2}{|Z|} \cdot \cos(\theta)$$

$$P = \text{"Real" Power (average)} = V \cdot I \cdot \text{pf} = I^2 \cdot |Z| \cdot \text{pf} = \frac{V^2}{|Z|} \cdot \text{pf}$$

otherwise....


I_R  V_R for resistors
 only part that uses
 real average power

$$P = I_R^2 \cdot R = \frac{V_R^2}{R}$$


Reactive Power

$$Q = \text{Reactive "power"} = V \cdot I \cdot \sin(\theta)$$

otherwise....

I_C  capacitors $\rightarrow -Q$

$$Q_C = I_C^2 \cdot X_C = \frac{V_C^2}{X_C}$$

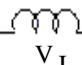I_L  inductors $\rightarrow +Q$

$$Q_L = I_L^2 \cdot X_L = \frac{V_L^2}{X_L}$$

BOLD is a complex number

units: watts, kW, MW, etc.

$\text{pf} = \cos(\theta) = \text{power factor}$

units: VAR, kVAR, etc. "volt-amp-reactive"

$$X_C = -\frac{1}{\omega C} \quad \text{and is a negative number}$$

$$X_L = \omega L \quad \text{and is a positive number}$$

Complex and Apparent Power

$$S = \text{Complex "power"} = P + jQ = VI_{\theta} = \mathbf{V} \cdot \mathbf{I} = I^2 \cdot \mathbf{Z}$$

complex conjugate

units: VA, kVA, etc. "volt-amp"

NOT $V \cdot I$ **NOR** $\frac{V^2}{Z}$

$$S = \text{Apparent "power"} = |S| = \sqrt{P^2 + Q^2} = V \cdot I$$

units: VA, kVA, etc. "volt-amp"

Power factor

$$\text{pf} = \cos(\theta) = \text{power factor (sometimes expressed in \%)} \quad 0 \leq \text{pf} \leq 1$$

θ is the **phase angle** between the voltage and the current or the phase angle of the impedance. $\theta = \theta_Z$


$\theta < 0$ Load is "Capacitive", power factor is "leading". This condition is very rare

$\theta > 0$ Load is "Inductive", power factor is "lagging". This condition is so common you can assume any power factor given is lagging unless specified otherwise. Transformers and motors make most loads inductive.


Industrial users are charged for the reactive power that they use, so for them, power factor < 1 is a bad thing.

Power factor < 1 is also bad for the power company. To deliver the same power to the load, they have more line current (and thus more line losses).

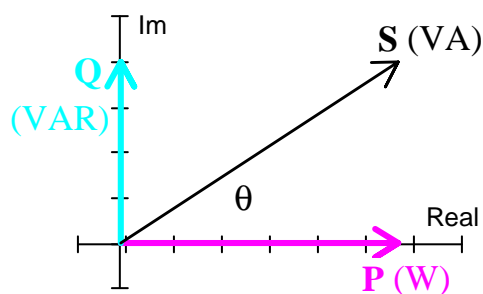Power factors are "corrected" by adding capacitors (or capacitive loads) in parallel with the inductive loads which cause the problems. (In the rare case that the load is capacitive, the pf would be corrected by an inductor.)



"Lagging" power

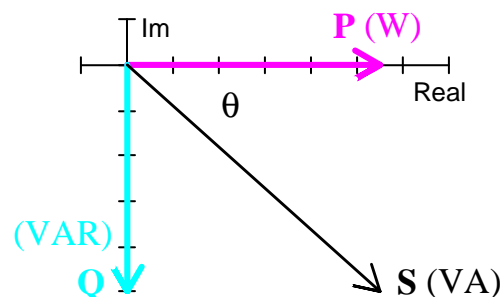

"Leading" Power