

Long-length Lines: over 200 miles (320 km)Need: line length: len m or kmResistance per unit length: R $\frac{\Omega}{m}$ or $\frac{\Omega}{km}$ Usually Assume: $G := 0 \cdot \frac{S}{km}$ $S :=$ siemensInductance per unit length: L $\frac{H}{m}$ or $\frac{H}{km}$ Capacitance per unit length: C $\frac{F}{m}$ or $\frac{F}{km}$

OR

Inductive reactance per unit length: ωL $\frac{\Omega}{m}$ or $\frac{\Omega}{km}$ Capacitance admittance per unit length: ωC $\frac{S}{m}$ or $\frac{S}{km}$

stick to the same unit length for all parameters

A calculator with hyperbolic trig functions

Find:

$$\text{Surge impedance: } \mathbf{Z_c} = \sqrt{\frac{j \cdot \omega \cdot L + R}{j \cdot \omega \cdot C + G}} \quad \Omega$$


$$\text{Propagation constant: } \gamma = \sqrt{(j \cdot \omega \cdot L + R) \cdot (j \cdot \omega \cdot C + G)} \quad \frac{1}{m} \text{ or } \frac{1}{km}$$

$$\text{Series impedance } \mathbf{Z_{series}} = \mathbf{Z_c} \cdot \sinh(\gamma \cdot len) \quad \Omega$$

$$\text{Shunt admittance: } \frac{\mathbf{Y_{shunt}}}{2} = \frac{\tanh\left(\frac{\gamma \cdot len}{2}\right)}{\mathbf{Z_c}} \quad S \text{ or } \frac{1}{\Omega}$$

OR
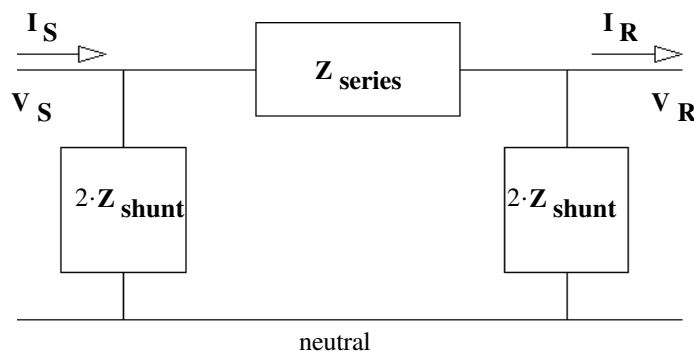
$$\text{Shunt impedance: } 2 \cdot \mathbf{Z_{shunt}} = \frac{\mathbf{Z_c}}{\tanh\left(\frac{\gamma \cdot len}{2}\right)} \quad \Omega$$



Model

Medium-length Lines: 100 to 200 miles (160 - 320 km)

Need: line length: len m or km

Resistance per unit length: R $\frac{\Omega}{\text{m}}$ or $\frac{\Omega}{\text{km}}$

Usually Assume: $G := 0 \cdot \frac{\text{S}}{\text{km}}$ $\text{S} := \text{siemens}$

Inductance per unit length: L $\frac{\text{H}}{\text{m}}$ or $\frac{\text{H}}{\text{km}}$

Capacitance per unit length: C $\frac{\text{F}}{\text{m}}$ or $\frac{\text{F}}{\text{km}}$

OR

Inductive reactance per unit length: ωL $\frac{\Omega}{\text{m}}$ or $\frac{\Omega}{\text{km}}$

Capacitance admittance per unit length: ωC $\frac{\text{S}}{\text{m}}$ or $\frac{\text{S}}{\text{km}}$ stick to the same unit length for all parameters

Find:


Series Resistance: $R_{\text{line}} = R \cdot \text{len}$ Ω

Series impedance $Z_{\text{series}} = (R + j \cdot \omega \cdot L) \cdot \text{len}$ Ω


Shunt admittance: $\frac{Y_{\text{shunt}}}{2} = j \cdot \omega \cdot C \cdot \frac{\text{len}}{2}$ S or $\frac{1}{\Omega}$

OR

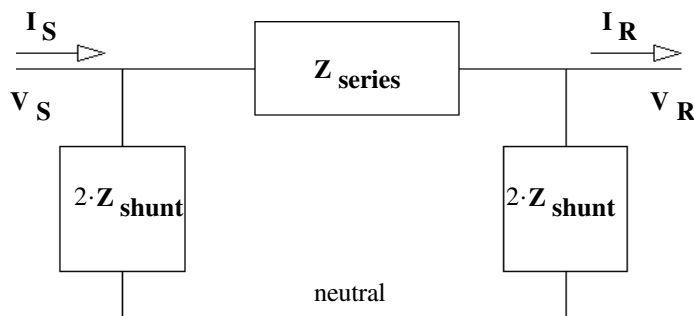Shunt impedance: $2 \cdot Z_{\text{shunt}} = \frac{2}{j \cdot \omega \cdot C \cdot \text{len}}$ Ω




OR:

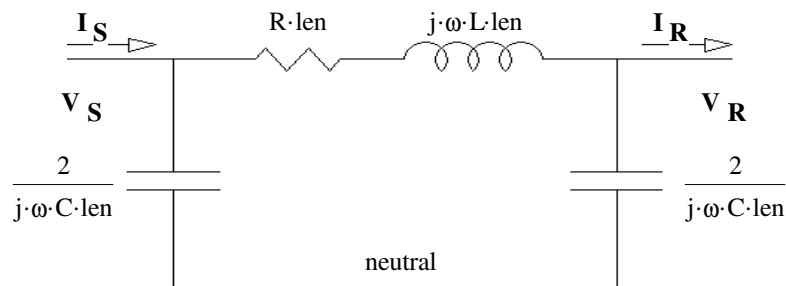

Short-length Lines: less than 100 miles (160km)

Same as above but without the capacitors

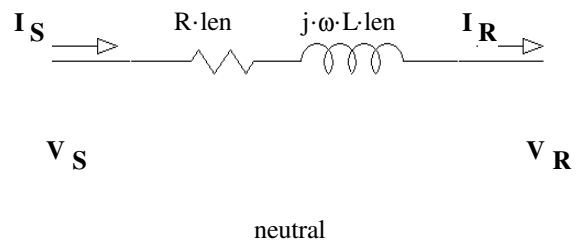

ECE 3600 Transmission Line notes p7

Ex1. A 500 kV transmission line is 500 km long and has line parameters shown in Table 4.1, p.4-10. Use the long-length model to find V_S and I_S if the line is loaded to 1.4 SIL and $|V_{RLL}|$ is 490 kV. Assume the phase angle of V_R is 0° and assume load pf = 1.

a

$$\text{len} := 500 \cdot \text{km} \quad V_{RLL} := 490 \cdot \text{kV} \quad V_R := \frac{V_{RLL}}{\sqrt{3}}$$

From Table 4-1, p.4-10

$$R := 0.029 \cdot \frac{\Omega}{\text{km}} \quad \text{Assume: } G := 0 \cdot \frac{\text{S}}{\text{km}}$$

$$\omega L := 0.326 \cdot \frac{\Omega}{\text{km}} \quad \omega C := 5.220 \cdot 10^{-6} \cdot \frac{\text{S}}{\text{km}}$$

Long-length line model:

Surge Impedance:

$$Z_c := \sqrt{\frac{j \cdot \omega L + R}{j \cdot \omega C + G}} \quad Z_c = 250.151 - 11.104j \cdot \Omega$$

Propagation constant:

$$\gamma := \sqrt{(j \cdot \omega L + R) \cdot (j \cdot \omega C + G)} \quad \gamma = 5.797 \cdot 10^{-5} + 1.306 \cdot 10^{-3}j \cdot \frac{1}{\text{km}}$$

Not used in my solution

$$\beta := \text{Im}(\gamma)$$

$$\beta = 1.306 \cdot 10^{-6} \cdot \text{m}^{-1}$$

$$\alpha := \text{Re}(\gamma)$$

$$\alpha = 5.797 \cdot 10^{-8} \cdot \text{m}^{-1}$$

Series impedance:

$$Z_{\text{series}} := Z_c \cdot \sinh(\gamma \cdot \text{len}) \quad Z_{\text{series}} = 12.508 + 151.772j \cdot \Omega$$

Shunt admittance:

$$Y_{\text{shunt}} := 2 \cdot \frac{\tanh\left(\frac{\gamma \cdot \text{len}}{2}\right)}{Z_c}$$

Not used in my solution

$$\frac{Y_{\text{shunt}}}{2} = 4.49 \cdot 10^{-6} + 1.353 \cdot 10^{-3}j \cdot \text{S}$$

Shunt impedance:

$$Z_{\text{shunt}} := \frac{Z_c}{2 \cdot \tanh\left(\frac{\gamma \cdot \text{len}}{2}\right)}$$

$$2 \cdot Z_{\text{shunt}} = 2.451 - 738.924j \cdot \Omega$$

load resistance for SIL


$$R_L := |Z_c|$$

$$\text{SIL} := \frac{V_{RLL}^2}{R_L}$$

$$\text{SIL} = 959 \cdot \text{MVA}$$

$$I_R := \frac{\left(\frac{1.4 \cdot \text{SIL}}{3}\right)}{\left(\frac{V_{RLL}}{\sqrt{3}}\right)}$$

$$I_R = 1581.7 \cdot \text{A}$$

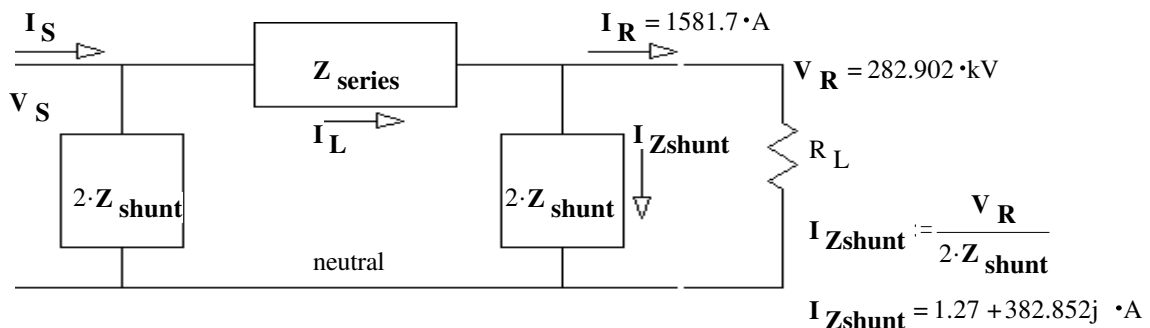

$$I_L := I_{Zshunt} + I_R$$

$$I_L = 1.583 \cdot 10^3 + 382.852j \cdot \text{A}$$

$$V_S := V_R + I_L \cdot Z_{\text{series}}$$

$$V_S = 2.446 \cdot 10^5 + 2.45 \cdot 10^5j \cdot \text{V}$$

$$|V_S| = 346.228 \cdot \text{kV} \quad \arg(V_S) = 45.052 \cdot \text{deg}$$

$$I_{ZshuntS} := \frac{V_S}{2 \cdot Z_{\text{shunt}}}$$

$$I_{ZshuntS} = -330.521 + 332.113j \cdot \text{A}$$

$$|\sqrt{3} \cdot V_S| = 599.685 \cdot \text{kV}$$

$$I_S := I_{ZshuntS} + I_L$$

$$I_S = 1.252 \cdot 10^3 + 714.966j \cdot \text{A}$$

$$|I_S| = 1442 \cdot \text{A} \quad \arg(I_S) = 29.719 \cdot \text{deg}$$

ECE 3600 Transmission Line notes p8

Ex 2. A 500 kV transmission line is 220 km long and has line parameters shown in Table 4.1, p.4-10. Use the medium-length model to find V_S and I_S if the line is loaded to 0.9 SIL and $|V_{RLL}|$ is 510 kV. Assume the phase angle of V_R is 0° and assume load pf = 1

$$\text{len} := 220 \cdot \text{km} \quad V_{RLL} := 510 \cdot \text{kV} \quad V_R := \frac{V_{RLL}}{\sqrt{3}}$$

$$\begin{array}{ll} \text{From Table 4-1, p.4-10} & R := 0.029 \cdot \frac{\Omega}{\text{km}} \\ & \omega L := 0.326 \cdot \frac{\Omega}{\text{km}} \\ \text{Assume:} & G := 0 \cdot \frac{\text{S}}{\text{km}} \\ & \omega C := 5.220 \cdot 10^{-6} \cdot \frac{\text{S}}{\text{km}} \end{array}$$

Medium-length line model:

$$\text{Surge Impedance:} \quad Z_c := \sqrt{\frac{\omega L}{\omega C}} \quad Z_c = 249.9 \cdot \Omega$$

$$\text{Series impedance:} \quad Z_{\text{series}} := (R + j \cdot \omega L) \cdot \text{len} \quad Z_{\text{series}} = 6.38 + 71.72j \cdot \Omega$$

$$\text{Shunt admittance:} \quad Y_{\text{shunt}} := j \cdot \omega C \cdot \text{len} \quad \frac{Y_{\text{shunt}}}{2} = 5.742 \cdot 10^{-4} j \cdot \text{S}$$

$$\text{Not used in my solution}$$

$$\text{Shunt impedance:} \quad Z_{\text{shunt}} := \frac{1}{j \cdot \omega C \cdot \text{len}} \quad 2 \cdot Z_{\text{shunt}} = -1.742 \cdot 10^3 j \cdot \Omega$$


load resistance for SIL

$$\text{SIL} := \frac{V_{RLL}^2}{R_L}$$

$$R_L := |Z_c|$$

$$\text{SIL} = 1041 \cdot \text{MVA}$$
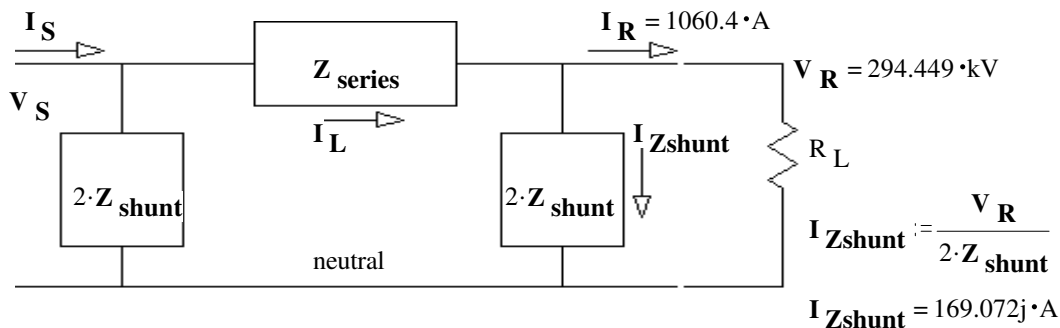
$$I_R := \frac{\left(\frac{0.9 \cdot \text{SIL}}{3} \right)}{\left(\frac{V_{RLL}}{\sqrt{3}} \right)} \quad I_R = 1060.4 \cdot \text{A}$$



$$I_L := I_{Zshunt} + I_R \quad I_L = 1.06 \cdot 10^3 + 169.072j \cdot \text{A}$$

$$V_S := V_R + I_L \cdot Z_{\text{series}} \quad V_S = 2.891 \cdot 10^5 + 7.713 \cdot 10^4 j \cdot \text{V}$$

$$|V_S| = 299.201 \cdot \text{kV} \quad \arg(V_S) = 14.939 \cdot \text{deg}$$

$$|\sqrt{3} \cdot V_S| = 518.232 \cdot \text{kV}$$

$$I_{ZshuntS} := \frac{V_S}{2 \cdot Z_{shunt}} \quad I_{ZshuntS} = -44.289 + 165.994j \cdot \text{A}$$

$$I_S := I_{ZshuntS} + I_L \quad I_S = 1.016 \cdot 10^3 + 335.067j \cdot \text{A} \quad |I_S| = 1070 \cdot \text{A} \quad \arg(I_S) = 18.25 \cdot \text{deg}$$