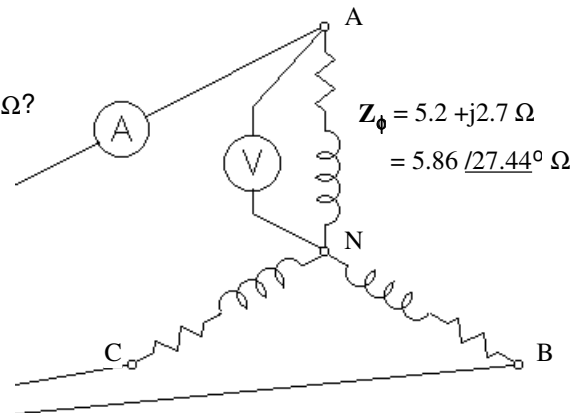


ECE 3600 homework # 4

a

Note: All voltages and currents are always assumed to be RMS unless said to be otherwise.

- The following are questions from p 78 of the textbook. These could be good closed-book exam questions.
 - 2.1. What types of connections are possible for three-phase generators and loads?
 - 2.2. What is meant by the term "balanced" in a balanced three-phase system?
 - 2.3. What is the relationship between phase and line voltages and currents for a wye (Y) connection?
 - 2.4. What is the relationship between phase and line voltages and currents for a delta (Δ) connection?
 - 2.5. What is phase sequence?
 - 2.7. What is a Y- Δ transform?
- Textbook 2-1. Three impedances of $4 + j3 \Omega$ are Δ -connected and tied to a three-phase 208-V power line. Find I_ϕ , I_L , P, Q, S (|S|), and the power factor of this load.
- A balanced three-phase 208-V source (three line-to-neutral voltages of 120 V) supplies a balanced three-phase inductive load. The load draws a total of 9 kW at a power factor of 0.9. Calculate the phase currents and the magnitude of the per-phase load impedances, assuming a Y-connected load. Draw a phasor diagram showing all three phase voltages and currents.
- Repeat problem 3, assuming a delta-connected load.
- The voltmeter shown measures 120 V. Let this voltage be the phase reference (0°). The phase impedance is $Z_\phi = 5.2 + j2.7 = 5.86 \angle 27.44^\circ \Omega$
 - What is V_{AB} as a phasor?
 - What would the ammeter measure?
 - What is the apparent power?
 - What is the real power?
 - Correct the power factor with capacitors connected in a delta configuration, that is, find the value of the capacitors.
- Three 230-V generators are connected in a wye configuration to generate three-phase power. The load consists of three balanced delta-connected impedances of $Z_L = 3.8 + j1.5 \Omega$.
 - An ammeter is placed in one line, what would it measure?
 - Find the total apparent power.
 - Find the total real power consumed by the load.
 - What is the phase angle between I_A and V_{AB} , assuming ABC rotation?




Answers

- 2.1. Y & Δ
 - 2.2. The 3 voltages are equal, the 3 currents are equal and the 3 loads are equal.

$$c) 2.3. V_\phi = \frac{V_{LL}}{\sqrt{3}} = \frac{V_L}{\sqrt{3}} \quad I_\phi = I_L \quad d) 2.4. V_\phi = V_{LL} = V_L \quad I_\phi = \sqrt{3} \cdot I_L$$


$$e) 2.5. abc \text{ or } acb \quad f) 2.7. Z_Y = \frac{Z_\Delta}{3} \quad 2. 41.6 \text{ A} \cdot \text{A} \quad 72.1 \text{ A} \quad 20.8 \text{ kW} \\ 15.6 \text{ kVAR} \quad 26.0 \text{ kVA}$$
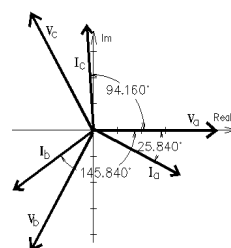
$$3. 27.8 \text{ A} \text{ lagging by } 25.8^\circ \quad 4.32 \Omega$$



$$4. 16 \text{ A} \angle 4.16^\circ$$

$$13 \Omega$$

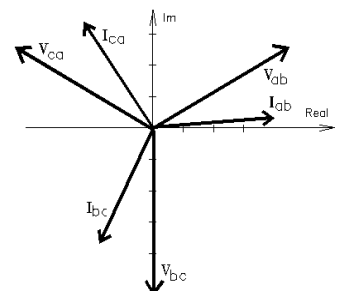

$$5. a) 208 \text{ V} \cdot e^{j30^\circ} \quad b) 20.5 \text{ A} \quad c) 7.37 \text{ kVA} \quad d) 6.76 \text{ kW} \quad e) 60.3 \mu\text{F}$$

$$6. 167 \text{ A} \quad 117 \text{ kVA} \quad 108 \text{ kW} \quad -51.541^\circ$$