


ECE 3600 homework # 11

Due: Tue, 10/20/09

1. A 3-phase system operates at 220 kVA and 11 kV. (Values given in this way are 3-phase power and V_L , also recall that V_L is V_{LL}). Using these quantities to find base values, find the base current and base impedance for the system.
2. 19 If 25 Ω and 125 A are the base impedance and base current, respectively, for a system, find the base kVA and base voltage.
3. 20 The percent values of the voltage, current, impedance, and voltamperes for a given power system are 90, 30, 80, and 150 percent, respectively. The base current and base impedance are 60 A and 40 Ω , respectively. Calculate the actual values of the voltage, current, impedance, and voltamperes.
4. 21 A single-phase transmission line supplies a reactive load at a lagging power factor. The load draws 1.2 pu current at 0.6 pu voltage while drawing 0.5 pu (true) power. If the base voltage is 20 kV and the base current is 160 A, calculate the power factor and the ohmic value of the resistance of the load.
5. 25 A 100-kVA, 20/5-kV transformer has an equivalent impedance of 10 percent. Calculate the impedance of the transformer referred to
 - a) the 20-kV side
 - b) the 5-kV side.

6. 23 The one-line diagram for a two-generator system is shown. Redraw the diagram to show all values as per-unit values referred to a 7000-kVA base. See the transformers for the V_{base} s in the 3 regions.

$$S_{base} := 7 \cdot \text{MVA}$$

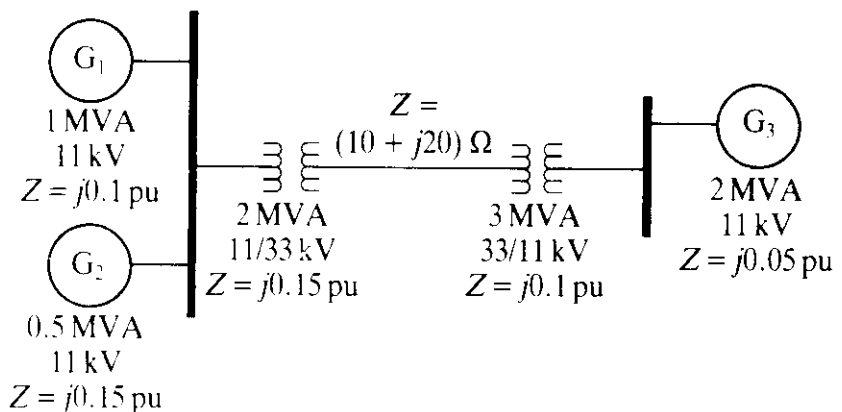

Correct your exam 1 for 5 more exam points

For each problem part you missed, (say 1f) work out the correct solution. Don't change or add to the writing on your exam-- work out the corrections on separate paper. Be sure to clearly label the problems and parts.

Hand in your correct solutions along with your exam Tuesday 10/20 in class for up to 5 more exam points. They will be returned Thursday, 10/22.

Don't Forget: Field Trip, Mon, 10/19/09

Our Field trip is scheduled for Monday 10/19/09 starting at 3:00 at the main Rocky Mountain Power building on North Temple. This is the red building north of the Gadsby power plant. We will meet at the north-west entrance.

Long pants, long-sleeved shirts + steel-toed boots and hard hats if you have them.

Answers

1. 6.35-kV 11.6-A 550- Ω
2. 390.6-kVA 3.125-kV
3. 2160-V 18-A
32- Ω 216-kVA
4. 69.4-% 43.4- Ω
5. 400- Ω 25- Ω

