

## ECE 3600 homework # 12

Due: Tue, 10/27/09


1. A single-phase generator delivers a voltage of 680 V rms at its terminals and a current of 32 A rms. The real power delivered is 15 kW. Find the reactive power  $Q$ . Give both possible answers.
2. A 3-phase synchronous generator operates onto a grid bus of voltage 12 kV (line value). The synchronous reactance is  $5 \Omega/\text{phase}$ . The magnitude of the generator emf equals the magnitude of the bus voltage. The machine delivers 18 MW to the grid. Find:
  - a) The power angle,  $\delta$ .
  - b) The complex phase current, (Assume the bus voltage phase angle is  $0^\circ$ ).
  - c) The magnitude and direction of reactive power.

## ECE 3600 homework # 13

Due: Fri, 10/30/09


1. A 60 Hz, 2-pole, 3-phase synchronous generator supplies power to a 12.5 kV bus. The synchronous reactance is  $4 \Omega/\text{phase}$ . The generator emf is  $7 \text{ kV} \angle 20^\circ$  (the angle is referenced to the terminal voltage). Find the following.
  - a) The total power generated.
  - b) The total reactive power generated.
  - c) The shaft torque from the prime mover, neglecting friction.
  - d) Increase the magnitude of the generator emf so that  $Q := 0 \cdot \text{VAR}$ . The prime mover torque does not change. Note: If the prime mover torque doesn't change, neither does  $P$ .  $\delta$  can change.
  - e) The new power angle,  $\delta$ .
  - f) Increase the magnitude of the generator emf so that  $Q := 9 \cdot \text{MVAR}$
  - g) The new power angle,  $\delta$ .

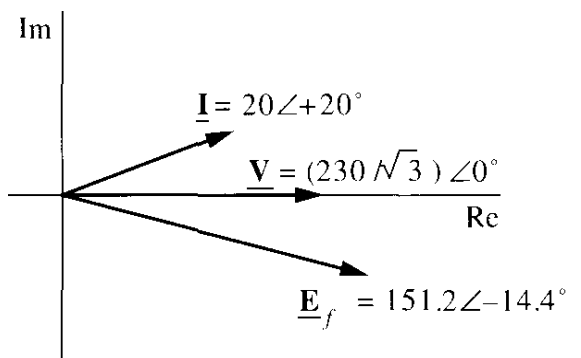2. 4.39 Refer to the per-phase phasor diagram at right. It is for a 12-pole, three-phase synchronous machine.
  - a) Is the machine operating as a motor or a generator?
  - b) What is the voltage and apparent power into/out of the machine?
  - c) Determine the synchronous reactance of the machine.
  - d) For the same real power, what magnitude of excitation voltage yields unity power factor?



3. 4.41. A cylindrical-rotor, 60-Hz, three-phase, 12-pole synchronous motor operates from 2300 V and produces 500 hp. The motor operates with unity power factor with an excitation voltage of  $E = 1620 \text{ V}$  per phase. Neglect losses. Determine the following:
  - a) The current.
  - b) The synchronous reactance.
  - c) The torque.
  - d) The rotor power angle.

4. 4.43. The per-phase phasor diagram for a three-phase, 60-Hz, 8-pole synchronous motor is shown. Note that all sides and two angles of the triangle are shown. The current/phase is 21 A.
  - a) Is the motor overexcited or underexcited?
  - b) What is the rotor power angle?
  - c) What is the power factor and is it leading or lagging?
  - d) Determine the synchronous reactance per phase.
  - e) Determine the output power and torque, neglecting mechanical losses.

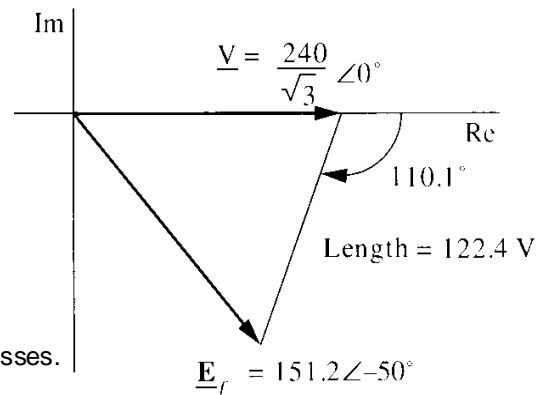**Answers**

1.  $\pm 15.8 \text{ kVAR}$     2. a)  $38.68\text{-deg}$     b)  $918\text{-A} \angle 19.34\text{-deg}$     c)  $-6.32\text{-MVAR}$

1. a)  $12.96\text{-MW}$     b)  $-3.459\text{-MVAR}$     c)  $3.437 \cdot 10^4 \cdot \text{N}\cdot\text{m}$     d)  $7.604\text{-kV}$     e)  $18.35\text{-deg}$     f)  $9.197\text{-kV}$     g)  $15.1\text{-deg}$   
 2. a) motor    b)  $132.8\text{-V}$      $7.97\text{-kVA}$     c)  $2\text{-}\Omega$     d)  $E_{af} = 138\text{-V}$   
 3. a)  $93.6\text{-A}$     b)  $9.92\text{-}\Omega$     c)  $5934\text{-N}\cdot\text{m}$     d)  $34.95\text{-deg}$   
 4. a) underexcited    b)  $-50\text{-deg}$     c)  $0.939$  lagging  
 d)  $5.83\text{-}\Omega$     e)  $11\text{-hp}$      $87\text{-N}\cdot\text{m}$