

1. Textbook problem 13-6 Repeat Example 13-2 if it a Double-Line fault between phases b and c.
2. Textbook problem 13-7
Repeat Example 13-2 if it a Double-Line fault between phases b and c with a fault impedance $Z_f = 0.15 \angle 0^\circ \text{ pu}$.
3. Textbook problem 13-8 Repeat Example 13-2 if it a Double-Line fault to ground with phases b and c grounded.
4. Textbook problem 13-10
Repeat Example 13-2 if it a single-line to ground fault on phase a of Bus-1.
The generator neutral is grounded through a resistance $R_n := 0.10 \text{ pu}$.
5. Textbook problem 13-11
Repeat Example 13-2 if there is a line-line to ground fault involving phases b and c of Bus-1.
The generator neutral is grounded through a resistance $R_n := 0.10 \text{ pu}$.
Just draw the schematic. You may leave out the X values, but show where R_n fits in and the value of that part.
6. Textbook problem 13-14
 - a) For the impedance relay of Fig. 13-20 applied to protect the transmission line from Bus-2 to Bus-3 in Example 13-2. It is placed at Bus-2. Calculate the point in the impedance plane (the impedance) for a three-phase fault that is 85% of the line length away from Bus-2.
 - b) Repeat this if the fault is 15% of the line length away from Bus-2.

Answers

1. $I_{\text{fault}} = I_b = 4.063 \text{ pu} \quad -173.38^\circ$
2. $3.588 \text{ pu} \quad \angle -155.4^\circ$
3. $5.304 \text{ pu} \quad 143.2^\circ$
4. $2.080 \text{ pu} \quad -63.78^\circ$
5. Be sure to triple R_n and show the open caused by the transformer winding.
6. a) 0.085 pu b) 0.015 pu