

Notes on Chapter 4

General Properties of Lossless Networks (see pp. 177, 178 - Text)

$$\begin{bmatrix} b_1 \\ b_2 \\ \vdots \\ b_N \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} & \dots & S_{1N} \\ S_{21} & - & - & S_{2N} \\ - & - & - & - \\ S_{N1} & - & - & S_{NN} \end{bmatrix} \begin{bmatrix} 0 \\ 0 \\ \vdots \\ a_i \\ \vdots \\ 0 \end{bmatrix}$$

$$b_1 = S_{1i} a_i$$

$$b_2 = S_{2i} a_i$$

$$b_N = S_{Ni} a_i$$

$$b_1 b_1^* + \dots + b_N b_N^* = (S_{1i}^* S_{1i} + S_{2i}^* S_{2i} + \dots + S_{Ni}^* S_{Ni}) a_i a_i^*$$

$$\sum_{k=1}^N S_{ki} S_{ki}^* = 1 \quad \text{for any } i \quad \begin{matrix} (4.53a) \\ \text{p. 178} \end{matrix}$$

Property 1 Sum of the squares of the S-parameters in any column = 1

II. Property 2 Let us feed power to any 2 ports say i, j

$$b_1 = S_{1i} a_i + S_{1j} a_j$$

$$b_N = S_{Ni} a_i + S_{Nj} a_j$$

$$b_1 b_1^* + \dots + b_N b_N^* = S_{1i}^* S_{1i} a_i a_i^* + S_{1j}^* S_{1j} a_j a_j^* + \dots + S_{Ni}^* S_{Ni} a_i a_i^* + S_{Nj}^* S_{Nj} a_j a_j^* + \dots$$

$$\left(\sum_{k=1}^N S_{ki} S_{ki}^* \right) a_i a_i^* + \left(\sum_{k=1}^N S_{kj} S_{kj}^* \right) a_j a_j^* + \left(\sum_{k=1}^N S_{ki} S_{kj}^* \right) a_i a_j^* + \left(\sum_{k=1}^N S_{ki}^* S_{kj} \right) a_i^* a_j = a_i a_i^* + a_j a_j^* \quad (1)$$

Since a_i and a_j are arbitrary both for magnitude and phase, we can select them in phase

From Eq. (1) we can write $\sum_{k=1}^N S_{ki} S_{kj}^* + S_{ki}^* S_{kj} = 0$

We can also select a_i, a_j to be 90° out of phase say $a_j^* = j a_i$ in which case we can write

so $\sum_{k=1}^N S_{ki} S_{kj}^* = \sum_{k=1}^N S_{ki} S_{kj} = 0 \quad (4.53b) \quad \text{for } i \neq j$

Stephen F. Adam

Microwave Theory and Applications

Prentice-Hall, Inc. 1969

3.2 FLOW GRAPH REPRESENTATION OF MICROWAVE NETWORKS

3.2.1 SCATTERING PARAMETERS

In analyzing microwave transmission line problems, one would like to find some generalized parameters to write for a network in question—parameters which can be measured with reasonable simplicity, even in microwave frequencies. Analysis of the energy flow through a two-port network is one way to do this.

A simple two-port network can be shown as a "black box" (Fig. 3.2-1).

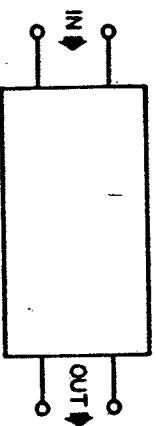


Fig. 3.2-1. Simple two-port network.

We are not interested in knowing what is built into the black box, but only in what it will do to a signal applied to either port. For example, if the black box contains an amplifier and we would like to know the various parameters, we can measure the input impedance while the output is short- and open-circuited and measure the output impedance while the input is short- and open-circuited. This will give us some of the commonly known z , y , and h parameters. However, this technique has some shortcomings at higher frequencies. Some devices may oscillate (probably at some frequency different from the measurement frequency) or have some unwanted, parasitic effects if they are terminated with a short or open circuit.

The ideal case would be to express a set of parameters when the input and output ports are terminated with their own characteristic impedances at all frequencies. The scattering (s) parameters are the set of parameters that are measured under such conditions. An added, inherent advantage of these

3.2 FLOW GRAPH REPRESENTATION OF MICROWAVE NETWORKS

parameters is that they describe the signal flow within the network. Kurokawa,¹ Penfield,^{2,3} and Youla⁴ studied generalized scattering parameters. Huntton⁵ used signal flow to analyze microwave-measurement techniques with s parameters and expressed them with flow graphs, since these parameters relate directly to the signal flow. Kuhn⁶ used a topographical approach for resolving these flow graphs.

3.2.2 BASIC FLOW GRAPHS

A flow graph can be drawn to analyze the energy flow of a two-port network. (See Fig. 3.2-2.) A flow graph has two nodes for each port, one for

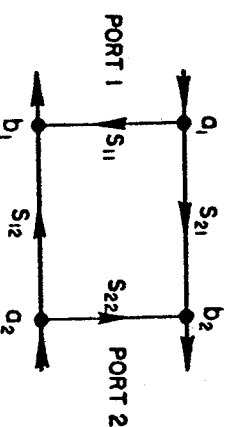


Fig. 3.2-2. Flow graph of a two-port network.

the entering (incident) wave and the other for the leaving (reflected) wave of that port. The incident node is the a node and the reflected node is the b node. In our example of the simple two-port network, when the incident wave enters the device at port 1, part of it will be returned through the s_{11} path and b_1 node. The remaining part of the incident wave goes through the s_{12} path and leaves the network through the b_2 node. If a device that has some reflections is connected to port 2, and if it will reflect part of the wave leaving b_2 , this reflection will reenter the network through the a_2 node. Then, part of that may be reflected, passing along the s_{22} path and leaving the network

¹ Kurokawa, K., *IEEE Trans.-AP*, March 1965, p. 194.

² Penfield, P., Jr., "Noise in Negative Resistance Amplifiers," *IRE Trans.-CT*, Vol. CT-7, June 1960, pp. 166-70.

³ Penfield, P., Jr., "A Classification of Lossless Three Ports," *IRE Trans.-CT*, Vol. CT-9, September 1962, pp. 215-23.

⁴ Youla, D. C., "On Scattering Matrices Normalized to Complex Port Numbers," *Proc. IRE*, Vol. 49, July 1961, p. 122.

⁵ Huntton, J. K., "Analysis of Microwave Measurement Techniques by Means of Signal Flow Graphs," *Trans. IRE*, Vol. MTT-8, March 1960, pp. 206-12.

⁶ Kuhn, Nicholas, "Simplified Signal Flow Graph Analysis," *The Microwave Journal*, November 1963, pp. 59-66.

through the b_2 node. The other part of the wave passes through the s_{12} path and leaves the circuit through the b_1 node.

Following the arrows in the flow graph, we can write the following equations.

$$b_1 = a_1 s_{11} + a_2 s_{12} \quad (3.2-1)$$

$$b_2 = a_1 s_{21} + a_2 s_{22} \quad (3.2-2)$$

By analyzing these equations, one can see that these parameters can be easily measured under certain conditions.

Assume that there is no signal entering at a_2 node (this can be achieved by terminating port 2 with its characteristic impedance). Then Eqs. (3.2-1) and (3.2-2) become

$$b_1 = a_1 s_{11}, \quad (3.2-3)$$

$$b_2 = a_1 s_{21}. \quad (3.2-4)$$

By reversing the network, that is, terminating port 1 with its characteristic impedance and applying the signal to port 2, Eqs. (3.2-1) and (3.2-2) will become

$$b_1 = a_2 s_{12}, \quad (3.2-5)$$

$$b_2 = a_2 s_{22}. \quad (3.2-6)$$

since $a_1 = 0$.

Expressing the scattering parameters from Eqs. (3.2-3), (3.2-4), (3.2-5), and (3.2-6), we can write the following:

$$s_{11} = \frac{b_1}{a_1} \quad \left| \quad a_2 = 0 \right. \quad (3.2-7)$$

$$s_{21} = \frac{b_2}{a_1} \quad \left| \quad a_2 = 0 \right. \quad (3.2-8)$$

$$s_{12} = \frac{b_1}{a_2} \quad \left| \quad a_1 = 0 \right. \quad (3.2-9)$$

$$s_{22} = \frac{b_2}{a_2} \quad \left| \quad a_1 = 0 \right. \quad (3.2-10)$$

Furthermore, these expressions show the means of measuring these parameters; s_{11} can be measured when port 2 is terminated with its characteristic impedance and only the ratio of reflected wave and incident wave has to be measured at port 1. We saw that in Chap. 2, where reflection coefficients were discussed. This means that s_{11} is really the input-reflection coefficient of the device.

s_{22} is measured in exactly the same manner as s_{11} , except that port 1 is terminated with its characteristic impedance and the signal is applied to port 2; s_{21} is the output-reflection coefficient of the network.

s_{12} is measured when port 2 is terminated with its characteristic imped-

ance and the signal is applied into port 1. The ratio of the signals measured at the b_2 and a_1 nodes (voltage between output and input ports) defines the value of s_{21} . Simply, s_{21} is the forward transducer coefficient.

s_{12} is measured by reversing the ports and terminating port 1 in its characteristic impedance and applying the signal to port 2. The ratio of the signals appearing at the b_1 and a_2 nodes will define the value of the s_{12} parameter. s_{22} is the reverse transducer coefficient of the network.

These parameters are vector values, and they have both magnitude and phase information.

It is much easier to make swept-frequency, wideband measurements of s parameters than of h , y , and z parameters, especially above 100 MHz. To use the many design techniques defined in terms of h , y , and z parameters, it is quite simple to convert data to any of these parameters from the scattering parameters. Table (3.2-1) shows the conversion equations for each of these parameters and the scattering parameters.

Table 3.2-1. Conversion Equations Between h , z , y , and s Parameters

$s_{11} = \frac{(z_{11} - 1)(z_{22} + 1) - z_{12}^2 z_{21}}{(z_{11} + 1)(z_{22} + 1) - z_{12}^2 z_{21}}$	$z_{11} = \frac{(1 + s_{11})(1 - s_{22}) + s_{12} s_{21}}{(1 - s_{11})(1 - s_{22}) - s_{12} s_{21}}$
$s_{12} = \frac{2z_{12}}{(z_{11} + 1)(z_{22} + 1) - z_{12}^2 z_{21}}$	$z_{12} = \frac{2s_{12}}{(1 - s_{11})(1 - s_{22}) - s_{12} s_{21}}$
$s_{21} = \frac{2z_{21}}{(z_{11} + 1)(z_{22} + 1) - z_{12}^2 z_{21}}$	$z_{21} = \frac{2s_{21}}{(1 - s_{11})(1 - s_{22}) - s_{12} s_{21}}$
$s_{22} = \frac{(z_{11} + 1)(z_{22} - 1) - z_{12}^2 z_{21}}{(z_{11} + 1)(z_{22} + 1) - z_{12}^2 z_{21}}$	$z_{22} = \frac{(1 + s_{22})(1 - s_{11}) + s_{12} s_{21}}{(1 - s_{11})(1 - s_{22}) - s_{12} s_{21}}$
$s_{11} = \frac{(1 - y_{11})(1 + y_{22}) - y_{12} y_{21}}{(1 + y_{11})(1 + y_{22}) - y_{12} y_{21}}$	$y_{11} = \frac{(1 + s_{11})(1 - s_{22}) + s_{12} s_{21}}{(1 + s_{11})(1 + s_{22}) - s_{12} s_{21}}$
$s_{12} = \frac{-2y_{12}}{(1 + y_{11})(1 + y_{22}) - y_{12} y_{21}}$	$y_{12} = \frac{-2s_{12}}{(1 + s_{11})(1 + s_{22}) - s_{12} s_{21}}$
$s_{21} = \frac{-2y_{21}}{(1 + y_{11})(1 + y_{22}) - y_{12} y_{21}}$	$y_{21} = \frac{-2s_{21}}{(1 + s_{11})(1 + s_{22}) - s_{12} s_{21}}$
$s_{22} = \frac{(1 + y_{11})(1 - y_{22}) - y_{12} y_{21}}{(1 + y_{11})(1 + y_{22}) - y_{12} y_{21}}$	$y_{22} = \frac{(1 + s_{11})(1 - s_{22}) + s_{12} s_{21}}{(1 + s_{11})(1 + s_{22}) - s_{12} s_{21}}$
$s_{11} = \frac{(h_{11} - 1)(h_{22} + 1) - h_{12} h_{21}}{(h_{11} + 1)(h_{22} + 1) - h_{12} h_{21}}$	$h_{11} = \frac{(1 + s_{11})(1 + s_{22}) - s_{12} s_{21}}{(1 - s_{11})(1 + s_{22}) + s_{12} s_{21}}$
$s_{12} = \frac{2h_{12}}{(h_{11} + 1)(h_{22} + 1) - h_{12} h_{21}}$	$h_{12} = \frac{2s_{12}}{(1 - s_{11})(1 + s_{22}) + s_{12} s_{21}}$
$s_{21} = \frac{-2h_{21}}{(h_{11} + 1)(h_{22} + 1) - h_{12} h_{21}}$	$h_{21} = \frac{-2s_{21}}{(1 - s_{11})(1 + s_{22}) + s_{12} s_{21}}$
$s_{22} = \frac{(1 + h_{11})(1 - h_{22}) + h_{12} h_{21}}{(h_{11} + 1)(h_{22} + 1) - h_{12} h_{21}}$	$h_{22} = \frac{(1 - s_{11})(1 - s_{22}) - s_{12} s_{21}}{(1 - s_{11})(1 + s_{22}) + s_{12} s_{21}}$

3.2.3 TOPOGRAPHICAL APPROACH TO RESOLVE FLOW GRAPHS¹

It was emphasized in the previous section that the scattering parameters are descriptive of signal flow; consequently, signal flow graphs can easily show the scattering parameters as signal flow elements. A two-port network has been described already. The flow graph of a three-port network can be realized in the same manner. Figure 3.2-3 shows such a flow graph.

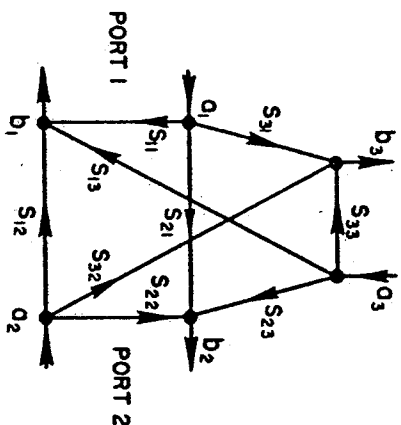


Fig. 3.2-3. Flow graph of a three-port network.

Nodes that represent waves entering and leaving the network are designated a_n and b_n , respectively. There is always a connecting line from an a_n node to a b_n node within the network flow graph, and these connecting lines always go from a to b . They are associated with an s parameter.

Networks can be cascaded one after the other, and their flow graphs can be cascaded similarly, as in Fig. 3.2-4, which shows two two-port networks treated in this way. It is interesting to note that node b_2 and a_1' are synonymous; a_2 and b_1' are also synonymous. In a flow graph, synonymous nodes can be connected with an arrow having a value of "1," meaning that there is no electrical length between them. These two groups of nodes should not be considered identical; the direction of the arrow between b_2 and a_1' is important. Basic transmission line elements can be divided into one-port, two-port, and multiport groups. Every port will have two nodes: one where the wave enters (a) and the other where the wave leaves that port (b).

Flow graph representation of some one-port networks is shown in Fig.

3.2.4 FLOW GRAPH REPRESENTATION OF MICROWAVE NETWORKS

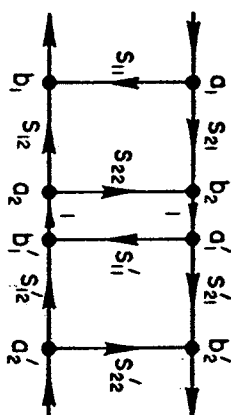


Fig. 3.2-4. Two two-port networks cascaded.

3.2-5. M is the meter reading of an indicator, as shown; K represents the law of the detector and does not change with power level so long as the detector law does not change with power level. Furthermore, M includes the effect of the transmission loss due to the detector's reflection $\sqrt{1 - \rho_d^2}$.

Flow graphs of some two-port networks are shown in Fig. 3.2-6. These flow graphs are only the most-used elements. Remember that Γ stands for

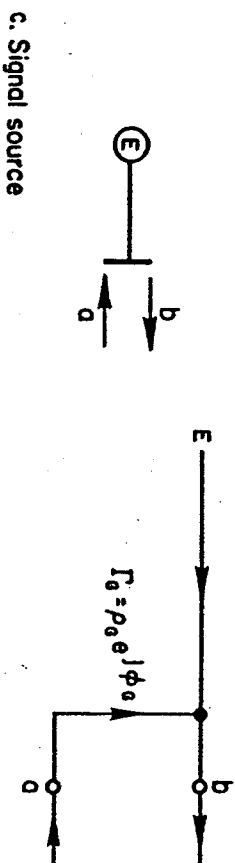
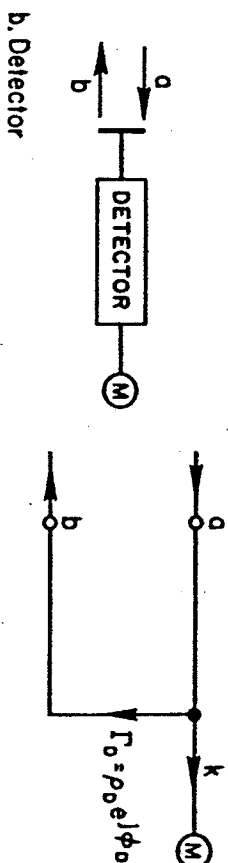
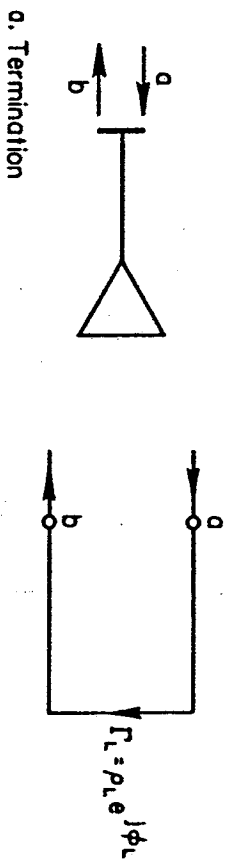



Fig. 3.2-5. Flow graph representation of some one-port networks.

¹ Kuhn, "Simplified Signal Flow Graph Analysis," *Microwave Journal*, November 1963.


Figure 3.2-18 shows the flow graph of a two-port network driven with a signal source and terminated with a load. One path goes from the generator to node b_1 ; its value is s_{11} . There are two paths from the generator to node b_1 . The values of these paths are s_{11} and $s_{11}\Gamma_1 s_{11}$.

If a path starts and finishes in the same node, it is called a "loop," rather than a path. A "first-order loop" is a path coming to a closure with no node passed more than once. The value of the loop is calculated as the value of the path, or the product of the value of all branches encountered en route.

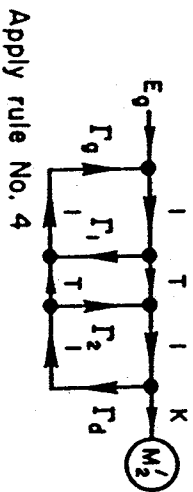
A "second-order loop" is defined as two first-order loops not touching each other at any node. The value of a second-order loop is the product of



Apply rule No. 4

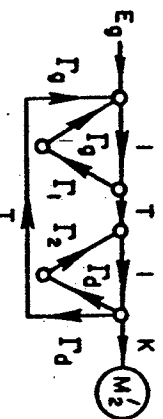

Apply rule No. 1

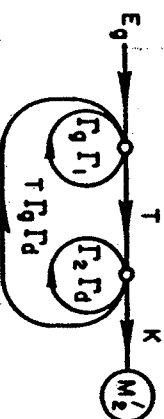

Apply rule No. 3



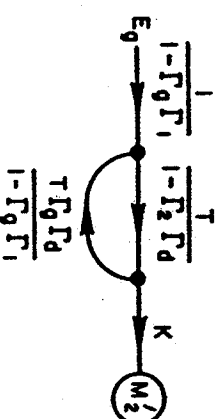



Fig. 3.2-17. Reduction of the measurement flow graph.

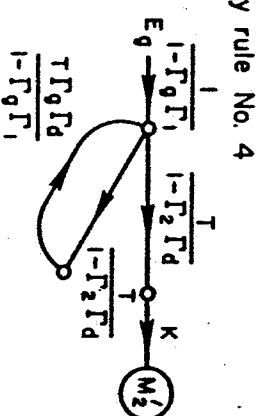


Apply rule No. 4

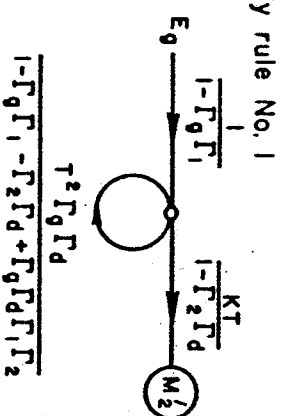

Apply rule No. 1

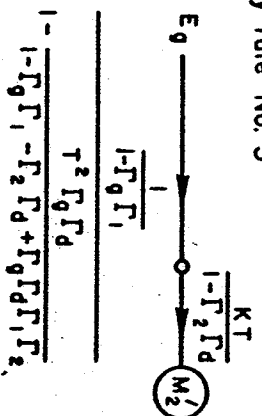

Apply rule No. 3

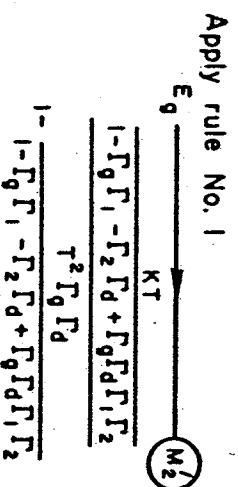

Apply rule No. 1

Fig. 3.2-17 (continued)

the values of the two first-order loops. Third- and higher-order loops are three or more first-order loops not touching each other at any point. Their values are calculated in the same manner as described above for the second-order loop, that is, by multiplying the coefficients of branches encountered.

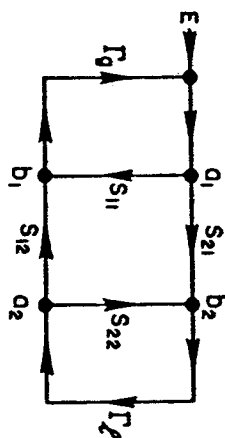


Fig. 3.2-18. Flow graph of a two-port network with a signal source and a load.

For example, in Fig. 3.2-18, there are three first-order loops ($s_{11}T$, $s_{21}T$, and $Ts_{21}T$) and one second-order loop ($Ts_{11}s_{21}T$).

The nontouching-loop rule³ can be applied to solve any flow graph. The equation in symbolic form is

$$T = \frac{P_1[1 - \Sigma L(1)^{(1)} + \Sigma L(2)^{(1)} - \dots] + P_2[1 - \Sigma L(1)^{(2)} + \Sigma L(2)^{(2)} - \dots] + P_3[1 - \Sigma L(1)^{(3)} + \dots] + P_4(1 - \dots)}{1 - \Sigma L(1) + \Sigma L(2) - \Sigma L(3) + \dots}$$

where $\Sigma L(1)$ stands for the sum of all first-order loops, $\Sigma L(2)$ is the sum of all second-order loops, and so on; P_1 , P_2 , P_3 , etc., stand for the values of all paths that can be followed from the independent variable, in most cases the generator, to the node whose value is desired; $\Sigma L(1)^{(1)}$ denotes the sum of those first-order loops which do not touch the path of P_1 at any node; $\Sigma L(2)^{(1)}$ denotes then the sum of those second-order loops which do not touch the path of P_1 at any point; $\Sigma L(1)^{(2)}$ consequently denotes the sum of those first-order loops which do not touch the path of P_2 at any point. Each path is multiplied by the factor in parentheses which involves all the loops of all orders that the path does not touch. T represents the ratio of the dependent variable in question and the independent variable.

The example shown in Fig. 3.2-18 can be calculated for two dependent variables. One is the reflection coefficient of the two-port network b_1/a_1 , and the second is the transmission coefficient b_2/E . In the first case, when b_1/a_1 is to be found, the generator is not involved, so it should be neglected. The solution is

$$\frac{b_1}{a_1} = \frac{s_{11}(1 - s_{21}T) + s_{21}Ts_{11}}{1 - s_{21}T}$$

s_{11} is the first path, P_1 , which has to be multiplied with $1 - \Sigma L(1)^{(1)}$. $s_{21}T$ is the first-order loop not touching the P_1 path; higher-order loops not touching the P_1 path do not exist. Path number two, P_2 , will be $s_{21}Ts_{11}$; since there are no first-order or any higher-order loops not touching this path, it will be multiplied by 1. The denominator shows the only first-order loop, $s_{21}T$, subtracted from unity.

³ Lorens, C. S., "A Proof of the Nontouching Loop Rule for the Solution of Linear Equations by Flow Graphs," Res. Lab. of Electronics, M.I.T., Cambridge, Mass., *Quarterly Progress Report*, January 1956, pp. 97-102.

⁴ Happ, W. W., "Lecture Notes on Signal Flow Graphs," from *Analysis of Transistor Circuits*, Extension Course, University of California, Catalog 834AB.

the only first-order loop not touching the P_1 path; higher-order loops not touching the P_1 path do not exist. Path number two, P_2 , will be $s_{21}Ts_{11}$; since there are no first-order or any higher-order loops not touching this path, it will be multiplied by 1. The denominator shows the only first-order loop, $s_{21}T$, subtracted from unity.

The entire flow graph, including the generator, is needed to write the solution for the transmission coefficient.

$$\frac{b_2}{E} = \frac{s_{21}}{1 - T[s_{11} - s_{21}T - T^2s_{11}s_{21} + T^2s_{11}s_{21}T]}$$

Because there is only one possible path from E to the b_2 node, and there are no loops not touching this path, only s_{21} will stay in the numerator. It can be seen that there are three first-order loops and a second-order loop in the denominator.

It would be interesting to see the attenuation measurement flow graph discussed in the topographical approach as another example. Figure 3.2-15 shows the flow graphs in question. Equations have to be written for M_1/E_0 and M_2/E_0 ; the values of M_1/E_0 and M_2/E_0 have already been found analytically.

$$\frac{M_1}{E_0} = \frac{k}{1 - T^2T_d}$$

since k is the only path and T_dT_d is the only loop.

$$\frac{M_2}{E_0} = \frac{kT}{1 - T^2T_d - T^2T_dT_d + T^2T_dT_dT_d}$$

Again the only path is kT , and all loops touch this path. Three first-order loops and a second-order loop can be found in the denominator.

It is worth mentioning that third- and higher-order loops can usually be neglected after careful analysis of the values of various coefficients in question. This is because values smaller than unity multiplied with each other become even smaller. This point will be emphasized later in the text.

Nontouching-Loop Rule

$$T = \frac{P_1(1 - \Sigma L(1)^{(1)} + \Sigma L(2)^{(1)} - \Sigma L(3)^{(1)} + \dots) + P_2(1 - \Sigma L(1)^{(2)} + \Sigma L(2)^{(2)} - \dots) + P_3(1 - \Sigma L(1)^{(3)} + \dots) + \dots}{1 - \Sigma L(1) + \Sigma L(2) - \Sigma L(3) + \dots}$$

$\Sigma L(1)$ Sum of all first-order loops

$\Sigma L(2)$ Sum of all second-order loops

P_1, P_2, P_3 Values of paths corresponding to indices

$\Sigma L(1)^{(1)}$ Sum of those first-order loops which do not touch P_1

$\Sigma L(2)^{(1)}$ Sum of those second-order loops which do not touch P_1

$\Sigma L(n)^{(m)}$ Sum of those n -order loops which do not touch P_m path


T Ratio of dependent variable in question and independent variable

$$P_o = 2.3 \text{ W (Typ.) } (\sim 10 \text{ GHz})$$

$$G_p = 5 \text{ dB (Typ.) } (\sim 10 \text{ GHz})$$


MITSUBISHI GaAs POWER FET
MGF-X34M
INTERNALLY MATCHING, FLIP-CHIP MOUNTING

S₁₁, S₂₂ vs. f

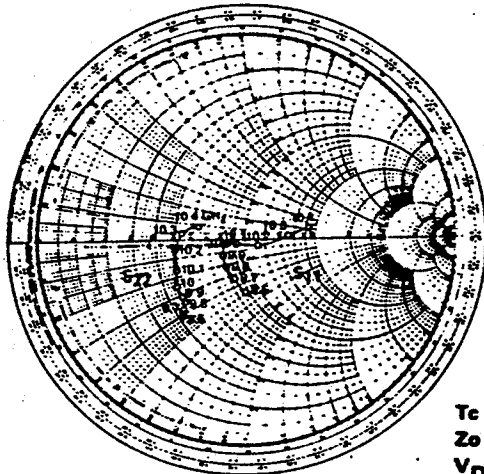

T_c = 25°C
 Z_o = 50 Ω
 V_{DS} = 9 V
 I_D = 900 mA

S₁₂, S₂₁ vs. f

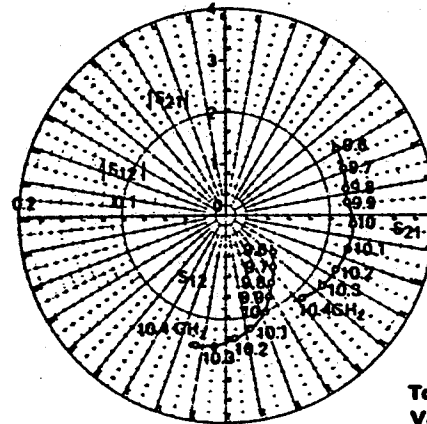

T_c = 25°C
 V_{DS} = 9 V
 I_D = 900 mA

S PARAMETERS (T_c = 25°C, V_{DS} = 9 V, I_D = 900 mA)

f (GHz)	S Parameters (TYP.)							
	S ₁₁		S ₁₂		S ₂₁		S ₂₂	
	Magn.	Angle (deg.)	Magn.	Angle (deg.)	Magn.	Angle (deg.)	Magn.	Angle (deg.)
9.6	0.253	-90.0	0.058	-39.4	2.51	31.2	0.470	-129.8
9.7	0.193	-105.5	0.068	-48.2	2.44	21.9	0.447	-132.8
9.8	0.154	-124.8	0.077	-55.4	2.37	13.1	0.409	-132.9
9.9	0.127	-143.6	0.087	-60.7	2.37	5.6	0.410	-136.5
10.0	0.097	-165.9	0.100	-68.4	2.43	-4.5	0.402	-145.4
10.1	0.036	-156.3	0.111	-78.0	2.42	-15.4	0.359	-155.5
10.2	0.068	-20.2	0.118	-85.8	2.36	-26.5	0.333	-171.7
10.3	0.203	3.5	0.126	-95.2	2.30	-37.5	0.301	173.3
10.4	0.309	10.3	0.128	-103.4	2.17	-48.2	0.227	164.7

Self reflection
coeff.

feedback
coeff.

forward gain

Self refl. coeff.

FHX04FA/LG Fujitsu HEMT (89/90), f=0 extrapolated; Vds=2V, Ids=10mA

f	s11	s21	s12	s22
0.0	1.000	0.0	4.375 180.0	0.000 0.0 0.625 0.0
1.0	0.982	-20.0	4.257 160.4	0.018 74.8 0.620 -15.2
2.0	0.952	-39.0	4.113 142.0	0.033 62.9 0.604 -28.9
3.0	0.910	-57.3	3.934 124.3	0.046 51.5 0.585 -42.4
4.0	0.863	-75.2	3.735 107.0	0.057 40.3 0.564 -55.8
5.0	0.809	-92.3	3.487 90.4	0.065 30.3 0.541 -69.2
6.0	0.760	-108.1	3.231 75.0	0.069 21.0 0.524 -82.0
7.0	0.727	-122.4	3.018 60.9	0.072 14.1 0.521 -93.6
8.0	0.701	-135.5	2.817 47.3	0.073 7.9 0.524 -104.7
9.0	0.678	-147.9	2.656 33.8	0.074 1.6 0.538 -115.4
10.0	0.653	-159.8	2.512 20.2	0.076 -4.0 0.552 -125.7
11.0	0.623	-171.1	2.367 7.1	0.076 -10.1 0.568 -136.4
12.0	0.601	178.5	2.245 -5.7	0.076 -15.9 0.587 -146.4
13.0	0.582	168.8	2.153 -18.4	0.076 -21.9 0.611 -156.2
14.0	0.564	160.2	2.065 -31.2	0.077 -28.6 0.644 -165.4
15.0	0.533	151.6	2.001 -44.5	0.079 -36.8 0.676 -174.8
16.0	0.500	142.8	1.938 -58.8	0.082 -48.5 0.707 174.2
17.0	0.461	134.3	1.884 -73.7	0.083 -61.7 0.733 163.6
18.0	0.424	126.6	1.817 -89.7	0.085 -77.9 0.758 150.9
19.0	0.385	121.7	1.708 -106.5	0.087 -97.2 0.783 139.1
20.0	0.347	119.9	1.613 -123.7	0.098 -119.9 0.793 126.6

ATF-21186 Typical Scattering Parameters, Common Source, $Z_0 = 50 \Omega$, $V_{DS} = 2 \text{ V}$, $I_{DS} = 15 \text{ mA}$

Frequency MHz	S_{11}		S_{21}		S_{12}		S_{22}	
	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
500	0.98	-49	3.77	147	0.069	62	0.34	-55
1000	0.92	-61	3.42	133	0.092	54	0.33	-63
2000	0.81	-87	2.85	108	0.131	39	0.32	-81
3000	0.72	-114	2.41	84	0.159	25	0.29	-105
4000	0.64	-143	2.11	61	0.178	13	0.26	-135
5000	0.62	-172	1.83	39	0.186	1	0.25	-170
6000	0.61	-162	1.69	19	0.189	-8	0.28	-162
7000	0.63	140	1.39	2	0.192	-15	0.33	-144
8000	0.65	123	1.25	-14	0.200	-20	0.37	-129

ATF-21186 Typical Scattering Parameters, Common Source, $Z_0 = 50 \Omega$, $V_{DS} = 2 \text{ V}$, $I_{DS} = 20 \text{ mA}$

Frequency MHz	S_{11}		S_{21}		S_{12}		S_{22}	
	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
500	0.98	-51	4.17	146	0.066	61	0.31	-62
1000	0.91	-64	3.78	132	0.087	54	0.30	-69
2000	0.80	-90	3.11	107	0.123	40	0.28	-87
3000	0.70	-118	2.60	83	0.150	27	0.26	-111
4000	0.63	-147	2.25	60	0.169	16	0.23	-142
5000	0.61	-176	1.94	39	0.180	5	0.23	-178
6000	0.61	159	1.68	20	0.187	-4	0.28	-155
7000	0.62	137	1.47	2	0.193	-11	0.33	-138
8000	0.64	120	1.32	-13	0.205	-17	0.36	-125

ATF-21186 Typical Scattering Parameters, Common Source, $Z_0 = 50 \Omega$, $V_{DS} = 3 \text{ V}$, $I_{DS} = 70 \text{ mA}$

Frequency MHz	S_{11}		S_{21}		S_{12}		S_{22}	
	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.	Mag.	Ang.
500	0.95	-30	6.69	156	0.04	74	0.31	-26
1000	0.87	-57	5.74	136	0.06	63	0.20	-58
2000	0.69	-105	4.30	102	0.10	48	0.18	-109
3000	0.63	-139	3.36	80	0.12	41	0.18	-149
4000	0.62	-170	2.63	60	0.14	33	0.22	-178
5000	0.63	165	2.12	42	0.15	28	0.27	-161
6000	0.67	147	1.76	26	0.17	23	0.33	-146
7000	0.71	133	1.49	13	0.18	18	0.39	-136
8000	0.74	126	1.29	5	0.19	16	0.43	-131

ATF-21186 Typical Noise Parameters, Common Source, $Z_0 = 50 \Omega$, $V_{DS} = 2 \text{ V}$, $I_{DS} = 10 \text{ mA}$


Frequency MHz	NF _{dB}	T_{opt}		RN/50 Ω
		Mag.	Ang.	
500	0.67	0.83	30	0.78
1000	0.61	0.80	39	0.58
2000	0.71	0.76	61	0.48
4000	0.90	0.72	109	0.23
6000	1.09	0.71	168	0.04
8000	1.29	0.73	-145	0.10

ATF-21186 Typical Noise Parameters, Common Source, $Z_0 = 50 \Omega$, $V_{DS} = 2 \text{ V}$, $I_{DS} = 15 \text{ mA}$

Frequency MHz	NF _{dB}	T_{opt}		RN/50 Ω
		Mag.	Ang.	
500	0.50	0.91	31	0.68
1000	0.55	0.87	40	0.49
2000	0.65	0.77	63	0.40
4000	0.84	0.66	111	0.29
6000	1.13	0.65	171	0.04
8000	1.23	0.79	-141	0.11

ATF-21186 Typical Noise Parameters, Common Source, $Z_0 = 50 \Omega$, $V_{DS} = 2 \text{ V}$, $I_{DS} = 20 \text{ mA}$

Frequency MHz	NF _{dB}	T_{opt}		RN/50 Ω
		Mag.	Ang.	
500	0.45	0.88	31	0.56
1000	0.50	0.84	41	0.43
2000	0.60	0.75	64	0.35
4000	0.82	0.65	113	0.16
6000	1.03	0.65	174	0.03
8000	1.24	0.69	-139	0.11

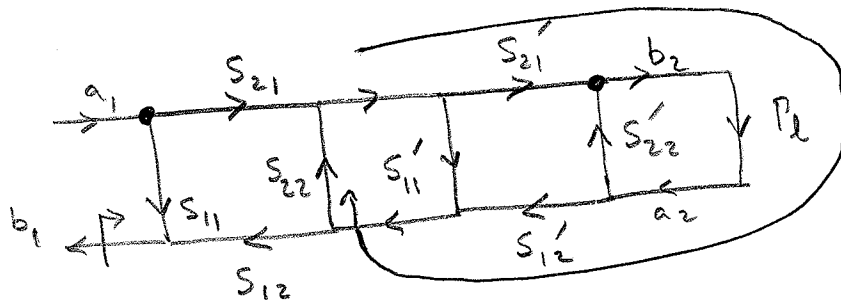

calculate $\frac{b_1}{a_1}$

Paths between b_1 and a_1

	Value	First order Non-touching Loops $L(1)$	2nd order Non-touching Loop $L(2)$
P_1	S_{11}	$S'_{11} S_{22}, P_L S'_{22}, S_{22} S'_{21} P_L S'_{12}$	$(S'_{11} S_{22})(P_L S'_{22})$
P_2	$S_{21} S'_{11} S_{12}$	$P_L S'_{22}$	0
P_3	$S_{21} S'_{21} P_L S'_{12} S_{12}$	—	—

$$P_1 = \frac{b_1}{a_1} = S_{11} + \frac{S'_{21} S'_{11} S_{12} [1 - P_L S'_{22}] + S_{21} S'_{21} P_L S'_{12} S_{12}}{1 - \{ S'_{11} S_{22} + P_L S'_{22} + S_{22} S'_{21} P_L S'_{12} \} + \underbrace{(S'_{11} S_{22})(P_L S'_{22})}_{\text{second order loop}}}$$

$$S_{11} |_{\text{total circuit}} = P_1 |_{a_2=0} \Rightarrow P_1 |_{P_L=0} = S_{11} + \frac{S'_{21} S'_{11} S_{12}}{1 - S'_{11} S_{22}}$$

$$\frac{b_2}{a_1} = \frac{S_{21} S'_{21} P_L S'_{12} S_{12}}{1 - (S'_{22} P_L + S'_{11} S_{22} + S'_{21} P_L S'_{12} S_{22}) + (S'_{11} S_{22})(P_L S'_{22})}$$


$$S_{21} T \rightarrow \frac{b_2}{a_1} \Big|_{\text{if } P_L=0} \Rightarrow \frac{S_{21} S'_{21}}{1 - S'_{11} S_{22}} \Rightarrow \frac{S_{21}^A S_{21}^B}{1 - S_{11}^B S_{22}^A}$$

Power delivered to the load (P_L) = $b_2 b_2^* (1 - |P_L|^2)$

Fractional power reflected = $\frac{b_1 b_1^*}{a_1 a_1^*}$

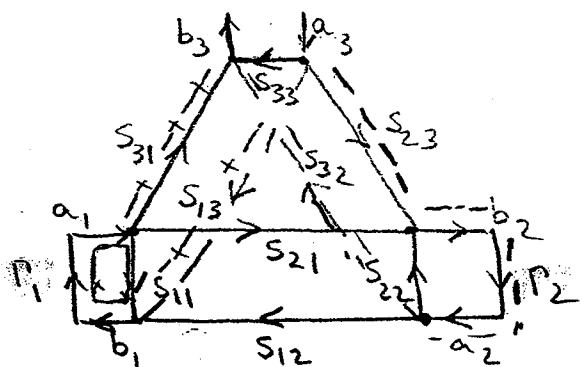Example of a 3 port network (see also p.90 of the handbook from Adams book) 2

Find the reflection coefficient at port 3 if ports 1 and 2 are mismatched with reflection coefficients Γ_1 and Γ_2 , respectively.



Do not draw any branches for which the value is zero

Paths between a_3 and b_3

	value	First order Non touching loops $L(1)$	Second order Non touching loops $L(2)$
Γ_1	S_{33}	$\Gamma_1 S_{11}, \Gamma_2 S_{22}, \Gamma_1 S_{21}, \Gamma_2 S_{12}$	$(\Gamma_1 S_{11})(\Gamma_2 S_{22})$
Γ_2	$S_{23} \Gamma_2 S_{32}$	$\Gamma_1 S_{11}$	—
Γ_3	$S_{13} \Gamma_1 S_{31}$	$\Gamma_2 S_{22}$	—
Γ_4	$S_{23} \Gamma_2 S_{12} \Gamma_1 S_{31}$	—	—
Γ_5	$S_{13} \Gamma_1 S_{21} \Gamma_2 S_{32}$	—	—

All First order loops touching or nontouching $L(1)$

$$\Gamma_1 S_{11}, \Gamma_2 S_{22}, \Gamma_1 S_{21}, \Gamma_2 S_{12}$$

All second order loops touching or nontouching $L(2)$

$$(\Gamma_1 S_{11})(\Gamma_2 S_{22})$$

$$\frac{b_3}{a_3} = S_{33} + \frac{S_{23} \Gamma_2 S_{32} (1 - \Gamma_1 S_{11}) + S_{13} \Gamma_1 S_{31} (1 - \Gamma_2 S_{22}) + S_{23} \Gamma_2 S_{12} \Gamma_1 S_{31} + S_{13} \Gamma_1 S_{21} \Gamma_2 S_{32}}{1 - (\Gamma_1 S_{11} + \Gamma_2 S_{22} + \Gamma_1 S_{21} \Gamma_2 S_{12}) + (\Gamma_1 S_{11})(\Gamma_2 S_{22})}$$

Power Gain of a microwave Amplifier

We have previously derived (for an imperfectly matched output)

$$\Gamma_1 = \Gamma_{in} = \frac{b_1}{a_1} = S_{11} + \frac{S_{22} S_{21} \Gamma_L}{1 - S_{22} \Gamma_L} \quad (11.3 a)$$

This equation can be used to obtain Z_{in} since $\Gamma_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0}$

We can similarly write Γ_2 (for an imperfectly matched input)

$$\Gamma_2 = \Gamma_{out} = \frac{b_2}{a_2} = S_{22} + \frac{S_{12} S_{21} \Gamma_S}{1 - S_{11} \Gamma_S} \quad (11.3 b)$$

By voltage division

$$V_1 = V_{in} = V_S \frac{Z_{in}}{Z_{in} + Z_S} = V_1^+ + V_1^- = V_1^+ (1 + \Gamma_{in}) \quad (1)$$

$$\text{Using } Z_{in} = Z_0 \frac{1 + \Gamma_{in}}{1 - \Gamma_{in}} \quad (2)$$

$$\text{and } \Gamma_S = \frac{Z_S - Z_0}{Z_S + Z_0} \text{ which gives } Z_S = Z_0 \frac{1 + \Gamma_S}{1 - \Gamma_S} \quad (3)$$

Combining Eqs. (1), (2), (3) we can write

$$V_1^+ = \frac{V_S}{2} \frac{1 - \Gamma_S}{1 - \Gamma_S \Gamma_{in}} \quad (11.4)$$

If peak values are assumed for all voltages, the average power delivered to the amplifier is

$$\begin{aligned} P_{in} &= |a_1|^2 - |b_1|^2 = \frac{|V_1^+|^2}{2 Z_0} (1 - |\Gamma_{in}|^2) \\ &= \frac{V_S^2}{8 Z_0} \frac{|1 - \Gamma_S|^2}{|1 - \Gamma_S \Gamma_{in}|^2} (1 - |\Gamma_{in}|^2) \quad (11.5) \end{aligned}$$

$$\text{Power delivered to the load} = |b_2|^2 - |a_2|^2 = \frac{|V_2^-|^2}{2 Z_0} (1 - |\Gamma_L|^2) \quad (4)$$

We have previously derived (on p. 3 of the handout)

$$\frac{b_2}{a_1} = \frac{V_2^-}{V_1^+} = \frac{S_{21}}{1 - S_{22} \Gamma_L} \quad (5)$$

Thus power delivered to the load

$$P_L = \frac{|V_1^+|^2}{2 Z_0} \frac{|S_{21}|^2 (1 - |\Gamma_L|^2)}{|1 - S_{22} \Gamma_L|^2} = \frac{V_S^2}{8 Z_0} \frac{|1 - \Gamma_S|^2 |S_{21}|^2 (1 - |\Gamma_L|^2)}{|1 - S_{22} \Gamma_L|^2 |1 - \Gamma_S \Gamma_{in}|^2} \quad (11.7)$$

The power gain can now be written in terms of S-parameters of the amplifier (4)

$$G = \frac{P_L}{P_{in}} = \frac{|S_{21}|^2 (1 - |\Gamma_L|^2)}{(1 - |\Gamma_{in}|^2) |1 - S_{22} \Gamma_L|^2} \quad (11.8)$$

Where Γ_{in} is given by Eq. 11.3 a.

Note that the power gain obtained in Eq. (11.8) is quite complex, involving as it does, P_L , also for P_{in} and the S-parameters also in Γ_{in} from Eq. 11.3

The maximum power available from the source (deliverable to the input) is for the condition $\Gamma_{in} = \Gamma_s^*$. Under this input conjugate matching condition, the maximum input power P_{avs} can be written from Eq. (11.5)

$$P_{avs} = P_{in} \Big|_{\Gamma_{in} = \Gamma_s^*} = \frac{|V_s|^2}{8 Z_0} \frac{|1 - \Gamma_s|^2}{(1 - |\Gamma_s|^2)} \quad (11.9)$$

Similarly the ^{output} power available from the amplifier is that delivered to a matched load for which $\Gamma_L = \Gamma_{out}^*$

From Eq. 11.7

$$P_{avn} = P_L \Big|_{\Gamma_L = \Gamma_{out}^*} = \frac{|V_s|^2}{8 Z_0} \frac{|S_{21}|^2 (1 - |\Gamma_{out}|^2) |1 - \Gamma_s|^2}{|1 - S_{22} \Gamma_{out}^*|^2 |1 - \Gamma_s \Gamma_{in}|^2} \quad (11.10)$$

However, in Eq. 11.10, Γ_{in} must be evaluated for the output load $\Gamma_L = \Gamma_{out}^*$. For this conjugate matched output condition

$$\Big|_{\Gamma_L = \Gamma_{out}^*} |1 - \Gamma_s \Gamma_{in}|^2 = \frac{|1 - S_{11} \Gamma_s|^2 (1 - |\Gamma_{out}|^2)^2}{|1 - S_{22} \Gamma_{out}^*|^2} \quad (6)$$

Substituting (6) into Eq. (11.10) gives maximum available output power

$$P_{avn} = \frac{|V_s|^2}{8 Z_0} \frac{|S_{21}|^2 |1 - \Gamma_s|^2}{|1 - S_{11} \Gamma_s|^2 (1 - |\Gamma_{out}|^2)} \quad (11.11)$$

From Eqs. 11.11 and 11.9, the available power gain can be written as

$$G_A = \frac{P_{avn}}{P_{avs}} = \frac{|S_{21}|^2 (1 - |\Gamma_s|^2)}{|1 - S_{11} \Gamma_s|^2 (1 - |\Gamma_{out}|^2)} \quad (11.12)$$

From Eqs. (11.7) and (11.9), the transducer power gain is

$$G_T = \frac{P_L}{P_{avs}} = \frac{|S_{21}|^2 (1 - |\Gamma_S|^2) (1 - |\Gamma_L|^2)}{|1 - \Gamma_S \Gamma_{in}|^2 |1 - S_{22} \Gamma_L|^2} \quad (11.13)$$

Special case I

For a special case where both input and output are matched for zero reflection i.e. $\Gamma_L = \Gamma_S = 0$, Eq. (11.13) reduces to

$$G_T \Big|_{\Gamma_L = \Gamma_S = 0} = |S_{21}|^2 \quad (11.14)$$

Special case II unilateral transducer power gain G_{TU} can be obtained if $S_{12} = 0$

For the case $S_{12} \approx 0$

From Eq. 11.3a, $\Gamma_{in} = S_{11}$

From Eq. 11.13

$$G_{TU} = \frac{|S_{21}|^2 (1 - |\Gamma_S|^2) (1 - |\Gamma_L|^2)}{|1 - S_{11} \Gamma_S|^2 |1 - S_{22} \Gamma_L|^2} \quad (11.15)$$

For the example 11.1 on p. 539 Text

$$G_{TU} = \frac{(2.05)^2 (1 - (0.429)^2) (1 - (0.25)^2)}{|1 + 0.429 \times 0.45 \angle 15^\circ|^2 |1 + 0.25 \times 0.4 \angle -15^\circ|^2}$$

$$= \boxed{4.654}$$

Calculation of Power Gain Expressions Using alternative procedure (5')

From Mason's formula

$$\frac{b_2}{a_1} = \frac{S_{21}}{1 - S_{22}\Gamma_L} \quad (1)$$

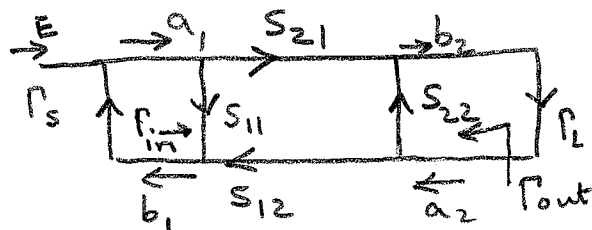


Fig. 1 Flow Graph of the amplifier of Fig. 11.1 with source and load mismatches

1. Power Gain = $\frac{\text{Power delivered to the load}}{\text{Power input to the amplifier}}$

$$= \frac{b_2 b_2^* (1 - |\Gamma_L|^2)}{a_1 a_1^* - b_1 b_1^*} = \frac{b_2 b_2^* (1 - |\Gamma_L|^2)}{a_1 a_1^* (1 - |\Gamma_{in}|^2)} = \frac{|S_{21}|^2 (1 - |\Gamma_L|^2)}{|1 - S_{22}\Gamma_L|^2 (1 - |\Gamma_{in}|^2)} \quad \text{from Eq. (1)}$$

Note that $b_1 = \Gamma_{in} a_1$ (2) (11.8)

2. Maximum power available from the source is for matching condition

$$\Gamma_{in} = \Gamma_s^*$$

$$P_{avs} = a_1 a_1^* - b_1 b_1^* = a_1 a_1^* (1 - |\Gamma_{in}|^2) = \frac{E E^* (1 - |\Gamma_{in}|^2)}{|1 - \Gamma_s \Gamma_{in}|^2} \quad \text{from (5)} \quad (3)$$

$$a_1 = E + \Gamma_s b_1 = E + \Gamma_s \Gamma_{in} a_1 \quad \text{from (2)} \quad (4)$$

Thus $a_1 = \frac{E}{1 - \Gamma_s \Gamma_{in}}$ (5)

Max. Power delivered to the load (for conjugate matched condition $\Gamma_L = \Gamma_{out}^*$)

$$P_{avn} = b_2 b_2^* (1 - |\Gamma_L|^2) = a_1 a_1^* \frac{|S_{21}|^2}{|1 - S_{22}\Gamma_L|^2} = \frac{E E^* |S_{21}|^2 (1 - |\Gamma_{out}|^2)}{|1 - \Gamma_s \Gamma_{in}|^2 |1 - S_{22}\Gamma_L|^2} \quad \text{from (5)} \quad (11.10)$$

The rest of the steps are the same as on p. 539 of the Text

$$\text{Available power gain } G_A = \frac{P_{avn}}{P_{avs}} = \frac{|S_{21}|^2 (1 - |\Gamma_s|^2)}{|1 - S_{11}\Gamma_s|^2 (1 - |\Gamma_{out}|^2)} \quad (11.12)$$

$$\text{Transducer power gain } G_T = \frac{P_L}{P_{avs}} = \frac{|S_{21}|^2 (1 - |\Gamma_s|^2) (1 - |\Gamma_L|^2)}{|1 - \Gamma_s \Gamma_{in}|^2 |1 - S_{22}\Gamma_L|^2} \quad (11.13)$$


For the condition when both input and output are well-matched

$$\Gamma_L = \Gamma_s = 0$$

$$\text{Transducer power gain } G_T = |S_{21}|^2 \quad (11.14)$$

ABCD parameters

.183

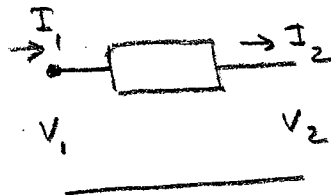

$$V_1 = A V_2 + B I_2$$


$$I_1 = C V_2 + D I_2$$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = 1$$


$$B = \left. \frac{V_1}{I_2} \right|_{V_2=0} = Z$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0} = 0$$

$$D = 1$$

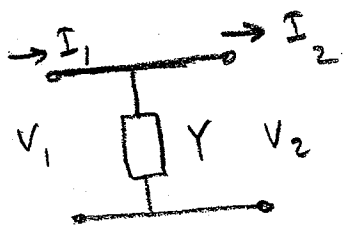
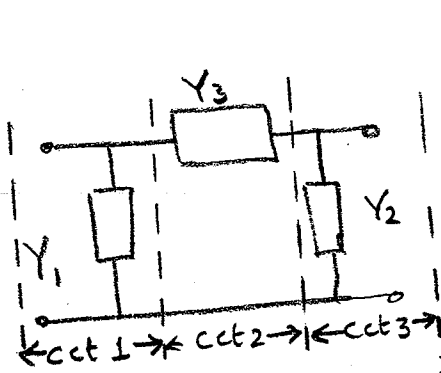
$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix}$$



$$\begin{bmatrix} 1 & 0 \\ Y_1 & 1 \end{bmatrix} \begin{bmatrix} 1 & \frac{1}{Y_3} \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ Y_2 & 1 \end{bmatrix}$$

$$= \begin{bmatrix} 1 & 0 \\ Y_1 & 1 \end{bmatrix} \begin{bmatrix} 1 + \frac{Y_2}{Y_3} & \frac{1}{Y_3} \\ Y_2 & 1 \end{bmatrix}$$

$$= \begin{bmatrix} 1 + \frac{Y_2}{Y_3} & \frac{1}{Y_3} \\ Y_1 \left(1 + \frac{Y_2}{Y_3}\right) + Y_2 & \frac{Y_1}{Y_3} + 1 \end{bmatrix}$$


Note that $AD - BC = \left(1 + \frac{Y_2}{Y_3} + \frac{Y_1}{Y_3} + \frac{Y_1 Y_2}{Y_3}\right) - \left(\frac{Y_1}{Y_3} \left(1 + \frac{Y_2}{Y_3}\right) + \frac{Y_2}{Y_3}\right)$

$$= 1$$

for all reciprocal circuits with bilateral performance

$$Z_{12} = Z_{21}; \quad Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}; \quad Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

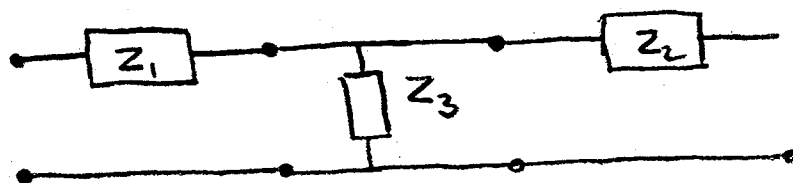ABCD Parameters of the circuit in item 6 of Table 4.1



This circuit may be considered to be composed of 3 circuits in cascade, as sketched above.

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & Z_1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ \frac{1}{Z_3} & 1 \end{bmatrix} \begin{bmatrix} 1 & Z_2 \\ 0 & 1 \end{bmatrix}$$

$$= \begin{bmatrix} 1 & Z_1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & Z_2 \\ \frac{1}{Z_3} & \frac{Z_2}{Z_3} + 1 \end{bmatrix}$$

$$= \begin{bmatrix} 1 + \frac{Z_1}{Z_3} & Z_1 + Z_2 + \frac{Z_1 Z_2}{Z_3} \\ -\frac{1}{Z_3} & \frac{Z_2}{Z_3} + 1 \end{bmatrix}$$

You may also be able to derive the ABCD parameters using the defining relationships given in (4.63)

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0}, \quad B = \left. \frac{V_1}{I_2} \right|_{V_2=0} \quad \text{etc.}$$

For homework problem, this basic approach should be followed.