

One Port Negative-Resistance Oscillators

$$Z_{IN}(A, \omega) = R_{IN}(A, \omega) + j X_{IN}(A, \omega)$$

$A \rightarrow$  amplitude of  $i(t)$

$$R_{IN}(A, \omega) < 0$$

The oscillator is constructed by connecting the device to a passive load impedance

$$Z_L(\omega) = R_L(\omega) + j X_L(\omega)$$

The one-port N/w is stable if:

$$\operatorname{Re}[Z_{IN}(A, \omega) + Z_L(\omega)] > 0$$

For oscillation to occur, the loop gain must be unity

$$|P_{IN}(j\omega)| |P_L(j\omega)| = 1$$

At the amplitude  $A = A_0$  & frequency  $\omega = \omega_0$ , the Nlw ② will oscillate when

$$P_{in}(A_0, \omega_0) P_L(\omega_0) = 1 \quad - (1)$$

$$P_{in}(A_0, \omega_0) = \frac{Z_{in}(A_0, \omega_0) - Z_0}{Z_{in}(A_0, \omega_0) + Z_0} \quad - (2)$$

$$P_L(\omega_0) = \frac{Z_L(\omega_0) - Z_0}{Z_L(\omega_0) + Z_0} \quad - (3)$$

From the three equations we get

$$Z_{in}(A_0, \omega_0) + Z_L(\omega_0) = 0$$

Equating real & imaginary part

$$R_{in}(A_0, \omega_0) + R_L(\omega_0) = 0$$

$$X_{in}(A_0, \omega_0) + X_L(\omega_0) = 0$$

The device is defined to be unstable over some frequency range  $\omega_1 < \omega < \omega_2$  if  $R_{in}(A, \omega) < 0$ . The one-port Nlw is unstable for some  $\omega$  if the range if the net resistance of the network is negative - i.e.

$$R_{IN}(A, \omega) > R_L(\omega) \quad - (A)$$

Under proper conditions, a growing sinusoidal current will flow through the circuit i.e. at the start of oscillations, when amplitude  $A$  is small ( $A$ ) must be satisfied. This is expressed in the form

$$|R_{IN}(0, \omega)| > R_L(\omega)$$

The oscillations will continue to build up as long as the loop resistance is negative.

The amplitude of the current must eventually reach a steady-state value (i.e. at  $A=A_0$  and  $\omega=\omega_0$ ), which occurs when the loop resistance is zero.

$Z_{IN}(A, \omega)$  is amplitude and frequency dependent. It is necessary to find another condition to guarantee a stable oscillation.

If the frequency dependence of  $Z_{IN}(A, \omega)$  can be neglected for small variations around  $\omega_0$ .

Kurokawa has shown that a stable oscillation is obtained when (16) & (17) are satisfied and the following condition is also satisfied.

$$\frac{\partial R_{IN}(A)}{\partial A} \left|_{A=A_0} \cdot \frac{\partial X_i(\omega)}{\partial \omega} \right|_{\omega=\omega_0} - \frac{\partial X_{IN}}{\partial A} \Big|_{A=A_0} \frac{\partial R_i(\omega)}{\partial \omega} \Big|_{\omega=\omega_0} > 0$$

In many cases

$$\frac{\partial R_i(\omega)}{\partial \omega} > 0$$

In a given oscillator design, the 1/p impedance of the active device is known for small-signal conditions.

A practical way of designing  $R_i$  is to select the value of  $R_i$  for maximum oscillator power.

If magnitude of -ve resistance is a linearly decreasing function of  $A$ , we can express  $R_{IN}(A)$  in the form

$$R_{IN}(A) = -R_0 \left[ 1 - \frac{A}{A_m} \right]$$

$-R_0$  is value of  $R_{IN}(A)$  at  $A=0$  &  $A_m$  is maximum value of  $A$ .

The power delivered to  $R_i$  by  $R_{IN}$  (for  $A < A_m$ )

$$P = \frac{1}{2} \operatorname{Re}[VI^*] = \frac{1}{2} |I|^2 R_{IN}(A) > \frac{1}{2} A^2 R_0 \left[ 1 - \frac{A}{A_m} \right]$$

Value of  $A$  that maximizes the oscillation power is found from

$$\frac{dP}{dA} = \frac{1}{2} R_0 \left[ 2A - \frac{3A^2}{A_m} \right] = 0$$

which gives desired value of  $A$ , denoted by  $A_{o,\max}$ , that maximizes the power

$$A_{o,\max} = \frac{2}{3} A_m$$

At  $A_{o,\max}$  the value of  $R_{IN}(A_{o,\max})$  is,


$$R_{IN}(A_{o,\max}) = -\frac{R_0}{3}$$

A convenient value of  $R_L$ , which maximizes the oscillator power

$$R_L = \frac{R_0}{3}$$
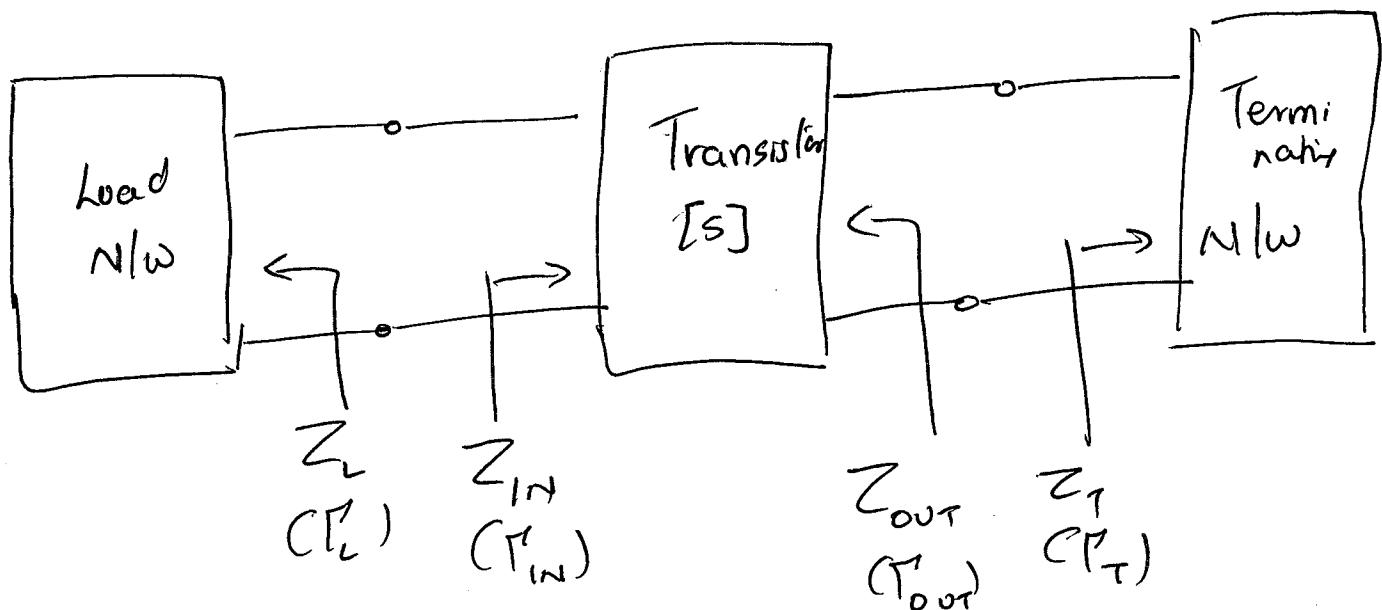
## Two-port Negative-Resistance Oscillators.

→ The general block diagrams for two-parts negative resistance oscillators are shown in figure (a) & (b)



- Either part can be used as the terminating part
- Once termination part is selected, the other part is referred to as the i/p part.
- The load-matching  $N/w$  is connected to the i/p part in agreement with the one part notation.
- When the two-part is potentially unstable, an appropriate  $Z_T$  permits the two-part to be represented as a one-part negative-resistance device with input impedance  $Z_{IN}$ .
- The conditions for a stable oscillation are:

$$R_{IN}(A_0, \omega_0) + R_L(\omega_0) = 0$$

$$X_{IN}(A_0, \omega_0) + X_L(\omega_0) = 0$$

$\delta$

$$\left| \frac{\partial R_{IN}(A)}{\partial A} \right|_{A=A_0} \left| \frac{\partial X_L(\omega)}{\partial \omega} \right|_{\omega=\omega_0} - \left| \frac{\partial X_{IN}(A)}{\partial A} \right|_{A=A_0} \left| \frac{\partial R_L(\omega)}{\partial \omega} \right|_{\omega=\omega_0} > 0$$

→ To start the oscillation, the value of  $R_L$  is selected according to

$$R_L = \frac{R_0}{3}, \text{ in general } R_L = \frac{|R_{IN}(0, \omega)|}{3}$$

When i/p port is made to oscillate, the terminating port also oscillates. The fact that both ports are oscillating can be proved as follows.

→ i/p port is oscillating when

$$\Gamma_{IN} \Gamma_L = 1$$

$$\Gamma_L = \frac{1}{\Gamma_{IN}} = \frac{1 - S_{22} \Gamma_T}{S_{11} - \Delta \Gamma_T}$$

$$\Gamma_T = \frac{1 - S_{11} \Gamma_L}{S_{22} - \Delta \Gamma_L}$$

$$\Gamma_{\text{OUT}} = \frac{S_{22} - A\Gamma_L}{1 - S_{11}\Gamma_L}$$

$$\Gamma_{\text{OUT}} \Gamma_T = 1$$

which shows that the terminating port is also oscillating

A design procedure for a two-port oscillator is as follows.

- 1) Use a potentially unstable transistor at the frequency of oscillation  $\omega_0$ .
- 2) Design the terminating Nlw to make  $|P_W| > 1$ . Series or shunt feedback can be used to increase  $|P_W|$
- 3) Design the load Nlw to resonate  $Z_{IN}$ , and to satisfy the start of oscillation condition. i.e

$$X_L(\omega_0) = -X_W(\omega_0)$$

8

$$R_C = \frac{R_o}{3}$$

5.3.1 Design 8 GHz GaAs FET

$$S_{11} = 0.98 \angle 163^\circ \quad S_{12} = 0.39 \angle -54^\circ$$

$$S_{21} = 0.675 \angle -161^\circ \quad S_{22} = 0.465 \angle 120^\circ$$

Soln

①  $K = ? \quad K = 0.529$

② Draw Terminating stability circle

a) Calculate

$$\rho_s = \left| \frac{S_{12} S_{21}}{|S_{11}|^2 - |\Delta|^2} \right| \quad C_s = \frac{(S_{11} - \Delta S_{22})^*}{|S_{11}|^2 - |\Delta|^2}$$

③ Choose a point in the unstable region

in the example we choose point A ( $\Gamma_T = 1 \angle -163^\circ$ )

The associated impedance  $Z_T = -j7.5 \Omega$

④ With  $Z_T$  connected the i/p reflection coefficient is found:

$$\Gamma_{IN} = \frac{S_{11} - \Delta \Gamma_T}{1 - S_{22} \Gamma_T}$$

$$\Gamma_{IN} = S_{11} + \frac{S_{12} S_{21} \Gamma_T}{1 - S_{22} \Gamma_T}$$

⑤ Calculate  $Z_{IN} = -58 - j2.6 \Omega$

⑥ Load matching N/w can be modeled as:

$$X_L(\omega_0) = -X_{IN}(\omega_0)$$

&

$$R_L = \frac{R_o}{3}$$

$$Z_L = 19 + j 2.6 \Omega$$


### Example 2

$$S_{11} = 0.5 \angle -95^\circ$$


$$S_{21} = 1.1 \angle 44^\circ$$

$$S_{12} = 0.35 \angle -31^\circ$$

$$S_{22} = 0.8 \angle 46^\circ$$

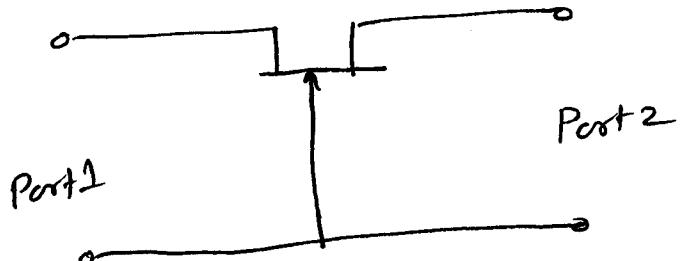

$$f = 9 \text{ GHz}$$

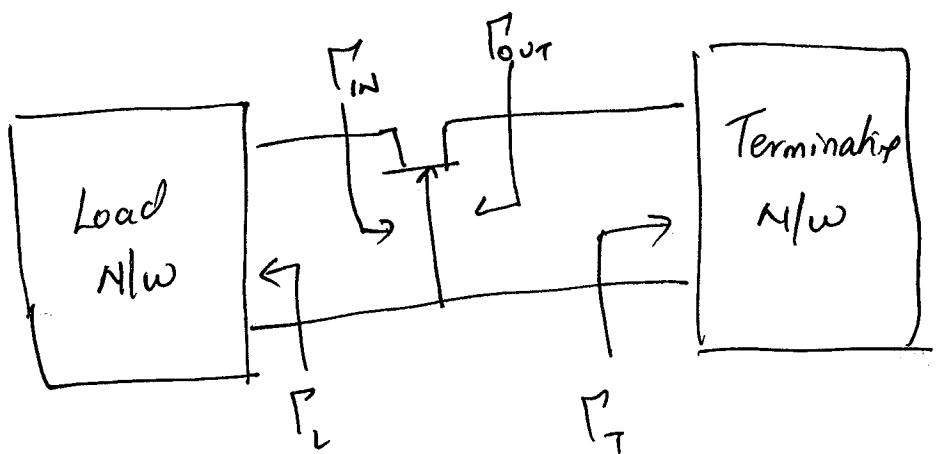

Soln

① Calculate  $K \& |\Delta|$

$$K = 0.355$$

$$|\Delta| = 0.405$$

Since  $K < 1$  the transistor is potentially unstable

② We use port 2 as the terminating port

③ Calculate  $R_L$  &  $C_L$

$$R_L = \left| \frac{S_{12} S_{21}}{(S_{22})^2 - |\Delta|^2} \right|$$

$$C_L = \frac{(S_{22} - \Delta S_{11}^*)^*}{(S_{22})^2 - |\Delta|^2}$$

We get  $R_T$  &  $C_T$

$$R_T = 0.808 \quad C_T = 1.493 L^{-59.8^\circ}$$

④ Any  $\Gamma_T$  in the shaded region will produce a negative resistance.

The reflection coefficient  $\Gamma_T$  is selected at a point for eq ( $1 L^{-67.38^\circ}$ )

$$Z_T = -j 75 \Omega$$

⑤  $\Gamma_{IN} = S_{11} + \frac{S_{12} S_{21} \Gamma_T}{1 - S_{22} \Gamma_T}$

$$\Gamma_{IN} = 1.49 L^{-100.43^\circ}$$

$$Z_{IN} = 16.25 - j 38.95 \Omega$$

$$X_L - X_{IN} = 38.95 \Omega$$

$$R_L = \frac{|R_{IN}|}{3} = \frac{16.25}{3} = 5.42 \Omega$$

For -ve resistance oscillators at microwave frequencies using BJTs the CB (common base) configuration is normally used. For FETs, the CG configuration is commonly used.


In these configurations the transistors are usually potentially unstable, and this is a very desirable condition in oscillator design.

- In -ve resistance oscillator, the capacitances of the transistor provide some or all of the feedback needed for oscillation.
- A properly designed series feedback N/w can significantly increase the -ve resistance presented by the two-part Network.


The unstable region of the two-part N/w can be enhanced by the use of series feedback.

- For BJTs a series feedback inductor of a few nanohenries enhances the unstable region. For FETs either a series-feedback inductor or a series-feedback capacitor of a few picofarads enhances the unstable region.
- The purpose of a series-feedback element is to provide positive feedback making the configuration more unstable.
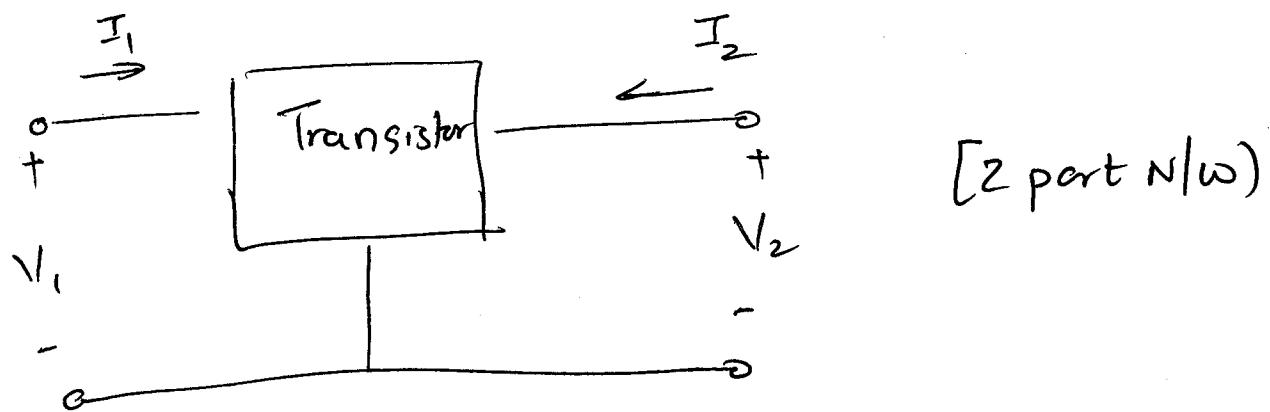
### Method for designing Series feedback N/w



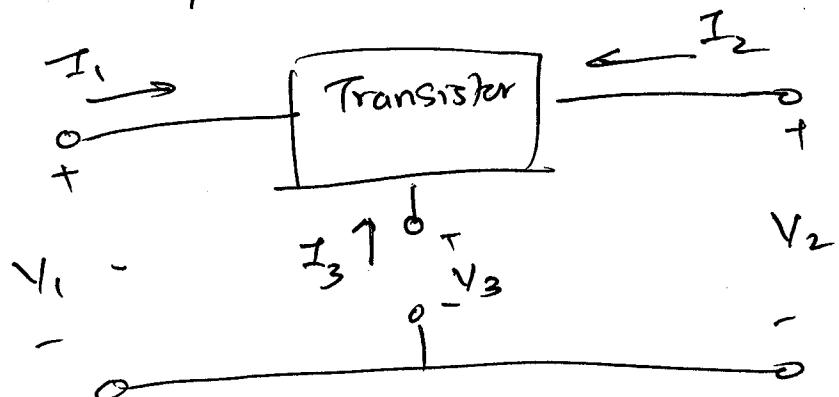Let  $\hat{S}$  be the 3-port scattering matrix &  $[S]$  be the two-port scattering matrix



The relation between 2-port & 3-port S-parameters can be written as:

$$\hat{S}_{11} = S_{11} + \frac{\sigma_{11} \sigma_{12}}{4-\sigma}$$

$$\hat{S}_{12} = S_{12} + \frac{\sigma_{11} \sigma_{21}}{4-\sigma}$$

$$\hat{S}_{13} = \frac{2\sigma_{11}}{4-\sigma}$$

$$\hat{S}_{21} = S_{21} + \frac{\sigma_{22} \sigma_{12}}{4-\sigma}$$

$$\hat{S}_{22} = S_{22} + \frac{\sigma_{22} \sigma_{21}}{4-\sigma}$$

$$\hat{S}_{23} = \frac{2\sigma_{22}}{4-\sigma}$$

$$\hat{S}_{31} = \frac{2\sigma_{12}}{4-\sigma}$$

$$\hat{S}_{32} = \frac{2\sigma_{21}}{4-\sigma}$$

$$\hat{S}_{33} = \frac{\sigma}{4-\sigma}$$

$$\sigma_{11} = 1 - S_{11} - S_{12}$$

$$\sigma_{12} = 1 - S_{11} - S_{21}$$

$$\sigma_{21} = 1 - S_{22} - S_{12}$$

$$\sigma_{22} = 1 - S_{22} - S_{21}$$

$$\sigma = S_{11} + S_{12} + S_{21} + S_{22}$$

&


$$S_{11} = \hat{S}_{11} - \frac{\hat{S}_{13} \hat{S}_{31}}{1 + \hat{S}_{33}}$$

$$S_{12} = \hat{S}_{12} - \frac{\hat{S}_{13} \hat{S}_{32}}{1 + \hat{S}_{33}}$$

$$S_{21} = \hat{S}_{21} - \frac{\hat{S}_{23} \hat{S}_{31}}{1 + \hat{S}_{33}}$$

$$S_{22} = \hat{S}_{22} - \frac{\hat{S}_{23} \hat{S}_{32}}{1 + \hat{S}_{33}}$$

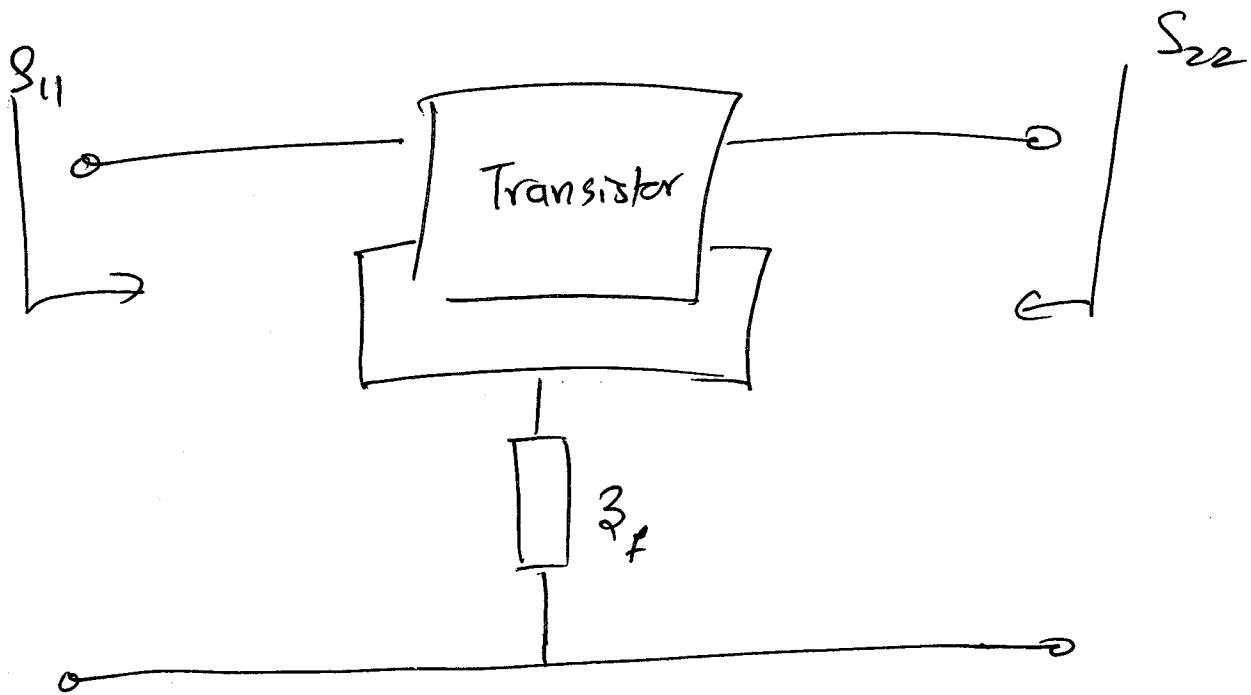If a series feedback impedance is used, as shown in figure below



$$Q_3 = \Gamma_f b_3$$

$1 + \hat{S}_{33}$  is replaced by  $\hat{S}_{33} - \left(\frac{1}{\Gamma_f}\right)$

$$S_{11} = \frac{\Delta_1 \Gamma_f - \hat{S}_{11}}{\hat{S}_{33} \Gamma_f - 1}$$

$$S_{22} = \frac{\Delta_2 \Gamma_f - \hat{S}_{22}}{\hat{S}_{33} \Gamma_f - 1}$$

$$\Delta_1 = \hat{S}_{11} \hat{S}_{33} - \hat{S}_{13} \hat{S}_{31}$$

$$\Delta_2 = \hat{S}_{22} \hat{S}_{33} - \hat{S}_{23} \hat{S}_{32}$$

The mapping of  $|P_f| = 1$  onto the  $S_{11}$  and  $S_{22}$  planes have centers & radii given by

$$C_1' = \frac{\hat{S}_{11} - \Delta_1 \hat{S}_{33}^*}{1 - |\hat{S}_{33}|^2}$$

$$r_1' = \frac{|\hat{S}_{13} \hat{S}_{31}|}{|1 - |\hat{S}_{33}|^2|}$$

$\ell$

$$C_2' = \frac{\hat{S}_{22} - \Delta_2 \hat{S}_{33}^*}{1 - |\hat{S}_{33}|^2}$$

$$r_2' = \frac{|\hat{S}_{23} \hat{S}_{32}|}{|1 - |\hat{S}_{33}|^2|}$$

for the  $S_{11}$  and  $S_{22}$  planes

The maximum value of  $|S_{11}|$  occurs at a point where

$$S_{11}(\max) = (|C_1'| + r_1') |C_1'|$$

$r_1(\max)$  is given by

$$z_f = j x_{1(\max)} = \frac{\Delta_1 + \hat{S}_{11} - S_{11(\max)}(1 + \hat{S}_{33})}{\Delta_1 - \hat{S}_{11} + S_{11(\max)}(1 - \hat{S}_{33})}$$

To properly orient the mapping, the  $z_f = \infty$  point maps onto the point

$$S_{11} = \frac{\Delta_1 - \hat{S}_{11}}{\hat{S}_{33} - 1}$$

$\ell z_f = 0$  maps onto the point

$$S_{11} = \frac{\Delta_1 + \hat{S}_{11}}{\hat{S}_{33} + 1}$$

||| we obtain

$$g_r = (|C_2'| + r_2') |C_2'|$$

$$z_f = j x_{2(\max)} = \frac{\Delta_2 + \hat{S}_{22} - S_{22(\max)}(1 + \hat{S}_{33})}{\Delta_2 - \hat{S}_{22} + S_{22(\max)}(1 - \hat{S}_{33})}$$

$\ell z_f = \infty$  point maps onto

$$S_{22} = \frac{\Delta_2 - \hat{S}_{22}}{\hat{S}_{33} - 1}$$

and  $Z_f=0$  point maps to

$$S_{22} = \frac{\Delta_2 + \hat{S}_{22}}{\hat{S}_{33} + 1}$$

## Design Procedure

1. Convert 2 port S parameter to 3-port
2. Calculate  $G_1'$ ,  $r_1'$ ,  $G_2'$  &  $r_2'$
3. Calculate  $S_{11(\text{max})}$ ,  $x_{1c(\text{max})}$ ,  $S_{22(\text{max})}$  &  $x_{2c(\text{max})}$
4. Plot mapping of the  $T_f$  plane onto the  $S_{11}$  &  $S_{22}$  planes.
5. Select appropriate  $Z_f$  value.

cgr

Design a 2.75 GHz oscillator using a BJT in common-base configuration. The S-parameters at 2.75 GHz, at a given Q point are.

$$S_{11} = 0.9 \angle 150^\circ$$

$$S_{21} = 1.7 \angle -80^\circ$$

$$S_{12} = 0.07 \angle 120^\circ$$

$$S_{22} = 1.08 \angle -56^\circ$$

Soln

1) Calculate K ( $K = -0.64$ )

We can use feedback to increase the region of instability. With  $L = 1.45 \text{ nH}$

The new S-parameters are

$$S_{11} = 1.72 \angle 100^\circ$$

$$S_{21} = 2.08 \angle -136^\circ$$

$$- S_{12} = 0.712 \angle 94^\circ$$

$$S_{22} = 1.16 \angle -102^\circ$$

Either port can be used as the terminating port.

The emitter-to-ground port was selected for this example for the load matching N/w; and the collector to ground port for the terminating N/w.

- From the Smith chart we observe that the center of the Smith chart is unstable. Hence a  $50\Omega$  termination will ensure  $|P_{in}| > 1$ .

Although this is simple there are a couple of issues:

- 1) For associated value of  $P_{in}$  the required value of  $P_T$  for the oscillator might be difficult to implement.
- 2) Some tuning capabilities are needed in the matching N/w to attain the desired frequency of oscillation.

The values of  $P_{in}$  and  $P_T$  are related by:

$$P_{in} = S_{11} + \frac{S_{12}S_{21}P_T}{1 - S_{22}P_T}$$


One way of choosing  $P_T$  is in the unstable region & calculating the associated value of  $P_{in}$ .

## Oscillator Design Using Large-Signal Measurements

- The previous design methods provide good practical results. However there is no assurance that the oscillator power is optimum.
- Here we develop a method that optimizes the oscillator power, based on large signal measurements.
- The method consists of designing the terminating  $N/lw$  so that the two port presents a negative resistance at the i/p port
- The resulting one port negative resistance  $N/lw$  can be placed in a nonoscillating circuit and be optimum load impedance as a function of power can be measured.
  - The terminating  $N/lw$  is designed so that  $Z_{in}$  presents -ve impedance at  $1/2e$  load port that has a real part with magnitude smaller than  $50\Omega$
  - This is necessary because the equipment used to measure the large signal characteristics of the clt has a  $50\Omega$  source impedance, and the total loop resistance must be positive in order to avoid oscillatory measurements

The large signal characterization is achieved, by measuring in the circuit shown below, the current amplitude and the impedance  $Z_{IN}(A, \omega_0)$ , as  $V_s$  is varied. The measurements are made at the desired frequency of oscillation  $\omega_0$ , and the source resistance is typically  $50\Omega$ .

With  $|R_{IN}(A, \omega_0)| < 50\Omega$  the circuit is stable.

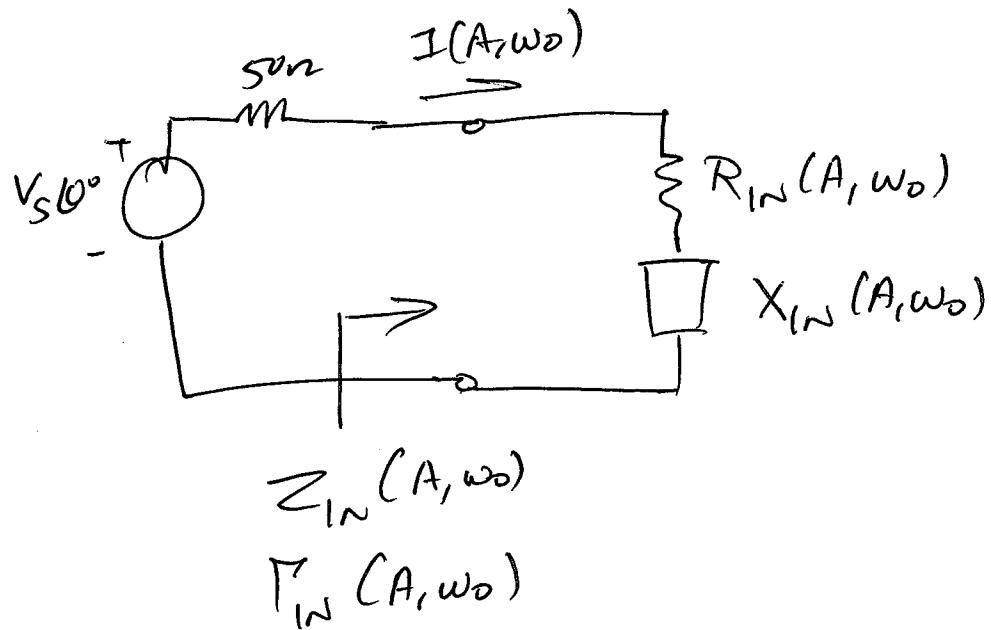

$$I(A, \omega_0) = \frac{V_s}{R_s + R_{IN}(A, \omega_0) + jX_{IN}(A, \omega_0)}$$

$$P_D(A, \omega_0) = \frac{1}{2} |I(A, \omega_0)|^2 |R_{IN}(A, \omega_0)|$$

Measurement of  $P_D(A, \omega_0)$  versus  $Z_{IN}(A, \omega_0)$  generates the large signal characteristics of the one port network.

If the one port is now terminated in the load impedance

$$Z_L(w_0) = -Z_{in}(A, w_0)$$

The power delivered to  $Z_L$  is given by  $P_L(A, w_0) = P_D(A, w_0)$

Measuring  $I(A, w_0)$  at microwave frequencies is difficult.  
The reflection coefficient  $R_{in}(A, w_0)$  as a function of the  
available power from the source is measured. The available  
power from the source is given by

$$P_{Avs} = \frac{V_s^2}{8R_s}$$

The power added  $P_{ADD}$  (ie reflected power-available power) is given by

$$P_{ADD} = P_{Avs} (|R_{in}|^2 - 1)$$

$$P_{ADD}(A, w_0) = \frac{V_s^2 |R_{in}(A, w_0)|}{2 [(R_{in}(A, w_0) + R_s)^2 + X_{in}^2]}$$

i.e  $P_{ADD}(A, w_0) = \frac{1}{2} |I(A, w_0)|^2 |R_{in}(A, w_0)|$

which shows that the added power is the power that the one port N/w will deliver to load  $Z_L(\omega_0) = -Z_{IN}(\omega_0)$

The design procedure uses the small-signal S parameters to establish the terminating impedance that results in a -ve resistance one-port N/w.

Then the one-port oscillator performance is described by the measured large-signal characteristics

$$\Gamma_{IN} = \frac{S_{11} - A\Gamma_T}{1 - S_{21}\Gamma_T}$$

describes the mapping of  $\Gamma_T$  plane into  $\Gamma_{IN}$  plane.

The mapping of the  $| \Gamma_T | = 1$  into the  $\Gamma_{IN}$  plane gives information about the passive impedance at the terminating port (i.e  $| \Gamma_T | < 1$ ) that will make  $| \Gamma_{IN} | > 1$ .

$$C_{IN} = \frac{S_{11} - AS_{22}}{1 - | S_{22} |^2}$$

$$g_{IN} = \frac{|S_{12} S_{21}|}{\left(1 - |S_{22}|^2\right)}$$

Largest ( $P'_{IN}$ ) is obtained when we select value of  $P'_{IN}$  on  $|P'_T| = 1 \circ$  that has the same phase as  $C_{IN}$ . The value of  $P'_T$  associated with  $P'_{IN,\max}$  produces the largest negative resistance for  $Z_{IN}$ , which can be realized using a passive terminating impedance. The magnitude of  $P'_{IN,\max}$  at 'a' is

$$|P'_{IN}| = |C_{IN}| + r_{IN}$$

phase

$$P'_{IN} = LC_{IN}$$

$$P'_{IN,\max} = (|C_{IN}| + r_{IN}) LC_{IN}$$

Value of  $P'_T$  at point a, .

$$P'_{T,0} = \frac{P'_{IN,\max} - S_{11}}{P'_{IN,\max} S_{22} - \Delta}$$