

$$4.13) G_A(\text{dB}) = 14 + 14 + 14 - 7.5 + 16 + 16 = 66.5 \text{ dB}$$

THE NOISE FIGURE OF THE LNB IS DETERMINED BY THE NOISE FIGURE OF THE LNA (I.E., THE FIRST 3 AMPLIFIERS).

$$F = F_1 + \frac{F_2 - 1}{G_{A1}} + \frac{F_3 - 1}{G_{A1}G_{A2}} = 10^{0.05} + \frac{10^{0.09} - 1}{10^{1.4}} + \frac{10^{0.11} - 1}{10^{1.4}10^{1.4}} = 1.131 \text{ OR } 0.54 \text{ dB}$$

THE CONTRIBUTION TO F FROM THE MIXER, AMP. 5, AND AMP. 6 IS NEGLIGIBLE.



$$4.15) G_{TU} = G_A G_o G_L, \quad G_{TU}(\text{dB}) = G_A(\text{dB}) + G_o(\text{dB}) + G_L(\text{dB})$$

$f(\text{GHz})$	$G_{A,\text{max}}(\text{dB})$	$G_o = S_{21} ^2(\text{dB})$	$G_{L,\text{max}}(\text{dB})$	$G_{TU,\text{max}}(\text{dB})$
1	2.3	14.05	4.25	20.6
2	1.86	9.97	3.6	15.43

NOISE CIRCLES CALCULATIONS:

$f(\text{GHz})$	$F_i(\text{dB})$	C_{F_i}	Y_{F_i}
1	2	$0.395 \angle 23^\circ$	0.378
	3	$0.286 \angle 23^\circ$	0.591
	4	$0.212 \angle 23^\circ$	0.708


2	2	$0.377 \angle 88^\circ$	0.261
	3	$0.304 \angle 88^\circ$	0.477
	4	$0.244 \angle 88^\circ$	0.604

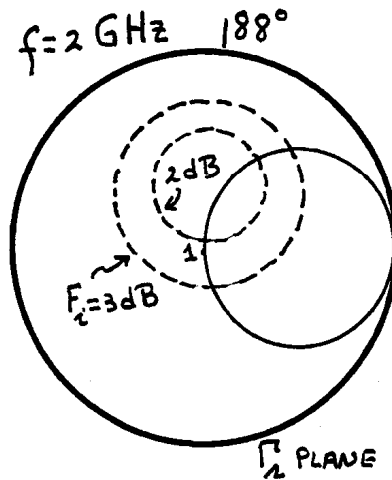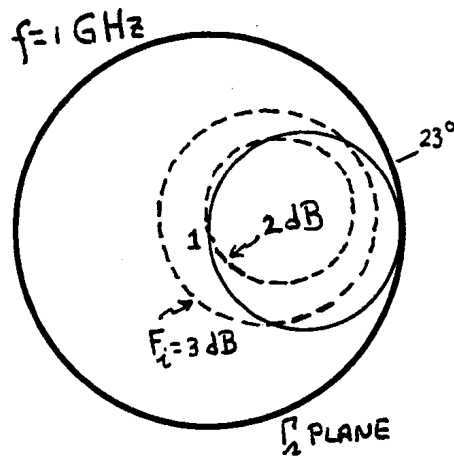

IT IS SEEN THAT THE NOISE FIGURE IS LESS THAN 3 dB AT 1 GHz AND 2 GHz WITH $\Gamma_{in}=0$. THE INPUT MATCHING NETWORK IS DESIGNED WITH $\Gamma_{in}=0$, AND IT FOLLOWS THAT $G_{in}=0\text{ dB}$.

A DESIGN FOR $G_{TU}=10\text{ dB}$ REQUIRES THAT $G_L=-4\text{ dB}$ AT 1 GHz, AND $G_L=0\text{ dB}$ AT 2 GHz. THAT IS,
 AT 1 GHz: $G_{TU}=0+14.05-4 \approx 10\text{ dB}$; AT 2 GHz: $G_{TU}=0+9.97+0 \approx 10\text{ dB}$

A MATCHING CIRCUIT FOR THIS DESIGN IS:

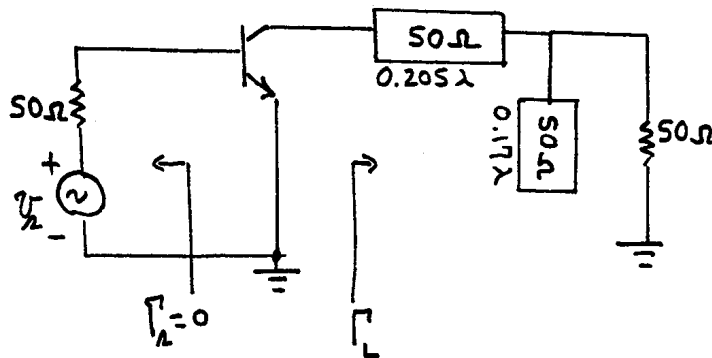

$$4.16) (a) \quad S_{11a} = S_{11b} = S_{11} \quad S_{21a} = S_{21b} = S_{21}$$

$$S_{12a} = S_{12b} = S_{12} \quad S_{22a} = S_{22b} = S_{22}$$

$$S_{11} = \frac{e^{-j\pi}}{2} (S_{11a} - S_{11b}) = 0, \quad (VSWR)_{in} = 1$$

$$S_{22} = \frac{e^{-j\pi}}{2} (S_{22a} - S_{22b}) = 0, \quad (VSWR)_{out} = 1$$

$$G_T = (0.5)^2 |S_{21a} + S_{21b}|^2 = (0.5)^2 [2(3.4)]^2 = 11.56 \text{ OR } 10.6 \text{ dB}$$

$$(b) \quad S_{11b} = 0.525 \angle 168^\circ, \quad S_{12b} = 0.084 \angle 63^\circ, \quad S_{21b} = 3.57 \angle 73.5^\circ, \quad S_{22b} = 0.42 \angle -42.75^\circ$$

$$S_{11} = \frac{e^{-j\pi}}{2} (0.5 \angle 160^\circ - 0.525 \angle 168^\circ) = 0.038 \angle -125.2^\circ, \quad (VSWR)_{in} = \frac{1+0.038}{1-0.038} = 1.08$$

$$S_{22} = \frac{e^{-j\pi}}{2} (0.4 \angle -45^\circ - 0.42 \angle -42.75^\circ) = 0.013 \angle -5^\circ, \quad (VSWR)_{out} = \frac{1+0.013}{1-0.013} = 1.03$$

$$G_T = (0.5)^2 |3.4 \angle 70^\circ + 3.57 \angle 73.5^\circ|^2 = 12.13 \text{ OR } 10.8 \text{ dB}$$

4.19) IF S_{11} IS APPROXIMATED BY $0.97 \angle 0^\circ$, THE ASSOCIATED $\gamma_{b'e}$ IS $3.28 \text{ k}\Omega$.

$$G_T = 10 = |S_{21}|^2 \Rightarrow S_{21} = -3.16$$

FROM (4.4.10):

$$R_2 = Z_0(1 - S_{21}) = 50(1 + 3.16) = 208 \Omega$$

THE VALUE OF g_m FOR $(VSWR)_{in} \approx 1$ AND $(VSWR)_{out} \approx 1$ FOLLOWS FROM (4.4.9). THAT IS,

$$g_m = \frac{R_2}{Z_0^2} = \frac{208}{50^2} = 83 \text{ mS}$$

$$4.24) (a) \Gamma_a = S_{11}^* = 0.75 \angle 100^\circ \quad \text{AND} \quad \Gamma_L = S_{22}^* = 0.7 \angle 50^\circ$$

$$(b) Y_a = \frac{1}{Z_a} = 7 - j23 \text{ mS}, \quad Y_L = \frac{1}{Z_L} = 4 - j9 \text{ mS}$$

$$(BW)_{IN}^i = \frac{2f_0 G_{A,M}}{|B_{A,M}|} = \frac{2(8 \times 10^9) 0.007}{0.023} = 4.87 \text{ GHz}$$

$$(BW)_{OUT}^i = \frac{2f_0 G_{L,M}}{|B_{L,M}|} = \frac{2(8 \times 10^9) (0.004)}{0.009} = 7.11 \text{ GHz}$$

$$(c) (BW)_{IN} = 20\% (BW)_{IN}^i = 974 \text{ MHz}$$

$$Y_{IN} = 7 + j23 \text{ mS}$$

THE REQUIRED VALUE OF C'_{IN} (FROM (4.6.5)) IS:

$$C'_{IN} = \frac{B_{IN,M}}{\omega_0} \left[\frac{(BW)_{IN}^i}{(BW)_{IN}} - 1 \right] = \frac{23 \times 10^{-3}}{2\pi(8 \times 10^9)} \left[\frac{4.87}{0.974} - 1 \right] = 1.83 \text{ pF}$$

$$(d) Y'_{IN} = Y_{IN} + j\omega C'_{IN} = (7 + j23) \times 10^{-3} + j2\pi(8 \times 10^9)(1.83 \times 10^{-12}) = 7 + j115 \text{ mS}$$

$$\Gamma'_{IN} = 0.98 \angle -160.4^\circ, \therefore \Gamma_a = \Gamma'_{IN}^* = 0.98 \angle 160.4^\circ, \Gamma_L = S_{22}^* = 0.7 \angle 50^\circ$$

$$G_{TU, \max} = \frac{1}{1 - (0.98)^2} (2.5)^2 \frac{1}{1 - (0.7)^2} = 309.4 \text{ OR } 24.9 \text{ dB}$$