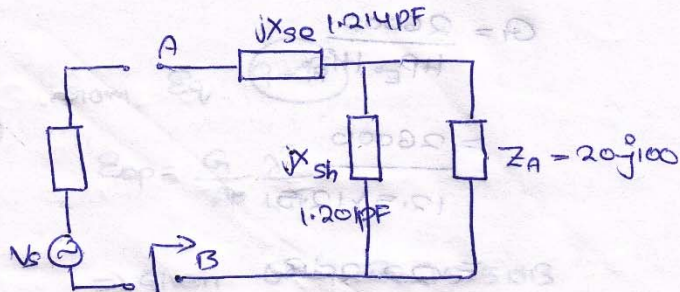


Antenna Theory and Design

Homework 12

(8-8-P)

14)



$$Z_{AB} = Z_s = 70 - j20$$

Calculating series reactance

$$Z_{AB} = \frac{jX_{sh}(20 - j100)}{20 + j(X_{sh} - 100)} + jX_{se} = \frac{20X_{sh}^2}{X_{sh} - 200X_{sh} + 10000} + jX_{se}$$

$$\Rightarrow \frac{-j100X_{sh}(X_{sh} - 100)}{X_{sh} - 200X_{sh} + 10000} + jX_{se}$$

If the real parts are made equal

$$X_{sh} = 69.09; 213.4$$

If Imaginary parts are made equal

$$|X_{sh}| = 69.2$$

If $f = 1900 \text{ MHz}$ and $C_{sh} = 1.214 \text{ pF}$

$$|X_{se}| = \frac{1}{\omega C_{se}} \Rightarrow C_{se} = 1.201 \text{ pF}$$

$$Z_{AB} = Z_S^* = 70 - j20 \Omega$$

$$V_{oc} = \sqrt{8 R_a P_a}$$

$$= \sqrt{8 \times 20 \times 600 \times 10^{-3}}$$

$$= 9.81$$

$$V_{oc(rms)} = \frac{V_{oc}}{\sqrt{2}}$$

$$= \frac{9.81}{\sqrt{2}}$$

$$= 6.97 \text{ V}$$

Power transferred to load $\Rightarrow I_{rms}^2 \text{Re} |Z_S|$

$$= \frac{6.97^2 \times 20}{(40)^2}$$

$$= 615.2 \text{ mW}$$