


Finite State Machines (FSMs).

①

We study two types of FSMs.

① Moore m/c & ② Mealy m/c.

The general structure of a Moore m/c.

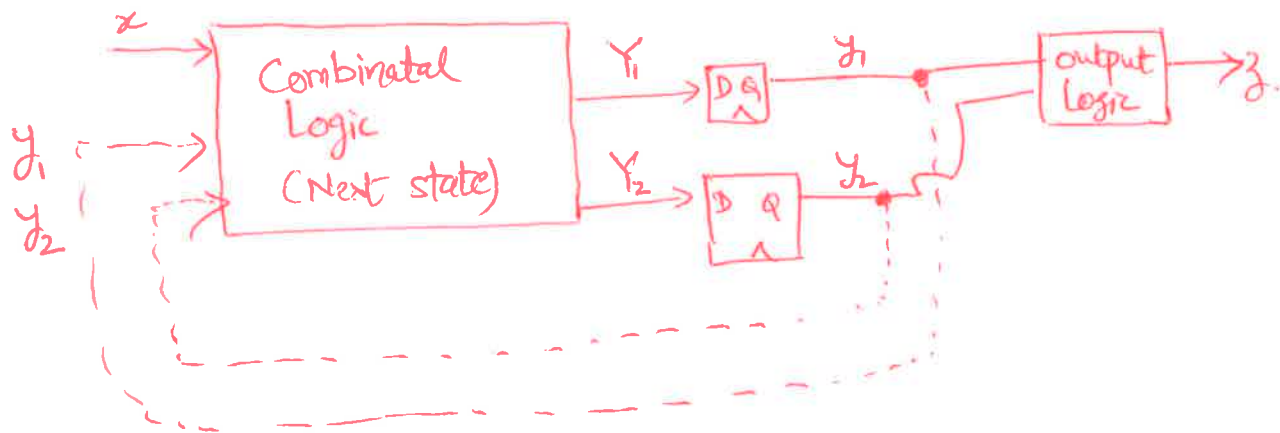

Moore m/c. = ~~FSM~~ $M = (\Sigma, O, S, S^0, \delta, \lambda)$

Σ = input label, O = output alphabet

S = set of states, $S^0 \in S$ = initial/reset state

$\delta: S \times \Sigma \rightarrow S$ transition function

$\lambda: S \rightarrow O$ output function.

$\{Y_1, Y_2, \dots\}$ = Next state signals (output of next state logic)

$\{y_1, y_2, \dots\}$ = Present state signals (input to next state logic)


Next state = function of present-state & inputs.

Output = " " present state only.

Moore FSM Design example:

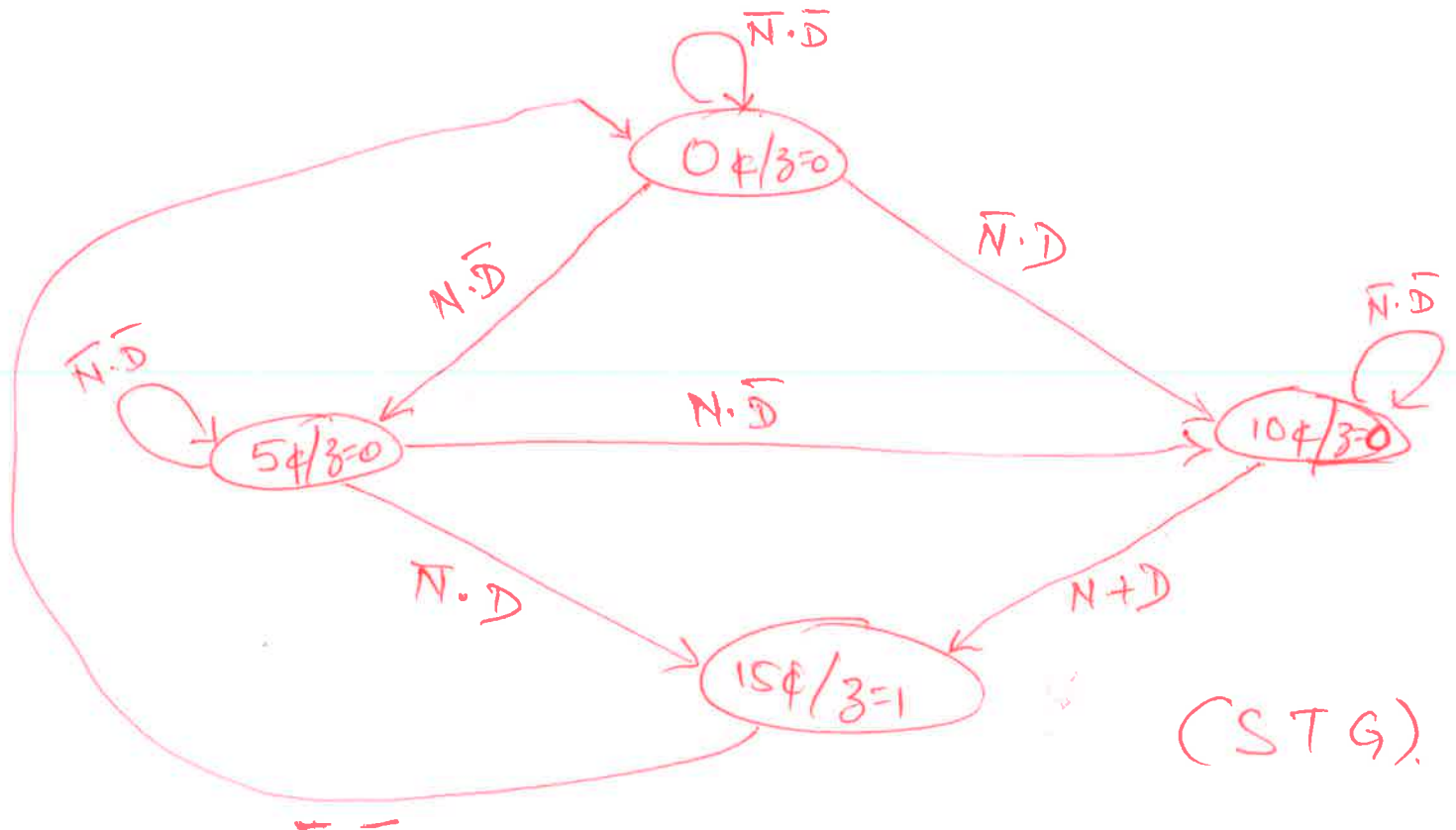(2)

Vending m/c controllers, takes $\text{\pounds}$ Nickels (N) & Dimes (D) as inputs, output $z=1$ (dispenser) when 15¢ are deposited.



State encoding: 4 states = 2 FFs. (Y_1, y_1) (Y_2, y_2)

0¢ = 00, 5¢ = 01, 10¢ = 10, 15¢ = 11

State Table.

P.S. (y_1, y_2)	$\bar{N} \cdot \bar{D}$	N.S. (Y_1, Y_2)			Output (z)
		$\bar{N} \cdot \bar{D}$	$\bar{N} \cdot D$	$N \cdot \bar{D}$	
0¢ = 00	00	10	01	x	0
5¢ = 01	01	11	10	x	0
10¢ = 10	10	11	11	x	0
15¢ = 11	00	00	00	x	1

Assumption: N & D cannot be input at the same time as there is only 1 coin-slot. Also, no change is given by m/c.

Logic for
 Y_1

$y_1 y_2$	ND			
	00	01	11	10
00		1	X	
01		1	X	1
11		0	X	
10	1	1	X	1

$$Y_1 = y_1 \bar{y}_2 + \bar{y}_1 D + \bar{y}_1 y_2 N$$

$y_1 y_2$	ND			
	00	01	11	10
00			(X)	(1)
01	(1)	(1)	X	
11			X	
10		(1)	(X)	(1)

$$Y_2 = \bar{y}_1 \bar{y}_2 N + \bar{y}_1 y_2 \bar{N} + y_1 \bar{y}_2 D + y_1 \bar{y}_2 N$$

$$\text{output } Z = Y_1 \cdot Y_2$$


The same m/c behaviour can be designed using a Mealy machine, by making the output depend on both present states and present inputs.

May result in a reduction of the number of states, but also may complicate the output logic.

For the same vending machine controllers.

(4)

Mealy

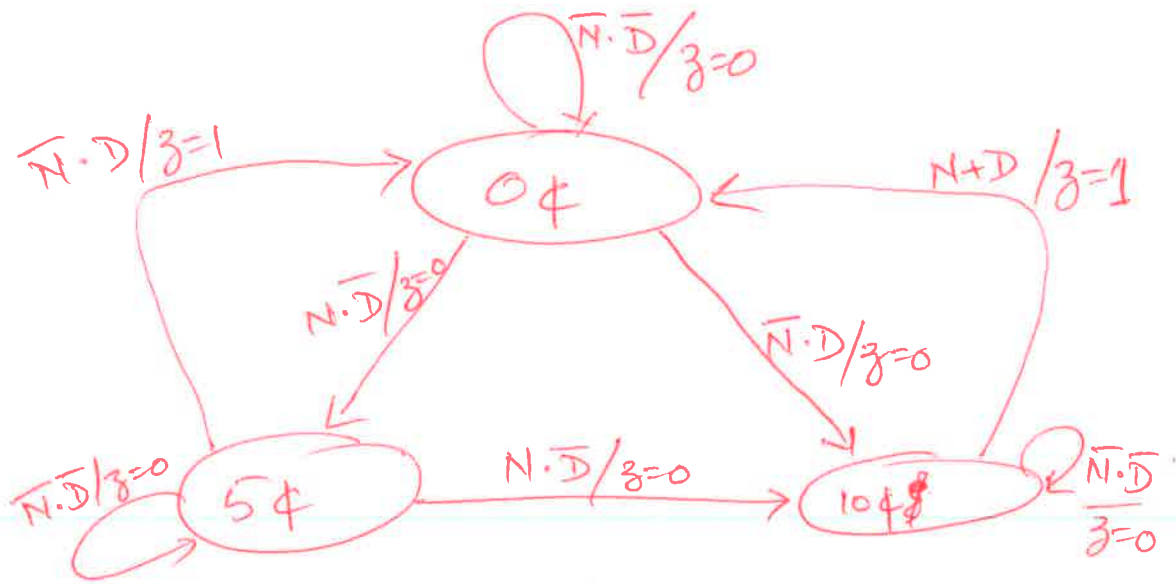

Encoding choice

0¢ = 11, 5¢ = 00
10¢ = 01

NS. (Y_1, Y_2) , z

P.S. (y_1, y_2)

0¢ = 11

5¢ = 00

10¢ = 01

11

Sequential
don't care

$\overline{N} \cdot \overline{D}$

11, 0

00, 0

01, 0

xx, x

$\overline{N} \cdot D$

01, 0

11, 1

11, 1

xx, x

$N \cdot \overline{D}$

00, 0

01, 0

11, 1

xx, x

$N \cdot D$

x

x

x

xx, x

← Unreachable
state of the m/c.

Primary input
D, C.

Next - state & output logic.

(5)

Y_1

$y_1 y_2 \backslash ND$	00	01	11	10
00		1	X	
01		1	X	1
11	1		X	
10	X	X	X	X

$$Y_1 = y_1 \overline{ND} + \overline{y_1} D + \overline{y_1} y_2 N$$

Y_2

$y_1 y_2 \backslash ND$	00	01	11	10
00		1	X	
01	1	1	X	1
11	1	1	X	
10	X	X	X	X

$$Y_2 = D + y_2 \overline{N} + \overline{y_1} N$$

Z

$y_1 y_2 \backslash ND$	00	01	11	10
00		1	X	
01		1	X	1
11			X	
10	X	X	X	X

$$Z = \overline{y_1} D + \overline{y_1} y_2 N$$

Try out yourself:

$$\left. \begin{array}{l} 0¢ = 00 \\ 5¢ = 01 \\ 10¢ = 10 \end{array} \right\} \text{encoding.}$$

<u>PS</u>	$\overline{N}\overline{D}$	$\overline{N}D$	$N\overline{D}$	ND
00	00,0	10,0	01,0	x
01	01,0	00,1	10,0	x
10	10,0	00,1	00,1	x
11	x	x	x	x

Synthesize logic for Y_1, Y_2 & Z with this encoding & compare the SOP literal cost of implementation:

So a Mealy m/c $M = (\Sigma, O, S, S^0, \delta, \lambda)$

where $\lambda: S \times \Sigma \rightarrow O$

