 



(a) The four possible cases

		Carry	Sum
x	y	c	s
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

(b) Truth table



(c) Circuit

 

(d) Graphical symbol

Figure 3.1. Half-adder.

c_i	x_i	y_i	c_{i+1}	s_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

(a) Truth table


$c_i \backslash x_i y_i$	00	01	11	10
0		1		1
1	1		1	

$$s_i = x_i \oplus y_i \oplus c_i$$

$c_i \backslash x_i y_i$	00	01	11	10
0			1	
1		1	1	1


$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

(b) Karnaugh maps

 


(c) Circuit

Figure 3.3. Full-adder.

 

(a) Naive approach

 

(b) Efficient design

Figure 3.6. Circuit that multiplies an eight-bit unsigned number by 3.

```

module addern (carryin, X, Y, S, carryout);
  parameter n = 32;
  input carryin;
  input [n-1:0] X, Y;
  output [n-1:0] S;
  output carryout;
  wire [n:0] C;

  genvar i;
  assign C[0] = carryin;
  assign carryout = C[n];
  generate
    for (i = 0; i <= n-1; i = i+1)
      begin:addbit
        fulladd stage (C[i], X[i], Y[i], S[i], C[i+1]);
      end
  endgenerate
endmodule

```

```

module fulladd (Cin, x, y, s, Cout);
  input Cin, x, y;
  output s, Cout;
  assign s = x ^ y ^ Cin,
    Cout = (x & y) | (x & Cin) | (y & Cin);
endmodule

```

Figure 3.29. A ripple-carry adder specified using the **generate** statement.

```

module adder_hier (A, B, C, D, S, T, overflow);
    input [15:0] A, B;
    input [7:0] C, D;
    output [16:0] S;
    output [8:0] T;
    output overflow;

    wire o1, o2; // used for the overflow signals

    addern #(n(16)) U1
    (
        .carryin (1'b0),
        .X (A),
        .Y (B),
        .S (S[15:0]),
        .carryout (S[16]),
        .overflow (o1)
    );
    addern #(n(8)) U2
    (
        .carryin (1'b0),
        .X (C),
        .Y (D),
        .S (T[7:0]),
        .carryout (T[8]),
        .overflow (o2)
    );

    assign overflow = o1 | o2;

endmodule

```

Figure 3.33. An alternative version of the code in Figure 3.32.

Multiplicand M	(+14)	0 1 1 1 0
Multiplier Q	(+11)	x 0 1 0 1 1
Partial product 0		0 0 0 1 1 1 0
		+ 0 0 1 1 1 0
Partial product 1		0 0 1 0 1 0 1
		+ 0 0 0 0 0 0
Partial product 2		0 0 0 1 0 1 0
		+ 0 0 1 1 1 0
Partial product 3		0 0 1 0 0 1 1
		+ 0 0 0 0 0 0
Product P	(+154)	0 0 1 0 0 1 1 0 1 0

(a) Positive multiplicand

Multiplicand M	(-14)	1 0 0 1 0
Multiplier Q	(+11)	x 0 1 0 1 1
Partial product 0		1 1 1 0 0 1 0
		+ 1 1 0 0 1 0
Partial product 1		1 1 0 1 0 1 1
		+ 0 0 0 0 0 0
Partial product 2		1 1 1 0 1 0 1
		+ 1 1 0 0 1 0
Partial product 3		1 1 0 1 1 0 0
		+ 0 0 0 0 0 0
Product P	(-154)	1 1 0 1 1 0 0 1 1 0

(b) Negative multiplicand

Figure 3.36. Multiplication of signed numbers.

Convert $(214.45)_{10}$

$$\frac{214}{2} = 107 + \frac{0}{2} \rightarrow 0 \text{ LSB}$$

$$\frac{107}{2} = 53 + \frac{1}{2} \rightarrow 1$$

$$\frac{53}{2} = 26 + \frac{1}{2} \rightarrow 1$$

$$\frac{26}{2} = 13 + \frac{0}{2} \rightarrow 0$$

$$\frac{13}{2} = 6 + \frac{1}{2} \rightarrow 1$$

$$\frac{6}{2} = 3 + \frac{0}{2} \rightarrow 0$$

$$\frac{3}{2} = 1 + \frac{1}{2} \rightarrow 1$$

$$\frac{1}{2} = 0 + \frac{1}{2} \rightarrow 1 \text{ MSB}$$

$$0.45 \times 2 = 0.90 \rightarrow 0 \text{ MSB}$$

$$0.90 \times 2 = 1.80 \rightarrow 1$$

$$0.80 \times 2 = 1.60 \rightarrow 1$$

$$0.60 \times 2 = 1.20 \rightarrow 1$$

$$0.20 \times 2 = 0.40 \rightarrow 0$$

$$0.40 \times 2 = 0.80 \rightarrow 0$$

$$0.80 \times 2 = 1.60 \rightarrow 1 \text{ LSB}$$

$$(214.45)_{10} = (11010110.0111001 \dots)_2$$

Figure 3.44. Conversion of fixed point numbers from decimal to binary.

```

module comparator (X, Y, V, N, Z);
  input [3:0] X, Y;
  output V, N, Z;
  wire [3:0] S;
  wire [4:1] C;

  fulladd stage0 (1'b1, X[0], ~Y[0], S[0], C[1]);
  fulladd stage1 (C[1], X[1], ~Y[1], S[1], C[2]);
  fulladd stage2 (C[2], X[2], ~Y[2], S[2], C[3]);
  fulladd stage3 (C[3], X[3], ~Y[3], S[3], C[4]);
  assign V = C[4] ^ C[3];
  assign N = S[3];
  assign Z = !S;

endmodule

```

```

module fulladd (Cin, x, y, s, Cout);
  input Cin, x, y;
  output s, Cout;
  assign s = x ^ y ^ Cin,
    Cout = (x & y) | (x & Cin) | (y & Cin);
endmodule

```

Figure 3.46. Structural Verilog code for the comparator circuit.

```

module comparator (X, Y, V, N, Z);
  parameter n = 32;
  input [n-1:0] X, Y;
  output reg V, N, Z;
  reg [n-1:0] S;
  reg [n:0] C;
  integer k;

  always @(X, Y)
  begin
    C[0] = 1'b1;
    for (k = 0; k < n; k = k + 1)
      begin
        S[k] = X[k] ^ ~Y[k] ^ C[k];
        C[k+1] = (X[k] & ~Y[k]) | (X[k] & C[k]) | (~Y[k] & C[k]);
      end
    V = C[n] ^ C[n-1];
    N = S[n-1];
    Z = !S;
  end

endmodule

```

Figure 3.47. Generic Verilog code for the comparator circuit.