
 


 


(a) Circuit

Clk	S	R	$Q(t+1)$
0	x	x	$Q(t)$ (no change)
1	0	0	$Q(t)$ (no change)
1	0	1	0
1	1	0	1
1	1	1	x

(b) Characteristic table




(c) Timing diagram

 

(d) Graphical symbol


Figure 5.5. Gated SR latch.

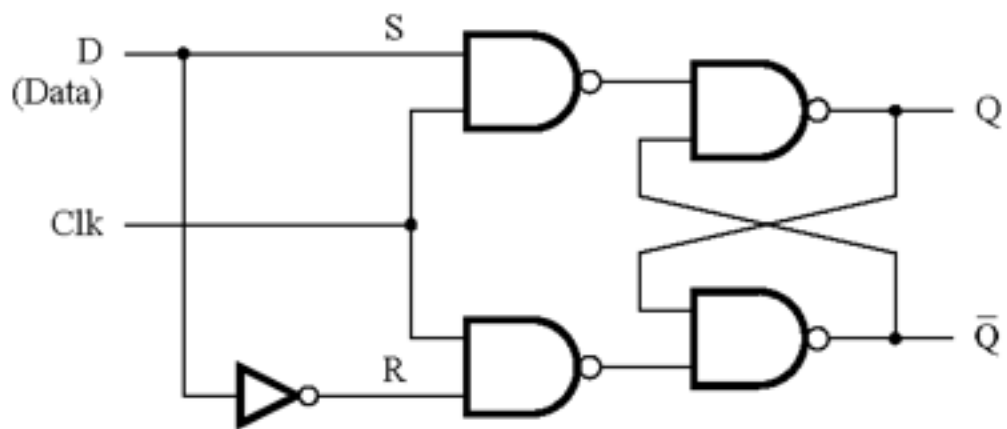


(a) Circuit

Clk	D	$Q(t+1)$
0	x	$Q(t)$
1	0	0
1	1	1

(b) Characteristic table

 


(c) Graphical symbol

 


(d) Timing diagram


Figure 5.7. Gated D latch.

 

(a) Circuit

 


(b) Timing diagram

 


(c) Graphical symbol

Figure 5.9. Master-slave D flip-flop.

 


(a) Circuit

 


(b) Timing diagram


Figure 5.10. Comparison of level-sensitive and edge-triggered D storage elements.

 

(a) Circuit

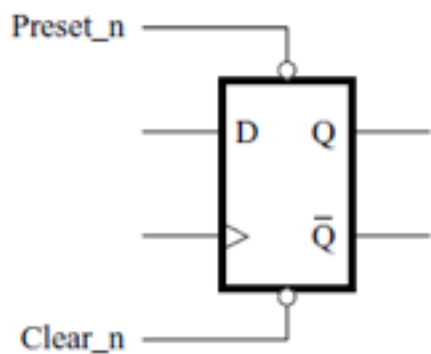


(b) Graphical symbol

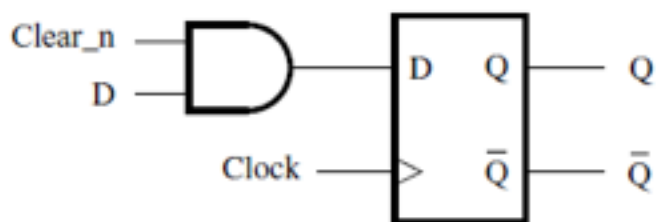

(c) Adding a synchronous clear


Figure 5.13. Positive-edge-triggered D flip-flop with *Clear* and *Preset*.

 


(a) Circuit

T	$Q(t+1)$
0	$Q(t)$
1	$\bar{Q}(t)$

(b) Truth table

 

(c) Graphical symbol

 

(d) Timing diagram

Figure 5.15. T flip-flop.

 


Figure 5.23. A four-bit counter with D flip-flops.


 


Figure 5.24. A counter with parallel-load capability.

 

(a) An n -bit ring counter

 


Figure 5.28. Ring counter.


 
 


Figure 5.32. Implementation of the schematic in Figure 5.30 in a CPLD.

 

(c) Push-button switch, LED, and 7-segment displays

Figure 5.61. A reaction-timer circuit.

```

module BCDcount (Clock, Clear, E, BCD1, BCD0);
    input Clock, Clear, E;
    output reg [3:0] BCD1, BCD0;

    always @(posedge Clock)
    begin
        if (Clear)
        begin
            BCD1 <= 0;
            BCD0 <= 0;
        end
        else if (E)
        begin
            if (BCD0 == 4'b1001)
            begin
                BCD0 <= 0;
                if (BCD1 == 4'b1001)
                begin
                    BCD1 <= 0;
                end
                else
                    BCD1 <= BCD1 + 1;
                end
            end
            else
                BCD0 <= BCD0 + 1;
            end
        end
    end

endmodule

```

Figure 5.62. Code for the two-digit BCD counter in Figure 5.27.

 


Figure 5.67. A 4-bit counter.

 


Figure 5.73. Circuit for Example 5.20.

 


Figure 5.75. A faster 4-bit counter.