
 


Chapter 7

Digital System Design

 

(a) Symbol



(b) Equivalent circuit

e	w	f
0	0	Z
0	1	Z
1	0	0
1	1	1

(c) Truth table

Figure 7.1. Tri-state driver.

 


Figure 7.2. A digital system with k registers.

 


Figure 7.3. Details for connecting registers to a bus.

 


Figure 7.4. Using multiplexers to implement a bus.

```
module regn (R, L, Clock, Q);
    parameter n = 8;
    input [n-1:0] R;
    input L, Clock;
    output reg [n-1:0] Q;

    always @(posedge Clock)
        if (L)
            Q <= R;

endmodule
```

Figure 7.5. Code for an n -bit register of the type in Figure 7.2.

```
module trin (Y, E, F);
  parameter n = 8;
  input [n-1:0] Y;
  input E;
  output wire [n-1:0] F;

  assign F = E ? Y : 'bz;

endmodule
```

Figure 7.6. Code for an n -bit tri-state module.

Please see “**portrait orientation**” PowerPoint file for Chapter 7

Figure 7.7. A digital system like the one in Figure 7.2.

Please see “**portrait orientation**” PowerPoint file for Chapter 7

Figure 7.8. Using multiplexers to implement a bus.

 


Figure 7.9. A digital system that implements a simple processor.

Operation	Function performed
Load $Rx, Data$	$Rx \leftarrow Data$
Move Rx, Ry	$Rx \leftarrow Ry $
Add Rx, Ry	$Rx \leftarrow Rx + Ry $
Sub Rx, Ry	$Rx \leftarrow Rx - Ry $

Table 7.1. Operations performed in the processor.

 


Figure 7.10. A part of the control circuit for the processor.

 


Figure 7.11. The function register and decoders.

	T_1	T_2	T_3
(Load): T_C	$External, R_{in} = X_i$, $Done$		
(Move): T_L	$R_{in} = X_i, R_{out} = Y_i$, $Done$		
(Add): T_B	$R_{out} = X_i, A_{in}$	$R_{out} = Y_i, G_{in},$ $AddSub = 0$	$G_{out}, R_{in} = X_i$, $Done$
(Sub): T_S	$R_{out} = X_i, A_{in}$	$R_{out} = Y_i, G_{in},$ $AddSub = 1$	$G_{out}, R_{in} = X_i$, $Done$

Table 7.2. Control signals asserted in each operation/time step.

```
module upcount (Clear, Clock, Q);
    input Clear, Clock;
    output reg [1:0] Q;

    always @(posedge Clock)
        if (Clear)
            Q <= 0;
        else
            Q <= Q + 1;

endmodule
```

Figure 7.12. A two-bit up-counter with synchronous reset.

Please see “**portrait orientation**” PowerPoint file for Chapter 7

Figure 7.13. Code for the processor.

Please see “**portrait orientation**” PowerPoint file for Chapter 7

Figure 7.14. Alternative code for the processor.

 


Figure 7.15. Timing simulation for the Verilog code in Figure 7.14.

```
B = 0 ;  
while A ≠ 0 do  
    if  $a_0 = 1$  then  
        B = B + 1 ;  
    end if;  
    Right-shift A ;  
end while;
```

Figure 7.16 Pseudo-code for the bit counter.

Please see “**portrait orientation**” PowerPoint file for Chapter 7

Figure 7.17. ASM chart for the pseudo-code in Figure 7.16.

 


Figure 7.18. Datapath for the ASM chart in Figure 7.17.

 


Figure 7.19. ASM chart for the bit counter control circuit.

Please see “**portrait orientation**” PowerPoint file for Chapter 7

Figure 7.20. Verilog code for the bit-counting circuit.

 


Figure 7.21. Simulation results for the bit-counting circuit.

Decimal	Binary	
$\begin{array}{r} 13 \\ \times 11 \\ \hline 13 \\ 13 \\ \hline 143 \end{array}$	$\begin{array}{r} 1\ 1\ 0\ 1 \\ \times 1\ 0\ 1\ 1 \\ \hline 1101 \\ 1\ 1\ 0\ 1 \\ 0\ 0\ 0\ 0 \\ 1\ 1\ 0\ 1 \\ \hline 1\ 0\ 001111 \end{array}$	Multiplicand Multiplier
		Product

(a) Manual method

```

 $P = 0;$ 
for  $i = 0$  to  $n - 1$  do
    if  $b_i = 1$  then
         $P = P + A;$ 
    end if;
    Left-shift  $A$ ;
end for;

```

(b) Pseudo-code

Figure 7.22. An algorithm for multiplication.

 


Figure 7.23. ASM chart for the multiplier.

Please see “**portrait orientation**” PowerPoint file for Chapter 7

Figure 7.24. Datapath circuit for the multiplier.

Please see “**portrait orientation**” PowerPoint file for Chapter 7

Figure 7.25. ASM chart for the multiplier control circuit.

Please see “**portrait orientation**” PowerPoint file for Chapter 7

Figure 7.26. Verilog code for the multiplier circuit.

 


Figure 7.27. Simulation results for the multiplier circuit.

$$9 \overline{)140} \\ \underline{9} \\ 50 \\ \underline{45} \\ 5$$

(a) An example using decimal numbers

The diagram illustrates a binary division process. On the left, the dividend is 00001111 and the divisor is 1001. The quotient is labeled $Q = 101$ and the remainder is labeled $R = 101$. The division is shown as follows:

$$\begin{array}{r} 00001111 \\ \hline 1001) 10001100 \\ \underline{1001} \\ 10001 \\ \underline{1001} \\ 10000 \\ \underline{1001} \\ 1110 \\ \underline{1001} \\ 101 \end{array}$$

(b) Using binary numbers

```

 $R = 0;$ 
for  $i = 0$  to  $n - 1$  do
    Left-shift  $R \| A$  ;
    if  $R \geq B$  then
         $q_i = 1$  ;
         $R = R - B$  ;
    else
         $q_i = 0$  ;
    end if;
end for;

```

(c) Pseudo-code

Figure 7.28. An algorithm for division.

Please see “**portrait orientation**” PowerPoint file for Chapter 7

Figure 7.29. ASM chart for the divider.

 


Figure 7.30. Datapath circuit for the divider.

Please see “**portrait orientation**” PowerPoint file for Chapter 7

Figure 7.31. ASM chart for the divider control circuit.



Clock cycle	R	rr ₀	A/Q
Load A, B	0 0 0 0 0 0 0 0 0	0	1 0 0 0 1 1 1 0 0
0 Shift left	0 0 0 0 0 0 0 0 0	1	0 0 0 1 1 1 0 0 0
1 Shift left, Q ₀ ← 0	0 0 0 0 0 0 0 0 1	0	0 0 1 1 0 0 0 0 0
2 Shift left, Q ₀ ← 0	0 0 0 0 0 0 0 1 0	0	0 1 1 0 0 0 0 0 0
3 Shift left, Q ₀ ← 0	0 0 0 0 0 0 1 0 0	0	1 1 0 0 0 0 0 0 0
4 Shift left, Q ₀ ← 0	0 0 0 0 0 1 0 0 0	1	1 0 0 0 0 0 0 0 0
5 Subtract, Q ₀ ← 1	0 0 0 0 1 0 0 0 0	1	0 0 0 0 0 0 0 0 1
6 Subtract, Q ₀ ← 1	0 0 0 0 1 0 0 0 0	0	0 0 0 0 0 0 0 1 1
7 Subtract, Q ₀ ← 1	0 0 0 0 0 1 1 1 1	0	0 0 0 0 0 0 1 1 1
8 Subtract, Q ₀ ← 1	0 0 0 0 0 0 1 0 1	0	0 0 0 0 1 1 1 1 1

Figure 7.32. An example of division using $n = 8$ clock cycles.

Please see “**portrait orientation**” PowerPoint file for Chapter 7

Figure 7.33. ASM chart for the enhanced divider control circuit.

Please see “**portrait orientation**” PowerPoint file for Chapter 7

Figure 7.34. Datapath circuit for the enhanced divider.

Please see “**portrait orientation**” PowerPoint file for Chapter 7

Figure 7.35. Verilog code for the divider circuit.

 


Figure 7.36. Simulation results for the divider circuit.

Please see “**portrait orientation**” PowerPoint file for Chapter 7

Figure 7.37. An algorithm for finding the mean of k numbers.

Please see “**portrait orientation**” PowerPoint file for Chapter 7

Figure 7.38. Datapath circuit for the mean operation.

Please see “**portrait orientation**” PowerPoint file for Chapter 10

Figure 7.39. ASM chart for the mean operation control circuit.

```
for  $i = 0$  to  $k - 2$  do
     $A = R_i$  ;
    for  $j = i + 1$  to  $k - 1$  do
         $B = R_j$  ;
        if  $B < A$  then
             $R_i = B$  ;
             $R_j = A$  ;
             $A = R_i$  ;
        end if ;
    end for;
end for;
```

Figure 7.40. Pseudo-code for the sort operation.

Please see “**portrait orientation**” PowerPoint file for Chapter 7

Figure 7.41. ASM chart for the sort operation.

 


Figure 7.42. A part of the datapath circuit for the sort operation.

 


Figure 7.43. A part of the datapath circuit for the sort operation.

Please see “**portrait orientation**” PowerPoint file for Chapter 7

Figure 7.44. ASM chart for the control circuit.

Please see “**portrait orientation**” PowerPoint file for Chapter 7

Figure 7.45. Verilog code for the sorting circuit.

Please see “**portrait orientation**” PowerPoint file for Chapter 7

Figure 7.46. Simulation results for the sort operation.

 


Figure 7.47. An H tree clock distribution network.

 


Figure 10.48. A flip-flop in an integrated circuit.

 


Figure 7.49. Flip-flop timing in a chip.

 


Figure 7.50. Asynchronous inputs.

 
 


Figure 7.51. Switch debouncing circuit.

```
Q = 0 ;
R = A ;
while ((R - B) > 0) do
    R = R - B ;
    Q = Q + 1 ;
end while ;
```

Figure P7.1. Pseudo-code for integer division.

 


Figure P7.2. The 555 programmable timer chip.