

# ECE/CS 5745/6745

# Testing and Verification of Digital Circuits

Lecture Slides for ATPG, Redundancy & Test Generation,  
Reducing Test Generation Effort, and the Check-Point Theorems




***Priyank Kalla***  
Professor  
Electrical & Computer Engineering

# ATPG: Path Sensitization

- First Try Single Path Sensitization
  - D-calculus:  $v/v_f = \text{fault-free/faulty value}$
  - $D=1/0$ ,  $\bar{D}=0/1$ ,  $0=0/0$ ,  $1=1/1$

$\bar{b}/1$

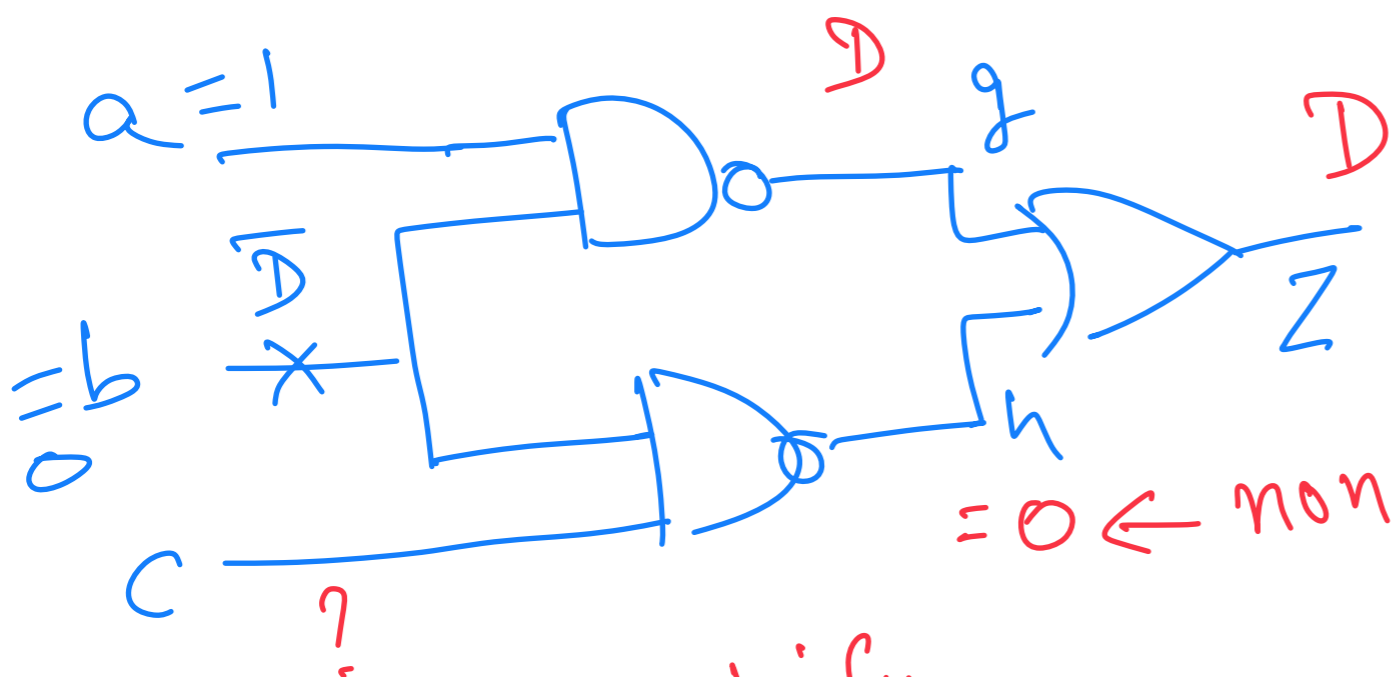

$b \rightarrow g \rightarrow Z$


$= 0 \leftarrow \text{non-controlling value}$

Cannot justify.


$b \rightarrow h \rightarrow Z$   
Same problem
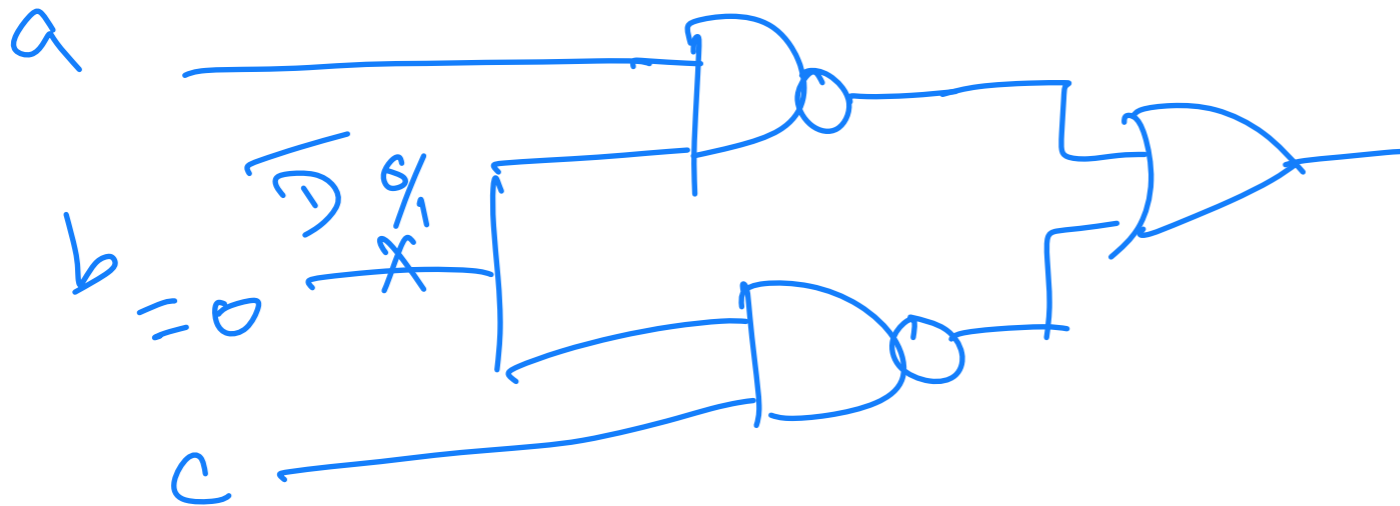
# ATPG: Path Sensitization

- Now Try Multi Path Sensitization
  - D-calculus:  $v/v_f = \text{fault-free/faulty value}$
  - $D=1/0$ ,  $\bar{D}=0/1$ ,  $0=0/0$ ,  $1=1/1$



# ATPG: No Test = Redundancy

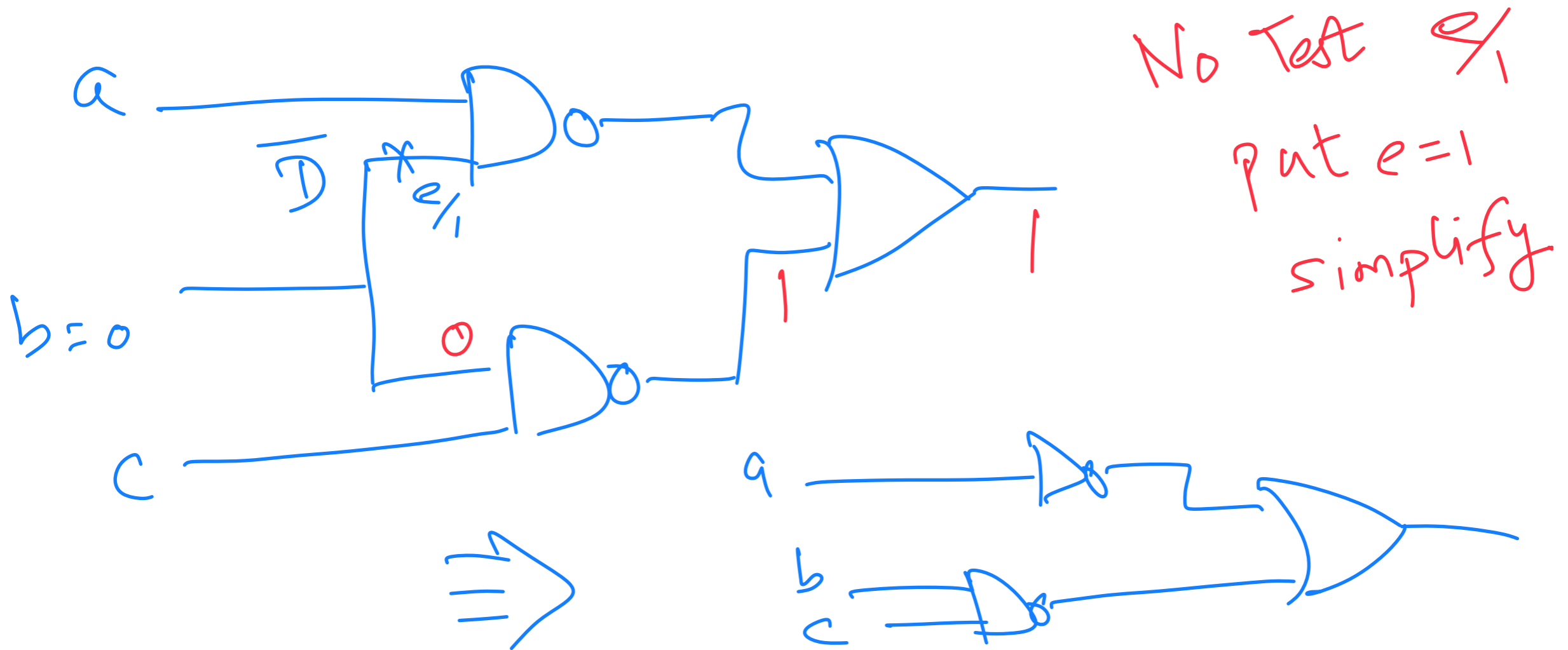

- Sometimes single-path sensitization works
- Sometimes multi-path sensitization works
- Sometimes, test does not exist = redundancy
- Redundancy removal via s-a-f propagation


# Testing using Boolean Difference

- Let  $x$  be a PI,  $Z$  the PO. Prove that Test for  $x/1$   $T_{x/1} = \bar{x} \cdot \frac{\delta Z}{\delta x} = \bar{x} \cdot [Z_x \oplus Z_{x'}]$
- Fault-free function  $Z$ , faulty function  $Z_f = Z(x = 1) = Z_x$
- $T_{x/1} = \underline{Z \oplus Z_x}$  = miter between faulty and fault-free circuit

Shannon's Expansion:  $Z = x Z_x + \bar{x} Z_{\bar{x}}$

$$\begin{aligned}
 T_{x/1} &= \underline{x Z_x} \oplus \bar{x} Z_{\bar{x}} \oplus \underline{Z_x} \\
 &= Z_x (x \oplus 1) \oplus \bar{x} Z_{\bar{x}} \\
 &= \bar{x} Z_x \oplus \bar{x} Z_{\bar{x}} \\
 &= \bar{x} [Z_x \oplus Z_{\bar{x}}] = \bar{x} \frac{\partial Z}{\partial x}
 \end{aligned}$$
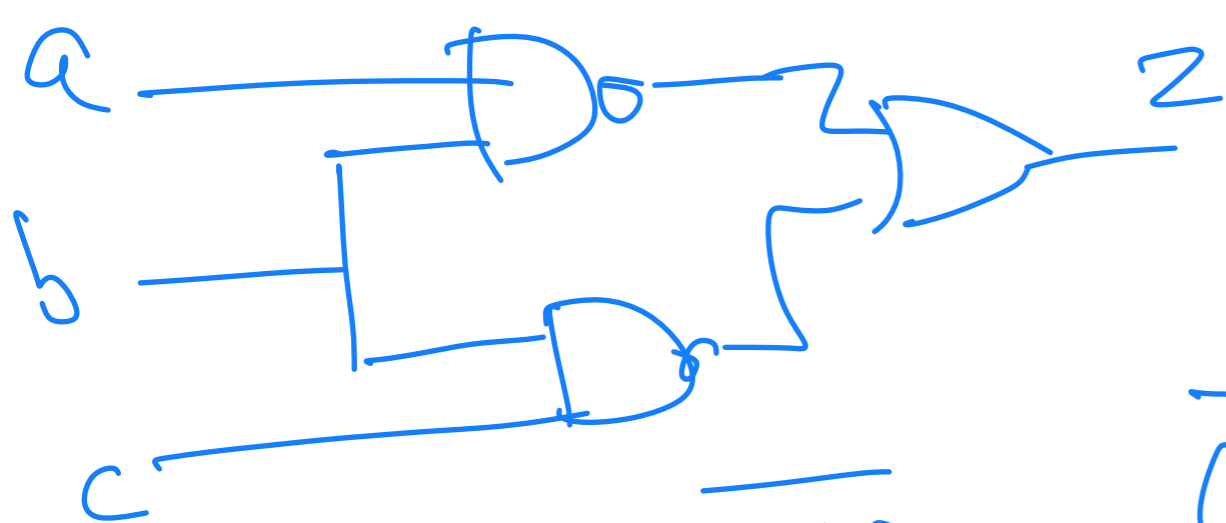
$$T_{x/0} = x \cdot \frac{\partial Z}{\partial x}$$



$$T_{b/0} : b \cdot \frac{\partial Z}{\partial b}$$

$$Z = \overline{(ab)} + \overline{(bc)}$$

$$\begin{aligned} \frac{\partial Z}{\partial b} &= Z_b \oplus Z_{\bar{b}} = \left[ \overline{(a \cdot 1)} + \overline{(1 \cdot c)} \right] \oplus \left[ \overline{0} + \overline{0} \right] \\ &= (\overline{a} + \overline{c}) \oplus 1 = \overline{(\overline{a} + \overline{c})} = ac \end{aligned}$$

$$T_{b/0} : b \cdot ac$$

$$T_{b/1} : \bar{b} \cdot ac$$

# Testability of Two-Level Logic Circuits

- Two level logic = sum of product forms
- Implementation on Programmable Logic Array (PLA)
- Exact minimization using K-maps
  - Make the cover prime and irredundant
  - Minimize area, minimize delay, also fully testable circuit!




$$f = ab\bar{c} + a\bar{b}c + \bar{a}bc + abc$$
$$= ab + ac + bc$$

a \ bc	00	01	11	10
0			1	
1		1	1	1

$$= a(bc) + bc = \text{factored form}$$

= multi-level ckt.

# Structure of PLAs

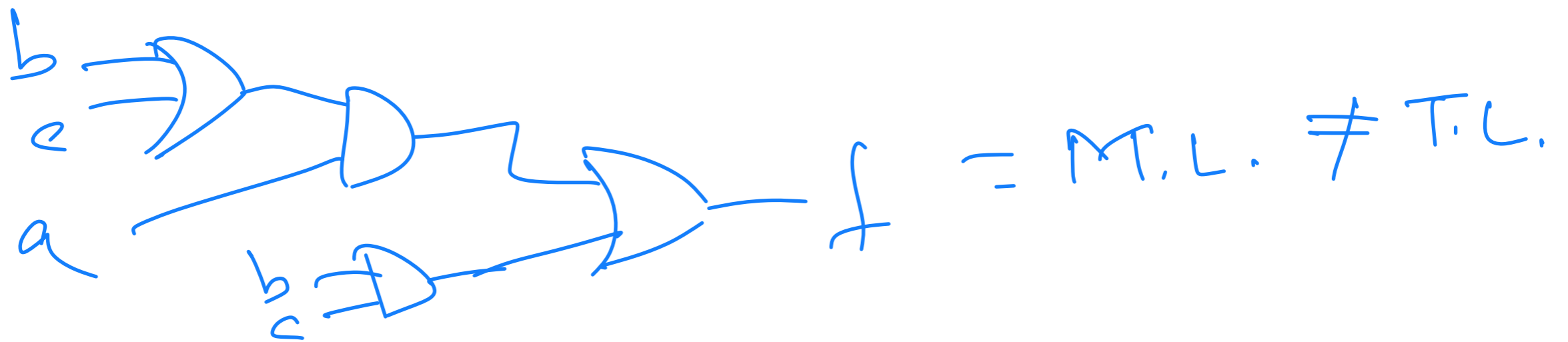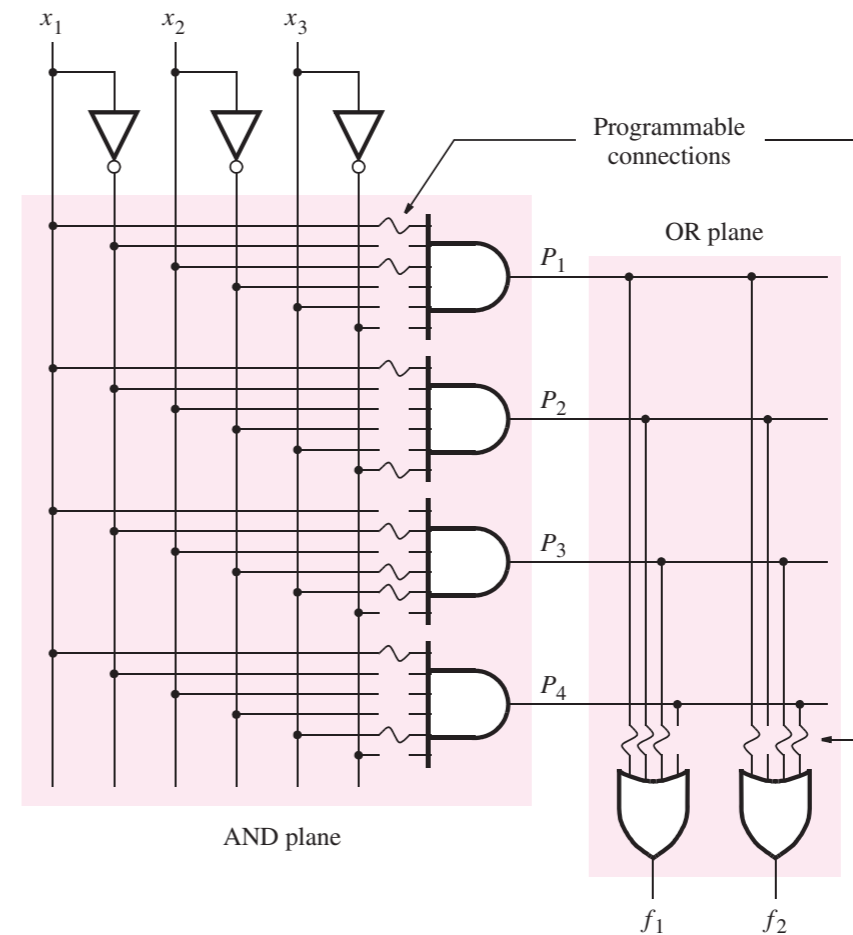
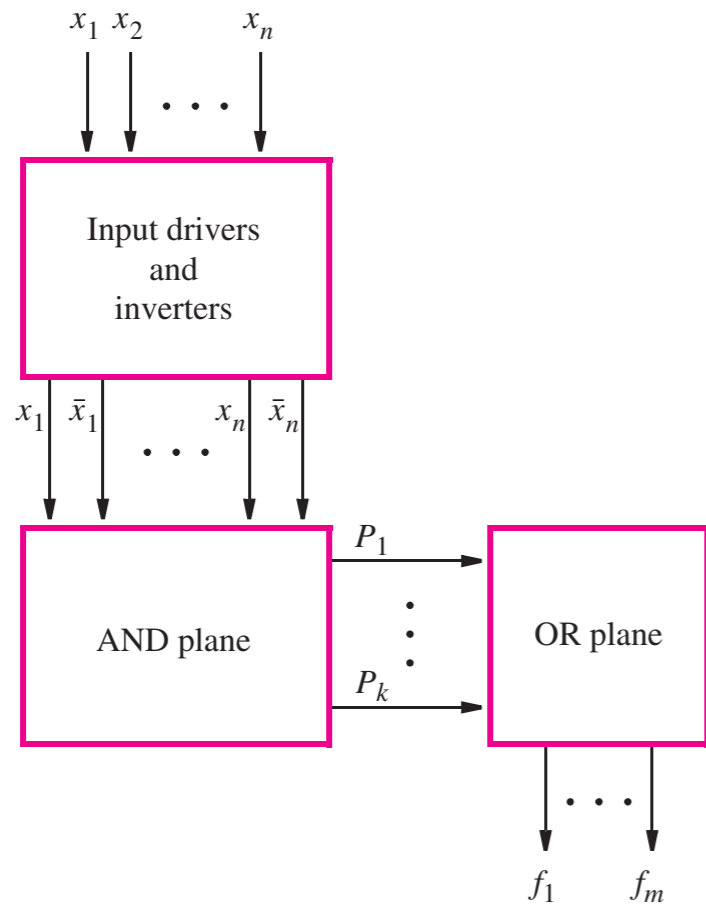




# ATPG: Redundant Cover


- Redundant cube = untestable s-a-0 fault at AND-gate output

$$f = ab + ac + b\bar{c}$$

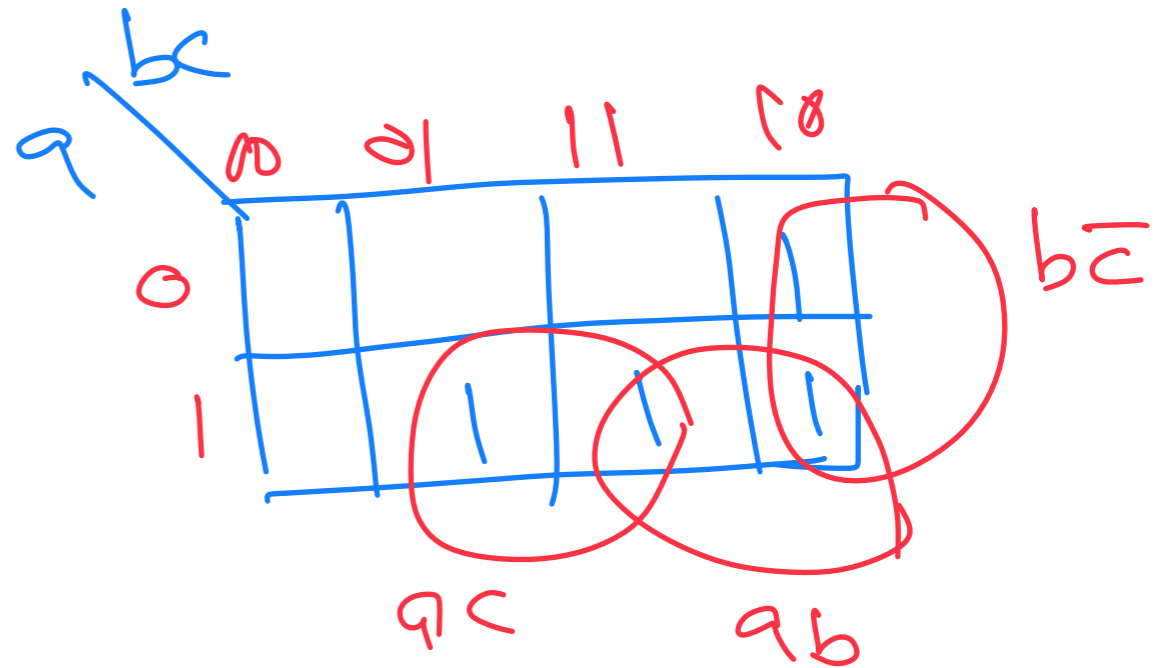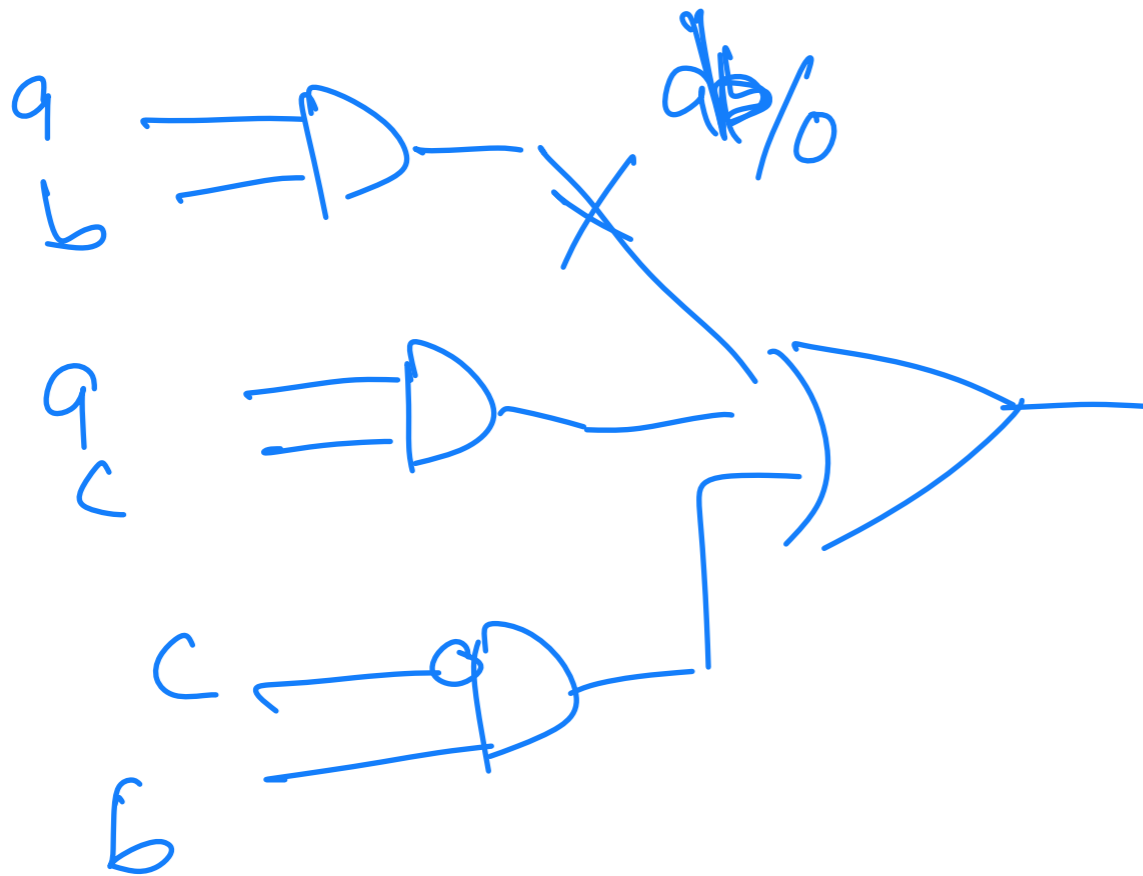
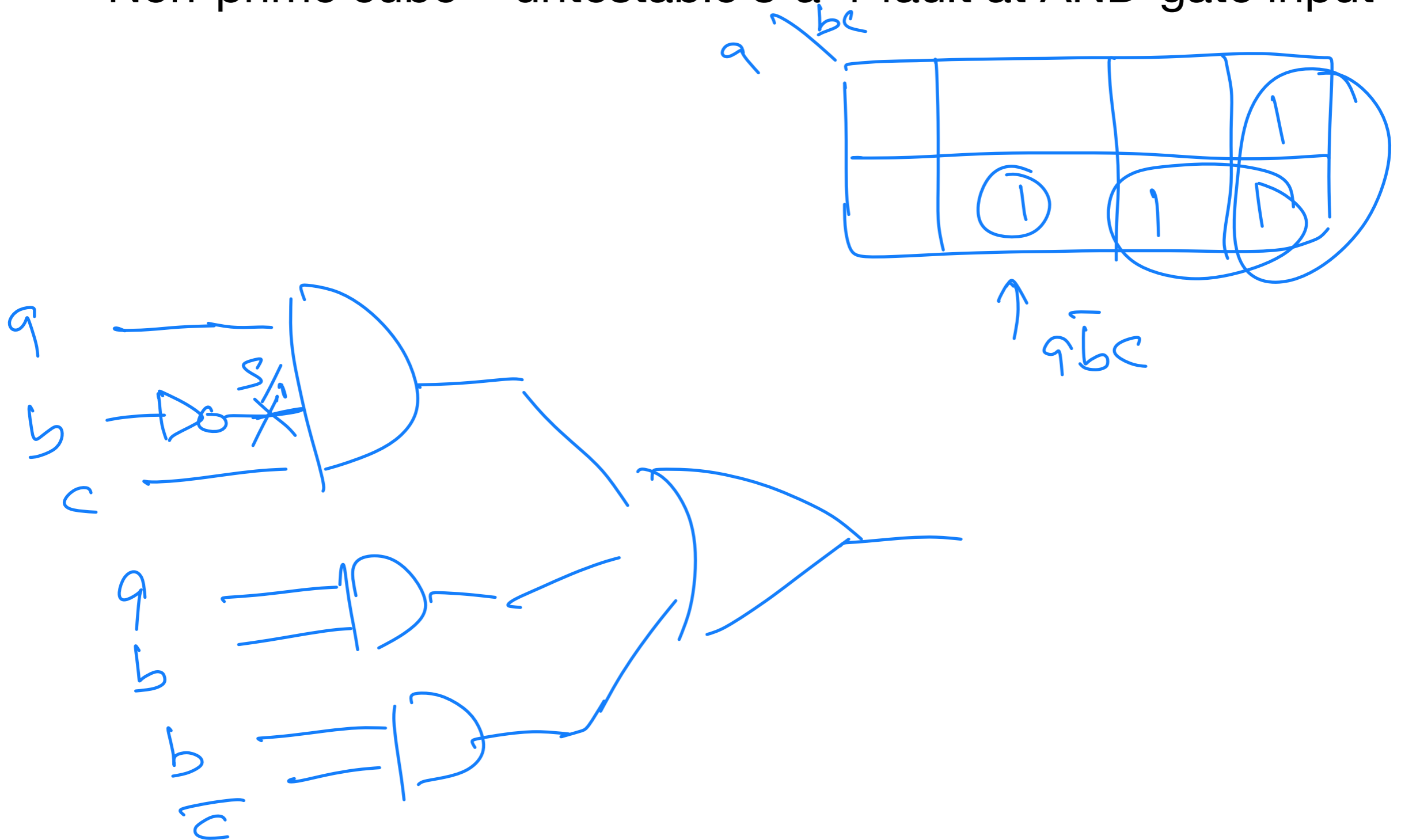
# ATPG: Non-prime Cover



- Non-prime cube = untestable s-a-1 fault at AND-gate input



# Prime & Irredundant 2-level Circuit = Fully Testable!

$$f = ab + ac + b\bar{c}$$

$$= ac + b\bar{c}$$

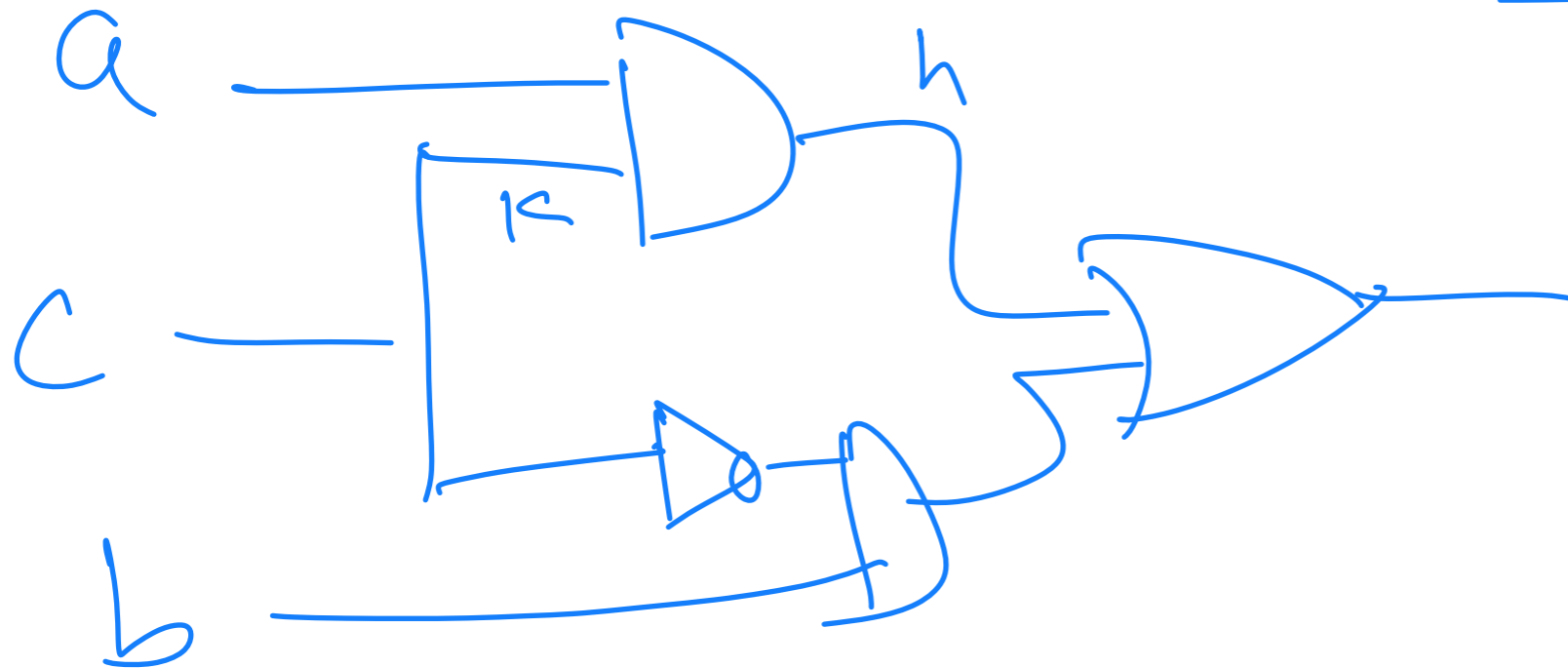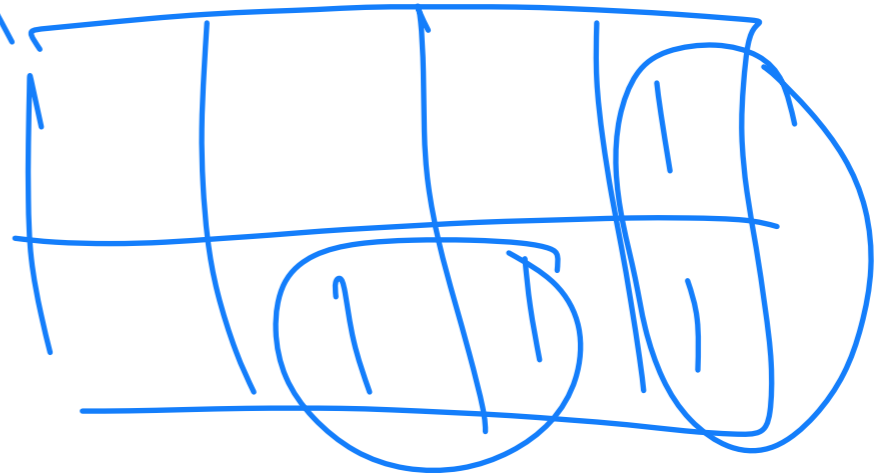


$\uparrow$   
K<sub>1</sub>

$\uparrow$   
K<sub>0</sub>

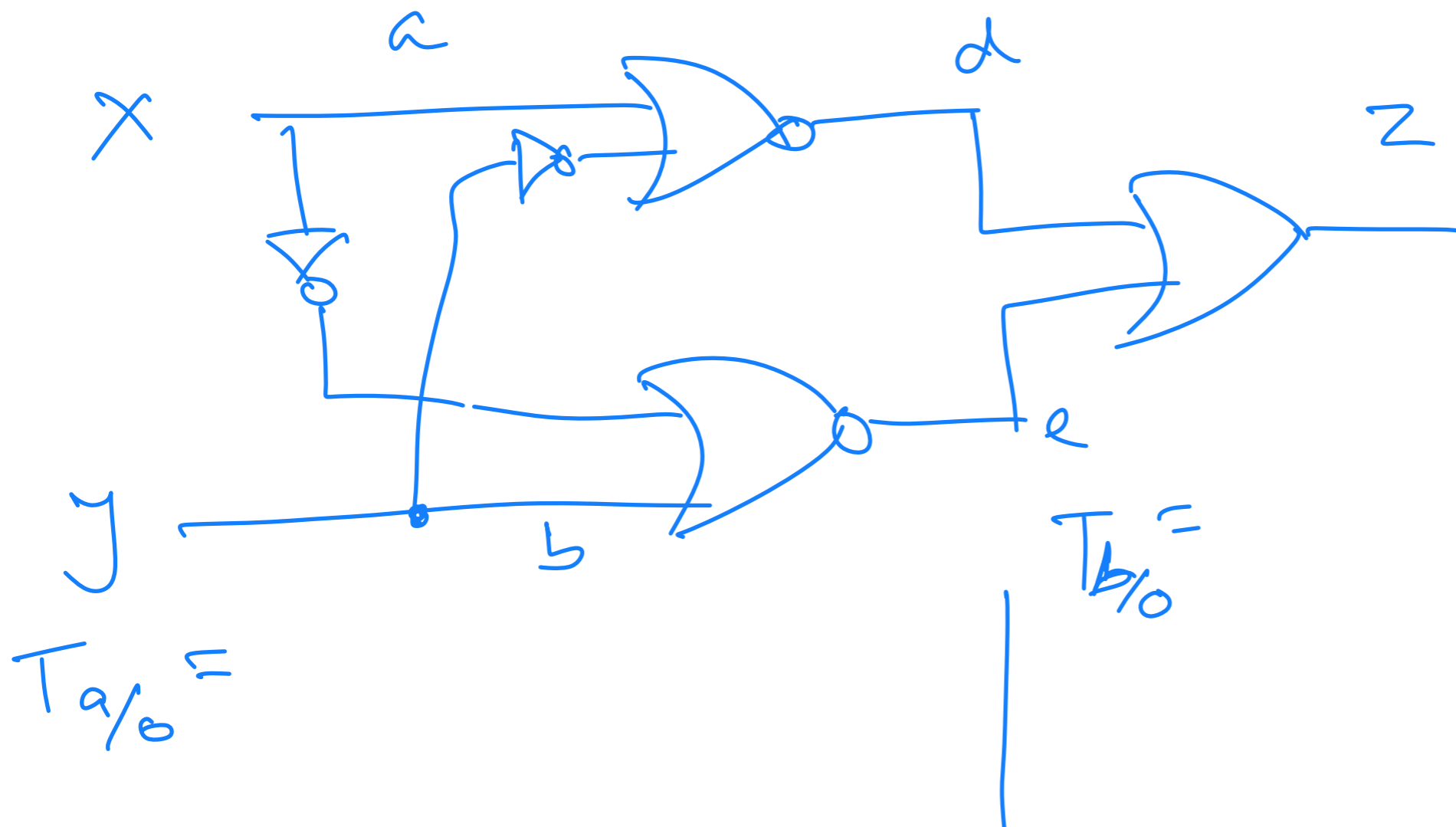
# Fault Equivalence

- Two faults are functionally equivalent if their effect cannot be distinguished
- Detect only 1 out of ALL equivalent faults
- Infeasible to identify all functionally equivalent faults, so we try a simple problem of structural equivalence



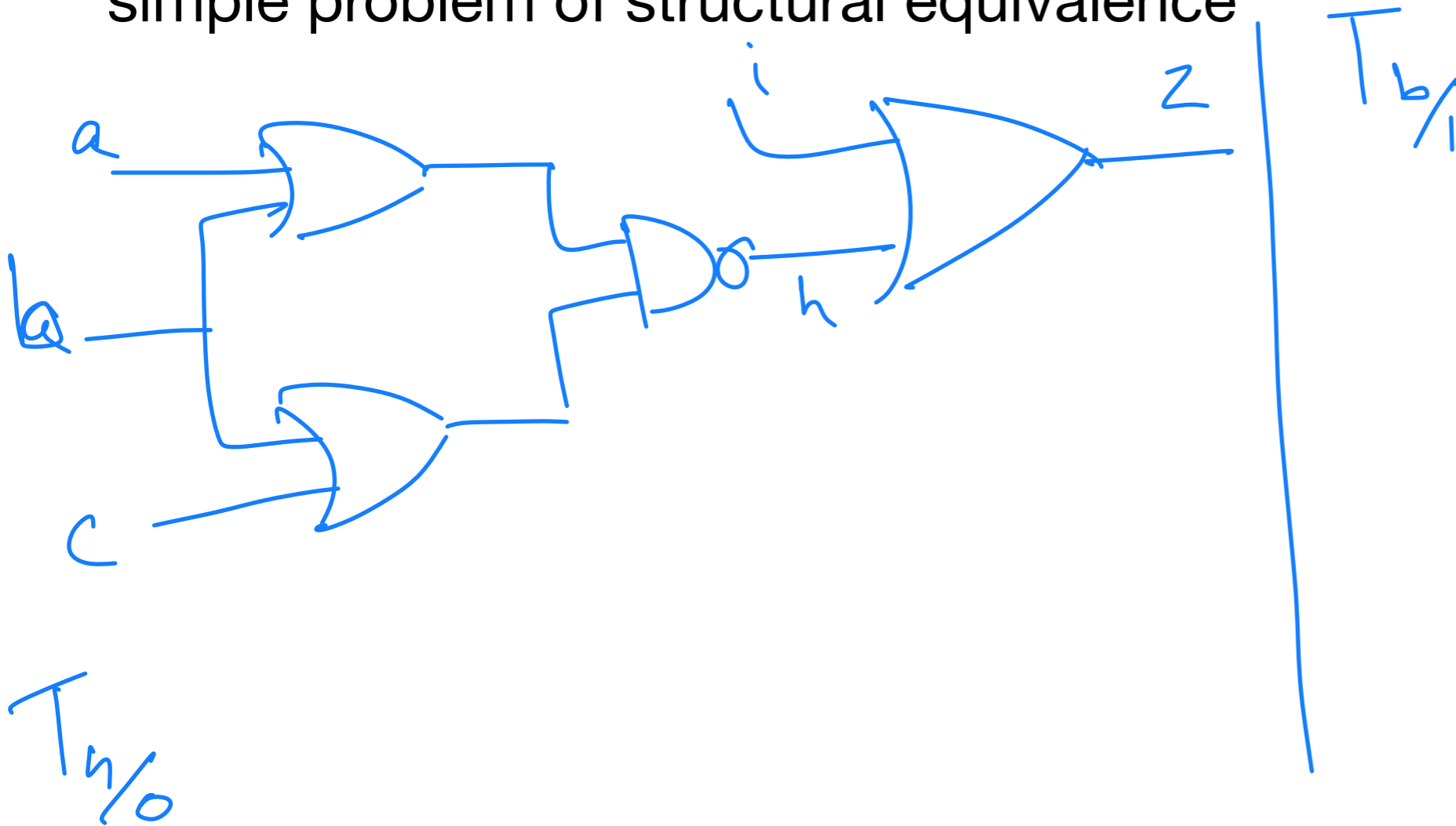
# Fault Equivalence

- Two faults are functionally equivalent if their effect cannot be distinguished
- Detect only 1 out of ALL equivalent faults
- Infeasible to identify all functionally equivalent faults, so we try a simple problem of structural equivalence



# Structural Fault Equivalence

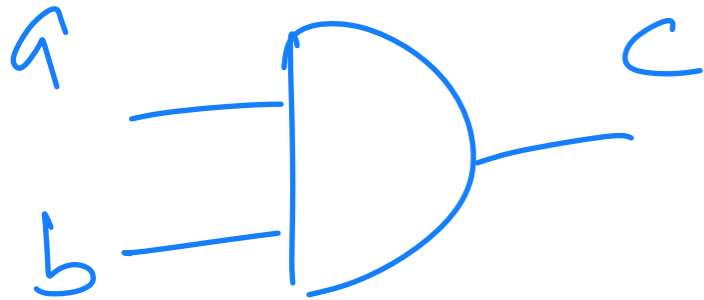

$a/0$


$b/0$

$c/0$

$a/1$


$b/1$

$c/1$


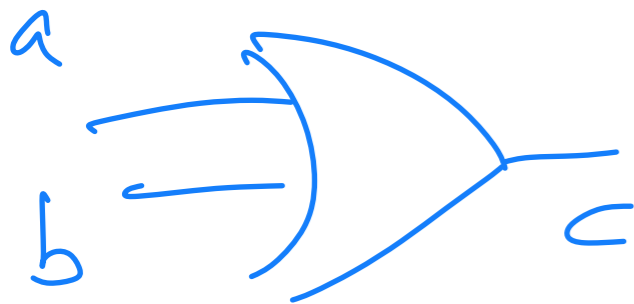

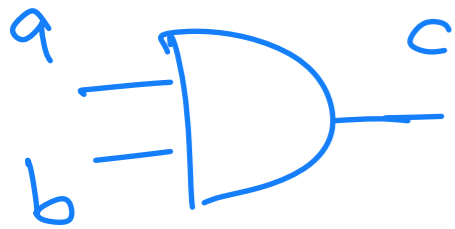
# Fault Dominance

- Let  $T_g$  be the set of all tests that detect fault  $g$
- Fault  $f$  dominates fault  $g$  if  $Z_f(t) = Z_g(t) \quad \forall t \in T_g$
- Clearly  $T_f \supseteq T_g$ .
- If the goal is fault detection (and not fault distinguishing/diagnosis), then  $T_f$  is not needed,  $T_g$  suffices to detect fault  $f$



$$c/1 \supseteq a/1, b/1$$

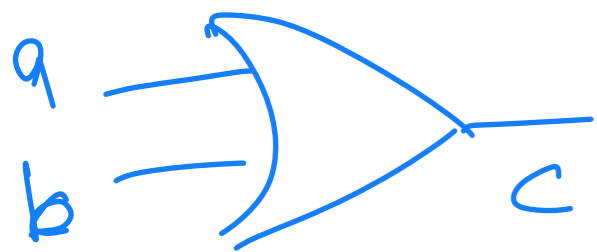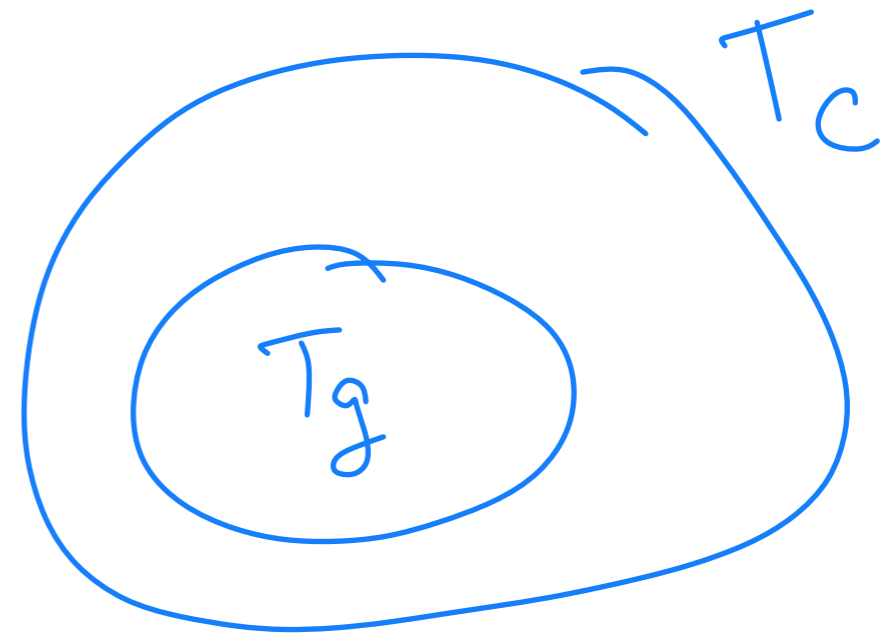

$$c/0 \supseteq a/0, b/0$$