

# Testing and Verification of Digital Circuits

## ECE/CS 5745/6745 – Fall 2025

Some make-up questions for HW 4 (Qs 1, 2, &3)

Due date: Fri Dec 5

Instructor: Priyank Kalla

These are make-up questions for Qs 1, 2, & 3 in HW4. So if you got any of those wrong, you may solve these instead, and I'll replace your grade with the better grade for each of these questions.

1) [**Multi-fault ATPG: 15 points**] Consider the circuit of Fig. 1.

 


Fig. 1. The circuit to test for single- and multi-faults

- Find a test for single fault  $x_3$  stuck-at-1 ( $x_3/1$ ).
- Find a test for single fault  $x_2$  stuck-at-0 ( $x_2/0$ ).
- Find a test for the multi-fault  $\{x_3/1, x_2/0\}$ .
- Does the multi-fault scenario invalidate the single-stuck-fault testing assumptions? Explain.

2) [**Fault Collapsing: 25 points**] For the circuit shown in Fig. 2.

- (10 pts) Suppose we wish to derive a set of tests to *distinguish* between all distinguishable single stuck-at faults in the circuit of Fig. 2. Identify a set of faults for which tests *need not* be derived.
- (5 pts) List all the checkpoint faults of this circuit.
- (10 pts) Find a *smallest/minimal* subset of checkpoint faults that must be targeted for test generation if the *detection* of all single stuck-at faults is the goal.

3) [**Stuck-at faults at fanout stems and branches: 20 points**] For the circuit shown in Fig. 2:

 


Fig. 2. The circuit diagram related to checkpoint faults, and to test  $k, m, n$  s-a-0

- Derive a test for the stuck-at-faults: (i)  $k/0$ ; (ii)  $m/0$ ; (iii)  $n/0$  using path sensitization. First attempt single path sensitization; and only then try multiple path sensitization, if needed.
- If any of the above faults is/are undetectable, remove the redundancy and simplify the circuit. Do not use Boolean algebra!