

ECE/CS 5745/6745: Testing and Verification of Digital Circuits

Hardware Verification Using Symbolic Computation

Prepared by *Priyank Kalla*

Fall 2025, Homework # 4

Due Date: Monday Oct 27, 2025. Upload on Canvas by midnight.

 


Fig. 1: Test for faults $b/1$, tests for distinguishing $a/0$ from $c/0$ and test for multi-fault $\{a/0, b/1\}$.

1) [ATPG: 15 points] For the circuit shown in Fig. 1:

- Find the set of all tests that detect single stuck-at fault $b \text{ s-a-} 1$.
- Find the set of all tests that distinguish between single stuck-at faults (i.e. their fault effects) $a \text{ s-a-} 0$ and $c \text{ s-a-} 0$.
- Derive a test for the multi-fault $\{a \text{ s-a-} 0, b \text{ s-a-} 1\}$.
- Based on the outcome of the above three tests, state your observations regarding the (un)testability of single and multi-faults. Refer to the appropriate class slides on multiple stuck-at faults, and the concept of test invalidation for multi-faults under the presence of redundancies.

2) [ATPG Checkpoints: 25 points] For the circuit shown in Fig. 2, solve the following:

- (10 pts) Suppose we wish to derive a set of tests to *distinguish* between all distinguishable single stuck-at faults in the circuit of Fig. 2. Identify a set of faults for which tests *need not*

be derived.

- b) (5 pts) List all the checkpoint faults of this circuit.
- c) (10 pts) Find a *smallest/minimal* subset of checkpoint faults that must be targeted for test generation if the *detection* of all single stuck-at faults is the goal.

 


Fig. 2: The circuit diagram related to Checkpoint faults

- 3) [Stuck-at faults at fanout stems and branches: 20 points] For the circuit shown in Fig. 2:
 - a) (15 pts) Derive a test that detects the following single faults (i) $k/1$; (ii) $m/1$; and (iii) $n/1$. You should use path-sensitization to derive these tests. Of course, you can check your answer by setting up the problem as a miter between a fault-free and a faulty circuit, and use the 'cec' command of ABC!
 - b) (5 pts) If any of the above faults is undetectable, remove the redundancy by removing redundant gates and/or lines, and draw the simplified circuit.
- 4) [20 points] This question is for ECE/CS 6745 students. ECE/CS 5745 students may solve it for extra credit. Let N be a combinational circuit composed only of NAND gates. Assume that all the primary inputs of the circuit have a fanout of exactly one (1). Show that any test set T that detects all single stuck-at-1 faults in the circuit, detects all single stuck-at-0 faults as well. *Note: Do not assume that the circuit is fanout-free. Only the primary inputs (PIs) are fanout free. (A fanout of 1 means that the gate output is connected to only 1 other gate input, and this gate is also referred to as being fanout-free).*

5) [10 points: Equivalence checking versus bug-detection in arithmetic circuits]. On the class website, along with this HW, I have uploaded two BLIF files. They correspond to a 16-bit Mastrovito GF multiplier (MastrovitoF_q16.blif) and another 16-bit Montgomery GF multiplier (MontgomeryF_q16.blif). As described in my book chapter, (which we will study in the next few lectures) these architectures perform modulo-multiplication, but are based on different mathematical concepts — these designs do not exhibit any internal structural or functional equivalences. As a result, SAT/AIG-based techniques are unable to prove equivalence between them because the AIG of the miter cannot be functionally reduced (fraig'ed). Instead of taking my word for it, you will gain a first-hand experience for yourself.

- Input the two designs into the ABC tool, and miter them.
- Using `print_stats`, `strash`, `ifraig`, `print_stats`, identify the structural similarity in the design. Let N_1 be the number of AIG nodes in the miter before *fraiging*, and N_2 be the number of AIG nodes after *fraiging*. Then $\frac{N_1 - N_2}{N_1}$ roughly depicts the structural similarity as a percentage.
- Solve sat on the miter (or equivalently run the 'cec' command) to perform the combinational equivalence check. Is it feasible to prove equivalence of (fairly small) 16-bit datapath circuits? ☺
- Now introduce a bug in any one of these circuits, by making any modification to any one of the BLIF files. Now run ABC-CEC and report whether bug catching or correctness proofs for arithmetic circuits is easier.

Describe your experiments and state your conclusions from these experiments.