

Q3

(3)

Design of a 3-bit Mastroiote Multiplier.

$$f_8 = f_2[x] \pmod{f(x) = x^3 + x + 1}$$

$$x^3 + x + 1 = 0 \Rightarrow x^3 = x + 1$$

$$x^4 = x^2 + x$$

$$Z = A \cdot B$$

$$A = a_0 + a_1x + a_2x^2$$

$$B = b_0 + b_1x + b_2x^2$$

$$A \cdot B = \left(\sum_{i=0}^2 a_i x^i \right) \cdot \left(\sum_{j=0}^2 b_j x^j \right) = (a_0 + a_1x + a_2x^2)(b_0 + b_1x + b_2x^2)$$

$$= a_0b_0 + a_0b_1x + a_0b_2x^2 + a_1b_0x + a_1b_1x^2 + a_1b_2x^3 + a_2b_0x^2 + a_2b_1x^3 + a_2b_2x^4$$

$$= \begin{pmatrix} a_0b_0 \\ + \\ a_1b_2 \\ + \\ a_2b_1 \end{pmatrix} + \begin{pmatrix} a_0b_1 \\ + \\ a_1b_0 \\ + \\ a_1b_2 \\ + \\ a_2b_1 \\ + \\ a_2b_2 \end{pmatrix} x + \begin{pmatrix} a_0b_2 \\ + \\ a_1b_1 \\ + \\ a_2b_0 \end{pmatrix} x^2$$

$$= z_0 + z_1x + z_2x^2$$

[See the singular file of the design + miter]