
DEMONSTRATION SESSION

ANALYZE

Rigorous verification of asynchronous circuits and systems.

Ken Stevens

Air Force Institute of Technology

GENERAL APPLICATION

Unbounded delay verification for all hazard models:

- Delay-insensitive (DI)
- Quasi delay-insensitive (QDI)
- Speed-independent (SI)
- Burst-mode (BM?)

Example 1: C-Element

1. Efficient SOP C-Element does not verify under SI hazard model.
2. Efficient SOP C-Element verifies under BM hazard model.

MATHEMATICAL RIGOR

1. Only tool based on a model proven to not create false positive results. Details:

- Bisimulation verification
- Complete Trace verification

2. Process Logic

- CCS (Milner's Calculus for Concurrent Systems)
- Model Checking
- Temporal logic (HML)

Example 2: Contrived circuit that gives false positive under AVER in burst-mode.

Example 3: Post Office SEQUENCER circuit

HIERARCHICAL

Can be used for top-down verification of systems, to the gate level.

- “Congruence” achieves hierarchical application
- Partial order for looseness of specification (“conformance”)

Examples of system verification (not included in this demo:)

1. CAM (Categorical Abstract Machine)
2. Parts of the AMULET
3. Sutherland’s MOVE machine (by Hans van Gageldonk)
4. Multirate FFT Chip

HIERARCHICAL (cont)

BISIMULATION CONFORMANCE FORMALIZATION

Bisimulation Conformance between implementation I and specification S is written as $I \succeq_b S$ and holds iff $\forall \alpha \in \text{Act}$ and $\forall \beta \in \overline{\mathcal{A}} \cup \{\tau\}$ and $\forall \gamma \in \mathcal{A}$

- (i) Whenever $S \xrightarrow{\alpha} S'$ then
 $\exists I'$ such that
 $I \xrightarrow{\widehat{\alpha}} I'$ and $I' \succeq_b S'$
- (ii) Whenever $I \xrightarrow{\beta} I'$ then
 $\exists S'$ such that
 $S \xrightarrow{\widehat{\beta}} S'$ and $I' \succeq_b S'$
- (iii) Whenever $I \xrightarrow{\gamma} I'$ and $S \xrightarrow{\gamma}$ then
 $\exists S'$ such that
 $S \xrightarrow{\gamma} S'$ and $I' \succeq_b S'$

EXAMPLES FROM PROCEEDINGS


1. Simple Latch Control – page 14.
2. COP – page 119
3. Boolean function unit – page 161
4. One place buffer – page 231
5. SCSI-init-send circuit – page 245

DIRECTIONS

1. Bounded delay verification
2. Conformance not as a partial order
3. Tool improvements
 - (a) Circuit generators
 - (b) HDL language interfaces
 - (c) Specification generators (Al's butterflies)
 - (d) Efficiency
 - (e) Graphical interface

EXAMPLE 1: C-ELEMENT

Specifications:

 


		ab			
		00	01	11	10
c	0	0	0	1	0
	1	0	1	1	1

$$\text{C-elt} \stackrel{\text{def}}{=} a.b.\bar{c}.\text{C-elt} + b.a.\bar{c}.\text{C-elt}$$

$$\text{C-elt} \stackrel{\text{def}}{=} (a,b).\bar{c}.\text{C-elt}$$


EXAMPLE 1: C-ELEMENT

 

$$\begin{aligned}
 \text{C-Imp} \quad \stackrel{\text{def}}{=} \quad & (\text{AND2}[c/b, ac/c] \quad \backslash \\
 & \text{AND2}[ab/c] \quad \backslash \\
 & \text{AND2}[c/b, bc/c] \quad \backslash \\
 & \text{OR3}[ac/a, ab/b, bc/c, c/d] \quad \backslash \\
 &) \setminus \{ac, ab, bc\}
 \end{aligned}$$


EXAMPLE 2: CONTRIVED CIRCUIT

$$\text{Spec} \stackrel{\text{def}}{=} a.\bar{c}.a.\bar{c}.\text{Spec} + b.\bar{c}.b.\bar{c}.\text{Spec}$$

 


EXAMPLE 3: PO SEQUENCER

The Sequencer Module

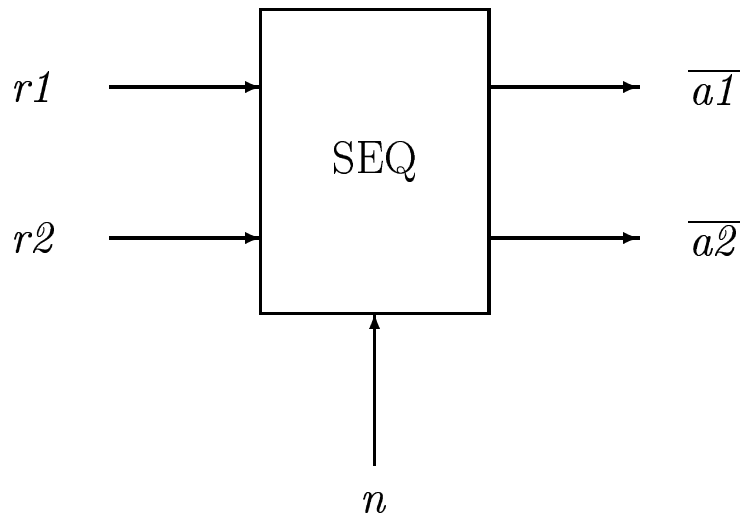

$SIfc$	$\stackrel{\text{def}}{=}$	$r.g1.g2.'a.'p.SIfc$
$SSem$	$\stackrel{\text{def}}{=}$	$'g1.n.'g2.p.SSem + n.'g1.'g2.p.SSem$
SEQUENCER	$\stackrel{\text{def}}{=}$	$(SIfc[r1/r, a1/a] \mid SIfc[r2/r, a2/a] \mid SSem) \setminus \{g1, g2, p\}$

EXAMPLE 3: PO SEQUENCER

 

2^{74} states; 3,664 Burst visited